

**DIGITAL MULTIMETERS FOR HOBBYISTS**

14278

# Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE FEBRUARY 1977/\$1.25

## NEW, PRACTICAL OP AMP CIRCUITS

includes a differential  
PC board tester

## HOW TO ADD DIGITAL FREQUENCY READOUT TO SHORTWAVE RECEIVERS

## TEST REPORTS:

Pioneer CT-F8282 Stereo Cassette Deck  
Acoustic Research AR-16 Speaker System

## BUILD A LOW-COST LOGIC ANALYZER

Data-domain instrument for troubleshooting  
microcomputers and other digital equipment




Retailers: Notice of display-allowance plan is within last three pages.


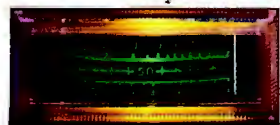
## THE COBRA 32XLR. A TECHNOLOGICAL PUNCHTHROUGH.

Cobra has a reputation for punching through loud and clear. The new Cobra 32XLR, of course, continues the reputation. And creates another—for



innovative design, superb engineering and technical superiority.

Start with the illuminated 4-in-1 meter. It tells you exactly how much power you're pushing out and pulling in. As well as monitoring your modulation in precise percentages. And measuring your punch with an SWR check. In short, the 32 XLR lets you keep an eye on your ears.

ScanAlert, Cobra's unique scanning system, continually monitors Channel 9 when you're on another channel. If an emergency comes up, the ScanAlert light goes on. And the incoming message automatically locks the receiver on the active channel.



The 32XLR's Digital Channel Selector is the very latest. With large LED numerals—for a read-out that registers clearly and quickly. Plus switchable "pulse block" noise blanking that rejects short-pulse noise not normally blocked by other systems. Which makes it the most effective in the business. Finally, add automatic noise limiting, Dynamike Plus (with built-in power mike) and Delta Tuning.

The new Cobra 32XLR. It has virtually everything. And it has everything to do just one thing. Punch through loud and clear.



**Punches through loud and clear.**

Cobra Communications Products  
DYNASCAN CORPORATION

6460 W. Cortland St., Chicago, Illinois 60635

# Remote Control Racer

*Computer logic has added a new fun way to control remote control products.*



*A new fun leisuretime activity made possible by the new electronics.*

The Remote Control Racer is a competition scale model race car controlled by a transmitter using computer logic.

Think of it. Remotely drive a model race car from as far as sixty feet—turning left and right, going forward and reverse. It's great fun for hobbyists, children and the whole family.

## DIGITALLY PROPORTIONAL CONTROL

The steering is controlled as you control the steering wheel on your remote control unit. Turn the wheel slightly to the right and the car wheels turn slightly to the right. Turn your control fully to the left and the car wheels turn fully to the left.

There is no transmission required to go from forward to reverse as the high quality servo motor simply reverses polarity to change gears. Press the forward lever on your remote unit and you go forward. Press the reverse lever and you go in reverse. It's just that quick.

## BUILT TO THE FINEST DETAIL

The camber caster-action front wheels parallel a full-sized car's suspension system and they actually tilt on the turns. An independent floating rear axle maintains positive traction even on rough terrain.

The Remote Racer replaces the gasoline powered remote control race cars that have

The Remote Control Racer is a well built, well engineered electronic instrument with a 90 day limited warranty. JS&A further guarantees your satisfaction—if you are not absolutely satisfied with the value, quality or fun you are having, fine—return your racer within ten days for a full refund. You can't lose.

To order, credit card buyers simply call our toll-free number below and specify the color and quantity you want. Or send a check for \$52.45 (\$49.95 for each Racer plus \$2.50 for postage, insurance and handling to the address shown below. (Ill. residents add 5% sales tax).

By return mail, you'll receive a Remote Control Racer, the remote control unit, batteries, a 90 day limited warranty and simple operating instructions. Your unit should never require service but if it should, JS&A's service-by-mail facility is as close as your mail box. JS&A is America's largest single source of space-age products and a substantial company—further assurance that your modest investment is well protected.


Find out the thrill and fun of racing model race cars remotely. Order one or two Remote Control Racers today.



*The remote control unit (left) controls the race car's electronics (center). The four "C" cell batteries fit in the underside of the Racer.*
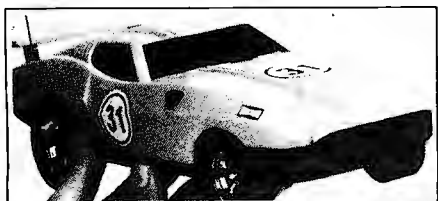
## SOPHISTICATED ELECTRONICS

The sophisticated electronics in the Remote Control Racer consists of 40 transistors. When you operate the control unit, the transmitter generates computer digital logic in a train of digital pulses which then are amplified and transmitted to the racer. The racer then has a sensitive receiver which receives the pulses and in turn translates them into data that eventually translates into power for the car.



*The sleek lines of the Remote Control Racer follows the designs of some of the more popular race cars. The car measures 3 1/2"x5"x12".*

sold for well over \$100 a unit. Remote gas powered models give off odors and are often temperamental. The Remote Racer is quiet so it can be run indoors and it is not dangerous so even children can safely play with it.

## START A RACE CLUB

You can run as many as six different cars in a race as each car will be on a separate remote control frequency. There are four different colors available, red, white, blue, and yellow and each racer comes equipped with its matching remote control unit.

Start a local competition race club, entertain guests with your new adult toy, or give it to your children as one of their most prized possessions. There are many fun ways to use your Remote Racer.

There are two separate circuits used for forward and for reverse. Each circuit utilizes two "C" cell batteries available anywhere. If you only go forward, the two forward batteries will last approximately two hours.

CIRCLE NO. 67 ON FREE INFORMATION CARD

**\$49<sup>95</sup>**

NATIONAL  
INTRODUCTORY  
PRICE

**JS&A** NATIONAL  
SALES  
GROUP

DEPT. PE JS&A Plaza  
Northbrook, Illinois 60062  
CALL TOLL-FREE . . . 800 241-8444  
In Georgia call . . . 800 282-1333  
© JS&A Group, Inc.

# SAVE UP TO 50% ON PARTS.

Hobbyist or professional, there are probably a lot of circuits you build just for the fun of it. And a lot you'd *like* to build, but never get around to.

One reason is the cost of parts. Parts you buy for one project, but can't re-use... because you haven't time to take them carefully apart. Or because of heat and mechanical damage that occur when you do.

Now, there's an easier way that can save you big money on parts *and hours on every project*, as well: *Proto-Board™ Solderless Breadboards*.

Now, assembling, testing and modifying circuits is as easy as pushing in—or pulling out—a lead. IC's, LED's, transistors, resistors, capacitors... virtually every kind of component... connect and inter-connect instantly via long-life, nickel-silver contacts. No special patch

MODEL	NO. OF TIE-POINTS	14-PIN DIP CAPACITY	SUGG LIST *	OTHER FEATURES
PB-6	630	6	\$15.95	Kit — 10-minute assembly
PB-100	760	10	19.95	Kit — with larger capacity
PB-101	940	10	29.95	8 distribution buses, higher capacity
PB-102	1240	12	39.95	Large capacity, moderate price
PB-103	2250	24	59.95	Even larger capacity, only 2.7¢ per tie-point
PB-104	3060	32	79.95	Largest capacity, lowest price per tie-point
PB-203	2250	24	75.00	Built-in 1%-regulated 5V, 1A low-ripple power supply
PB-203A	2250	24	120.00	As above plus separate 1/2-amp +15V and -15V internally adjustable regulated outputs

\*Manufacturer's suggested list  
Prices and specifications subject to change without notice

cords or jumpers needed—just lengths of ordinary #22-30 AWG solid hookup wire.

Circuits go together as quickly as you can think them up. And parts are re-usable, so as your "junk box" builds, you build more and more projects for less and less money.

Before you invest in your next project, invest in a CSC breadboard. See your dealer or order by phone: 203-624-3103 (East Coast) or 415-421-8872 (West Coast)—major charge cards accepted. You've got nothing to lose... and a lot to gain.

CONTINENTAL SPECIALTIES CORPORATION



44 Kendall Street,  
Box 1942, New Haven, CT 06509  
203-624-3103 TWX 710-465-1227  
West Coast office: Box 7809, San Francisco, CA  
94119 • 415-421-8872 TWX 910-372-7992

© 1976, Continental Specialties Corporation

CIRCLE NO. 18 ON FREE INFORMATION CARD



# Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

## FEATURE ARTICLES

MULTIMETERS FOR ELECTRONICS .....	Clayton L. Hallmark	31
<i>Part 2—Digital multimeters.</i>		
NEW, PRACTICAL OP AMP CIRCUITS .....	Sol D. Prensky	47
<i>Including a differential pc board tester.</i>		
CURRENT "FOLDBACK" PROTECTS POWER SUPPLY & LOAD .....	Jerome May	59
<i>How a 723 IC can be used for load and supply regulation.</i>		
NOAA WEATHER RADIO OPERATING LOCATIONS .....		92

## CONSTRUCTION ARTICLES

LOW-COST DIGITAL LOGIC ANALYZER .....	G. Muething, I. Spector & C. Wong	40
<i>Data-domain instrument for troubleshooting digital equipment.</i>		
DIGITAL FREQUENCY READOUT FOR SHORTWAVE RECEIVERS .....	David L. Mattis	49
<i>Programmable counter provides accurate display of receiver frequency.</i>		
CONFERENCE TALK TIMER .....	Walter W. Schopp	62
<i>Compact, versatile project has selectable time intervals.</i>		
QUIZ-GAME ELECTRONICS .....	Michael S. Robbins	64
<i>Player-response circuit imitates quiz shows.</i>		

## COLUMNS

STEREO SCENE .....	Ralph Hodges	17
<i>Halloween at the Waldorf.</i>		
SOLID STATE .....	Lou Garner	66
<i>Timers and Counters.</i>		
EXPERIMENTER'S CORNER .....	Forrest M. Mims	75
<i>Flip-flops and Decade Counters.</i>		
HOBBY SCENE Q&A .....	John J. McVeigh	77
CB SCENE .....	Ray Newhall	85
<i>PURAC—A Voice For CB'ers.</i>		
AMATEUR RADIO .....	Herbert S. Brier	87
<i>Speech Processors.</i>		
COMPUTER BITS .....	Stephen B. Gray	89
<i>Computer Stores.</i>		

## JULIAN HIRSCH AUDIO REPORTS

TAPE RECORDER HEADROOM EXPLAINED .....	23
PIONEER MODEL CT-F8282 CASSETTE DECK .....	24
ACOUSTIC RESEARCH MODEL AR-16 SPEAKER SYSTEM .....	26

## ELECTRONIC PRODUCT TEST REPORTS

HEATHKIT MODEL IM-2202 DIGITAL MULTIMETER .....	78
SHARP MODEL CB-800A AM MOBILE CB TRANSCEIVER .....	79

## DEPARTMENTS

EDITORIAL .....	Art Salsberg	4
<i>Hanging Fire.</i>		
LETTERS .....		6
NEW PRODUCTS .....		12
NEW LITERATURE .....		16
OPERATION ASSIST .....		94
ELECTRONICS LIBRARY .....		96

POPULAR ELECTRONICS, February 1977, Volume 11, Number 2, Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S., \$9.98; U.S. Possessions and Canada, \$12.98; all other countries, \$14.98 (cash orders only, payable in U.S. currency). Second Class postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada, and for payment of postage in cash.

POPULAR ELECTRONICS including ELECTRONICS WORLD, Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature. COPYRIGHT 1977 BY ZIFF-DAVIS PUBLISHING COMPANY. ALL RIGHTS RESERVED.

Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review.

Material in this publication may not be reproduced in any form without permission. Requests for permission should be directed to Jerry Schneider, Rights and Permissions, Ziff-Davis Publishing Co., One Park Ave., New York, NY 10016.

Editorial correspondence: POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models.

Forms 3579 and all subscription correspondence: POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address. Include your old address, enclosing, if possible, an address label from a recent issue.

**EDGAR W. HOPPER**  
Publisher

**ARTHUR P. SALSBERG**  
Editorial Director

**LESLIE SOLOMON**  
Technical Editor

**JOHN R. RIGGS**  
Managing Editor

**STEPHEN B. GRAY**  
Senior Editor

**ALEXANDER W. BURAWA**  
Feature Editor

**EDWARD I. BUXBAUM**  
Art Director

**JOHN McVEIGH**  
Associate Editor

**ANDRE DUZANT**  
Technical Illustrator

**PATRICIA GIRRIER-BROWN**  
Production Editor

Contributing Editors  
**HAL CHAMBERLIN, LOU GARNER**  
**GLENN HAUSER, JULIAN HIRSCH**  
**RALPH HODGES, ART MARGOLIS**  
**FORREST MIMS, RAY NEWHALL**  
**SOL PRENSKY, WILFRED SCHERER**

**JOSEPH E. HALLORAN**  
Advertising Director

**JOHN J. CORTON**  
Advertising Sales

**LINDA BLUM**  
Advertising Service Manager

**PEGI McENEANEY**  
Executive Assistant

**STANLEY NEUFELD**  
Associate Publisher

ZIFF-DAVIS PUBLISHING COMPANY  
Popular Electronics  
Editorial and Executive Offices  
One Park Avenue New York, New York 10016  
212-725-3500

Hershel B. Sarbin, President  
Furman Hebb, Executive Vice President  
John R. Emery, Senior Vice President, Finance and Treasurer  
Phillip T. Heffernan, Senior Vice President, Marketing  
Edward D. Muhlfeld, Senior Vice President, Sports Division  
Philip Sine, Senior Vice President  
Frank Pomerantz, Vice President, Creative Services  
Arthur W. Butzow, Vice President, Production  
Lawrence Sporn, Vice President, Circulation  
George Morrissey, Vice President  
Sydney H. Rogers, Vice President  
Sidney Holtz, Vice President  
Al Traina, Vice President  
Philip Korsant, Vice President  
Paul H. Chook, Vice President, Market Planning  
Charles B. Seton, Secretary  
Edgar W. Hopper, Vice President, Electronics Div.  
William Ziff, Chairman  
W. Bradford Briggs, Vice Chairman

Midwestern Office  
The Patis Group, 4761 West Touhy Ave.,  
Lincolnwood, Illinois 60644, 312 679-1100  
GERALD E. WOLFE, THOMAS HOCKNEY  
Western Office  
9025 Wilshire Boulevard, Beverly Hills, CA 90211  
213 273-8050; BRadshaw 2-1161  
Western Advertising Manager, BUD DEAN

Japan: James Yagi  
Oji Palace Aoyama; 6-25, Minami Aoyama  
6 Chome, Minato-Ku, Tokyo 407-1930/6821,  
582-2851



Member Audit Bureau  
of Circulations



The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



## Editorial

### HANGING FIRE

The October 1976 issue of the *IEEE Spectrum* (an electrical engineering society publication) had an interesting editorial focus entitled: "What Went Wrong?" In addition to covering such failures as the Northeast electrical blackout of '65 and a multi-million-dollar radar project that flopped, promising developments that got sidetracked or delayed were discussed. These included electronic video recording (EVR), ovonic devices, thermoelectricity, the video telephone, emitter-coupled logic, AM stereo, and two-way cable TV.

None of the above is "dead," but they have not exhibited the growth that the excitement of their debuts hopefully promised. Offhand, I can add easily to the list of slow-start concepts that float around. Some, like a virus, come to life many years later; others are not widely adopted for one reason or another.

For example, I edited a cover-story article on microwave ovens in 1959, which indicated that sales were expected to skyrocket. *What went wrong?* A scathing attack was presented by *Consumer Reports* on the appliance's safety (causing tightened standards) that turned off consumers for more than a decade.

Attending a press meeting in the early Sixties, I was treated to a new concept in hi-fi—a servo-feedback system, called "Integrand, that was supposed to counter distortion emanating from speakers." *What went wrong?* I have no idea, but it simply never got off the ground, though the more recent Philips "Motional Feedback" system uses the same general concept.

I recall, too, going to a final task force meeting on the type of stereo FM that should be recommended to the FCC. The majority of attendees chose the Crosby System, which did not degrade the signal-to-noise ratio of the second channel. *What went wrong?* The GE/Zenith proposals were adopted because it was felt by the FCC that many FM broadcasters would not be able to survive without an SCA channel to supplement income, which GE/Zenith retained (together with higher noise) and Crosby did not.

Then there was Educating, using four channels multiplexed on FM, with receivers built by Sylvania Electric; Norelco's 45-rpm automobile record player (which I owned prior to auto tape's introduction); Ampex's floppy magnetic audio disc; wireless microphones; 35-mm audio magnetic tape introduced by Everest Records; a flame loudspeaker whereby flames modulated the air stream (Stanford Research Institute); the magnetic amplifier, which the Bureau of Ships, U.S. Navy, called "... the rising star of electronics in 1960"; and so on.

There are new, promising electronic stars on the horizon today. I wonder how they will fare when faced by the perspective of a few decades? These include the video disc (introduced in 1966) which is supposed to reach the marketplace sometime this year. (I viewed a third V-D system last week, Telefunken's TED. Color was great, but 10-minutes play time for a flexible disc that will sell for \$4 to \$10 on a machine that is expected to cost at least \$500 appears to be out of the running for the public when contrasted with RCA's and Philips' longer playing time systems.) There is also a Class D audio amplifier that has been touted now for three years. And then there are Bubble Memories, which by their great density capability could take over the computer memory world if the price is driven down.

I won't count out any of the concepts, products, devices or systems that never live up to their promise, however. Not when I think of Michael Faraday's observation of semiconductor properties in 1833 and wireless detectors that were used in 1906. Just a little research laboratory twist, and a combined transfer and varistor device emerged in 1948. It is called a transistor.

# you don't listen to the Realistic Mach One...

# you experience it!



Realistic® and Radio Shack lower the cost of thrilling theatre-like sound. 22 years of design know-how and sales of a million speakers annually have shown us how. Powerful 15" woofer. Multi-cell midrange horn. High-compliance tweeter horn. Removable grille for easily balancing midrange and treble response. And genuine walnut veneer cabinetry. It's a real experience to hear the Mach One at live-performance listening levels. Bring in your favorite LP and we'll give you a thundering demonstration that will change your notions about who's really pioneering in hi-fi. Buy the amazing Mach One and we'll also give you a 5-year limited warranty. Ask for 40-4024 at your nearby Radio Shack store or participating dealer. **199<sup>50\*</sup>**



Use your credit card  
at most stores

SOLD ONLY WHERE YOU SEE THIS SIGN:

# Radio Shack®

A TANDY COMPANY • FORT WORTH, TEXAS 76107  
5000 LOCATIONS IN NINE COUNTRIES

\*Price may vary at individual stores and dealers.

FEBRUARY 1977

CIRCLE NO. 53 ON FREE INFORMATION CARD

## Empire's Blueprint For Better Listening

No matter what system you own, a new Empire phono cartridge is certain to improve its performance.

The advantages of Empire are threefold.

One, your records will last longer. Unlike other magnetic cartridges, Empire's moving iron design allows our diamond stylus to float free of its magnets and coils. This imposes much less weight on the record surface and insures longer record life.

Two, you get better separation. The small, hollow iron armature we use allows for a tighter fit in its positioning among the poles. So, even the most minute movement is accurately reproduced to give you the space and depth of the original recording.

Three, Empire uses 4 poles, 4 coils, and 3 magnets (more than any other cartridge) for better balance and hum rejection.

The end result is great listening. Audition one for yourself or write for our free brochure, "How To Get The Most Out Of Your Records." After you compare our performance specifications we think you'll agree that, for the money, you can't do better than Empire.



# EMPIRE

Already your system sounds better.

Empire Scientific Corp.  
Garden City, New York 11530

## Letters

### HIGH-LEVEL FEEDBACK & TIM

The various articles in the "Special Focus on Audio" section in the September 1976 issue of POPULAR ELECTRONICS all propose operational amplifiers with input-to-output gains of one, meaning that very large amounts of feedback are employed. Dr. Matti Otala of Finland has shown that transient intermodulation distortion (TIM) becomes significant when feedback exceeds about 20 dB and is severe for larger feedback factors. Personal experience with high-gain op amps in a preamp circuit was that amplitude-versus-frequency response was controlled within 0.25 dB, but it "just didn't sound right." When I became aware of "Otala distortion," it was pretty obvious that this was the fault.—*Paul W. Klipsch, Klipsch & Associates, Inc., Hope, AR.*

### SWITCH TO NEW SWITCH

In "Build the Roadmate CB Converter" (October 1976), a dpst switch is specified in the Parts List. This should be a dpdt switch.—*Andrew Ciffer, Somerset, NJ*

### IDENTIFYING THE COMPUTER

In "How To Select a Hobbyist Microcomputer" (December 1976), the lead photo has no caption identifying the equipment shown. Could you please tell me what this equipment is?—*Claude Jolly, Granite City, IL*

*The CRT terminal shown on page 51 is the Model D301 made by Informer, Inc., 8332 Osage Ave., Los Angeles, CA 90045. It sells for \$1890.*

### A BETTER CAPACITANCE METER

I suggest the following changes for the "Low-Cost Capacitance Meter" featured in the October 1976 issue of POPULAR ELECTRONICS. First, to prevent the voltage rating from being exceeded with 3-, 6-, or 9-volt capacitors under test, two 1N914 diodes can be connected in series across BP1 and BP2, with the anode of the pair going to BP1 and the cathode to BP2. This will limit the terminal potential to 1.5 volts maximum. Second, by installing a 47-ohm, 1/2-watt resistor between the rotor of S2A and ground, the switch contacts will last longer and the charge on the capacitor under test will discharge less rapidly. Third, by removing the connection between the OFF position of S1A and the anode of D1,

no excessive current will flow through Q1 as C3 and C4 discharge. Fourth, a mini DIP, such as the MC1558 or any dual 741 or amp, can be used to replace the two IC's if desired.—*Marvin J. Moss, Atlanta, GA.*

### PE SPARKS EXPERIMENTING

I feel I owe POPULAR ELECTRONICS a letter of thanks and commendation. I hadn't dabbled in electronics since the dawn of the solid-state era until January of this year. Since then, PE has been very helpful in updating my knowledge of semiconductor theory and application and refreshing my memory on general electronics. I was planning to build a chess clock by coupling together two digital clock kits until I noticed two articles in PE that made me opt for a better design. As a result of the sequence generator described in the February 1976 Experimenter's Corner and "How Multiplexed LED Displays Simplify Circuits" in the March 1976 issue, I was able to design my improved chess clock. Many thanks for accelerating my project to reality and elevating it to an interesting experience.—*James H. Williams, Knoxville, TN.*

### HAM/CB'ER FOR SHARING BAND

I would like to compliment you on your Editorial, "Majority Rules—The Bitter Pill" (November 1976). As both a Ham (W6TNS/7) and an avid CB'er, I can vouch for the wisdom of your words. I am inexorably convinced that there must be a "common meeting ground" where hams and CB'ers can intermingle and learn from each other. CB'ers are extremely susceptible to peer pressure, and I do not buy the argument that this "unwashed multitude" will ruin whatever they touch.

The pressure on the amateur 220-MHz band by 15- to 30-million people is going to mount in the next few years in direct proportion to the skip interference on the Citizens Band. It seems to me that the amateur fraternity would be well-advised to invite the CB'ers to share this relatively unused band, rather than lose it as they did 11 meters.—*Donald L. Stoner, Mercer Island, WA*

### QUESTION OF SAFETY

There is a serious error in "Propagation Forecasts For Radio Communications" (November 1976) on page 36, column 2. A Wratten No. 4 is not a neutral-density filter, per Kodak publication No. B-3 titled "Kodak Filters For Scientific and Technical Uses." The No. 4 is a light yellow filter. Neutral densities are Wratten No. 96, available in densities from 80% light transmission to 0.01% (neutral density 0.1 to 4.0). These are supplied in gelatin only. Should you wish to obtain these in glass, they can be supplied by Tiffen Mfg. Co., 71 Jane St., Roslyn, N.Y.—*John H. Rose II, Warren, MI*

*Thanks. We endorse your recommendation. The author, however, confirms that he has been using the No. 4.*

# WHY SETTLE FOR LESS— THAN A 6800 SYSTEM

## MEMORY—

All static memory with selected 2102 IC's allows processor to run at its maximum speed at all times. No refresh system is needed and no time is lost in memory refresh cycles. Each board holds 4,096 words of this proven reliable and trouble-free memory. Cost—only \$125.00 for each full 4K memory.

## INTERFACE—

Serial control interface connects to any RS-232, or 20 Ma. TTY control terminal. Connectors provided for expansion of up to eight interfaces. Unique programmable interface circuits allow you to match the interface to almost any possible combination of polarity and control signal arrangements. Baud rate selection can be made on each individual interface. All this at a sensible cost of only \$35.00 for either serial, or parallel type

## PROCESSOR—

"Motorola" M6800 processor with Mikbug® ROM operating system. Automatic reset and loading, plus full compatibility with Motorola evaluation set software. Crystal controlled oscillator provides the clock signal for the processor and is divided down by the MC14411 to provide the various Baud rate outputs for the interface circuits. Full buffering on all data and address busses insures "glitch" free operation with full expansion of memory and interfaces.

## POWER SUPPLY—

Heavy duty 10.0 Amp power supply capable of powering a fully expanded system of memory and interface boards. Note 25 Amp rectifier bridge and 91,000 mfd computer grade filter capacitor.


## DOCUMENTATION—

Probably the most extensive and complete set of data available for any microprocessor system is supplied with our 6800 computer. This includes the Motorola programming manual, our own very complete assembly instructions, plus a notebook full of information that we have compiled on the system hardware and programming. This includes diagnostic programs, sample programs and even a Tic Tac Toe listing.

*Mikbug® is a registered trademark of Motorola Inc.*

**SWTPC 6800**  
Computer System

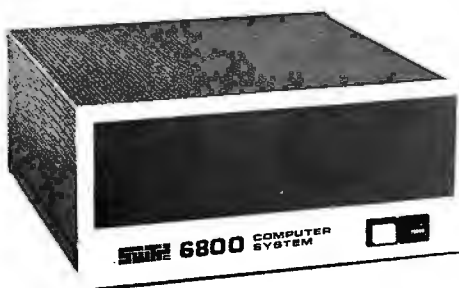with serial interface and 4,096 words of memory. . . . . \$395.00



- ☐ Enclosed is \$395 for my SwTPC Computer Kit ☐ Send Data
- ☐ or BAC \_\_\_\_\_ # \_\_\_\_\_
- ☐ or MC \_\_\_\_\_ Ex Date \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

Southwest Technical Products Corp., Box 32040, San Antonio, Texas 78284

# Only NRI

# 25" designed-

DIAGONAL

# Color TV



# Quadraphonic



Two home training schools give you a hobby-kit Color TV to assemble. Two others give you a commercial set right off the shelf. Neither was designed to teach you how to repair Color TV's. Only NRI invested the time and money to design equipment with learning in mind!

No other home training school gives you both a solid state Color TV and SQ™ Quadraphonic Receiver complete with four speakers . . . all in one course. In fact, to even match this kind of thorough training at another school, you'd have to take an extra

course costing hundreds of dollars more. And only NRI courses in Color TV/Audio servicing let you learn on equipment designed specifically for training.

It's the only way you can (1) get the feel of typical commercial circuitry, (2) learn bench techniques while building complete units from the "ground" up, (3) perform over 35 "in-set" experiments during construction, and (4) end up with a 25" diagonal solid state Color TV with cabinet and a 4-channel Audio Center.

#### **NRI passes the savings on to you**

NRI engineering eliminates the cost of buying from an outside source. We pay no salesman's commission. Students are enrolled by mail only. The savings are passed on to you in the form of low tuition fees, extras like the TV's console cabinet and the Quadraphonic System; professional test instruments like a 5" triggered sweep oscilloscope, CMOS digital frequency counter, and integrated circuit Color TV pattern generator. You can pay hundreds of dollars more for similar courses and not

™ Trademark of CBS, Inc.

# gives you this for-learning ...plus complete Audio Center.

get a nickel's worth more in training and equipment.


## **More know-how per dollar**

It all boils down to the quality of training you get for your money. In our 62-year history, more than a million students have come to NRI and we're fully approved for career training under the G.I. Bill. We know the right way to make home training pay dividends for you.

Some of those "right" things are bite-size lessons to ease understanding and speed learning . . . personal consultation, and prompt grading of all tests . . . a full-time staff of engineer/instructors to help if you need it . . . the right kind of kits and experiments to give you hands-on training . . . and fully professional programs oriented to full or part-time career needs.
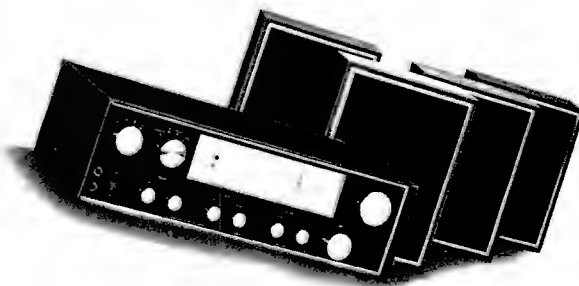
## **Also CB, Computer, & Other Courses**

NRI offers not one, but five TV/Audio servicing courses so you can tailor your training to your budget. Or you can study other opportunity fields like Digital Computer Electronics, Citizens Band Radio, Communications, Aircraft or



Marine Electronics,  
Mobile Radio and more.  
Send for your free catalog and  
see for yourself that no one gives you  
more training and equipment for your  
dollar. There's no obligation and no  
salesman will call.

If card is missing, write to:



**NRI SCHOOLS**  
McGraw-Hill Continuing  
Education Center  
3939 Wisconsin Avenue,  
Washington, D.C. 20016



## New Products

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Reader Service Card inside the back cover or write to the manufacturer at the address given.

### MAGITRAN CB THEFT ALARM

From Magitran, the CB 10-33 Touch-Activated Alarm is a self-contained mobile equipment protection system. An ear-piercing 100-dB signal is emitted the instant a CB unit is



touched. Small enough to be concealed under the dash, the unit operates on a 9-volt transistor battery that will continuously sound the alarm for over three hours, according to the manufacturer. \$29.95.

CIRCLE NO. 92 ON FREE INFORMATION CARD


### HEATHKIT "COMPUTER" COLOR TV

Heathkit's Model GR-2001 color TV receiver kit features a 25" (63.5-cm) black-matrix ultra-rectangular picture tube, PLL horizontal and vertical-hold circuits and high-quality sound. With optional accessories, the receiver has complete programming capability through a computer-like system that can be set up for up to 32 channel changes during any two 12- or 24-hour viewing periods. Programming is via a calculator-type keyboard. Once accomplished, the programmer takes over operation of the receiver, changing channels automatically at the appropriate times. Other optional items include an on-screen digital clock and an automatic antenna rotor control. The latter automatically rotates the antenna to the pre-selected directions for best reception on each channel with each change of channels. Basic receiver kit price is \$279.95; accessory items and cabinet are extra.

CIRCLE NO. 90 ON FREE INFORMATION CARD
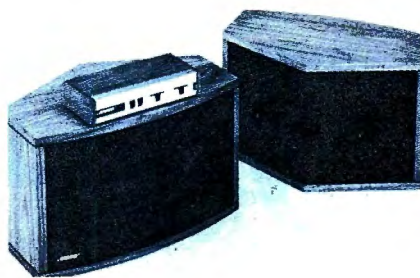
### BOSE SPEAKER SYSTEM

The Bose Model 901 Series III speaker system retains the basic concepts used in the original Model 901 while providing better efficiency, low-bass capability, and adaptability



to a wider range of listening environments. It employs the 901's direct/reflected sound concept, multiple full-range drivers, active equalization, and uniform power radiation. New driver design and an Acoustic Matrix™ enclosure provide better efficiency. The one-piece plastic enclosure has partially isolated chambers, one for each driver. Each chamber joins one of three Reactive Air Columns to provide a controlled interaction between the different drivers. The enclosure does not affect system frequency or transient response. It is designed to reduce cone motion to increase accuracy and the dynamic range of the bass response. \$749 for two speaker systems and equalizer unit.

CIRCLE NO. 93 ON FREE INFORMATION CARD


### PRIDE FREQUENCY COUNTER & CLOCK

The Pride TF-1000 is a combined frequency counter and selectable 12- or 24-hour digital clock for CB and amateur radio use. The six-digit unit switches automatically from clock to frequency counter when the transmitter is activated. The clock continues to count, and the time is again displayed when transmission is completed. The TF-1000 operates from 1 to 40 MHz and can be used with CB and amateur transceivers with outputs from 3 to 200 watts. Measures 9 3/4"D x 8 1/2"W x 3"H (21.6 x 7.6 x 24.8 cm). \$179.95.

CIRCLE NO. 94 ON FREE INFORMATION CARD
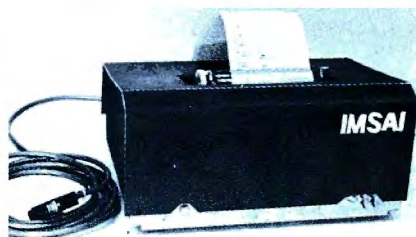
### IMSAI PRINTER

The Imsai Printer is a new 44-column dot-matrix printer designed for use with the Imsai 8080 and many other computers. The printer interfaces to an 8-bit parallel port. It is said to be simple to program and install. It is self-contained, with case, cable, power supply,



timing, control and character generation included. The font is the standard 64-character ASCII subset; double-size characters are software selectable. An automatic line-wraparound feature prints lines with more than 44 characters on two lines. Multiple copies can be printed using carbon or NCR paper. \$399 kit, \$549 assembled.

CIRCLE NO. 95 ON FREE INFORMATION CARD

### JENSEN THREE-WAY CAR SPEAKER

Jensen's flush-mount Triaxial is said to be the only car stereo speaker on the market with a woofer, tweeter and midrange driver in one unit. The woofer is 6" x 9", the 3" midrange is direct-radiating, 2" tweeter is solid state. Rated at 35 watts, the speakers are compatible with 4- and 8-ohm radio or tape units. The kit includes two speakers with 20-oz magnets, grilles, mounting hardware, and connecting cables, at \$114.95.

CIRCLE NO. 91 ON FREE INFORMATION CARD

### GE 40-CHANNEL CB TRANSCEIVER

General Electric's Model 3-5812 40-channel mobile CB transceiver features a warning light that alerts the user that the antenna system needs adjustment. Other features include internal burnt-out protection for up to five minutes of transmission time, switchable noise blanker, ANL, delta tuning, PA,



squelch, and modulation indicator. Power output is rated at the 4-watt legal maximum; adjacent channel selectivity is 50 dB at  $\pm 10$  kHz; and receiver sensitivity at 0.5  $\mu$ V. Measures 8"D x 6 1/2"W x 2 1/4"H (20.3 x 16.5 x 5.7 cm). \$174.95.

CIRCLE NO. 96 ON FREE INFORMATION CARD

### CROWN STEREO EQUALIZER

The Crown Model EQ-2 is an 11-band/channel stereo equalizer that provides full equalization from 20 Hz to 20 kHz. Each band features a  $\pm 15$  dB boost or cut capability. The filters are half-octave, constant-bandwidth design, set nominally on octave centers. Each filter has an associated control that allows a



$\pm 0.5$ -octave adjustment of the center frequency. The two channels can be cascaded to produce a full-range, half-octave equalizer. Shelving-type tone controls permit adjusting bass or treble frequency response before detailed equalization. LED clipping-level indicators monitor four critical internal points to signal overloading. Automatic 5-to-7-second muting at turn-on prevents the passing of system turn-on transients to the speakers. Frequency response is 10 Hz to 100 kHz

POPULAR ELECTRONICS

# What you don't hear is as impressive as what you do.

Up to now the most you could expect from a medium-priced cassette deck was rather medium performance. But now there's the RS-630US. The medium-priced cassette deck with high-priced performance.

We started by going to work on the sounds you don't want to hear with any cassette deck. When we finished, we ended up with virtually inaudible wow and flutter (0.09% WRMS). Negligible distortion. Transistorized switching that reduces signal loss. And a S/N ratio where there's practically no room for noise (-63dB with Dolby\* and CrO<sub>2</sub> tape).

That's what you won't hear. What you will hear is a frequency response of 30Hz to 16kHz (CrO<sub>2</sub> tape). That means cymbals, brass and strings will sound crisp, smooth and natural. The reasons: A super alloy tape head formed under intense heat and pressure. As well as high-grade premium transistors.

You can also forget tape hiss. Because we use a two-stage direct-coupled equalizer as well as Dolby.\* So that soft musical passages will remain quiet.

The RS-630US also has highly accurate peak-check meters that let you set the recording levels without the fear of overload distortion. So you get highly accurate recordings. With excellent dynamic range.

There are also dual output level controls. A CrO<sub>2</sub> tape selector switch. A lockable pause control. And Auto-Stop at the end of the tape in both record and playback modes.


So if you've been looking for a cassette deck with outstanding performance, audition the RS-630US. It only sounds expensive.

\*Dolby is a trademark of Dolby Laboratories, Inc. Cabinetry is simulated wood.

## Technics

by Panasonic

CIRCLE NO. 61 ON FREE INFORMATION CARD

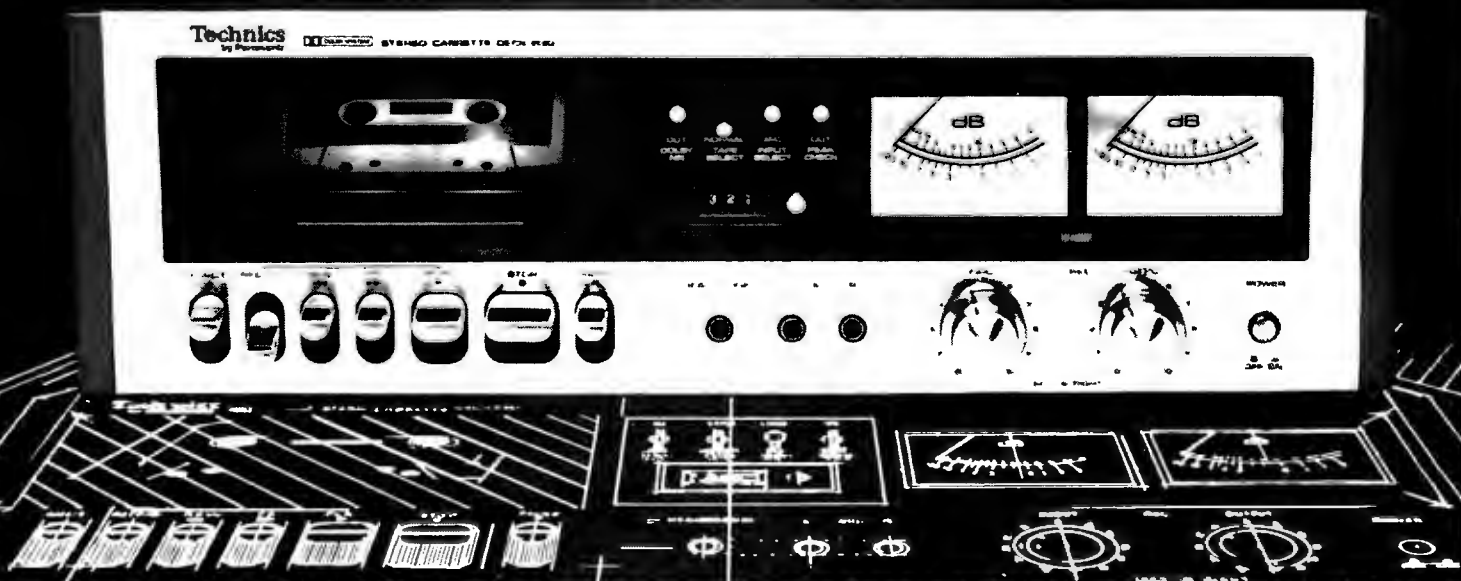

# VALUE & PERFORMANCE

EICO's 30 Years Experience  
Assures More Electronics Value  
For Your Money!

## TEST INSTRUMENTS



### EICO 388 COLOR BAR GENERATOR

Pocket-size, battery operated with LED Indicator. MOS LSI IC provides 9 digitally controlled, stable patterns. Crystal controlled chroma and timing oscillators. Simply connects to TV's VHF antenna terminals.

**Wired \$89.95**


### EICO 390 FUNCTION/SWEEP GENERATOR

Outstanding features include: Sine, Square, Triangle Waveforms; 2 Hz to 200 KHz frequency range; Linear and Log Sweep; Calibrated attenuator, VCO for External Frequency Control; BNC Front Panel Output.

**Wired \$169.95**

## EICOCRAFT™ IC KITS

### EC-5000 SCA ADAPTOR KIT ONLY \$12.95

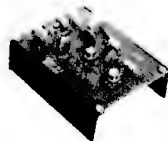


Convert your FM radio or receiver to pick up the official FCC-licensed background music service (SCA). IC decoder/adaptor permits hearing uninterrupted, commercial-free music broadcast by many FM stations (For personal, non-commercial use only).

### IC PROJECT KITS NOW AVAILABLE

EC-5100 ESP Tester \$10.95  
EC-5200 "Decision Maker" \$9.95  
EC-5400 Stereo Power Amplifier \$10.95  
EC-5500 Stereo Pre-Amp \$9.95  
EC-5600 Electronic Lock \$11.95  
EC-5700 Universal Power Amp \$8.95

## BURGLAR/FIRE ALARMS

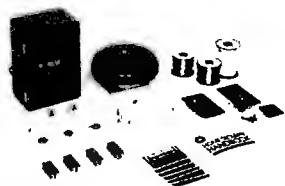

### SS-500 BURGLAR/FIRE ALARM SYSTEM

Professional Security System designed for easy do-it-yourself installation. Features EICO FC-100 Control Center with AC/DC automatic transfer to battery operation. Complete system includes Installation Handbook. Add additional sensors, bells, to suit your own needs. **\$159.95**

### SD-75 BATTERY OPERATED FIRE/SMOKE ALARM

Ionization-type detector gives earliest possible fire warning. Mounts directly to ceiling with 2 screws. "Beeps" when battery needs replacement. U.L. listed. **\$39.95**

## CB ACCESSORIES



### EICO 700 CB FREQUENCY COUNTER

Compact in-line mobile frequency counter for the serious CB'er/Hobbyist. Operates automatically on transmit. 10 Hz to 30 MHz. **\$99.95**

### EICO LR-3 "LONG RANGER" INLINE PREAMP

Bring in those distant/weak signals. Boosts receiver sensitivity up to 20 db. Automatic transmit/receive switching. **\$29.95**

### EICO CM-2 "CHANNEL MONITOR" AUTO-SWITCH

Automatically silences car radio when CB call is received/transmitted. **\$29.95**

## HOBBY/AUTOMOTIVE



### BW-300 ALPHA BRAINWAVE MONITOR

Lowest cost, battery operated, professional Biofeedback System. IC Circuit design features an active filter and 5-microvolt sensitivity. Complete with stethoscopic earphone, electrode headband and instructions.

**Kit \$34.95 Wired \$59.95**

### 885 "TUNEMASTER" ENGINE ANALYZER

Automatic all-in-one test bench for all 6 or 12 volt ignitions—conventional or transistorized. Giant 6" meter with 6 color coded scales. Complete with tune-up and trouble-shooting manual.

**Wired \$59.95**

## FREE EICO CATALOG

The more you know about electronics, the more you'll appreciate EICO. Every EICO product is designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"BUILD-IT-YOURSELF" and save up to 50% with our famous electronic kits.

For the latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO-283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative  
electronics since 1945.



±0.3 dB; 20 Hz to 20 kHz ±0.1 dB. Measures 19"W x 14½"D x 7½"H (48.3 x 36.8 x 19 cm). **\$899.**

CIRCLE NO. 97 ON FREE INFORMATION CARD


## RAIDER ROOF-TOP CB ANTENNA

Designed for permanent installation, the Model 700 roof-top antenna from Raider is for pickup trucks, station wagons, campers, recreational vehicles and standard passenger cars. The snap-in mount provides support for the antenna, which is said to be largely unaffected by high wind velocities. The only tools required for installation are an electric drill with a ⅜" bit, adjustable wrench, and a pair of wire cutters. The 700 comes with a stainless-steel whip, chrome-plated shock spring, or snap-in mount, and 17 feet of coaxial cable with a standard PL-259 plug at one end. **\$19.95.**

CIRCLE NO. 98 ON FREE INFORMATION CARD
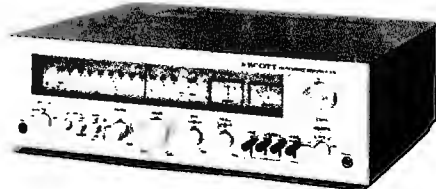
## SCOTT STEREO RECEIVER

Scott's new medium-price Model R336 AM/stereo FM receiver, features clutched bass and treble controls. Rated at 42 watts per



channel with less than 0.3% THD, the receiver has less than 0.15% IM distortion. The receiver features two independent tape monitors, signal-strength and center tuning meters, and a three-position FM deemphasis switch. **\$400.**

CIRCLE NO. 99 ON FREE INFORMATION CARD

## EDSYN DESOLDERING TOOL

The "Silverstat Soldapult" from Edsyn is a manual desoldering tool said to protect sensitive FET and MOSFET devices from failure due to static electricity, while isolating the operator from a direct short. The tool is a hand-held spring-loaded vacuum device with fully enclosed loading shaft, high/low vacuum adjustment, and fast bayonet-type disassembly. A conductive plastic tip and barrel housing is said to allow any built-up static charge to drain off harmlessly through the hand to ground.

CIRCLE NO. 100 ON FREE INFORMATION CARD

## ONEIDA COLOR PICTURE TUBE RESTORER

From Oneida, the Nu-Color restorer is said to restore all needed colors to old color picture tubes. The restorer plugs into most 70° and 90° picture tubes and has separate slide-potentiometer adjustments for the three colors. The original color strength is restored through "boosted and individual biasing networks that increase emission and maintain constant color levels." Two models (70A and 90A) accommodate most 12" (30.5-cm) through 25" (63.5-cm) color picture tubes. **\$24.95 each.** Address: Oneida Electronic Mfg., Inc., Meadville, PA 16335.

# news

## HIGHLIGHTS

### Semiconductor Industry Booms

Sales of consumer electronics products reached approximately \$10 billion in 1975. According to a report by the Business Communications Company, \$2.5 billion of these sales came from a new group of products that include CB radios, scanners, hand-held calculators, wide-screen TV and telephone answering devices. Tied to the rapidly changing lifestyle of the typical consumer, this new group is expected to become a \$7.7 billion market by 1980, reaching \$13.5 billion by 1985.

### Solar-Powered Calculator

Royal Solar I, a solar-powered hand-held electronic calculator, has been introduced by Litton Industries. The pocket-size unit operates without conventional batteries, recharging itself continuously when exposed to artificial light or sunlight. It uses 46 miniature solar cells on its surface. The display is a liquid crystal device with 8-digit capacity, signs for memory usage, minus sign and capacity overflow. It is expected to retail for \$99.95.

### Direct-to-Disc LP's

"Direct-to-disc" phono albums are being made available by Audio Technica. Unlike conventional LP's, direct-to-disc records bypass the tape recording stage of production. Studio performances are mixed and recorded directly onto a master disc, eliminating the problems of tape noise, distortion and limited dynamic range. The albums, available under the "Umbrella" label, will retail at \$12.95.

### 1 × 2 Callsigns

The FCC has announced an amendment to its Rules to permit the issuance of specific 1 × 2 callsigns (callsigns with one letter, one digit and two letters) in the Amateur Band, with suffixes beginning with the letter "X" or prefixed by the letter "N." These will be available to eligible Amateur Extra Class applicants.

### E.I.A. Activities

The EIA has spoken out against proposed legislation by Congress to form a new Federal agency to act as consumer advocate in all types of consumer action. The Consumer Electronics Group of the EIA questioned the need for this proposed agency as costly and unnecessary with the potential for creating problems for both business and the consumer. The threat of a presidential veto caused sponsors to drop the measure for the present. However, revised legislation is expected to be introduced in the future.

The American National Metric Council recently formed to study metrication and start a "think metric" program in the United States has named the EIA as secretariate to its Electronic Equipment and Components Sector Committee.

### 3-D Television

Three-dimensional television is no longer a science fiction writer's fantasy. A method of wide-screen 3-D video projection, developed by Bruce D. Stephens, a television producer and consultant, enables stereoscopic presentations of live or prerecorded television programming with the image size and width of a wide-screen motion picture. As is required of all stereoscopic methods, the left and right eye orientations of the same scene must be segregated and assigned to the appropriate eye of each observer. In this technique, the two differing orientations are projected through a polarizer and re-directed toward the screen so they are superimposed. "Polalite" viewing spectacles allow each eye to see only the viewpoint intended for it, resulting in full depth perception. Motion picture 3-D presentations used this principle in the past.

### Kirlian Photography Debunker

Kirlian photography—recording on film the aura emanating from a human body—is said to be due to an electrical phenomenon related to the amount of moisture in the skin, according to researchers in *Science*. Some had purported that the brightness of an aura, as depicted in a Kirlian photograph, reflected one's mental and physical health. Researchers have found that the amount of water in the skin determines the size and brightness of the aura recorded on film. The dryer the skin, the brighter the aura. The moisture is said to be transferred to the film, changing the electrical discharge pattern that is triggered by the metal plate under the film.

### Holiday Inns' CB Network


Holiday Inns has announced plans to provide a nationwide citizens band network to assist motorists who need road information or help due to mechanical breakdown. The program is currently being tested among 15 Holiday Inns in the Boston area. Also being studied is an arrangement set up by the Maryland State Troopers in cooperation with that state's department of tourism, where a separate channel has been reserved for dispensing road information. This eliminates most of the interference and interruptions that occur on the regular channels.

### Hams to Sail

Licensed hams will be able to operate a high-power amateur station on board the *Santa Mercedes*, during a 56-day cruise offered by Prudential Lines. Departing from San Francisco April 26 (from Los Angeles April 28) the ship will cruise to Mexico, the Caribbean and completely around South America. Instruction in code classes and license upgrading will be available along with a variety of social activities. For additional information write: Prudential Lines, One California Street, San Francisco, CA 94111.

# The phono cartridge that doesn't compromise any modern record.

## AT15Sa

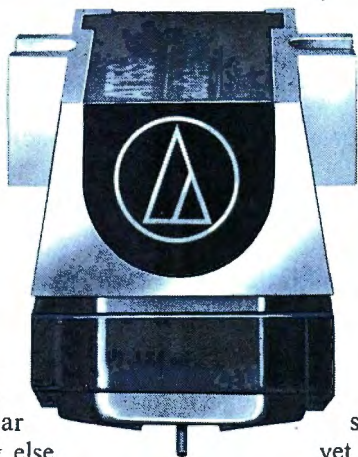

Choosing an AT15Sa can add more listening pleasure per dollar than almost anything else in your hi-fi system. First, because it is one of our UNIVERSAL phono cartridges. Ideally suited for *every* record of today: mono, stereo, matrix or discrete 4-channel. And look at what you get.

Uniform response from 5 to 45,000 Hz. Proof of audible performance is on an individually-run curve, packed with every cartridge.

Stereo separation is outstanding. Not only at 1 kHz (where everyone is pretty good) but also at 10 kHz and above (where others fail). It's a result of our exclusive Dual Magnet\* design that uses an individual low-mass magnet for each side of the record groove. Logical, simple and *very* effective.

Now, add up the benefits of a *genuine* Shibata stylus. It's truly the stylus of the future, and a major improvement over any elliptical stylus. The AT15Sa can track the highest recorded frequencies with ease, works in

\*TM. U.S. Patent Nos. 3,720,796 and 3,761,647.

any good tone arm or player at reasonable settings (1-2 grams), yet sharply reduces record wear. Even compared to ellipticals tracking at a *fraction* of a gram. Your records will last longer, sound better.



Stress analysis photos show concentrated high pressure with elliptical stylus (left), reduced pressure, less groove distortion with Shibata stylus (right).

The AT15Sa even helps improve the sound of old, worn records. Because the Shibata stylus uses parts of the groove wall probably untouched by other elliptical or spherical styli. And the AT15Sa Shibata stylus is mounted on a thin-wall *tapered* tube, using a nude *square*-shank mounting. The result is less mass and greater precision than with common round-shank styli. It all adds up to lower distortion and smoother response. Differences you can hear on every record you play.

Don't choose a cartridge by name or price alone. Listen. With all kinds of records. Then choose. The AT15Sa UNIVERSAL Audio-Technica cartridge. Anything less is a compromise.

## audio-technica

INNOVATION □ PRECISION □ INTEGRITY

AUDIO-TECHNICA U.S., INC., Dept. 27P, 33 Shiawassee Ave., Fairlawn, Ohio 44313

CIRCLE NO. 69 ON FREE INFORMATION CARD



## New Literature

### ELECTRONIC PROJECT CATALOG

Graymark Enterprises offers a catalog listing over 50 electronic projects and 1000 electronic components. Among the items listed are a strobe light, color organ, metal detector and amplifier. Address: Graymark Enterprises, Box 17359, Irvine, CA 92713.

### DIGITAL INSTRUMENT CATALOG

An 8-page catalog entitled "Digitals" covers a wide variety of digital instruments ranging from programmers, digital clocks, a digital clock/thermometer and timers, to digital frequency counters. Each instrument is illustrated and complete specs are provided. Address: ESE, 505½ Centinela Ave., Inglewood, CA 90302.

### BUYER'S GUIDE TO MULTIMETERS

A new brochure from Amprobe Instrument, "Buying One of the More Popular VOM's," describes features and applications of comparable VOM's from three major manufacturers. The brochure includes specification information on resistances, ac and dc current, temperature, sensitivity, fuse protection, ranges, dimensions and standard accessories. Address: Amprobe Instrument Div. of SOS Consolidated, Inc. 630 Merrick Rd., Lynbrook, NY 11563.

### EDMUND CATALOG

Edmund Scientific's new 164-page catalog, #771, contains over 4500 items for experimenters, students and hobbyists. Among the many items described are an ultraminiature AM radio that measures only 1 11/16" x 1 3/16" x 11/16"; solar collector panels for house and water heating; and Biosone II, an alpha/theta monitor that identifies electrochemical activity in the human body. Address: Edmund Scientific Co., 380 Edscorp Bldg., Barrington, NJ 08007.

### DATA COMMUNICATIONS BULLETIN

A new, 5-page bulletin from Tele-Dynamics describes its line of data communications equipment, including modems, acoustic couplers, frequency division multiplex subsets and test equipment. Each product is illustrated and specifications and applications information are provided. Also included is a section on available accessories. Address: Tele-Dynamics Division of AMBAC Industries, Fort Washington, PA 19034.



# Stereo Scene

By Ralph Hodges

## HALLOWEEN AT THE WALDORF

**N**EW YORK'S annual Audio Engineering Society convention (held at the Waldorf Astoria) generally falls on and around October 31. Since the business of this distinguished gathering is to exchange tricks and (one hopes) treats, the date is highly appropriate.

I had hoped in this single column to cover most of the highlights of the 1976 convention. As things have turned out, I've barely found room to deal with three papers out of dozens that were presented. All three do relate to a common subject, however—one that is perhaps especially seasonal because it involves a trick and also a bit of a masquerade.

**The Ultimate Illusion.** Many feel that the ultimate audio illusion—and the final objective of high fidelity—is to be able to turn (acoustically) a small room into a large one, a large room into an open-air environment, and an open-air environment back into a small room. As usual, several papers dealing with aspects of this subject were presented. Ignoring the quadraphony papers for the moment (or at least until I understand them), the rest dealt with how the illusion of acoustic space (i.e., large and small rooms, or no room at all) can be *simulated* with the ever-growing resources for signal processing we now have available. "Faking it" in this way bothers some purists, including myself. But it is probably true that if we *can* learn to fake it successfully, we will learn in the process how to design and place microphones so as to properly capture the real thing.

First of all, what makes rooms acoustical entities, identifiable as large or small, dead or bright, when we hear music played in them? Sound reflections reaching us from the room's surfaces, of course. But then, what differences in reflections account for the different sounds of rooms? Depending on the room, reflections differ in their arrival times (how long they take to reach us after the sound coming directly from the musical

instrument is heard), spectral shape (alterations in the reflections' frequency balance), and density (number of reflections heard per unit of time).

To paraphrase Daniel Queen's latest paper (which he did not officially present, but which was available if you cornered him in the corridor and asked for it), arrival times of reflections fall into three categories (see Fig. 1): arrivals within 1 millisecond, those within 65 milliseconds, and those within 1, 2, or even 4 seconds. The 1-millisecond arrivals, if strong enough, are bad: they interfere with our localization of the original sound source (confuse the stereo image, if you will). Arrivals within 1 to 65 milliseconds are generally good; they "fuse" with the direct sound, making it seem louder (however, they also profoundly affect the perceived spectral shape of the sound, which may not always be good). Arrivals after 65 milliseconds can be good or bad; they are perceived as room reverberation detached from the original sound, and they may be heard as a rich afterglow or a ragged string of echoes. As Queen points out, they tend to diminish intelligibility, but they are vital to our appreciation of certain types of music.

Fortunately, arrivals within 1 millisecond are rarely troublesome, because the reflecting surface has to be

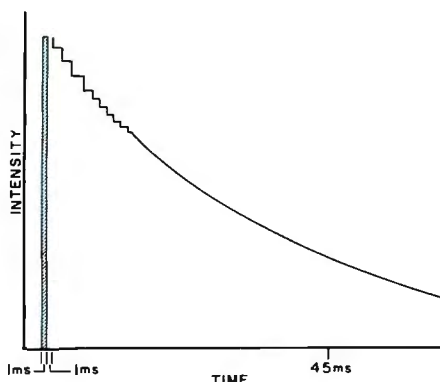


Fig. 1. A 1-ms sonic impulse and its reverberation train.

very close to either the sound source or the listener for them to occur (although the cabinets of some speaker systems provide such surfaces, as do the cases and lids of grand pianos, which can make them exasperatingly difficult to record). Arrivals within 65 milliseconds dominate in small rooms, which is why music sounds so loud in them. But after 65 milliseconds the absorptive materials in the small room have soaked up almost all this reflected sound energy.

In a large room such as a concert hall, a sound may easily have travelled for 65 milliseconds (roughly corresponding to 65 feet) before it undergoes even its *first* reflection from a wall or ceiling. Since it is these "bounces" from walls and ceilings that account for much of the absorption of sound (and in a small room many bounces will take place within 65 milliseconds for all possible sound paths), a concert hall doesn't even begin to assert its absorptive influence until many milliseconds have passed. That is why large auditoriums tend to have such prominent reverberation, and why architects strive so mightily to make that reverberation sound "nice." (This is not to say that concert halls provide the listener *no* reflective arrivals within 65 milliseconds; a good hall provides many, and they are very important.)

**Turning the Trick.** Well, that seems simple (although lengthy) enough. All we need do to turn our pitiful listening rooms into splendid opera houses is to provide reflected sounds persisting longer than 65 milliseconds. And we can provide that (since our rooms cannot) with delayed sounds coming either from distantly spaced microphones (four-channel recordings of the "ambient" type, in other words), or with artificially created delays (tape delays, bucket-brigade or even digital delays, reverberation systems using metal plates, springs, or tiled bathrooms, long cardboard tubes with a speaker at one end and a microphone at the other, almost *ad infinitum*). Hence our resources are vast. Unfortunately, the results achieved with them have been generally disappointing.

Many people have by now heard four-channel stereo or some other technique that attempts to alter acoustical space. Few, I suspect, have ever heard the walls of the listening room seem to disappear, as they should. We admire the ingenuity of the hardware, the onward march of separation figures, and the exquisite construction of the theoretical foundation. We even hear improvement

# Be the “New Professional” in electronics

**CREI trains you at home  
for one of the most important  
career levels in electronics—  
plus offers you special  
arrangements for engineering  
degrees**

Most people think there are only two levels of careers in electronics: the technician level and that of the degree engineer.

There is, however, a third and very important level. It is that of the engineering technician or *practical* engineer. The growing importance of this career level has created what might well be called the “New Professional” in electronics.

If you look at the various levels of employment in electronics, you will understand why this “New Professional” is so important.

The average technician is a person who has had vocational training in electronics. He understands the basic principles of electronics so he can trouble-shoot, repair and maintain equipment. He usually works under close supervision in performing his duties.

The engineer has college training in electronics. He usually supervises technician personnel and is responsible for planning and developing of electronic equipment and systems. Frequently, however, engineers are more heavily trained in the scientific principles of electronics and less in their practical application.

The engineering technician, by contrast, is a specialist in the practical application of electronics. His training usually consists of a two-year college program in electronic engineering technology. In many organizations, the engineering technician handles several of the responsibilities of the degree engineer. He often has the title of engineer.

CREI programs are designed to give you at home the same level and depth of training you receive in a two-year college program in electronic engineering technology. CREI programs are, in fact, more extensive than you will find in many colleges. And CREI gives you the opportunity to specialize in your choice of the major fields of electronics.

## **Unique Design Lab**

CREI gives you both theory and practical experience in circuit design with its Electronic Design Laboratory Program. The professional equipment included in this program allows you to construct, test out and correct the circuits you design until you have an effective circuit.

This Lab Program helps you understand advanced electronics. It also gives you practical experience in many other important areas of electronics, as in pro-

# Career Training at Home

tototype construction, breadboarding, test and measurement procedures, circuit operation and behavior, characteristics of electronic components and how to apply integrated circuits.

Only CREI offers the unique Lab Program. It is a complete college Lab and, we believe better than you will find in most colleges. The "Lab" is one of the factors that makes CREI training interesting and effective. And the professional equipment in this program becomes yours to keep and use throughout your professional career after you complete the training.

## Engineering Degree

CREI offers you special arrangements for earning credit for engineering degrees at certain colleges and universities as part of your home study training program. An important advantage in these arrangements is that you can continue your full time job while "going to college" with CREI. This also means you can apply your CREI training in your work and get practical experience to qualify for career advancement.

## Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

## Free Book

In the brief space here, there isn't room to give you all of the facts about CREI college-level, home study programs in electronics. So we invite you to send for our free catalog (if you are qualified to take a CREI program). The catalog has over 80, fully illustrated pages describing your opportunities in advanced electronics and the details of CREI home study programs.

## Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Send for this **FREE Book** describing your opportunities and CREI college-level programs in electronics



Mail card or write describing qualifications to

**CREI** **CAPITOL  
RADIO  
ENGINEERING  
INSTITUTE**

**McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue Northwest  
Washington, D.C. 20016**

**Accredited Member National Home Study Council**

## GI Bill

*CREI programs are approved for training of veterans and servicemen under the G.I. Bill.*



of sorts in each new generation of equipment. But we rarely, if ever, cross the threshold into a shift of perceived reality. The trick just doesn't get turned.

**Heroic Measures.** The shortcomings of these techniques have been acknowledged reluctantly (if at all) by the audio industry. But behind the scenes researchers have been occupied with them all the same. The main approach, if I may crudely generalize, has been a complicated and taxing game of "find the flaw"—explain why a system that seemingly should work doesn't.

It's good to see the opposite tack being taken at last; that is, the tack of creating something that does work, no matter what, and finding out why, rather than starting with something that doesn't work (too well, anyway) and attempting to discover why not. Two papers presented at the convention appear to adopt this pragmatic approach, taking as their starting points techniques of simulation—that is, their only intent is to deceive the listener with a *seemingly* realistic experience; for the present they are largely content to forget about absolute realism and its pursuit.

Audio/Pulse manufactures a digital reverberation "simulator" that is intended merely to process ordinary stereo programs, with its output ideally appearing at one or more pairs of "rear" speakers, the key pair of which is located to either side and perhaps above and just behind the listener. In a paper prepared by Audio/Pulse's Peter Mitchell and Richard DeFreitas, five "essential characteristics" of concert-hall ambience are laid down, which become five conditions to be met by a successful reverb simulator. In condensed form:

(1) A satisfactory simulator probably doesn't have to provide a duration of reverberation (reverberation time) equivalent to that of a typical concert hall. Instead, it should be able to feed off whatever reverberation has been captured in the recording to prolong the reverberation time.

(2) The spectral shape of the reverberant energy will inevitably be altered by the hall in which the music is played. The playback system should copy this spectral change, but it is not the function of the reverberation simulator itself to supply this equalization; nor should it.

(3) The simulator should be capable of closely approximating the arrival-time density of concert-hall reverberation. This density tends to be high.

(4) So far as is possible, the simulator should provide arrival times that are ran-



*Fig. 2. The Acoustic Research Digital Time Delay System, showing six of the sixteen speaker channels and a side view of electronics.*

domly spaced. Regularly spaced arrivals cause effects such as "flutter echo."

(5) In a concert hall, the reverberant field can't be localized and is diffuse. The simulator's artificial field should have the same characteristics.

As a recipe for a successful reverb simulator (and the Audio/Pulse device has been shown to be capable of successful spatial illusions in several demonstrations), the above five points are gratifyingly straightforward. If we examine current four-channel systems in their light, several points stand out right away. For one thing, the usual rear-channel content of an ambient four-channel recording is merely a more distant miking of what the front channels reproduce. It is localizable in most cases, although localization is diminished somewhat by distance, and fixed microphone spacing and the nature of certain microphone arrays may prevent it from being sufficiently random in arrival times. Does this point the way to any new procedures for quadraphonic recording? Your guess is as good as mine.

**AR's Acoustic Arena.** Recent work at Acoustic Research has led to an especially interesting research tool for ambience experiments: a sixteen-channel concert-hall simulator (Fig. 2). This may recall Bolt Beranek & Newman's concert-hall simulator, which I described in this column almost two years ago. However, while BB&N's system derives signals from tape delays and reverb chambers, the AR configuration employs simple digital delays determined by a study of computerized models of real acoustical spaces.

To judge from a paper (by Paul Milner) distributed by AR at the AES convention, the AR experiments are beginning to bear fruit in determining the *minimum* and perhaps even *optimum* re-

quirements for creating a spatial illusion. Milner used a six-channel system for his listening tests, with various combinations of simple fixed delays being fed to the four "rear" loudspeakers. By inference, the result was a satisfactory spatial effect. Then Milner progressively narrowed the frequency band over which the delays occurred, to learn at what point the spatial illusion would start to deteriorate. In other words, all four "ambience" speakers always reproduced a full-range signal, but the frequency band over which these signals underwent delays was increasingly narrowed. Outside of the delay band, the signal was not delayed.

Without going further into Milner's procedures, we can tackle the results (gleaned from the statistically analyzed impressions of a small listening panel) right away. They were that, below about 200 Hz, delaying the signal did little or nothing to enhance the spatial illusion. Likewise, eliminating delays above 6 kHz harmed nothing and in some cases improved conditions for certain listening positions in the room where long-delayed sharp transients would otherwise confuse localization.

For a digital delay system, such limiting of the delay bandwidth would bring very attractive reductions in the cost of each channel. And the apparent unimportance of processing frequencies below 200 Hz opens the door to a common bass system instead of full-range speakers for each channel.

These findings have been anticipated by others in the past, but never so well documented under real music-listening conditions. Put the AR results together with those of Audio/Pulse and you may see the emergent beginnings of a truly effective spatial-illusion system—perhaps even a genuine four-channel system—somewhere around the corner. ◇



## Audio Reports

### TAPE RECORDER HEADROOM EXPLAINED

**A**LTHOUGH the term "headroom" is frequently used in connection with tape recorders, it is not specifically defined by any single measurement standard. Nevertheless, it is one of the most important characteristics of a tape deck (actually more important in most cases than frequency response) and its significance must be appreciated if one is to realize the machine's potential.

Every tape recorder has some form of recording level indicator, usually a pair of meters that show the level in each channel and occasionally these are supplemented by a single fast-responding LED indicator that flashes on high-level peaks that are too brief in duration to register on the meters. The relationship between these two levels—the meter reading and the instantaneous peak—is closely connected with the concept of headroom and is the reason for its importance.

The level meter usually indicates the signal voltage present at some part of the recording amplifier. Depending on the characteristics of the recording head and the tape for which the machine is adjusted, the calibrated 0-dB meter level corresponds to some specific flux density recorded on the tape. Each manufacturer is free to choose his own "zero level," although there are several standard levels used in professional machines and some home recorders.

Flux levels are expressed in nanowebers per meter (nW/m) of tape width. The actual number of flux lines is of little importance to the user. Doubling the width of the recorded track on the tape doubles the number of flux lines passing the playback head gap during a given linear tape movement, which in turn doubles the output voltage from the head. This is the reason for the superior signal-to-noise (S/N) ratio of wider tape formats (e.g., half-track versus quarter-track, or any of the 1/4" tape formats versus cassette tape).

A given tape formulation can be magnetized only up to a certain point before its magnetic coating begins to saturate. Beyond this point, a further increase in recording level does not produce a proportional increase in tape magnetization (and, correspondingly, in playback output). This affects the playback signal in two ways. First, the dynamics of the program are compressed, since a program peak that drives the tape into saturation does not produce more output during playback than a lower level portion of the pro-

gram. Secondly, the distortion of the playback signal increases.

Although the magnetic storage ability of a tape is a function of frequency, we can simplify this discussion by assuming that the tape response is uniform across the audio band. Because of the recording head characteristics, however, it is usually necessary to preemphasize or boost the higher frequencies during recording to obtain a flat playback frequency response. Thus, the maximum tolerable level before which saturation occurs will decrease as the frequency increases. Since this effect becomes more severe at lower tape speeds, a cassette recorder is inherently inferior to an open-reel recorder in its ability to record high levels without saturation, especially at high frequencies.

Now let us return to that recording level meter, whose 0-dB mark supposedly indicates the maximum permissible recording level. It does, but that level is not the same for all machines. Ordinary meters respond relatively slowly to brief transients and may not give any indication on a peak that far exceeds the tape saturation level. Music and voice program material may have instantaneous peaks from 10 to 20 dB greater than their average levels as indicated by a typical level meter. For most amateur recording purposes, the lower figure is probably more realistic, especially if the program has already been recorded or broadcast, in which case its peaks have already been limited.

Suppose that a recorder's meters have been calibrated to indicate 0 dB when the signal is 5 dB lower than the low-frequency saturation level, which is usually considered to be the level that produces 3% distortion in the playback output. If the average level indicated by the meter is about -5 dB, one can reasonably expect to make a recording without serious peak compression, assuming a 10-dB peak/average ratio. In fact, one can often operate even closer to the 0-dB mark on such a machine (which is typical of many cassette recorders) without serious loss of quality. The headroom of this hypothetical recorder, at low and middle frequencies, is 5 dB. It is the difference between the indicated maximum recording level and the point where tape saturation occurs.

But what about the high frequencies, which are boosted during recording? Obviously, they will saturate with a lower input level than the low and middle

frequencies. Because of this, tape recorder frequency response is measured at a reduced input level, usually -10 to -15 dB for open-reel machines and -20 dB for cassette recorders. A cassette recorder that gives a flat record/playback frequency response at -20 dB will have a marked loss of high frequencies in playback if the recording is made at 0 dB. Our test reports show both curves, giving some idea of the loss of high-frequency headroom, which is largely a function of the design of the recording head as well as of the tape characteristics.

Although each recorder manufacturer selects his own 0-dB level, many use the so-called "Dolby level" of 200 nW/m for cassette recorders. If all recorders used this level as a 0-dB reference, it would be easy to compare their midrange headroom. However, in the design of a recorder, there are trade-offs between frequency response, distortion, and S/N ratio, with each manufacturer selecting his own criteria. If the 0-dB level is set higher than 200 nW/m, the apparent S/N compared to a 0-dB level is increased. This is only "apparent" because the true S/N rating should be referred to the level giving 3% playback distortion instead of to the recorder's 0-dB reference. Since such a recorder will distort with only a slight overload, the user will speedily learn to keep his average recording level around -10 dB, which points up the fallacy of trying to "extend" dynamic range in this way.

The opposite effect occurs when the 0-dB point is set at a lower flux level, as in the Pioneer Model CT-F8282 reviewed this month. Pioneer has made 0 dB correspond to 160 nW/M, which is about 3 dB below the Dolby level. In effect, this gives an extra 3 dB of

apparent headroom over the recorder's zero level before the reference distortion level is reached. When the total frequency-response characteristics of the machine are studied, it can be seen that Pioneer has not attempted to extend the high-frequency response beyond the 13,000-to-15,000-Hz range. Instead, the recording equalization and bias have been matched to the head characteristics to give a rather good high-frequency headroom characteristic so that a strong response is maintained to 10,000 Hz or beyond, even at 0 dB. This makes the published specifications less impressive than they might have been, but it results in cleaner, less compressed recordings. There is little or no audible loss from the attenuation of frequencies beyond 13,000 Hz or so, and the quality improvement from the headroom increase is much more likely to be heard and appreciated by the user.

To interpret our test data on cassette recorders (the same thing applies, to a much smaller degree, to open-reel machines), look at the S/N ratio referred to the 3% distortion level and the meter reading corresponding to that level. This will reveal, in a rough way, how high the average recording levels can be set to realize the full dynamic range of the machine. Then, look at the 0-dB and -20-dB frequency-response curves to see how much distance there is between them, and if and where they intersect. Most machines have an intersection of these curves between 12,000 and 18,000 Hz but some have curves that never intersect. The greater the gap between the two curves, and the higher their intersection frequency, the better the headroom.



## PIONEER MODEL CT-F8282 CASSETTE DECK

*Front-load deck features operating simplicity and solenoid controls.*



Pioneer's Model CT-F8282 front-loading cassette deck has a two-motor, solenoid-

operated tape transport, with a servo-controlled dc-motor capstan drive. A separate high-torque dc motor operates the tape hubs in fast-forward and rewind. The transport controls are short levers that extend horizontally from the front panel below the cassette well.

They operate with a very light touch, since they merely energize the solenoids that perform the actual mechanical and electrical switching operations. The levers can be operated in any sequence, without going through STOP, obviating the risk of damaging the tape. A separate PAUSE switch is located to the right of the control levers. The deck can be set up in advance for unattended recording or playback, and will go into operation when power is applied by an ex-

ternal timer switch. It shuts down mechanically and disengages the heads when the tape ends.

The styling of the cassette deck matches other Pioneer components. The control panel and controls are satin-finished aluminum, and the wooden case is finished in walnut-grain vinyl. The deck measures 17 $\frac{3}{4}$ "W  $\times$  13 $\frac{1}{2}$ "D  $\times$  7 $\frac{5}{8}$ "H (45  $\times$  34.3  $\times$  19.4 cm) and weighs 27 lb (12.3 kg). \$400.

**General Description.** The cassette is installed vertically through a large opening in the front panel and can be covered by a swing-down clear-plastic window. Unlike other cassette decks, this one does not have an EJECT lever. Instead, with the tape stopped (even in the PAUSE mode) the cassette is simply pulled off the drive hubs and removed by hand. This is just about the simplest and easiest withdrawal system we have seen. It leaves the cassette completely visible while it is in the machine. The re-

cord/playback and erase heads feature ferrite construction.


To the right of the cassette well, the upper portion of the control panel contains two large illuminated level meters that are calibrated from  $-20$  to  $+3$  dB, the latter indicated as the Dolby level for calibration purposes. During playback, the meters show the level actually present at the LINE outputs and are controlled by the OUTPUT level controls. Between the meters, a red LED indicator comes on when the deck is in the RECORD mode and another flashes when program peaks reach  $+5$  dB to warn of potential distortion from over-recording.

Below the meters are a three-digit index counter and four pushbutton switches. One switch activates the MEMORY REWIND feature, stopping the tape in REWIND when the index counter returns to a previously set 000 reading. Another turns on and off the DOLBY system, and an indicator light above the button. The remaining switches are labelled BIAS and EQ, with STD settings for high-performance ferric-oxide tapes and  $\text{CrO}_2$  settings for chromium-dioxide tapes or the cobalt-treated equivalent tapes, such as TDK SA and MAXELL UD-XL II. When both buttons are depressed, a  $\text{CrO}_2$  indicator above them lights. For recording on ferrichrome tapes, the STD bias and  $\text{CrO}_2$  EQ settings are used;  $\text{CrO}_2$  EQ should be used for their playback. A chart in the instruction manual suggests switch settings for most popular tapes.

Below the pushbutton switches are concentric INPUT level controls for the two channels and another concentric pair of OUTPUT playback level controls. At the right side of the panel are two  $\frac{1}{4}$ " (6.35-mm) MIC and PHONES jacks. At the lower left of the panel is the pushbutton POWER switch.

On the rear panel of the deck are the input and output phono jacks, a DIN socket, and a switch that connects the recording inputs to either the phono jacks or the DIN socket. The DIN switch also inserts a 10-dB attenuator in the recording inputs and can be used when high-level output microphones are plugged into the front panel jacks (replacing the LINE inputs with the MIC signals) to prevent overloading the input stages. There is also a single unswitched ac outlet on the rear panel.

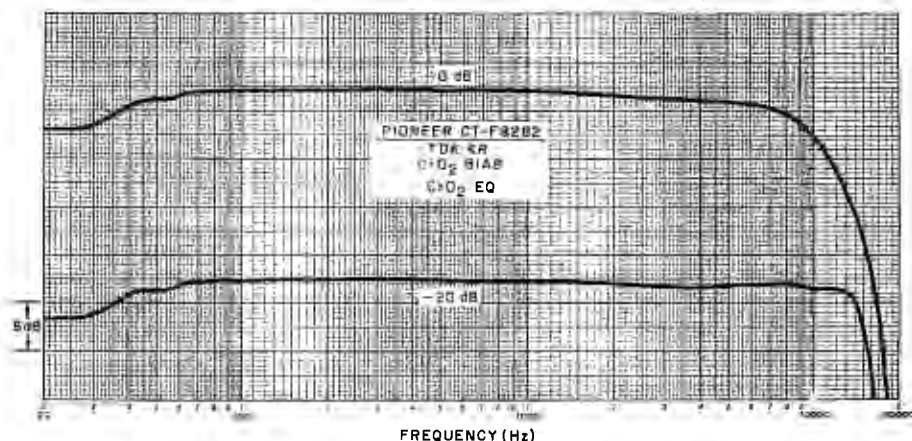**Laboratory Measurements.** Although the instruction manual suggests control settings for many tape types, there was no indication of which specific tapes had been used at the factory for



*Response with TDK KR tape using  $\text{CrO}_2$  bias and equalization.*

bias adjustments. Therefore, we measured the record/playback frequency response with a number of high quality tapes, including TDK Audua, SA, and KR ( $\text{CrO}_2$ ), Maxell UD-XL I and UD-XL II, Scotch Master, and two ferrichrome tapes, Scotch Classic and Sony FeCr.


The response varied little among the several ferric-oxide tapes, but TDK Audua seemed to yield a bit better high-frequency response and was chosen for further tests with the STD bias and EQ settings.

The TDK SA and Maxell UD-XL II tapes gave identical responses, but TDK KR gave the flattest overall response and was used with the  $\text{CrO}_2$  bias and EQ. The Sony FeCr gave good results with the recommended FeCr settings, but Scotch Classic exhibited the loss of high frequencies, which we have observed in machines that have been biased for the Sony tape. Playback frequency response was measured using the new TDK AC-331 test tape for STD (120  $\mu\text{s}$ ) equalization, and with a Teac tape for  $\text{CrO}_2$  (70  $\mu\text{s}$ ) equalization.

The playback equalization was accurate with both switch settings, varying less than  $\pm 1$  dB over the 63-

to-10,000-Hz range of the TDK tape and between  $+1.5$  and  $-3$  dB over the 40-to-10,000-Hz range of the Teac tape. Most of the variation in both cases took place below 100 Hz. The record/playback response with TDK "Audua" tape was flat within 0.5-dB overall from 60 to 8000 Hz, dropping off to  $-3$  dB at 35 and 12,000 Hz. Overall, the variation was  $\pm 3$  dB from 20 to 13,500 Hz. TDK KR tape gave an almost ruler-flat response of  $\pm 1$  dB from 37 to 13,500 Hz and  $\pm 3$  dB from 20 to 15,000 Hz. The other tapes were generally similar to the TDK Audua in their response, with the output sloping off gently above 10,000 Hz and more rapidly above 13,000 Hz.

For a recording level of 0 dB, an input of 57 mV was required at the LINE inputs and 0.14 mV at the MIC inputs. The MIC circuit overloaded at a fairly safe 105 mV, which could have been increased to more than 300 mV with the DIN switch. The maximum output level from a 0-dB recording was between 0.6 and 0.75 volt, depending on the tape used. With the OUTPUT control set for a 0-dB meter deflection, the output was 0.5 volt. The PEAK indicator flashed at exactly  $+5$  dB, with an abrupt switching characteristic

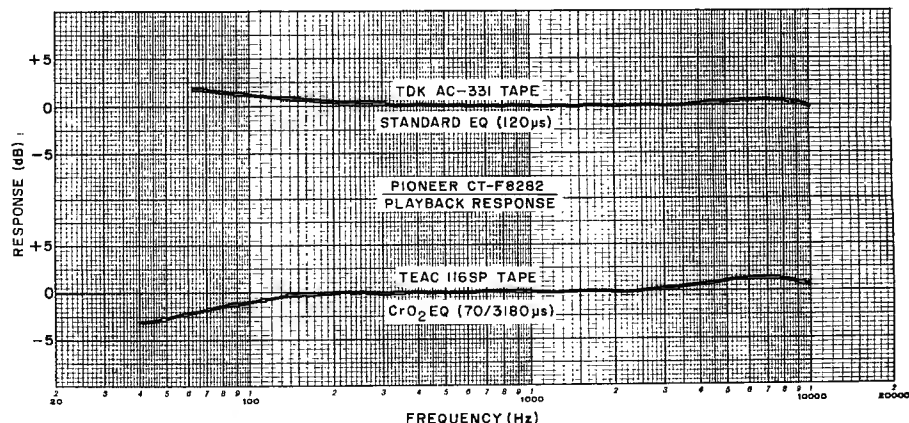

*Playback response with two tapes at different equalization settings.*

that eliminated the ambiguity sometimes associated with LED-type peak indicators. The meter ballistics were slightly underdamped, giving a 2-dB overshoot with 0.3-second tone bursts. The cross-talk from track 2 to track 1 at 1000 Hz, measured with a TDK AC-352 test tape, was -40 dB.

At a 0-dB recording level (3 dB below the Dolby standard level of 200 nW/m), the harmonic distortion on playback was a very low 0.5% with TDK KR, about 0.9% with TDK Audua, and 1% with TDK SA tapes. The distortion increased gradually up to +5 dB, where it was respectively 0.9%, 2%, and 0.9%. To achieve a 3% playback distortion level, we had to record at +7 dB with Audua, +8 dB with KR, and +8.5 dB with SA tapes. These levels are far off scale on the meters giving the assurance that, so long as the PEAK indicator does not flash more than occasionally, the distortion should be negligible.

The S/N ratio was checked with the three tapes with and without Dolby and unweighted and with IEC "A" and CCIR weighting. The unweighted S/N, referred to the 3% distortion level, was 48 dB with Audua and 54 to 55 dB with the KR and SA tapes. Using "A" weighting and the Dolby system, the S/N was 61.5 dB with Audua and 63 to 64 dB with the other tapes. Using Dolby's preferred CCIR weighting, these figures were improved by 0.5 to 1.5 dB. Through the mic inputs, at maximum gain, the A-weighted noise level increased by 10 dB, but at normal settings of the gain control the increase was much less. On our test unit, the Dolby circuit "tracking" error at a

-20-dB level caused a dip of about 5 dB in the response in the 3000-to-6000-Hz range. At other recording levels, this effect was much less.

The wow was 0.02%, which is approximately the residual of the test tape and flutter (unweighted rms) was 0.1%. In a combined record/playback measurement, the results were identical.

In the fast-forward and rewind modes, a C-60 cassette was moved from end to end in 59 seconds.

**User Comment.** The "human engineering" that went into the design of the deck makes it very easy to use, especially since there is almost literally nothing one can do to operate it improperly, other than selecting the incorrect bias or equalization. Tape loading and removal procedures are ideal for eye-level operation and nearly as good at waist level. We appreciated not having the cassette pop out noisily as it does on some tape decks, and its insertion and removal are as simple as reaching into the roomy compartment and grasping the sides of the cassette. In addition, the transparent cover allows the exact playing status of the cassette to be seen at a glance, including how much tape remains to be played.

Even though most solenoid-operated tape transports use pushbuttons of one type or another to energize the solenoids, the lever system on this deck is equally convenient to use, with the advantage that the levers remain mechanically depressed after they are pushed. Hence, the operating status of the machine can be seen without re-

course to signal indicators. The very light finger pressure required to operate the levers is an immediate "giveaway" to their electromechanical operation. Another nicety, which we have not seen on many recorders, is the access hole in the cassette head cover for azimuth alignment.

Although, technically speaking, the published record/playback frequency response ratings of the deck were met in our tests, it is clear that the response beyond 13,000 Hz has been slightly sacrificed in favor of low distortion and improved high-frequency "headroom." From the user's point of view, this is the proper compromise to make (and some compromise is always necessary in designing a cassette recorder) since frequencies beyond 13,000 Hz are rarely present in the program material. Their absence will rarely be noticed, whereas distortion, noise, and high-frequency tape saturation will. This deck has above-average performance in each of these respects.

The meters read line output levels in playback, rather than showing the playback level ahead of the OUTPUT control as in most recorders. Also, the usual Dolby level of 200 nW/m as a 0-dB reference is not employed. Pioneer uses -3 dB, or 160 nW/m. These criticisms, to be sure, are minor and do not in any way detract from the fact that the Pioneer CT-F8282 is a fine-sounding, easy-to-use, and handsomely styled tape deck. In the popular-price range (for top-quality two-head machines), the deck compares favorably with any competitive decks in sound and performance.

CIRCLE NO. 102 ON FREE INFORMATION CARD

## ACOUSTIC RESEARCH MODEL AR-16 SPEAKER SYSTEM

*Small, 2-way system delivers true bass, smooth middles and highs.*



The Acoustic Research people recently have designed some new speaker systems that supplement, but do not at present supersede the older, well-known AR systems. The smallest and least expensive of the new generation of AR speaker systems is the Model AR-16. This true bookshelf-size two-way system has an 8" (20.3-cm) acoustic-suspension woofer that crosses over at 1300 Hz to a 1" (2.54-cm) dome tweeter. A three-position toggle switch on the rear of the enclosure provides a modest increase or decrease in high-frequency output, relative to the normal or "flat" condition.

The compact speaker system measures 19 $\frac{1}{8}$ "  $\times$  9 $\frac{1}{8}$ "  $\times$  8 $\frac{1}{2}$ " D (50.5  $\times$  25  $\times$  21.6 cm) and weighs 21 lb (9.5 kg). Value is \$115 with walnut-grain veneer, \$99.95 with walnut-grain vinyl.

**General Description.** The AR-16's nominal system impedance is 8 ohms, and efficiency is similar to that of many small acoustic suspension systems. AR rates the speaker system to deliver an 85-dB sound pressure level (SPL) at a distance of 1 meter with 1 watt of drive power. Although it can be used satisfactorily with a 25-watt/channel amplifier, the speaker system is designed to withstand the output of a 100-watt/channel amplifier, driven to clipping 10% of the time with ordinary music program material. According to AR, the free-air resonance of the woofer is 25 Hz, and system resonance is at 55 Hz.

# CB servicing is PROFITABLE with the B&K-PRECISION 40-channel CB Test Bench



MODEL 1040  
\$250

The B&K-PRECISION CB servicemaster is designed for rapid programmed testing and trouble shooting of any CB transceiver—even 40-channel models!


**When used with a scope and signal generator, you can:**

- Measure signal-to-noise ratio of CB receiver
- Measure audio output power
- Measure audio distortion percentage
- Measure receiver sensitivity
- Check AGC
- Measure effectiveness of CB noise limiter or blanker (when used with an impulse noise generator)
- Measure squelch threshold
- Measure adjacent channel rejection on any channel
- Measure transmitter AM power output—even mobile!
- Measure SSB power output with TRUE peak-reading RF Wattmeter
- Check AM modulation
- Check SSB modulation with a two-tone test—the only accurate way!
- Measure antenna SWR—even mobile!
- Check the transceiver in the car to determine if the problem is in the antenna system or the transceiver

You can save \$500—\$1,500 in equipment costs because the CB Servicemaster eliminates many of the test instruments you would otherwise need for CB servicing. These instruments, or their functions, are built into the unit:


- Audio wattmeter • Audio generator • Distortion meter • RF wattmeter/dummy load • DB meter • SWR bridge

These instruments—which you should have, if you don't own them already, are all you need to get the maximum use from your CB Servicemaster. And the B&K-PRECISION CB Servicemaster is compatible with most oscilloscopes, frequency counters, signal generators and power supplies on the market today.

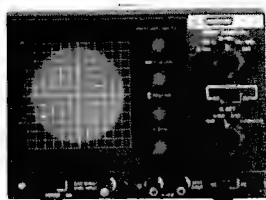

MODEL 1403A—3", 5 MHz  
Recurrent Sweep Oscilloscope

Checks CB modulation and provides viewing of 27MHz CB envelope when used with the Model 1040. Small, compact and inexpensive, it frees other scopes for more effective use. **\$209**

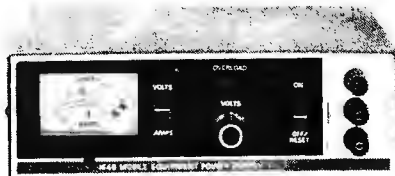


MODEL 1640—Regulated Power Supply

Designed especially for CB and other mobile equipment, the 1640 eliminates changes in supply voltage due to load variations. A stable power supply is essential to precise testing of the transceivers. Less than 0.8% variation from zero to full load, 3 amps continuous, 5 amps surge. Adjustable to any output from 11 to 15 VDC. Suppressed zero scale for greater accuracy. Overload protected. **\$100**



MODEL 1801—  
Digital Frequency Counter

To quickly determine the exact frequency of a CB channel, the 1801 automatically displays it for you in large, easy-to-read digits. You can tune oscillators precisely, conduct audio frequency analysis tests. Six digit display is updated five times per second. Accuracy guaranteed to 40MHz; 60MHz typical. **\$240**

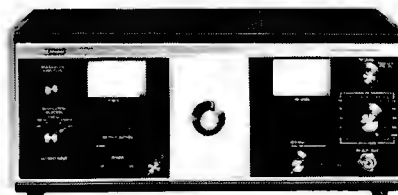

MODEL 2040—40-Channel CB Signal Generator

Covers all 40 channels, AM and SSB with built-in capability. Ultra-stable crystal-controlled, phase-locked-loop frequency generation. Has 5 ppm accuracy. Output attenuator and vernier provide calibrated outputs from 100,000  $\mu$ V to 0.1  $\mu$ V for receiver sensitivity measurements. Includes EIA standard noise test signal generator to check receiver noise suppression. Internal 400, 1000 and 2500 Hz modulating frequencies—can also be externally modulated. Internal protection against 5W RF input. **\$475**


## B&K PRECISION

DYNASCAN CORPORATION  
Makers of Cobra CB Equipment

6460 W. Cortland Avenue, Chicago, Illinois 60635 • 312/889-9087  
In Canada: Atlas Electronics, Ontario

For additional information, contact your B&K-PRECISION distributor for our comprehensive brochure describing the operation of the Model 1040 CB Servicemaster and the CB Service Center—or write us for your free copy.

CIRCLE NO. 14 ON FREE INFORMATION CARD

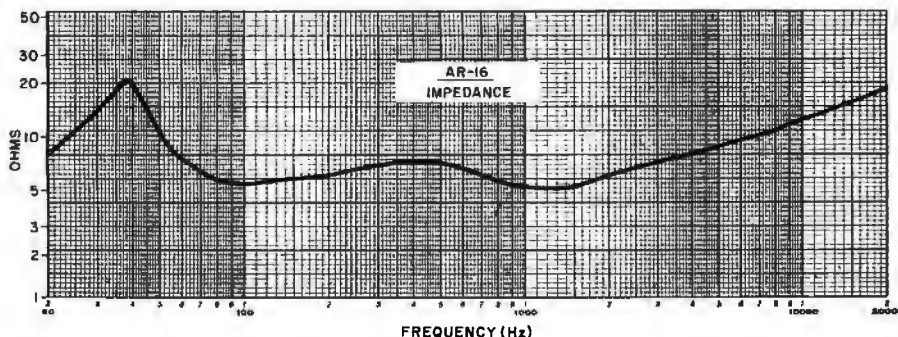

*Impedance curve shows peak slightly below rated system resonance.*

To minimize diffraction effects, which can occur when the speaker drivers are recessed behind the mounting board and which can produce an irregular polar response, the drivers are mounted flush with the front surface of the speaker board. The front is finished to match the rest of the cabinet, and the drivers are covered by a removable acoustically transparent foam plastic grille.

**Laboratory Measurements.** The frequency response of the speaker system was measured in the reverberant field of our test room at a distance of 12' to 15' (3.7 to 4.8 m) from the speakers over a frequency spectrum ranging from 100 Hz upward. The woofer response, up to several hundred hertz, was measured with a closely spaced microphone to simulate anechoic conditions and eliminate the influence of the room on the measurement. Splicing the two curves, and correcting for the known response of the microphone and room, we obtained an unusually "flat" frequency response of  $\pm 1.5$  dB from 100 to 15,000 Hz. There was a 3.5-dB rise at the bass resonance of about 60 Hz. The overall response variation was an impressive  $\pm 2.5$  dB from 30 to 15,000 Hz.

Our measurements were made with the tweeter switch set to NORMAL. A boost or cut of 3 to 5 dB at frequencies above 1500 Hz was measured with the

switch set to its other positions. Driving the speaker with the equivalent of 1 watt into an 8-ohm load (2.8 volts), the total harmonic distortion (THD) below 100 Hz was less than 2% down to 45 Hz and increased smoothly to 10% at 33 Hz and 20% at 26 Hz. When we increased the drive level to 10 watts, the distortion characteristic had a similar shape, but the actual distortion levels were considerably higher. The measured distortion at 10 watts was between 3% and 7% from 100 to 45 Hz and increased to 20% at 36 Hz.

The system impedance was about 6 ohms at its minimum points of 100 and 1300 Hz, but it was typically 6 to 8 ohms over much of the audio range. It rose to a peak of 20 ohms at 38 Hz (well below the rated system resonance of 55 Hz) and climbed smoothly beyond 2000 Hz to 20 ohms at 20,000 Hz. The impedance was not significantly affected by the setting of the tweeter level switch.

In our "efficiency" measurement (actually a sensitivity measurement), when the speaker system was driven at a nominal 1-watt level by an octave of random noise centered at 1000 Hz, the SPL was 91 dB at a distance of 1 meter from the front surface. This is slightly higher than we have measured from some other larger acoustic-suspension systems, even when allowance is made for the 1.25-dB apparent increase in efficiency

due to the actual impedance's being 6 ohms instead of 8 ohms at the test frequency.


Noting that there was no sign of the crossover frequency in the response curve, we carefully examined the tone burst response in the crossover region as well as at lower and higher frequencies. We could find no trace of the anomaly that sometimes occurs in the tone-burst response at the crossover point. The tone bursts were reproduced very well at all frequencies.

**User Comment.** In the simulated live-versus-recorded listening test, the Model AR-16 was a very accurate reproducer, though not quite "perfect" on any of the music selections we used in this test. The departures from facsimile reproduction of the live sound were difficult to define in terms of frequency response. In general, they took the form of a slight "coolness" or "dryness" in the lower midrange. It is in this frequency range that the speaker system was notably free of the artificial emphasis that is all too common with other systems.



The sound from the Model AR-16 belies its compact dimensions. It is not surprising, though nonetheless gratifying, to find a small, inexpensive speaker system that can deliver a smooth, well-dispersed middle- and high-frequency response, but we have come to expect a certain thinness of low bass from such systems. This was not our experience with the Model AR-16; it can deliver a room-filling, true bass when required.

This is not a speaker system that can be played loud enough to rattle the walls, unless you are willing to accept appreciable distortion levels. The 10-watt distortion curve clearly illustrates that, although the woofer does not "fall apart" when driven hard, it is not at its best under these conditions. AR suggests that a pair of Model AR-16's, driven with 25 watts/channel of amplifier power will produce a 103-dB SPL in a typical 3000 cu ft (85 cu m) living room. We did not attempt to verify this because we were satisfied that the speaker system is more than equal to the task of supplying larger-than-life, clean sound in a typical home environment, with no obvious coloration.

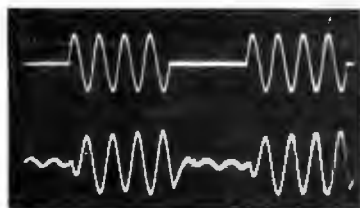The Model AR-16, in our opinion, is a worthy addition to the AR product line. Comparing it to its predecessors should convince anyone that there has been substantial progress in speaker system performance, much of which is embodied in this diminutive system.



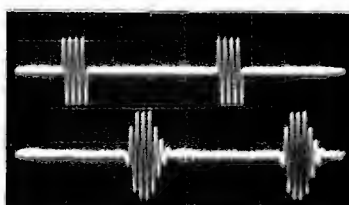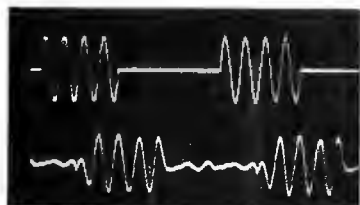*Tone-burst responses at 100 Hz (left), 1300 Hz (below left), and 10,000 Hz (below).*



# afs® / Kriket® CB speaker Sound and Safe!



**kamel™**

Hump mount speaker

**Speakers are our only business.**

**They have to be better!**

Designed with security and superior sound in mind, the AFS® / KRIKET® KAMEL KC-3085 hump-mount external speaker rests snugly on the transmission hump while driving. CB dials are readily visible.

CB transceiver mounts on speaker base forming single unit. No installation problems. For maximum security, unplug antenna and power leads, lift unit and place in trunk. No screws to unscrew. No hassle. No annoying rattles while driving. Solid!

"WORKING WALL" enclosure of cross-laminated fiberboard deadens static and channel noise, eliminates voice distortion.

AFS makes having an expensive CB rig in your car or truck safe and worthwhile. Isn't it about time somebody did?

Available at CB dealers everywhere



**ACOUSTIC FIBER SOUND SYSTEMS, INC.**

7999 KNUE ROAD, SUITE 116 INDIANAPOLIS, INDIANA 46250 (317) 842-0620

Canadian Distributor Muntz Canada Ltd. 1149 Pioneer Road Burlington Ontario, Canada (416) 639-5373

All AFS®/KRIKET® speakers are manufactured in the U.S.A. using American materials and craftsman.

Copyright 1976 Acoustic Fiber Sound Systems, Inc.

*Kriket Cares*

# Experience the excitement of owning the finest *personal* computer – IMSAI 8080

Waiting for you – all the incredible performance and power of the IMSAI 8080. And at a price you would normally pay for a home music system: \$699 in kit; \$931 assembled.

## WORLD OF USES

The IMSAI 8080 is a superbly engineered, quality computer. It is versatile, expandable and powerful, putting literally hundreds of

applications and uses at your fingertips. Imagine sitting at your desk and enjoying interaction with your IMSAI 8080! Press the on switch and you're ready for game playing, research, education, business applications, or for laboratory instrument control. It has all the power you need, and more, to make your application ideas come alive.

## GROWS WITH YOU

The IMSAI 8080 is designed for many years of pleasure. With its open-chassis engineering you can expand your system by adding peripherals and interfaces. The 22-slots and 28 amp power supply mean that you can plug-in today's, plus tomorrow's modules.


Right now you can add a module for displaying color graphics and characters on TV; a ready-to-use keyboard; small and large printers, and a single interface that lets you attach multiple devices including a cassette tape recorder. Expect the latest, exciting equipment from IMSAI. We are committed to leadership in this expanding technology.

## EASY TO PROGRAM

With our BASIC language you can operate the IMSAI 8080 quickly and easily. Technically knowledgeable? Use our assembly language to develop sophisticated and unique software.

If you're thinking personal computer,  
treat yourself to the very best –  
IMSAI 8080

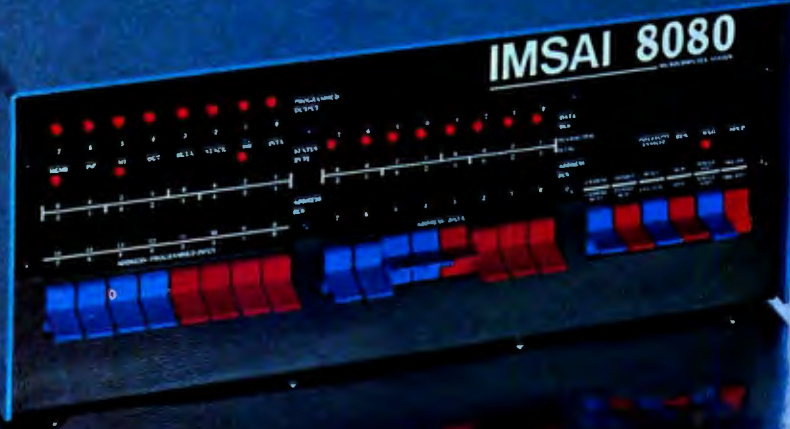Send for free four-color brochure  
or \$1 for catalog. Call or write for  
name of nearest dealer.



## IMSAI

IMSAI Manufacturing Corporation  
14860 Wicks Blvd.  
San Leandro, CA 94577  
(415) 483-2093  
TWX 910-366 7287

European Distributor  
Harper Industry Products Ltd.  
6079 Spremlingen  
West Germany

Prices: USA Domestic

CIRCLE NO. 36 ON FREE INFORMATION CARD



# MULTIMETERS FOR ELECTRONICS

BY CLAYTON L. HALLMARK

## PART 2: *Digital Multimeters*

**L**AST MONTH, we discussed the traditional VOM and analog, or meter-type, electronic multimeters. Here, the focus is on the newest type of electronic multimeter—the digital multimeter, or DMM.

DMM's offer most of the advantages of analog-type instruments, plus a few that are unique. The use of numeric displays in place of meter movements, for example, makes reading measurements easier and eliminates interpretation errors common with multi-scale analog meters. They also make possible a more

accurate instrument, since a measurement with more digits is obtained than is possible with an analog instrument.

**Technical Details.** The accuracy of a DMM is stated in percentage of reading, rather than in percentage of full-scale. This means a more uniform accuracy throughout a given range. To illustrate, a DMM with a 2% accuracy on the 100-volt dc range would be accurate to within 2 volts at 100 volts and 0.4 volt at 20 volts. Therefore, at 20 volts, the DMM would be five times as accurate as

the analog meter. (In practice, this disparity might be even greater, considering that many DMM's are more accurate than the 2% figure in our example.)

In addition to the stated accuracy, the DMM may be off by  $\pm 1$  count in the least-significant (farthest right) digit. This means that, if 1000 volts is displayed by an instrument with a 0.1%,  $\pm 1$  digit accuracy, the actual potential being measured can be anywhere between 998 and 1002 volts, based on a deviation of 1 volt for the 0.1% error and 1 volt for the one-digit error.

**Ac accuracy.** Ac voltage accuracy is usually somewhat worse than the dc accuracy and is usually limited to a specified bandwidth. Outside the specified frequency range, the accuracy drops off rapidly. Also, ac accuracy is usually specified for a sine-wave input; any other type of waveform will degrade the accuracy. In addition, distorted sine waves produce serious accuracy errors.

**Resistance power.** Sounding like a contradiction in terms, resistance power simply means how much current/voltage will be applied to the device under test by the DMM when using the instrument in the resistance-measuring mode. On low ohmic ranges, the excessive current or voltage can be sufficient to damage sensitive semiconductors.

**Protection.** You will pay good money for a DMM, so you will want to use it as long as possible. Always keep in mind that someday you might use the resistance-measuring function to try to measure line voltage. Unless your meter is protected on all ranges and functions, it will likely be damaged beyond repair. And if you accidentally set it up on the wrong range or function, it may cost almost as much to repair as to replace it, if it is damaged.

**Ruggedness.** If you are going to use your DMM in the field, make sure it has an "impact-resistant" case and, if possi-


ble, a case that will protect the knob and switch controls and display from damage if the instrument is dropped onto a hard surface on its face.

**Digits.** A common way of classifying DMM's is by the number of digits in its display. This can often be confusing because an instrument that displays a maximum count of 1999 has 3½ digits, not 4 as a first glance might lead you to believe. The initial digit is actually a half digit that is either blanked or displayed as a 1 and only a 1. The half digit is sometimes called the "overrange" digit, since it permits measurements to be made somewhat beyond the selected range.

If a 3-digit instrument with overranging is used to measure a potential that changes from 99.9 to 100.2 volts, the second potential could be read to the nearest 0.1 volt without having to change ranges. Without overranging capability, the meter would have to be



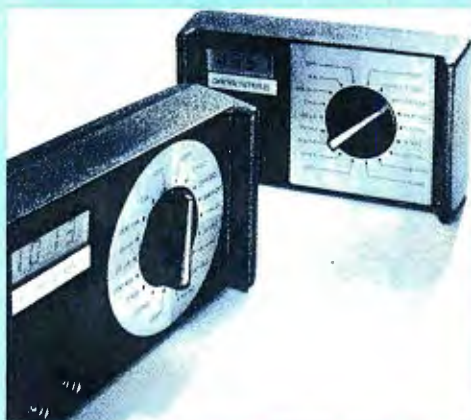**B&K Precision Model 280**  
(shown also on preceding page).



**Danameter 2000A and Danameter II 2000A**



**Viz WD-750A VoltOhmyst**



**John Fluke Model 8030A**



**Simpson Model 380**



**Data Tech Model 21**

# Shakespeare's White Knight. The best antenna going. And coming.

Shakespeare comes on strong for the new 40 channel era. With high performance CB antennas that turn on the power on all 23 or 40 channel CB transceivers.

Shakespeare's new White Knight Antenna combines the rugged, mechanical strength of gleaming white fiberglass with precision engineered electronic components. Components like the high quality loading coil permanently fused in a solid polycarbonate thermoplastic base. Totally impervious to the environment. And pre-tuned to an SWR of 1.9 to 1 or less over the 40 channel band (1.3 to 1 or less at the center). To assure maximum range and peak performance everytime you key the mike. That's what sets the White Knight antenna apart from all the others.

Ride full tilt into the 40 channel era with the new White Knight CB Antenna. And take the Shakespeare performance route home.

**The White Knight Antenna,**  
Style 430/available in a variety  
of pre-assembled mounting  
styles. Complete with cables  
and connectors. Under \$25.



*Shakespeare*

**Coming on strong for the Knights of the Road.**

Shakespeare Company/Antenna Group, P.O. Box 246, Columbia, S.C. 29202  
In Canada: Len Finkler Ltd., Ontario.

switched to the 1000-volt range, where it would correctly indicate 100 volts to the nearest 1 volt instead of the nearest 0.1 volt.

**Overranging.** This is sometimes specified as a percentage by which this feature extends the range capability of the instrument. Hence, if a 4½-digit DMM has a maximum display capability of 19999, it is said to have 100% overranging because 19999 is about 100% greater than 9999. And if a 4½-digit DMM has a maximum display count of 11999, it is said to have 20% overranging because the maximum without overranging would be 9999.

**Resolution.** A related DMM specification is resolution, which is one part in the maximum reading. The resolution of a 4-digit instrument with 20% overranging is one part in 11,999.

**Sensitivity.** This is sometimes confused with resolution and is the lowest displayable increment of voltage that is

represented by the least-significant digit in the display when the meter is set to its lowest range. A 4-digit meter with a 100-mV lowest range and the capability of displaying 100.00 mV has a sensitivity of 10 microvolts.

**DMM's For Servicing.** There are many digital multimeters from which the service technician and hobbyist can choose. (A list of manufacturers of such instruments is given in the table. The manufacturers can supply technical literature and prices for the digital instruments they make.) Most instruments for servicing and hobby use are in the low- and moderate-price ranges. They offer a wide variety of ranges, functions, and features that can be matched to just about any test and measurement job you might have.

**Controls.** The front-panel controls and jacks on most DMM's are similar to and serve the same purposes as in the

VOM. This means that the typical DMM is operated in a manner similar to that of a VOM. The **RANGE** and **FUNCTION** switches in DMM's are generally separate controls. The "hot" input jack is usually labelled  $V \Omega$  for ac and dc voltage and resistance and **MA** for ac and dc current, both referenced to a **COM** jack. Some DMM's also have a **ZERO** control that is used to set the display to all zeros when the two test probes are shorted to each other.

**Overrange indication.** The "over-range" indication is displayed whenever the input to the instrument is greater in magnitude than the setting of the **RANGE** switch allows. In some instruments, the indicator for this condition is an **OVER** (or **OVERRANGE**) lamp, while in others the overload is indicated by a 1 in the half-digit position with the other digits blanked or by some other distinctive display feature.

**Polarity display.** Almost all modern

(continued on page 38)




Data Precision Model 175



Hewlett-Packard Model 3476A



Hickok Model 3300A

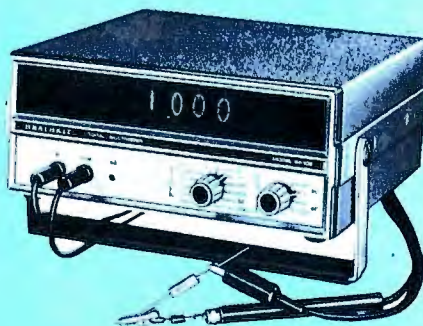

Heathkit Model IM-102



Non-Linear Systems Model LM-3.5



Sencore Model DVM35

# The ultimate base

For people who want the finest in CB radio, there is the Tram D201 base station. Each base station is hand assembled with care, patience and infinite skill to produce a radio with superb performance and a host of outstanding features.

The Tram D201 base station is rigidly inspected and subjected to the industry's most thorough and demanding testing procedures. The result is a distinctive precision instrument created by craftsmen for people who appreciate owning the very best.

Find out more about the ultimate base and the complete line of Tram mobile CB radios. Send for a free brochure or see your local CB dealer.

The mark of CB quality since 1960

**TRAM** TRAM/DIAMOND CORPORATION  
Lower Bay Road, P.O. Box 187, Winnisquam, NH 03289  
(603) 524-0622.



Now you can buy an Altair™ 8800b or an Altair 680b computer right off the shelf. Altair plug-in boards, peripherals, software and manuals are also available. Check the list below for the MITS dealer in your area.



# off the shelf.

**ALTAIR COMPUTER CENTER**  
8105 SW Nimbus Ave.  
**BEAVERTON, OR 97005**

**COMPUTER KITS (S.F. area)**  
1044 University Ave.  
**BERKELEY, CA 94710**  
(415)-845-5300

**THE COMPUTER STORE**  
(Arrowhead Computer Co.)  
820 Broadway  
**SANTA MONICA, CA 90401**  
(213)-451-0713

**GATEWAY ELECTRONICS, INC.**  
OF COLORADO  
2839 W. 44th Ave.  
**DENVER, CO 80211**  
(303)-458-5444

**COMPUTER SHACK**  
3120 San Mateo N.E.  
**ALBUQUERQUE, NM 87110**  
(505)-883-8282; 883-8283

**ALTAIR COMPUTER CENTER**  
4941 East 29th St.  
**TUCSON, AZ 85711**  
(602)-748-7363

**ALTAIR COMPUTER CENTER**  
2801 Cornhusker Hwy.  
**LINCOLN, NE 68504**  
(402)-466-1853; 466-6759

**COMPUTER PRODUCTS UNLIMITED**  
2412 Broadway  
**LITTLE ROCK, AR 72206**  
(501)-371-0449

**ALTAIR COMPUTER CENTER**  
110 The Annex  
5345 East Forty First St.  
**TULSA, OK 74135**  
(918)-664-4564

**ALTAIR COMPUTER CENTER**  
5750 Bintliff Drive  
**HOUSTON, TX 77036**  
(713)-780-8981

**COMPUTERS-TO-GO**  
4503 West Broad St.  
**RICHMOND, VA 23230**  
(804)-335-5773

**MICROSYSTEMS (Washington, D.C.)**  
6605A Backlick Rd.  
**SPRINGFIELD, VA 22150**  
(703)-569-1110

**THE COMPUTER STORE**  
Suite 5  
Municipal Parking Building  
**CHARLESTON, W. VA. 25301**  
(304)-345-1360

**THE COMPUTER ROOM**  
3938 Beau D'Rue Drive  
**EAGAN, MN 55122**  
(612)-452-2567

**THE COMPUTER STORE**  
OF ANN ARBOR  
310 East Washington Street  
**ANN ARBOR, MI 48104**  
(313)-995-7616

**THE COMPUTER STORE, INC.**  
(Hartford area)  
63 South Main Street  
**WINDSOR LOCKS, CT 06096**  
(203)-627-0188

**CHICAGO COMPUTER STORE**  
517 Talcott Rd.  
**PARK RIDGE, IL 60068**  
(312)-823-2388

**GATEWAY ELECTRONICS, INC.**  
8123-25 Page Blvd.  
**ST. LOUIS, MO 63130**  
(314)-427-6116

**BYTE'N'ONICS**  
Suite 103  
1600 Hayes St.  
**NASHVILLE, TN 37203**  
(615)-329-1979

**THE COMPUTER STORE, INC.**  
120 Cambridge St.  
**BURLINGTON, MA 01803**  
(617)-272-8770

**ALTAIR COMPUTER CENTER**  
269 Osborne Road  
**ALBANY, NY 12211**  
(518)-458-6140

**THE COMPUTER STORE**  
OF NEW YORK  
55 West 39th St.  
**NEW YORK, NY 10018**  
(212)-221-1404

**THE COMPUTER SYSTEMCENTER**  
3330 Piedmont Road  
**ATLANTA, GA 30305**  
(404)-231-1691

**MARSH DATA SYSTEMS**  
5405 B Southern Comfort Blvd.  
**TAMPA, FL 33614**  
(813)-886-9890



## GOING FROM ANALOG TO DIGITAL

Digital circuits cannot by themselves measure such analog parameters as voltage, current, and resistance. It is necessary, therefore, for the digital circuits in a DMM to be preceded by analog-to-digital (A/D) converters that present analog information in a form that digital circuits can use. Essentially, the A/D converter feeds a set number of pulses to the digital counting circuits, the number of pulses depending on the magnitude of the parameter being measured. The greater the magnitude of the analog parameter (or the longer a gate is held open), the greater the number of pulses delivered to the counting circuits. There are basically two types of converters used in DMM's today. One is the single-slope converter shown in diagram A, the other is a dual-slope converter, shown in diagram B.

The single-slope converter, used in many low-cost DMM's, contains a capacitor that is linearly charged from a constant-current source. The potential across the capacitor is applied to the inverting (-) input of a voltage comparator, a form of operational amplifier. The unknown voltage to be measured is applied to the noninverting (+) input of the comparator. In a voltage comparator, when the potential at the + input is greater than that at the - input, the output from the comparator is high.

As the potential across the capacitor, and hence across the - input of the comparator, reaches a level that just slightly exceeds, by a few millivolts, the potential at the + input, the comparator switches to a low-output state.

The output of the comparator is fed to a three-input gate, along with the pulses from a stable oscillator of known frequency and a control signal that can be either high or low. When both the comparator and control signals are high, the oscillator pulses can pass through the gate and on to the counter circuit. If either the comparator output or the control signal are low, the gate will be disabled, preventing the oscillator pulses from passing through to the counter.

In operation, the control signal causes the counter to reset to zero and, via elec-

tronic switching, turns off the gate and discharges the capacitor. Hence, the oscillator signal cannot pass through the constant-current source. As the unknown voltage at the input is greater than the potential across the capacitor, the output of the comparator is high and allows the oscillator signal to pass on to the counter. As soon as the capacitor potential exceeds the unknown voltage, the comparator switches state and disables the gate, preventing any more oscillator pulses to be passed on to the counter. Another signal then causes the display to indicate the state of the counter. After a predetermined interval, the special control signal resets the gate, discharges the capacitor, and prepares for the start of a new cycle.

Note that the accuracy of the single-slope converter depends on the stability of the oscillator, voltage comparator, and constant-current source and the quality of the capacitor. Noise on the input signal can produce faulty indications in this system.

Better digital multimeters use dual-slope conversion (circuit B). This system also uses a capacitor that is charged by a constant-current source, but charging is performed by an integrator circuit, using an op amp. In this manner, the capacitor can be linearly charged and then linearly discharged to provide the voltage/time conversion required. This eliminates long-term drift due to component instability, temperature variations, and noise on the input signal and provides for better accuracy, the last between 0.5% and 0.01%.


In circuit B, let us assume that the system has been reset so that the integrating capacitor has been discharged and the counter/display is at zero. The control signal connects the comparator input to the unknown input voltage, which is negative in this case. Due to the arrangement of the circuit, at time T<sub>0</sub>, the output at the integra-

tor will be slightly negative and the output of the comparator, whose + input is referenced to ground, will be low. Under these conditions, the gate will not allow the oscillator signal to pass through, since its other input is low.

The unknown potential at the input applied to the - input of the integrator causes the op amp to charge the capacitor. As this voltage passes through zero (time T<sub>1</sub>), it turns on the comparator which, in turn, allows the oscillator pulses to pass through the gate to the counting circuits. The capacitor continues to charge and the counter continues to count until it reaches, in this case, the 10-volt count. At this time, the counter generates an "overrange" signal. The overrange signal occurs at time T<sub>2</sub> and electronically switches the integrator input from the unknown input voltage to an internal fixed dc reference voltage of positive polarity. Note that the time from T<sub>1</sub> to T<sub>2</sub> completely fills the counters once. This time is not fixed because the charging rate is determined by the level of the unknown voltage. A high voltage reduces the T<sub>1</sub>-to-T<sub>2</sub> period, while a low voltage increases it.

At time T<sub>2</sub>, the reference voltage starts the integrator in the opposite direction and linearly discharges the capacitor. The reference voltage is held stable by internal circuitry. The linear discharge continues, as does the count (gate held open by the high level of the comparator's output), until the decreasing ramp passes through zero (time T<sub>3</sub>), forcing the comparator to change output state and shut down the gate to stop the counter.

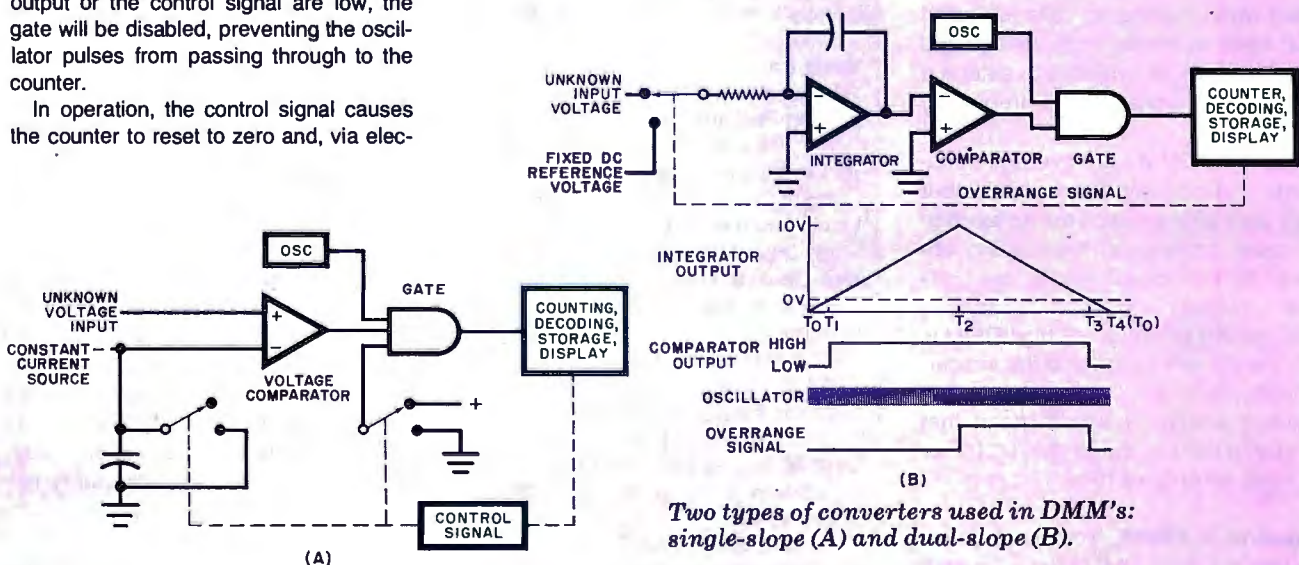When the gate shuts down, the counters display a count that is directly proportional to the ratio of the unknown voltage to the reference voltage. If a high-quality integrator capacitor and a stable reference voltage are used in the circuit, the accuracy of the system can be quite good.



Two types of converters used in DMM's: single-slope (A) and dual-slope (B).

## COMPARISON OF METER SPECIFICATIONS

		DVM	VTVM	FETVOM	VOM
<b>Accuracy (%)</b>	(S*) 0.1-2 (L*) 0.4-0.004		3-5 1-3	3-4 1-2	1-5
<b>Frequency Limit</b>	(S) 20Hz-20 kHz  (L) To 100 MHz		To 4 MHz, 250 MHz with probe To 700 MHz	To 3 MHz, 250 MHz with probe To 1 MHz, 500 MHz with probe	To 100 kHz
<b>Ac impedance</b>	(S) 10 megohms  (L) 1-10 megohms		10 megohms	1-10 megohms 10 megohms	0/5 kilohms per volt 20 kilohms per volt
<b>Waveform response</b>	(S) Avg. (L) Avg., rms		Peak, p-p Avg., rms	Peak, p-p Avg.	Avg.
<b>Voltage readings</b> (min. and max.)	(S) 10 $\mu$ V- 1000 V  (L) 1 $\mu$ V- 1000 V		0.2 mV- 1500 V 20 $\mu$ V- 1000 V	0.1 mV- 1500 V 200 $\mu$ V- 1000 V	5 mV- 6000 V
<b>Resistance readings</b>	(S) 1 ohm- 10 megohms  (L) 0.0001 ohm- 10 megohms		0.2 ohm- 1000 megohms 0.2 ohm- 5000 megohms	0.2 ohm- 1000 megohms 0.2 ohm- 500 megohms	0.2 ohm- 100 megohms

\*S = Service type. L = Laboratory type.

DMM's feature automatic polarity indication in the display, activated by internal circuitry according to the polarity of the dc voltage or current being measured. (In some instruments, + is implied, while other instruments display both + and -.) With the autopolarity feature built into a DMM, there is no need to transpose test probes or to flip a polarity-reversing switch, which further simplifies instrument operation. And positioning of the decimal point in the display is also automatic whenever the RANGE switch is operated.

**Probes.** Some DMM's come with probes that have switchable isolation resistors in them to prevent capacitive loading when making dc voltage and r-f circuit measurements. High-voltage and r-f probes are also available to extend a meter's basic voltage and frequency ranges.

Since most DMM's are average-sensing and rms-calibrated, any input other than a pure sine wave on the ac function can cause an error in the reading obtained. At low signal levels, the  $\pm 1$ -count ambiguity can lead to serious measurement errors. If a 3-digit DMM is set to the 0.1-volt range and the indicated display is 0.010, for example, the one-count ambiguity would mean that the true potential could be 0.009 or 0.011 volt, an error of 10%.

**Choosing a DMM.** You must determine which type of DMM best suits your needs. If you plan on using your DMM

as a bench-only instrument, a line-powered DMM will probably be your first choice. On the other hand, if you intend to use your DMM almost exclusively in the field, battery power is a must. An instrument that must be used for both field and bench testing should be capable of being operated on battery power in the field and line power on the bench.

The number of digits in the display will influence the type or model instrument you choose. In most cases, every added digit boosts the cost of the DMM. So, if you are working with 20% resistors and capacitors and most schematic diagrams indicate tolerances to only two decimal places, a 2½-digit DMM is all you really need. Of course, if you are working with high-level technology, do not look for an instrument with less than 3½ digits in the display.

The type of display you choose may also be important. The three most popular types used in DMM's today are the red LED, orange gas-discharge, and LCD (liquid crystal display) displays. Except for the gas-discharge type, which can be either seven-segment or individual 0-through-9 format, the displays are arranged in seven segments. For most indoor work, the LED display is convenient. You can work with an instrument with a LED display even where ambient light levels are quite low, since the display itself lights up. For outside work, where the ambient light is very bright, a LED display is likely to wash out and become unreadable unless a light hood is used. Here, the LCD offers a high degree of legibility, since contrast increases with increasing light levels. The disadvantage of the LCD is that it is very difficult to read when the light level is relatively low. The gas-discharge display bridges the gap between the LED and LCD displays.

Although most DMM's that would be used by the experimenter/hobbyist have a 10-megohm input resistance, you may find instruments with different input impedances specified. Keep in mind that the input resistance will be in parallel with the device or circuit being measured and that even a 10-megohm input resistance across a 10,000-ohm load represents a loading error of 0.1% that must be added to the instrument's accuracy specifications. If you are thinking of using a DMM with a 1000-megohm or greater input resistance to avoid loading effects, remember that changing temperature will introduce errors in the measurement. Also keep in mind that there is quite a difference between input resistance and input impedance. Input

## DMM MANUFACTURERS

### **Ballantine Laboratories, Inc.**

Box 97, Boonton, NJ 17005

### **B&K Precision**

6460 W. Cortland, Chicago, IL 60635

### **Dana Laboratories, Inc.**

2401 Campus Dr., Irvine, CA 92713

### **Data Precision Corp.**

Audubon Rd., Wakefield, MA 01880

### **Data Technology Corp.**

2700 S. Fairview Rd., Santa Ana, CA 92704

### **DeForest Electronics**

40 Fairfield Pl., W. Caldwell, NJ 07006

### **Dynascan Corp., B&K**

1801 W. Belle Plaine Ave., Chicago, IL 60613

### **John Fluke Mfg. Co.**

Box 43210, Mountlake Terrace, WA 98043

### **Heath Co.**

Benton Harbor, MI 49022

### **Hewlett-Packard**

1501 Page Mill Rd., Palo Alto, CA 94304

### **Hickok Electrical Inst. Co.**

10514 Dupont St., Cleveland, OH 44108

### **Leader Instrument Corp.**

151 Dupont St., Plainview, NY 11803

### **Non-Linear Systems Inc.**

Box N, Del Mar, CA 92014

### **Sencore Inc.**

3200 Sencore Dr., Sioux Falls, SD 57107

### **Simpson Elect. Co., Div. of AGM**

853 Dundee Ave., Elgin, IL 60120

### **Systron-Donner Corp., Instrument Div.**

10 Systron Dr., Concord, CA 94518

### **Tektronix Inc.**

Box 500, Beaverton, OR 97077

### **Viz Test Instrument Group**

335 E. Price St., Philadelphia, PA 19144

resistance is specified for dc measurements, while input impedance is for ac measurements. Too, besides input resistance, there is also input resistance due to capacitance of the test-probe cable with which to contend.

Depending on the type of work you will be doing, even a basic DMM may not be what you need. If you do a lot of alignment, where tuned circuits must be "tweaked" for maximum or minimum response at some particular frequency, you will need a "trend" indicator incorporated into your DMM. This device is usually an analog-type meter movement. The numeric display will indicate the value of the parameter being measured, while the meter movement will indicate the trend taking place.

There are some mechanical considerations, too. For a portable field instrument, look for a handle that can also double as a tilt stand to elevate the front of the instrument at a convenient viewing angle. Such handles are usually standard equipment on modern DMM's. Another thing to look for is nonskid rubber "feet" on the bottom of the instrument's case. The feet will not only prevent the DMM from being accidentally brushed off your workbench onto a hard floor, it will also make using the DMM easier by keeping it in place when you press a switch with only one hand.

The matter of instrument size is usually a personal taste. Obviously, if you plan to use the DMM primarily for field service, the smaller the better. You may also want a very compact instrument on your workbench, which is fine if the instrument packs all the ranges, functions, and features you need. But bear in mind that larger instruments often offer functions and conveniences not available in a compact DMM.

Actually, which digital multimeter you buy depends on the applications for which it is intended and how much money you have to spend. You would not, for example, pay the premium price demanded for a 0.01% laboratory-grade DMM when a 0.1% accuracy is all you will ever need.

The best advice is to tailor the instrument to the type of work you will be doing. Once you fulfill your needs for functions, ranges, features, and size, look into such things as accessories, auto-ranging, etc., if your budget will allow them. The new DMM's on the market (and those still to come) are offering features and functions that either did not exist before or commanded very high prices in the past. The newer instruments offer more for less money. ♦



## THE 25MHz "NOW" SCOPE with 5sec-1μsec DELAYED SWEEP DUAL TRACE/DUAL CHANNEL


- Built-in delay circuitry, continuously variable, from 1μsec to 5sec... plus 5mV/Div sensitivity.
- Selectable synchronization — automatic, normal, single trace and reset modes with H-F rejection.
- X10 magnification; ±3% overall accuracy, both chan's.
- Displays leading edge of pulse or pulse train for quick functional determination.
- 20,000:1 delay jitter — X-Y phase difference below 3° @ 100KHz.
- External Sweep Sensitivity: (X-Y) 5mV/Div to 2V/Div, 10 steps. \$1395. with accessories

**LEADER**  
Instruments Corp.

151 Dupont Street, Plainview, N.Y. 11803 (516) 822-9300  
West Coast: 7733 Denmore Ave., Van Nuys, Calif. 91406 (213) 989-2760 In Canada: Omnitronix Ltd., Montreal, Quebec

CIRCLE NO. 42 ON FREE INFORMATION CARD
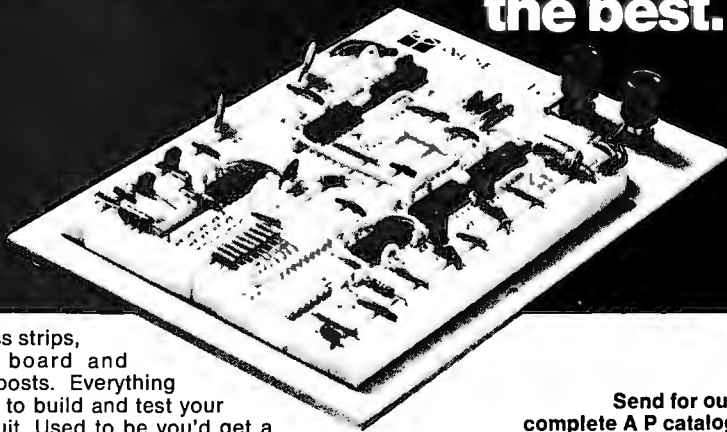
## You've seen the rest...now try the best.



Solderless strips, backing board and binding posts. Everything you need to build and test your own circuit. Used to be you'd get a circuit idea, lay out a pc board, print it, solder everything together, troubleshoot, change your layout, try a new board, and spend absolutely too much time breadboarding. Now A P ACE All Circuit Evaluators let you breadboard in a fraction of the time. Make your changes immediately. Keep full leads on your components. Avoid the heat damage possible with repeated soldering and desoldering. A P made the first modern solderless breadboard, and we still make them best.

**Pick an ACE for Faster and Easier solderless circuit building and testing.**

Part No.	ACE Model No.	Tie Points	DIP Capacity	No. Buses.	No. Posts	Board Size (inches)	Price Each
923333	200-K (kit)	728	8 (16's)	2	2	4-9/16x5-9/16	\$18.95
923332	208 (assem.)	872	8 (16's)	8	2	4-9/16x5-9/16	28.95
923334	201-K (kit)	1032	12 (14's)	2	2	4-9/16x7	24.95
923331	212 (assem.)	1224	12 (14's)	8	2	4-9/16x7	34.95
923326	218 (assem.)	1760	18 (14's)	10	2	6-1/2x7-1/8	46.95
923325	227 (assem.)	2712	27 (14's)	28	4	8x9-1/4	59.95
923324	236 (assem.)	3648	36 (14's)	36	4	10-1/4x9-1/4	79.95



**A P PRODUCTS INCORPORATED**  
Box 110-H Painesville, OH 44077  
(216) 354-2101 TWX: 810-425-2250

Order from your A P distributor today.  
Our distributor list is growing daily.  
For the name of the distributor nearest you call Toll-Free 800-321-9668.

CIRCLE NO. 1 ON FREE INFORMATION CARD

**D**igital circuitry has spawned a variety of troubleshooting aids, including logic probes, pulse generators, IC clip-type testers, logic comparators, and multiple-trace oscilloscopes. All are most useful—up to a point. That point is reached when the digital equipment contains a microprocessor, as in computers, scanning monitors, video games, microwave ovens, etc.


In such cases, how does one examine a number of operating interdependent circuit lines for debugging purposes? Industry knows how—with a “logic analyzer,” an instrument with a bottom price of about \$2500. Now, however, you can build your own logic analyzer for less than \$190.

The Logic Analyzer presented here features eight input lines and an ability to examine sequential data before or after a reference event, displaying a truth table consisting of 1's and 0's on any oscilloscope CRT. This is called a data-domain logic analyzer. (There are, of course, other types of analyzers, one of which displays a timing diagram on a scope's CRT.)

**Why a Logic Analyzer?** Because digital logic operates at two different voltage levels (0's and 1's), the first special-digital test instrument was the simple digital probe. The digital probe uses some type of indicator, usually a LED, to indicate the presence or absence of a signal at any selected single point in a circuit. Since digital circuits usually consist of a number of IC's that all operate from a common timing clock, even if a single digital probe gives a proper indication at a given test point, there is no way of determining if the observed pulse is correctly timed.

The shortcomings of the digital probe led to the development of the IC “clip” tester in which 14 or 16 LED's could indicate the logic states at each of the IC pins. Note that the status of the logic is of interest only at a specified instant in time related to the clock. This brings up another problem—clock speed. With most clock rates, single 14/16-pin LED indicator probes may display only a blur (except at the ground and power pins of the IC), with the blur rate, or light intensity, a function of the clock speed. Hence, unless you are able to drastically slow down the clock rate, you still will not be able to discover anything but the presence or absence of signals, whether or not they are correctly timed.

Using a logic analyzer with an oscilloscope, you can display a “truth table” of the digital circuit being tested under ac-

**BREAKTHROUGH PROJECT**

# Low-Cost Digital Logic Analyzer

*Data-domain instrument for troubleshooting any type of digital system including microcomputers.*

**BY G. MUETHING, I. SPECTOR, AND C. WONG**


tual operating conditions. Simply by selecting a “trigger word” consisting of a particular set of 1's and 0's, the analyzer will freeze the 15 8-bit digital words that precede the selected trigger word and display the data so that it can be analyzed at your leisure. A switch also allows the observation of the 15 digital words that follow the trigger word if the problem is thought to lie in that direction. By changing the trigger word, which is brightness accented in the display, as you step through the truth table, it becomes possible to examine the digital logic from start to finish. In essence, then, the Logic Analyzer is a form of electronic “time machine” that can freeze digital events before or after any selected point in time.

Because a computer consists of a number of interlocking digital circuits, each carefully timed from a common clock signal, the misplacement of one bit among thousands can cause a great deal of trouble. Programs that can be properly written will not run because of an erroneous bit being generated within the system.

Why not use a conventional oscilloscope? True, you can see a small group of bits at any given time. But if the system under test is running at the usual clock rates, the picture displayed will

keep changing and be blurred. The scope can display a signal only after it has been triggered. If you happen to trigger on the problem itself, you have further complications. Because computers, peripherals, ROM's, and other digital devices may not repeat the same state over and over again, a scope without storage capability cannot display a “snapshot” of a one-time logic event for subsequent analysis. In some cases, the scope is a necessity, as only a scope can display the detailed waveform information that can give the user an insight by an intuitive process where a waveform “just doesn't look right”. A good scope can also show up fast transient “glitches” that, although they disturb circuit operation, may not show up on an analyzer. However, if you rely strictly on a scope for analysis, solving many system problems would be virtually impossible.

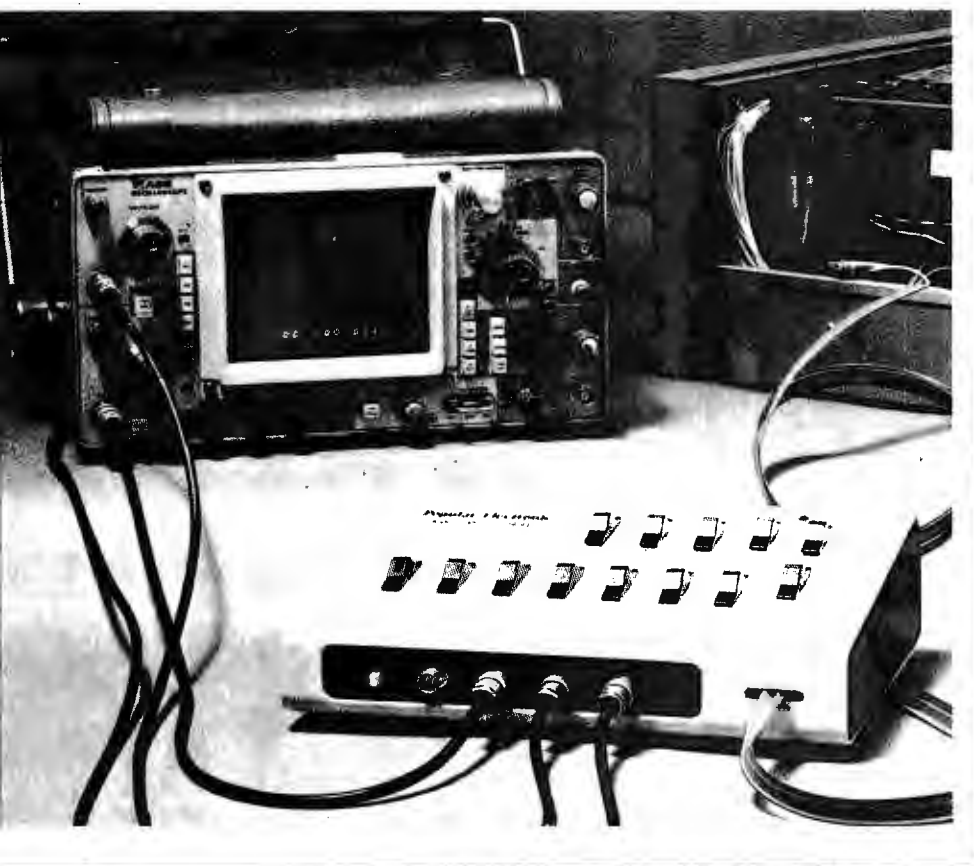The low-cost Logic Analyzer in this article will add a form of storage to any oscilloscope, perform the sixteen 8-bit data word freeze as previously described, and provide the electronics experimenter with a state-of-the-art digital test instrument that rivals those costing several hundred dollars more. In use, you simply connect the three analyzer outputs to the horizontal, vertical, and



blanking inputs of a scope and connect the eight data-input and the clock and ground probes to the circuit being analyzed. When the trigger word keyed in via control-panel switches appears, the Analyzer will automatically trigger, collect, store, and display 16 sequential 8-bit words in either octal or hex format, as shown in Fig. 1. The analyzer will accept data rates as high as 8-million bytes/second.

Another front-panel control allows the user to select either "positive time" in which the selected trigger word appears intensified on the top of the CRT screen with the next 15 sequential data words below it, or "negative time" in which the 15 data words leading up to the trigger word appear first with the brightened trigger word at the bottom of the screen.

One other control provides the choice of a "snapshot" that catches and displays an individual 16-word table for as long as you like or a "moving picture" display in which the data for each table is collected and automatically displayed so you can dynamically observe the operation of the circuit. The specifications for the logic analyzer are shown in the box.

**Circuit Operation.** Operation of the analyzer can best be understood by referring to the block diagram of Fig. 2.

(The complete schematic diagram is shown in sections in Figs. 3 through 7.) The inputs to the system are the 8-bit signals (BIT 0 through BIT 7), the system clock, and the common or ground bus of the digital circuit under test. The data and clock inputs are buffered by IC1 and IC2. The eight data signals are latched by IC4 and IC5 before loading into data memory IC6 and IC7. This 16-word data memory is the "heart" of the analyzer. It stores sequential data words from the digital system under test.



The buffered clock signal is fed to half of IC2 that can be set to operate on either the negative or positive edge, depending on the setting of S10. This signal is applied to the display control logic made up of IC11 through IC15. The other input to the display logic is from comparator IC3. This circuit uses S1 through S8 to set up the desired trigger word, with the switches set to either 1, 0, or X as required. (The X is a "don't care" state.) When the comparator receives the input data word that matches its switches, a signal is passed to the display control logic. When S11 is set to the POS TIME position, for example, data collection begins when the comparator detects the trigger word. After 16 clock pulses, data collection stops so that the memory contains the trigger word followed by the next 15 data words. In the NEG TIME position of S11, the memory stores data continuously until the trigger word occurs. When this happens, data collection is halted, leaving the memory with the 15 data words leading up to the trigger, plus the trigger word itself.

During the data collection period, the display control logic sends a signal to the blanking logic system made up of IC22 through IC24, Q1, and Q2 to inhibit the display. At the end of this period, the blanking signal is removed and a bit-by-bit scan of the memory contents is initiated. Scanning is accomplished by data multiplexer IC16, which is controlled by three of the eight output bits of horizontal control ROM IC19. Thus, even though the data memory provides a full 8-bit wide data word to the input of the multiplexer, only one bit at a time is sent to the 1-0 character generator made up of half of IC20, and Q3.

The character generator uses this information and the CRT beam positioning signals from the IC20 horizontal D/A (di-

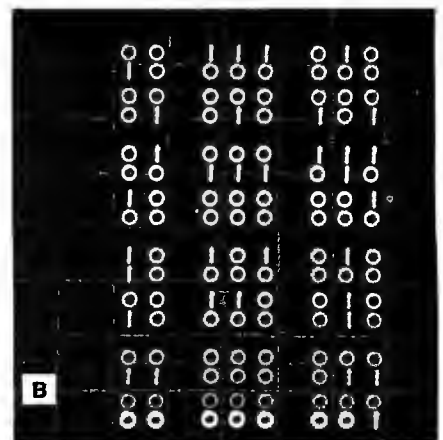


Fig. 1. Trigger word is intensified at top of hex display (A) with the 15 following data words. In octal display (B), trigger word is at bottom with the 15 data words leading up to it.

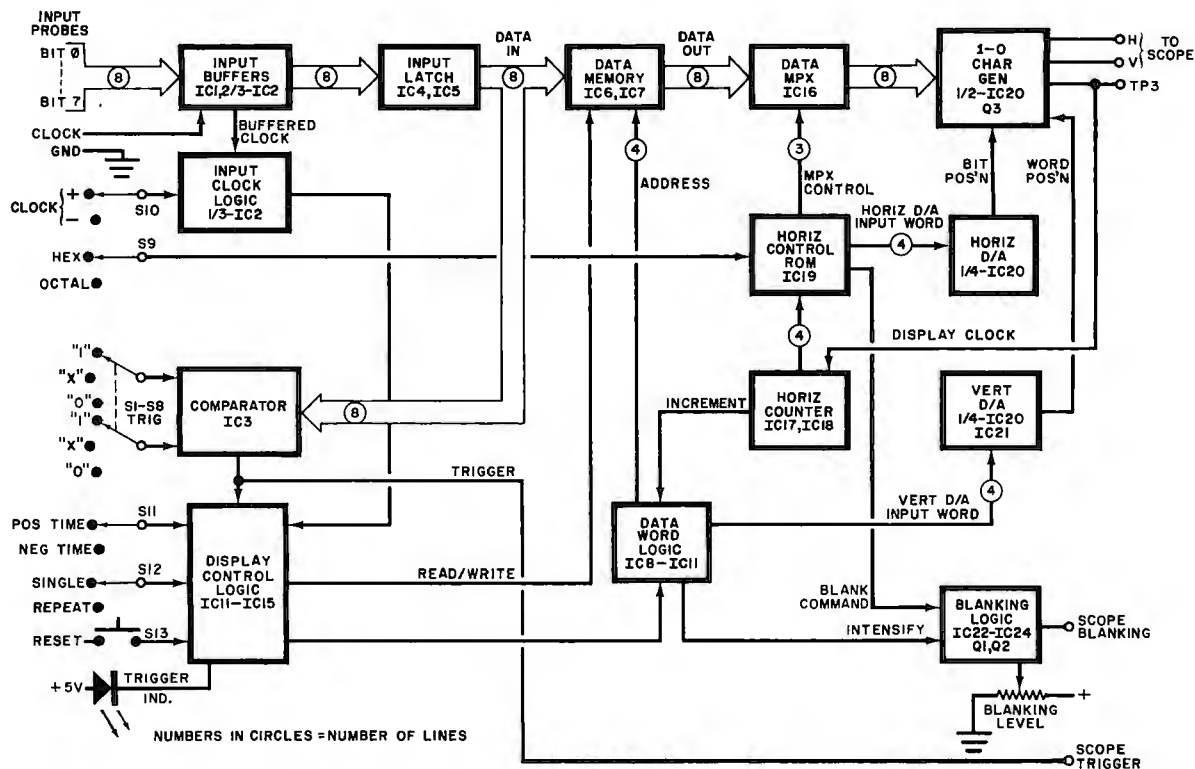


Fig. 2. Block diagram of analyzer shows basic signal routing.

## PARTS LIST

C1—2200- $\mu$ F, 16-volt electrolytic capacitor  
 C2—220- $\mu$ F, 50-volt electrolytic capacitor  
 C3—10- $\mu$ F, 50-volt electrolytic capacitor  
 C4, C5—150-pF, 10% disc capacitor  
 C6—15-pF, 10% disc capacitor  
 C7, C8, C9, C10—0.1- $\mu$ F, 20% disc capacitor  
 C11—300-pF, 10% disc capacitor  
 C12—180-pF, 10% disc capacitor  
 C13—0.01- $\mu$ F, 20% disc capacitor  
 D1, D2, D3—1N4002 or similar rectifier diode  
 IC1, IC2—74LS14 Schmitt-trigger input hex inverter (Fairchild 15-V input only)  
 IC3—74LS15 open-collector output triple three-input AND gate  
 IC4, IC5, IC9—74LS175 quad latch  
 IC6, IC7—7489 RAM (16 $\times$ 4)  
 IC8—74LS161 four-bit synchronous counter  
 IC10—74LS83 four-bit adder  
 IC11, IC12, IC22—7400 quad two-input NAND gate  
 IC13, IC14, IC18—74LS73 dual JK flip-flop (do not substitute)  
 IC15—7473 dual JK flip-flop (do not substitute)  
 IC16—74LS151 8-to-1 multiplexer  
 IC17—74LS90 decade counter  
 IC19—8223 256-bit open-collector output PROM, or similar  
 IC20—LM3900 quad current amplifier  
 IC21—7407 open-collector output hex buffer  
 IC23—74LS21 dual four-input AND gate  
 IC24—7406 open-collector output hex inverter  
 IC25—LM309K 5-volt regulator  
 J1 through J4—UG-625 BNC connector

LED1—Light-emitting diode (any color)  
 Q1, Q3—2N3904 silicon transistor  
 Q2—2N3905 silicon transistor  
 The following resistors  $\frac{1}{4}$  watt, 5%:  
 R1 through R27—4700 ohms  
 R28—3300 ohms  
 R29—470 ohms  
 R30—1000 ohms  
 R31, R32, R33—8200 ohms  
 R34, R35, R36—2700 ohms  
 R37—1800 ohms  
 R38—2000 ohms  
 R39, R40—33,000 ohms  
 R41, R42—56,000 ohms  
 R43, R44, R45—22,000 ohms  
 R46, R47—24,000 ohms  
 R48, R49—130,000 ohms  
 R51, R52—180 ohms  
 R53—47,000 ohms  
 R54, R55—11,000 ohms  
 The following resistors  $\frac{1}{4}$ -watt, 2% tolerance:  
 R56—4700 ohms  
 R57—2400 ohms  
 R58—5100 ohms  
 R59—2700 ohms  
 R50—5000-ohm trimmer potentiometer (Spectrol 43P502 or similar)  
 S1 through S8—double-pole 3-position pc-mounted switch  
 S9 through S12—dpdt pc-mounted switch  
 S13—momentary-action dpst pc-mounted switch  
 S14—spst switch (panel mount)  
 T1—dual-winding power transformer with 16-volt CT and 22-volt winding

Misc.—Line cord, strain relief, mounting hardware, 3 feet of Spectra-Strip multicolored flat ribbon cable (26 gauge), 16-pin DIP socket, 16-pin flat ribbon DIP plug, heat sink for voltage regulator, hookup wire, solder, suitable case and mounting brackets, probe tip connectors, etc.

Note: The following items are available from Paratronics, Inc., Dept. 100, Los Gatos, CA 95030: Complete kit of parts, No. LA-100KIT, with tested IC's, power supply, pc board, case, and manual for \$189.00. For separate parts: drilled double-sided printed circuit board, No. LA-100 PC, \$29.95; programmed horizontal control ROM, No. LA-100ROM, \$15.95; power supply, No. LA-100PS, \$39.95; complete set of switches, connectors, hardware and data probes, No. LA-100HW, \$39.95; Case, No. LA-100CASE, \$39.95. Comprehensive applications and assembly manual, LA-100MAN \$4.95. Please add 5% to above items for shipping and handling within U.S., 10% outside the U.S. California residents, add 6% sales tax.

Free copies of etching and drilling guides for the pc board, components-placement diagram, and horizontal control PROM programming information are available on request by sending a self-addressed stamped 9"  $\times$  12" envelope with 26¢ postage to: POPULAR ELECTRONICS, Dept. LA, One Park Ave., New York, NY 10016.

gital/analog) and the IC20-IC21 vertical D/A circuits to write a 1 or 0 at the proper location on the CRT screen.

The horizontal D/A circuit receives its 4-bit data word from the horizontal con-

trol ROM, which receives its address data from the horizontal counter made up of IC17 and IC18. It is the incrementing of the horizontal counter that causes the beam to move from right to left

across the face of the CRT as the data word is written.

When the last bit is displayed, horizontal counter IC17-IC18 "rolls over" to 0 and sends the increment signal to the

data word logic IC8 through IC11. This causes the address of the data memory to advance to the next word location and simultaneously sends a command to the vertical D/A converter that causes the CRT beam to move down one row in preparation for display of the next word. This process continues until all sixteen of the words of interest have been written on the CRT screen.

If S12 is set to the SINGLE mode, the display control logic prevents the data memory from collecting new input data so that the same information is written on the CRT screen. The writing speed is fast enough so that a flicker-free "snapshot" of the memory contents is displayed.

This snapshot will remain on the screen until the RESET switch S13 is operated, at which time the TRIGGER LED comes on and the analyzer is armed to "capture" another 16-word data set. When S12 is in the REPEAT mode, the display control logic provides an automatic reset signal after the display of each 16-word truth table.

Blanking between bits is provided by the remaining bit of the horizontal control ROM. This ROM performs three separate functions: control of the data multiplexer, control of the horizontal D/A converter, and blanking control. This use of a ROM as a controller is called "microprogramming," an efficient design

technique used in a number of high-level computers. An "intensify" command from the data-word logic permits the trigger word to appear brighter than the other data words on the CRT screen.

The trigger pulse generated by comparator IC3 occurs each time the trigger word appears. The resultant output pulse can be connected to the sync input of an oscilloscope anytime it is necessary to "look" at a specific signal in the circuit under test. This important feature is useful for troubleshooting equipment for glitches, timing, or intermittent problems that occur only during particular logic states.

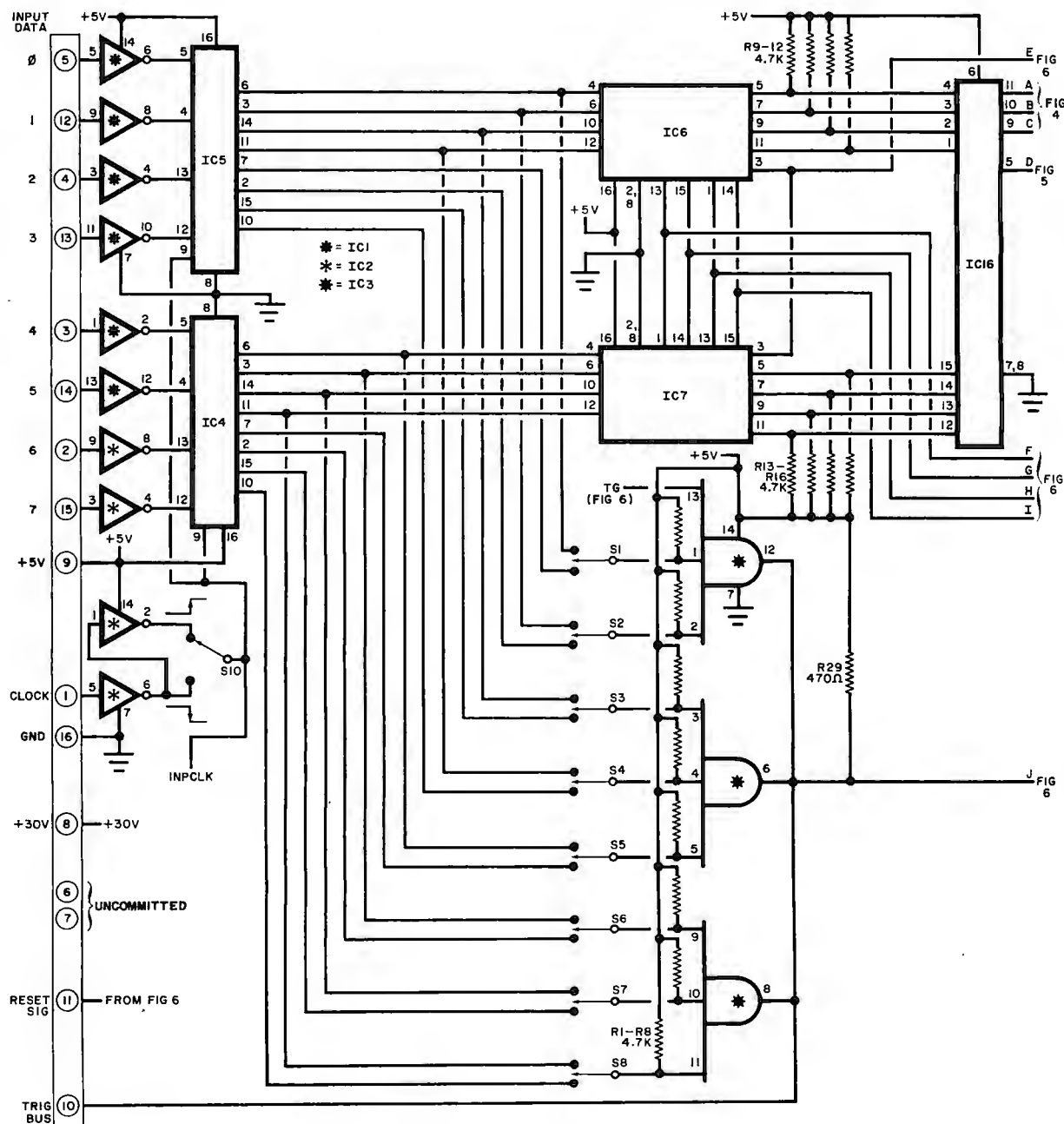


Fig. 3. Input buffers, trigger detector, memory, and data multiplexer.

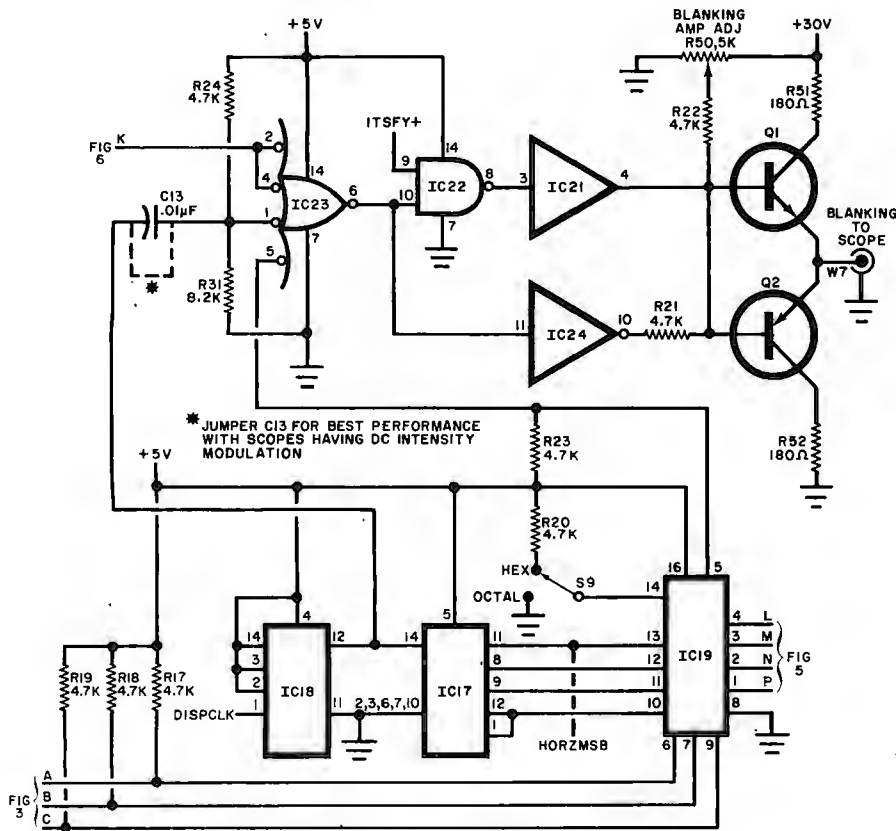


Fig. 4. Vertical control and blanking.

**Construction.** Because of the complexity of the circuit, and the critical placement of certain components, such as the 1-0 character generator, a high-quality, two-sided pc board with plated-through holes is highly recommended for this project. (See Note in Parts List for source from which etching and drilling guide, component layout diagram, and programming information for the horizontal control ROM can be obtained).

Both sides of the pc board contain components. Start assembly by installing the optional sockets for all the IC's on the side of the board labelled IC SIDE. Then mount all resistors, capacitors, and diodes, making sure that polarity-sensitive devices are correctly oriented.

Mount voltage regulator IC25 in place, using silicone grease, or a thermally conductive gasket between its case and the board. A suitable heat sink should be used if the board is to be mounted inside a case. The case provided with the kit comes with a heat sink. Install the IC's, transistors, and blanking control R50. The IC side of the board should look like the assembled board shown in Fig. 8 when you are finished.

Turn the board over to the SWITCH SIDE and mount the 13 control switches. Then, making sure that its base is high enough off the board so that it can pro-

trude through its hole on the top of the case, mount LED1. Install the 16-pin DIP socket for the flat ribbon probe cable. This completes the assembly of the board.

Mount the BNC scope connectors and on-off switch S14 on the front of the case. Then drill a hole so that the blanking amplitude potentiometer mounted on the pc board can be adjusted from outside the case. The top of the case should be punched to accept the 13 switches and the LED indicator. Make sure that all switches can be moved into all their positions. Then put a slot in the front apron to accommodate the flat ribbon cable.

Mount the transformer wherever convenient at the rear of the case. Bring the three-wire ac line cord into the case through a strain-relief.

The input probe cable is made up of a 3' (about 1-m) length of 10-conductor, flat-ribbon cable. The last conductor in the cable is coded black for ground. Connect the ribbon cable to the 16-pin DIP plug with the black cable (ground) mating with pin 16. The other conduc-

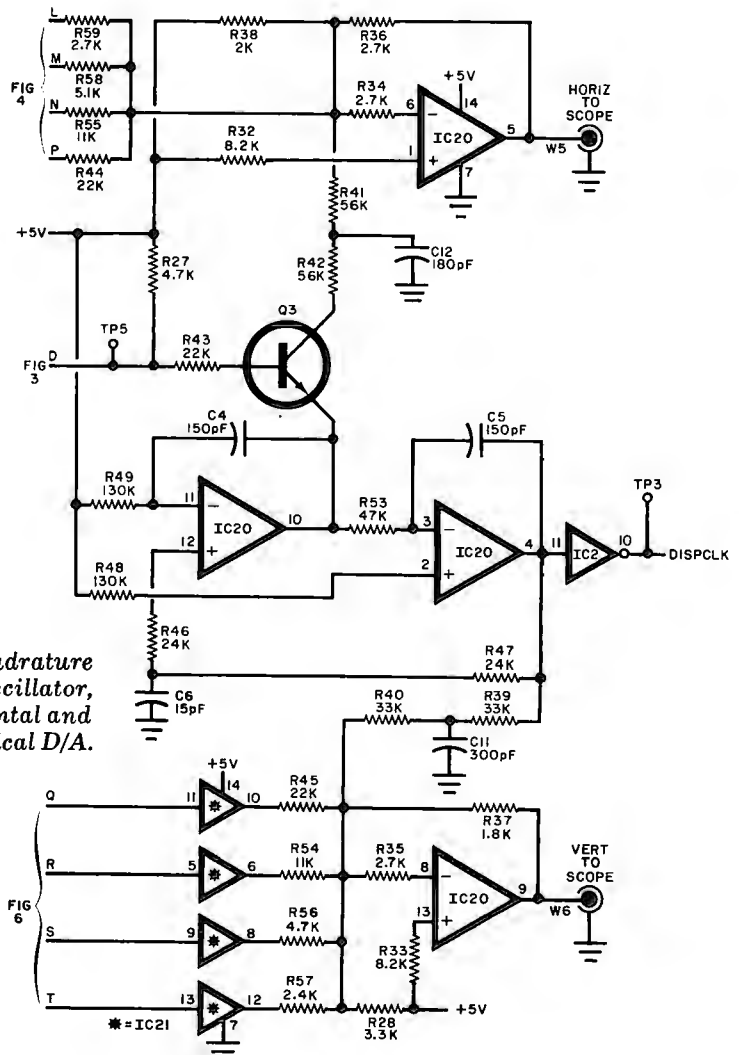


Fig. 5. Quadrature oscillator, horizontal and vertical D/A.

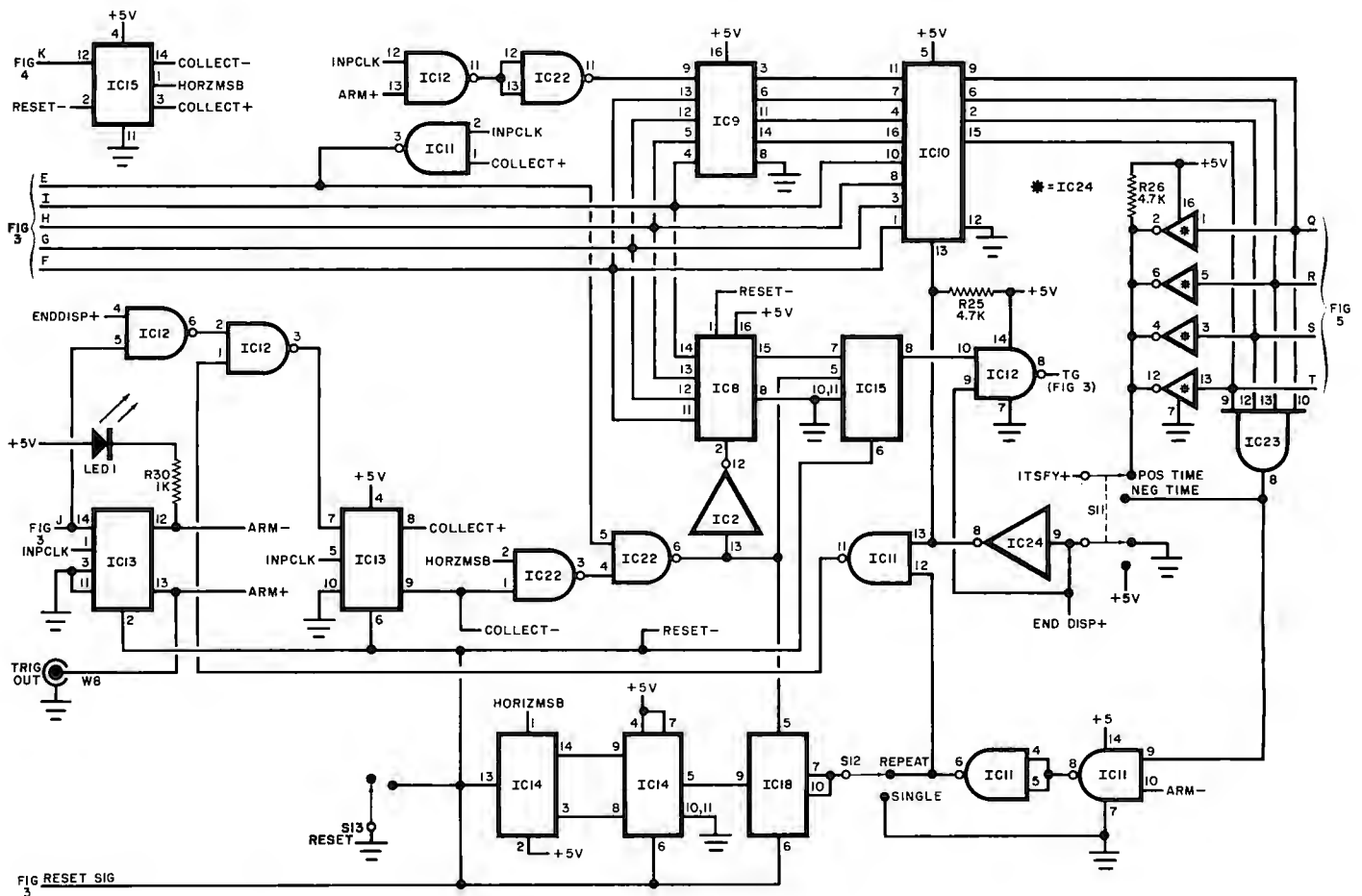


Fig. 6. Horizontal logic and mode control logic.

tors can go to the plug pins in a color-coding scheme.

At the free end of the ribbon cable, separate the 10 leads at least 4" (10.2 cm) and attach universal pin connectors. This type of connector will mate with conventional IC clips and wrapped-wire pins. If desired, ball clips or EZ hooks can be substituted. Plug the probe assembly connector into its socket on the pc board and pass the cable out of the case through its slot on the front apron and assemble the case.

**Checkout.** Plug the line cord into an ac outlet and turn on the power. Verify the output of the 5-volt power supply at TP1 using a voltmeter. With an oscilloscope, check for the presence of an approximately 20-kHz clock at TP3.

Activate the blanking output at W7 by placing the eight trigger switches to the "X" (center) position, selecting the SINGLE mode, depressing the RESET pushbutton to activate the front-panel LED, and flipping the clock polarity switch (S10) one or more times. This last step generates switch contact bounce that simulates an incoming clock pulse train. When the LED goes off, the blanking

signal will appear at board pad W7.

Using the oscilloscope, measure the peak amplitude of the blanking pulse. This pulse can be adjusted up to approximately 30 volts by adjusting R50. **Do not** exceed the manufacturer-specified blanking requirements for your scope.

Set the scope vertical attenuator to approximately 0.5-volt/cm and check the D/A signals at W5 (horiz) and W6 (vert). The waveforms should appear as "descending staircase" waveforms, with the W5 signal much higher in frequency.

Using the scope in the XY mode, connect the horizontal, vertical, and blanking outputs of the analyzer to the appropriate scope connectors. To assure a clean display, it is suggested that you

use coaxial cables for the interconnections between the analyzer and scope.

Place the scope horizontal and vertical amplifiers to approximately 0.5-volt/cm. With the analyzer input probes unconnected, and the trigger switches still set to the "X" (center) position, depress the RESET pushbutton to illuminate the LED. When the clock polarity switch (S10) is flipped, a truth table should appear on the CRT. Adjust the scope controls until the display is centered on screen and fills most of it.

Adjust the focus and intensity controls to obtain a clear well-defined display.

One interesting feature of the Logic Analyzer is that it can be used to observe and learn its internal operation.

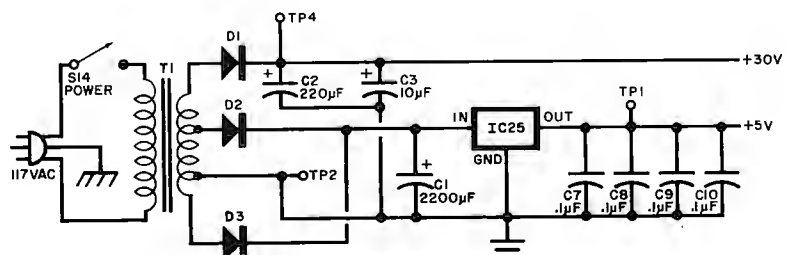


Fig. 7. Power supply is 5 volts, regulated.

For example, to see how the 4-bit address of the data memory sequentially changes during data collection, connect the first four data probes (BIT 0 through BIT 3) to pins 14, 13, 12, and 11 respectively, of IC8. The remaining four probes should remain unconnected. Connect the input clock probe to IC2 pin 10 (or TP3) and set the analyzer controls to HEX, REPEAT, NEG TIME, and the clock-polarity switch to the falling edge position. Set the first four trigger switches (S1 through S4) to 1111 and the last four to X. The selected trigger word should appear intensified at the bottom of the table, with the 15 prior binary address words listed in sequence above it.

## LOGIC ANALYZER SPECIFICATIONS

**Trigger Word:** 0 to 8 bits wide; selected by eight 3-position switches; choose 0, 1, or X (don't care).

**Display Format:** Sixteen sequential 8-bit words arranged in an octal or hexadecimal truth table.

**Positive Time Display:** Trigger word intensified at top of truth table with next 15 data words listed below.

**Negative Time Display:** Trigger word intensified at bottom of truth table with prior 15 data words listed above.

**Single Mode:** Continuous display of one 16-word truth-table until RESET button is activated.

**Repeat Mode:** Display of sequential 16-word truth tables.

**Maximum Input Data Rate:** 8 million bytes/second.

**Input Clock:** Provides timing reference for input data; selectable positive or negative clock edge.

**Trigger Indicator:** LED on front panel indicates when trigger word has occurred.

**Trigger Output:** Auxiliary scope sync pulse; generated when trigger word occurs.

**Input Probes:** Constructed of color-coded flat-ribbon cable terminated in universal pin connectors.

**Input Load:** Inputs are buffered for minimal loading and have hysteresis for noise rejection.

**Power Supply:** +5 volts at 700 mA, +30 volts at 25 mA.

**Logic Family Compatibility:** TTL, DTL, RTL, MOS, CMOS, to 15-volt logic swing.

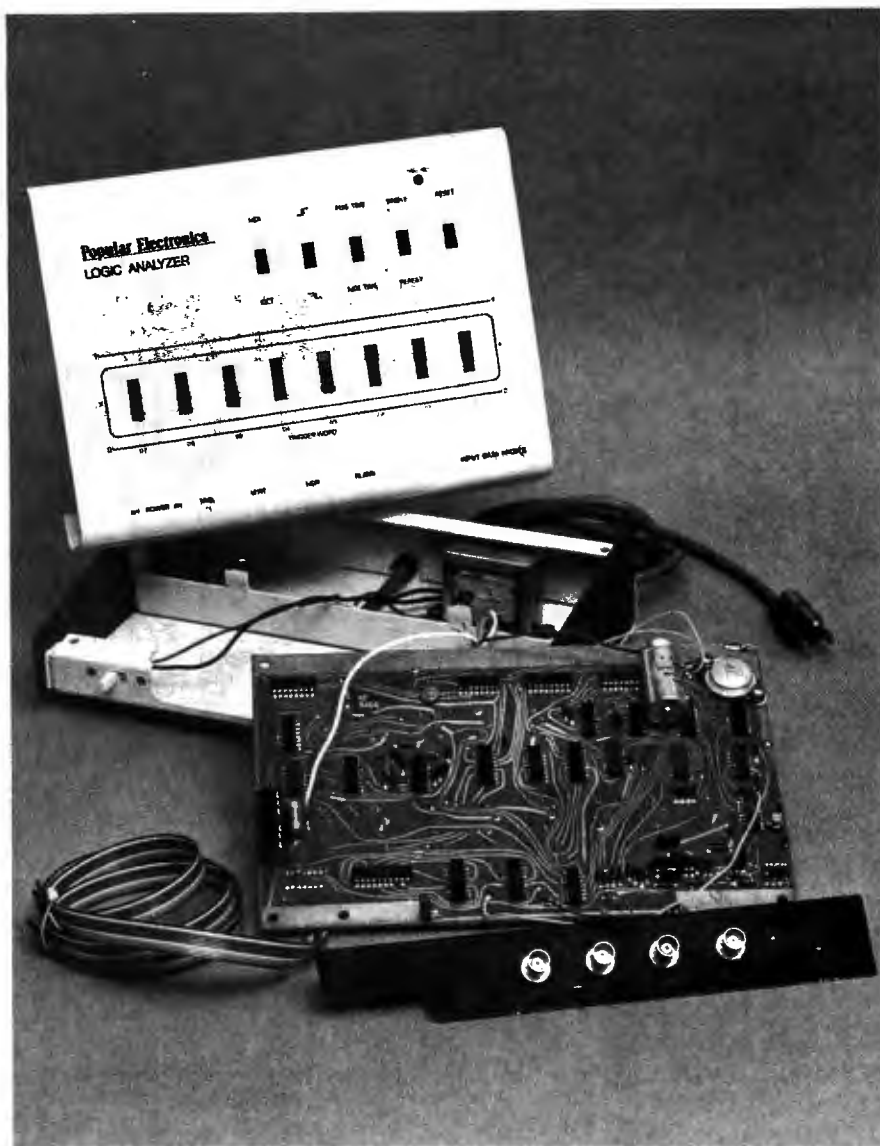


Fig. 8. Completed board and connector panel ready for assembly.

Continue to familiarize yourself with the operation of the analyzer by triggering from different address locations and changing the settings of the display control switches. The probes can be moved to other portions of the circuit, such as the horizontal counter, display-control logic, and the data-word logic.

You can couple the first four probes to the counter (7490 or similar) in any digital counter circuit to examine the operation of that circuit. In fact, the right side of the hex portion of the display in Fig. 1 shows the output of a "good" 4-bit counter while the left side shows the output of a counter whose MSB (most significant bit) is stuck at 0. Using this technique, you can follow the signals through almost any digital circuit and be able to "snapshot" any block of pulses so that they can be examined for faulty pulses.

The analyzer shows its flexibility when

used to check a computer or program. The octal portion of Fig. 1 shows the steps of a typical 8080 ADD and STORE program leading up to a branch instruction. The trigger word 00 000 001 is the branch address and is intensified at the bottom of the display.

**In Closing.** The Logic Analyzer we have described can be used for all types of testing and troubleshooting of digital circuits and systems. However, its true flexibility is revealed when the instrument is used for testing and troubleshooting digital-computer and other time-dependent circuits and systems. What makes our Logic Analyzer particularly attractive is its relatively low price. Used as an accessory to an existing oscilloscope and built from scratch, it costs only a fraction of commercially made logic analyzers on the market. ◇

# NEW, PRACTICAL OP AMP CIRCUITS

BY SOL D. PRENSKY

## including a differential pc board tester

**AS WE WILL** learn from the two very useful circuit applications described here, the operational amplifier (or op amp) can be used in strikingly different ways.

**In-Circuit Current Testing.** Since an op amp is basically a differential amplifier, it can be used in a unique metering circuit to determine the presence of current flow in a conductor—and approximately the amount of cur-

rent—whether or not the conductor is a copper wire or a pc foil trace. This can be done without breaking the conductor.


Such a metering device can come in handy if you have a crowded pc board and you suspect one of the active elements (transistor, diode, or IC) is not working. Instead of risking pc board damage due to the heat required to remove the suspect semiconductor, or having to cut a trace to insert a meter, all you have to do is press a couple of

sharp probe tips to the copper trace at (for example) the supply bus, and see if that particular element is drawing current, and if the magnitude of the current is within specifications.

The circuit for the current tester is shown in Fig. 1 in two forms—depending on whether you want to use a low-level (1-volt) dc voltmeter or a current meter as the readout.

Operation is based on the fact that at room temperatures, all conductors have


Fig. 1. Op amp in (A) measures slight voltage differential between two probes, amplifies it, and drives dc voltmeter. Addition of another op amp in (B) permits driving ammeter.

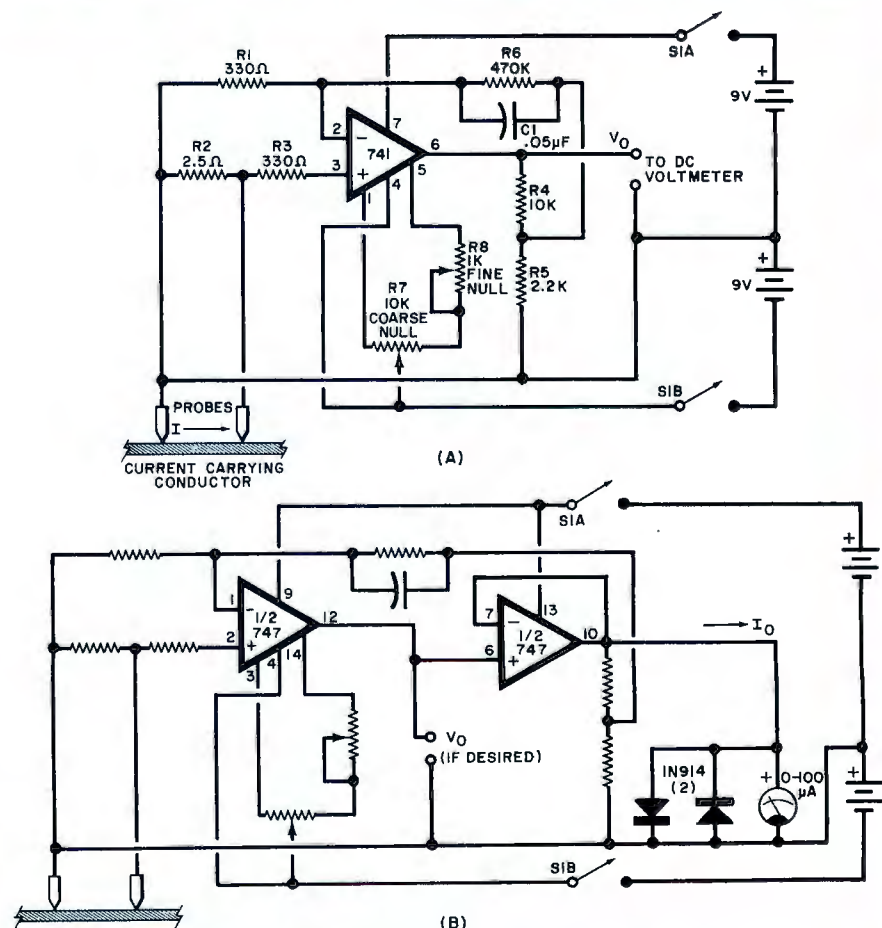
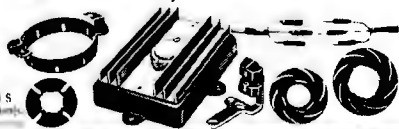
# ★ PUT THE "IGNITION OF THE FUTURE" ON YOUR CAR TODAY!

MODERNIZE and Bring Your Car "UP-TO-DATE"  
with the MOST EFFICIENT Ignition ever invented!

★ End "Tune-Up" Problems FOREVER  
caused by Points and Condensor



## **ALLISON XR-700**

with the Exclusive...Solid-State Voltage Regulator.

The ONLY Ignition System that has COMPLETELY overcome  
the Problems that have baffled the Auto Industry for Years!  
**SO RELIABLE (99.9+%)... SO PERFECTED...**  
that it will soon be STANDARD on most Future new Cars!

ALLISON Rated #1 by Official Testing Laboratory  
as the BEST "Fuel Saving" Ignition System  
of ALL the Different Ignition Systems Tested!

★ The "XR-700" is a COMPLETELY NEW Ignition System  
employing the Most Advanced Technology, that replaces the  
inefficient Points and Condensor with an Infrared Light Beam  
to Trigger the Latest type of Solid-State Power Components.  
Once installed... "XR-700" has NO moving Parts to wear out  
or adjust. It works without Friction or wear. Not affected by  
Dirt, Oil, Moisture, Vibration or extreme Engine Temperatures!  
**RUGGED and RELIABLE!**

★ The "XR-700" is engineered to OUTLAST YOUR CAR!

★ The "XR-700" produces the MAXIMUM "High Energy"  
Long Duration Spark... from your present car's Ignition Coil.  
This permits the Positive Firing of Spark Plugs, even under the  
most Adverse conditions. Also, Eliminates "Engine Misfire,"  
resulting in more COMPLETE COMBUSTION! Thus you get  
IMPROVED Fuel Mileage, a HIGHER Performance Level...  
keeps Plugs FROM FOULING and gives LONGER Plug Life!

### Customers Report:

- ★ "IT MORE THAN PAYS FOR ITSELF!"
- ★ INCREASES Gas Mileage up to 30%!
- ★ SAVES Money on Costly "Tune-Ups"!
- ★ Gives Continuous PEAK Performance!
- ★ QUICKER Starting in Any Weather!
- ★ Smoother Running... Faster Acceleration!
- ★ Plugs Last Up to 4-Times LONGER!

★ Reliability PROVEN in Millions of Customer Miles to be so  
exceptionally GOOD... that every "XR-700" has a LIFETIME  
WARRANTY! FREE Repair or Replacement for as long as  
you OWN the Unit!... and even if you CHANGE Cars, Allison  
will supply you the necessary PARTS to fit ANY Point-Type  
Distributor... FREE! (Include \$2 for Postage & Handling).

★ FITS ALL CARS, Domestic & Foreign, 4, 6 or 8-Cylinder.

### ★ DO-IT-YOURSELF...EASY INSTALLATION!

The New "XR-700" is Completely Factory Assembled...  
Thoroughly TESTED! New Precision "Drop-In" Mounting  
Bracket, with color-coded, "Snap-Together" wire connections  
No Distributor Removal necessary Protected against Incorrect Hook

● Thousands sold at \$59.95 ● ONLY  
**\$39.95**  
NOW! Allison's Production  
Technology offers you the  
same Premium Quality XR-700  
at this SPECIAL LOW Price... (Cal. Res. add Tax)  
**COMPLETE**  
THAT'S EVERYTHING...INCLUDING POSTAGE & INSURANCE

★ ORDER WITH CONFIDENCE...  
install the "XR-700", and prove to your own SATISFACTION  
that it is as advertised, or return it within 30 days for a FULL  
Refund of the Purchase Price

★ SAVE! ORDER FACTORY DIRECT.  
Send Check or M.O., State Car Make, Year, No. Cylinders

★ MASTER CHARGE or BANKAMERICARD Card Holders:  
ORDER by TOLL-FREE PHONE. (800) 423-6625, Ext. 2  
or Send us (1) Your Number, (2) Interbank No., (3) Exp. Date.

★ SEND for FREE BROCHURE  
and Comparison Sheet.

"CB" USERS: The "XR-700" completely ELIMINATES  
the Major Cause of Primary Ignition Noise Interference.

★ If you have already installed a "Capacitive Discharge" Ignition  
Convert your "C-D" Unit to BREAKERLESS!  
INCREASE ITS EFFICIENCY with "XR-CD"... only \$29.95

★ America's Oldest and Largest Manufacturer  
of Opto-Electronic Ignition Systems. (E)



**ALLISON AUTOMOTIVE CO.**

1267 - PO, East EDNA PL., COVINA, CAL. 91722

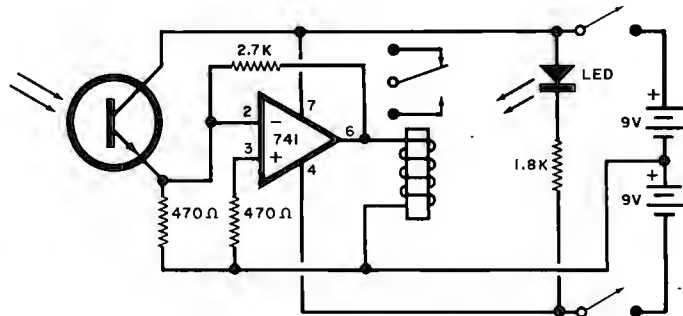


Fig. 2. Phototransistor and op amp unite to form light-sensitive relay driver that can be activated by a flashlight across the room.

some resistance (albeit small) and, when current flows through the conductor, there is a slight voltage drop between any two points along the conductor. Typically, such voltage drops are in the microvolt range; but with a voltage amplifier having a gain of 1000 or more, the minute voltage can be brought up to a reasonably measurable value.

The basic circuit shown in Fig. 1A uses an 8-pin mini DIP 741 with a dc voltmeter. This circuit takes advantage of the high common-mode rejection ratio (CMRR) of the op amp to reject any noise pickup voltages that are common to both input terminals. To keep the value of feedback resistor  $R_6$  to a reasonable value, the output of the op amp (pin 6) drives the combination of  $R_4$  and  $R_5$  with the feedback taken from the junction of these two resistors. This voltage divider action in the feedback voltage multiplies the conventional gain  $(1 + R_6/R_1)$  by the voltage divider ratio  $(R_4 + R_5)/R_5$  to produce a theoretical voltage gain of approximately 1400 times 5.5 or 7700.

Since any residual offset voltage generated within the op amp is also multiplied by this factor, two offset (coarse and fine) potentiometers ( $R_7$  and  $R_8$ ) are provided to trim the offset close to zero with the input probes shorted.

Figure 1B uses a 747 dual op amp package to drive a 100- $\mu$ A meter that is used as the readout. Two diodes are used to protect the meter from accidental overloads. Operation of the circuit is otherwise the same as that of Fig. 1A.

In experiments with these circuits, probing a current-carrying conductor produced "ball-park" figures of 12 mV/inch or 12  $\mu$ A/inch, for each milliampere of current flow. In general, it would be too much to expect either precision or close calibration results from such a general-purpose circuit as opposed to a specialized (and expensive) instrumen-

tation amplifier. Nevertheless, the circuits of Fig. 1 do indicate current flow in a conductor and can be reasonably calibrated. For improved stability, a premium op amp such as Precision Monolithics OP2, National LF156, etc., may be used. Where currents greater than approximately 1.5-mA are concerned, the sensitivity of the circuit can be reduced by lowering the value of feedback resistor  $R_6$ .

**Photo Switch.** The circuit shown in Fig. 2 illustrates how an op amp, in conjunction with a phototransistor and relay, can be used to activate a relay with a conventional flashlight used as the remote "transmitter." With the relay connected across the speaker coil leads, this circuit makes an excellent "commercial killer." The op amp's pinout is for an 8-pin mini DIP.

The phototransistor is connected to the op amp to produce an inverter amplifier gain of about 50. For most "across the room" distances, using a typical flashlight, the output of the op amp will be sufficient to energize a sensitive relay. (A Sprague 401-A050-A05 requires about 6 mA at 3 volts, for example.) If any other type of relay is to be used, keep in mind that the op amp can deliver only about 10 mA at best, so if higher currents are required, a transistor relay driver must be used.

Although almost any type of sensitive phototransistor can be used, the prototype involved half of an opto-isolator (LED and phototransistor in one package) that had been sawed in half. In these units, the phototransistor sensitive area is protected from ambient light by a built-in IR filter so that the quiescent current before flashlight illumination is practically negligible. The LED power-on indicator requires about 10 milliamperes for operation and may be eliminated if it is not required.

**A**LTHOUGH "beginner's" shortwave receivers provide an inexpensive entry to a fascinating hobby, they do have limitations. A major one is poor dial calibration, which makes monitoring and QSL procedures difficult.

Fortunately, external circuitry can compensate for this limitation. The digital frequency display project presented here will allow the user to determine a transmitter's frequency to the nearest kilohertz on a bright, stable LED display. It accepts an input signal from the receiver's local oscillator, converts the signal to a TTL-compatible form which is then counted. Programmable counters are pre-loaded to compensate for the receiver i-f, thus allowing direct readout of the received frequency. The project will work with most single- and multiple-conversion receivers from the longwave broadcast band through 10 meters (30 MHz). Total project cost is about \$110.

**About the Circuit.** The schematic diagram of the digital frequency readout is shown in Fig. 1. An input signal from the receiver's local oscillator is coupled through *C1* and *R1* and applied to the gate of *Q1*, an n-channel FET. Diodes *D1* and *D2* clip signals exceeding + or -0.7 volt, protecting the FET from excessive signal voltages. The output of *Q1*, developed across *R3*, drives emitter follower *Q2*, an npn bipolar transistor. This combination results in a two-stage amplifier presenting a high input impedance to minimize local oscillator loading and a low-impedance output at TTL lev-

BY DAVID L. MATTIS

# DIGITAL FREQUENCY READOUT FOR SHORTWAVE RECEIVERS

*Programmable counters  
provide direct  
display of received  
frequency to 30 MHz.*

els. Ferrite beads *L1* and *L2*, together with disc capacitor *C3*, are used for r-f decoupling on the +5-volt line.

A two-stage Schmitt trigger composed of NAND gates *IC1A* and *IC1B* converts the amplified local oscillator signal into a square wave, which is then gated by *IC1C*. The gating interval (10 milliseconds) is provided by a crystal controlled time base and divide chain. A 4-MHz square wave generated by *IC19* is first divided by 4 by the flip-flops in *IC2*. The 1-MHz output of the second flip-flop is further divided by two dual decade counters (*IC3* and *IC4*) to yield a 100-Hz reference signal. The second decade counter in *IC4* is wired as a bi-quinary counter to provide a symmetrical square-wave output signal. This counter also supplies three control signals to *IC5*, which generates the latch and preset control pulses at the end of each counting (gate) interval which govern the counting and display *IC's*.

For a 10-ms counting interval, a 50-Hz gating signal is required. It is obtained by dividing the symmetrical 100-Hz output of *IC4* by two. This is performed by *IC6*, a JK flip-flop. The 50-Hz square


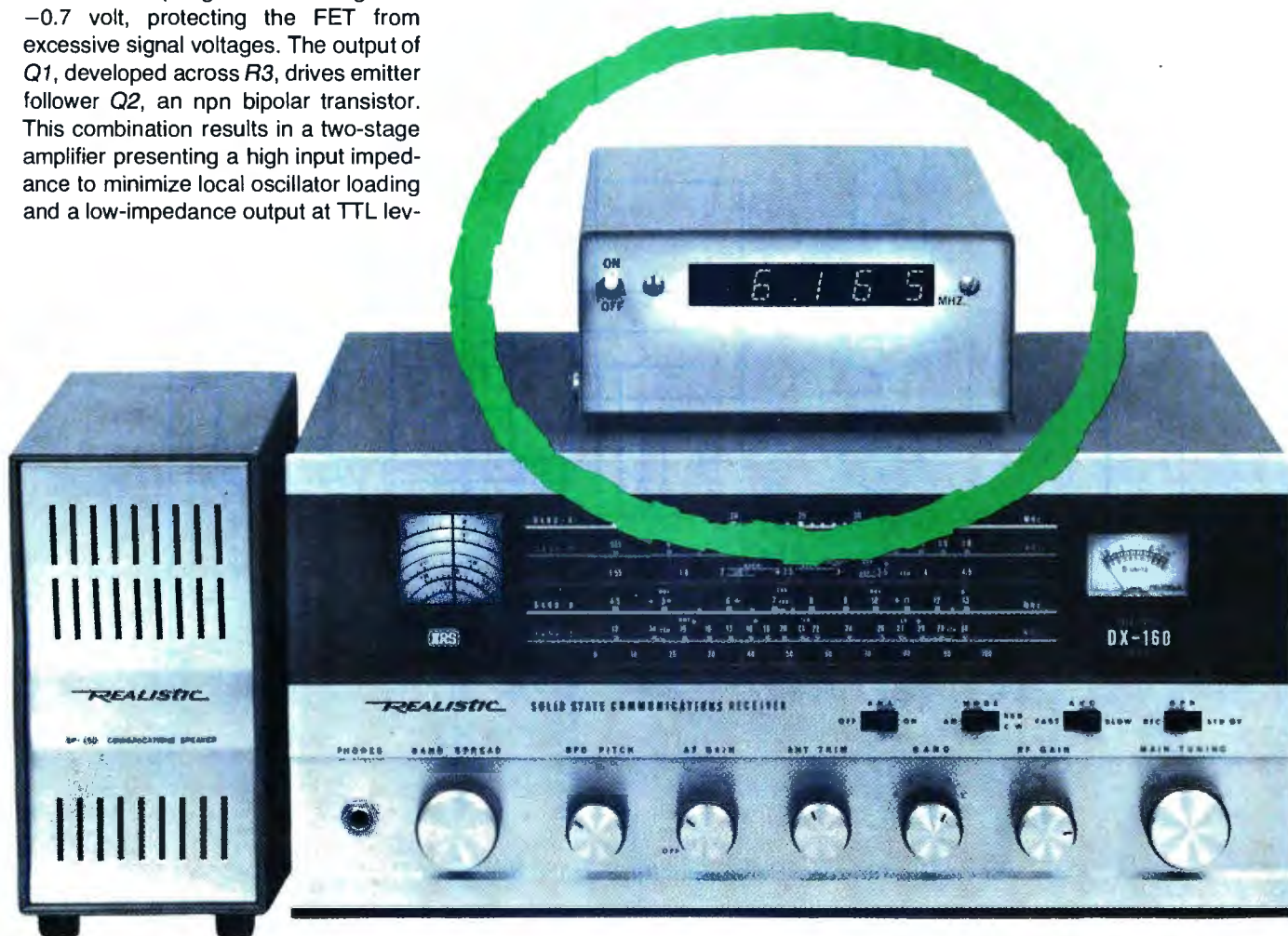


Fig. 1. Schematic diagram. For simplicity, only one decade of display is shown.

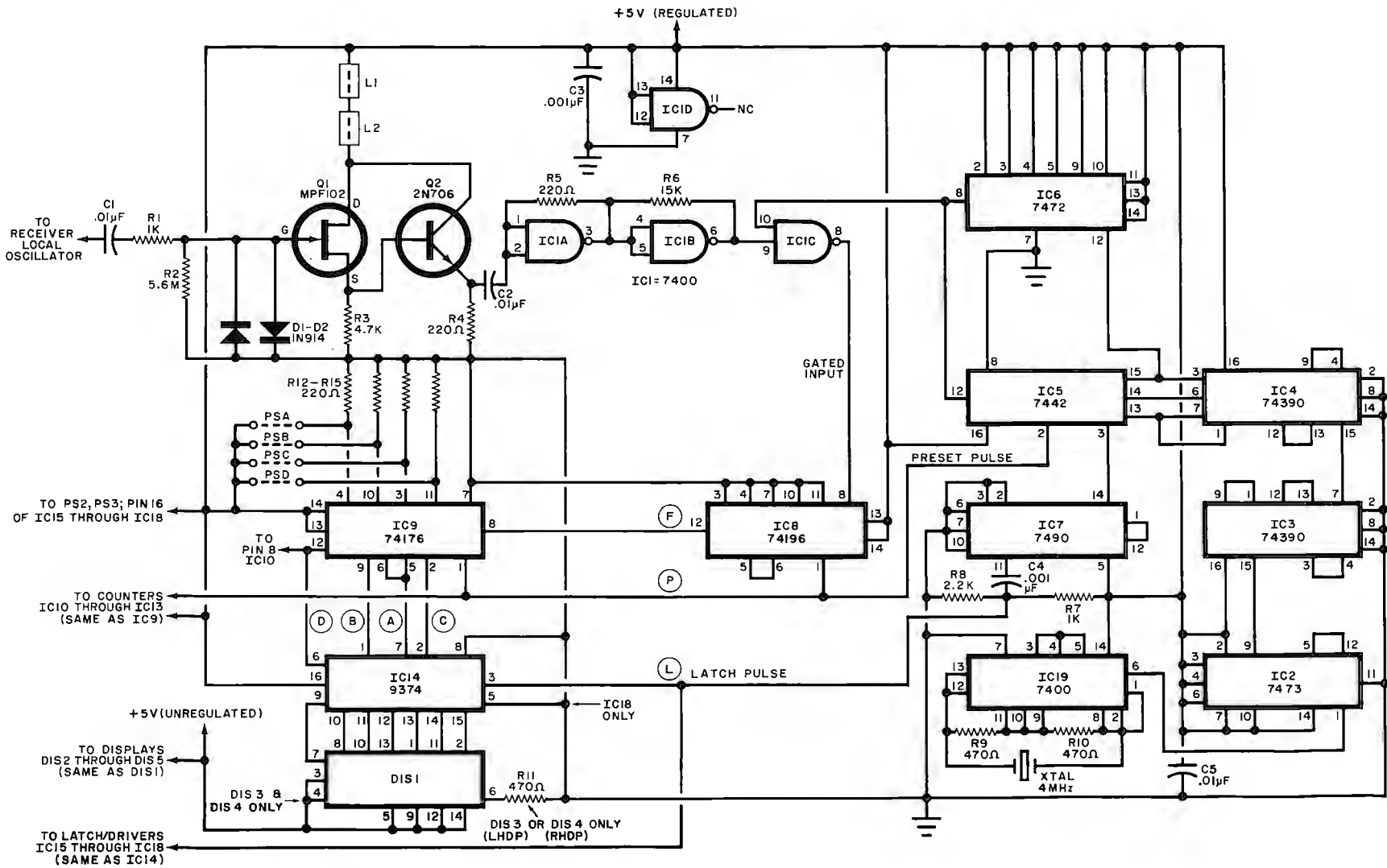

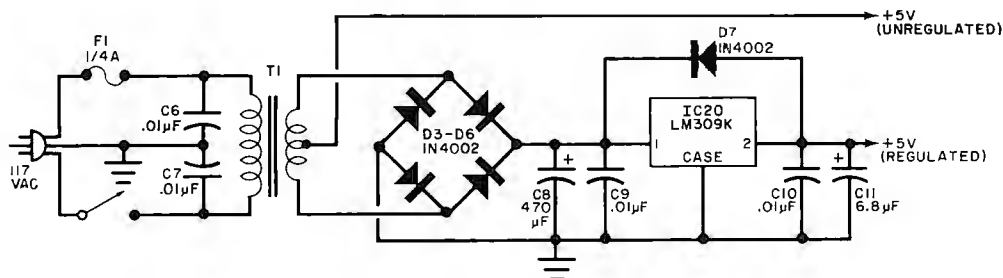


Fig. 2. Schematic diagram of the power supply.

wave is applied to both IC5 and to one input of NAND gate IC1C. When the gate signal is high (for 10 ms), IC1C passes an inverted version of the squared local oscillator signal to counters IC8 through IC13. During the 10-ms "low" period, IC5 produces the latch and preset control pulses.

Even though the counters resolve the local oscillator frequency to the nearest 0.1 kHz during the 10-ms gate interval, the received frequency is displayed only to the nearest kilohertz. The use of the undisplayed 0.1-kHz counter (IC8) eliminates the bothersome "bobble" in the least significant digit in other frequency readouts, thus providing a steady frequency display. A 1-kHz bobble occurs only when the counter is at the borderline between two frequencies—for example, 6.1649 and 6.1650 MHz.

Counter IC8 is specified as a 74196 programmable counter IC, but IC9 through IC13 are specified as 74176 IC's. The 74196 is used to insure reliable performance to 30 MHz. However, a hand-picked 74176 which can function up to 30 MHz can be used in place of the costlier 74196. The preset feature of these IC's permits the display of the re-

ceived signal's frequency, even though the counters are working with the local oscillator frequency, which is actually higher or lower by the intermediate frequency of the receiver. Counters IC9 through IC13 can be pre-loaded with any value determined by programming jumpers or switches at points PSA through PSD. The counters are loaded with this number at the reception of the preset pulse prior to the initiation of each counting interval.

At the end of every tenth counting cycle, a latch pulse appears at the output (pin 11) of IC7. It is then differentiated by C4, R8, and R7 and applied to latch/decoders IC14 through IC18. When this happens, the binary information accumulated in the programmable counters is transferred, stored, and decoded for display on seven-segment LED readouts DIS1 through DIS5. The latch pulse is generated by IC5. Although preset pulses are produced after each counting interval, only one in every ten counts is transferred to the 9374 latch/decoders (IC14 through IC18). This is so because IC7 divides the input signal from IC5 to produce a latch pulse with a frequency of 10 Hz.

As a result, the display flickers noticeably when the frequency is changing. Also, blurring and readout of spurious eight's—common problems with seven-segment displays—do not occur during a shift in frequency. Rather, the 10-Hz latch rate permits the display to track each frequency change with legible readout values.

The project's power supply (Fig. 2) is



Fig. 3. Photo of prototype.

## PARTS LIST


C1, C6, C7, C9—0.01-μF, 1000-volt disc ceramic capacitor  
C2, C5, C10—0.01-μF, disc ceramic capacitor  
C3, C4—0.001-μF disc ceramic capacitor  
C8—470-μF, 25-volt electrolytic capacitor  
C11—6.8-μF, 25-volt tantalum capacitor  
D1, D2—1N914 switching diode  
D3 through D7—1N4002 rectifier  
DIS1 through DIS5—MAN-1 or MAN-64 common anode seven-segment LED display  
F1—¼-ampere, 250-volt, 3-AG slow-blow fuse  
IC1, IC19—7400 quad 2-input NAND gate  
IC2—7473 dual JK master-slave flip-flop  
IC3, IC4—74390 dual 4-bit decade counter (Texas Instruments)  
IC5—7442 BCD-to-decimal decoder  
IC6—7472 JK master-slave flip-flop  
IC7—7490 decade counter  
IC8—74196 45-MHz presettable decade counter (see text)  
IC9 through IC13—74176 25-MHz presettable decade counter

IC14 through IC18—F9374PC latch/7-segment decoder/driver (Fairchild)  
IC20—LM309K 5-volt regulator  
L1, L2—Ferrite bead (¼" × ⅛" or 3.2 × 3.2 mm)  
Q1—MPF102 n-channel JFET  
Q2—2N706 npn transistor  
The following resistors are ¼-watt, 5% tolerance:  
R1, R7—1000 ohms  
R2—5.6 megohms  
R3—4700 ohms  
R4, R5, R12 through R29—220 ohms  
R6—15,000 ohms  
R8—2200 ohms  
R9 through R11—470 ohms  
S1—SPST miniature toggle switch  
PS1 through PS3—DIP switches (see text)  
T1—12.6-volt, 1.2-ampere center-tapped transformer  
XTAL—4 MHz, 0.0025% tolerance crystal  
Misc.—Suitable enclosure (7¼" × 6¼" ×

2¾" or 18.4 × 15.9 × 7 cm suggested); red Plexiglas bezel (5¼" × 1" or 13.3 × 2.5 cm); transistor sockets; IC sockets or Molex Soldercons; heat sink compound; TO-3 heat sink (1¼" or 3.2-cm fins); metal spacers; machine hardware; line cord; coaxial cable; rubber grommets; hookup wire; solder; fuseholder; etc.

Note: The following are available from Mattis Electronics, Box 162, Morton Grove, IL 60053. Set of three etched, drilled and plated pc boards (No. SW-1), \$18.95; 4-MHz precision crystal (No. SW-2), \$9.95; Five F9374PC latch/decoder/driver IC's (No. SW-3), \$15.95; Kit of parts including three pc boards, crystal, IC's, discrete semiconductors and pc board components (No. SW-4), \$74.95; Complete kit of parts including enclosure and power-supply components (No. SW-5), \$109.95. All prices include shipping charges within the USA. Illinois residents add 5% sales tax.

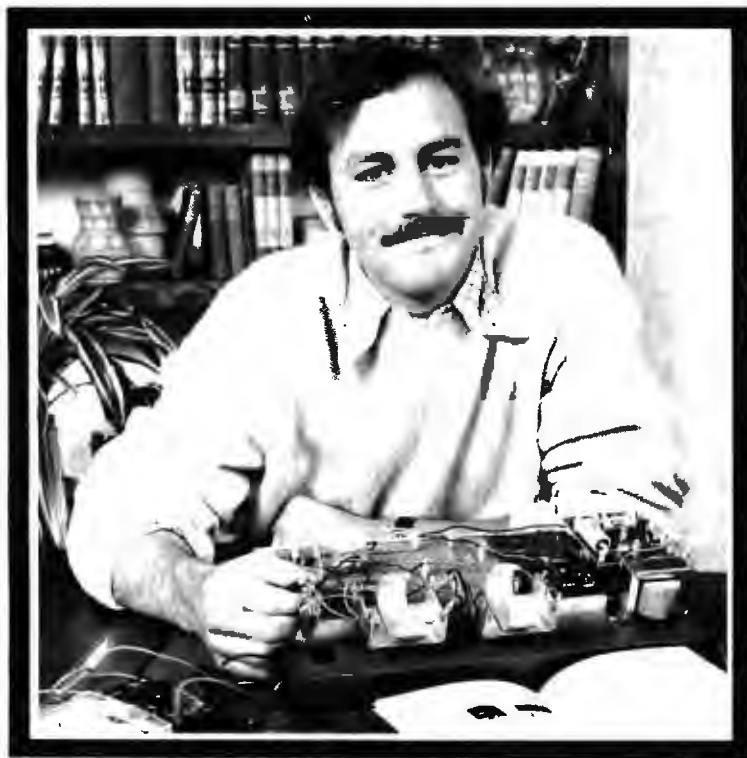**CIE has  
a terrific idea  
for a few people  
who know what  
they want.**



# If you want success in electronics... if you want the skills people are glad to pay for... find out about CIE training.

## It's a terrific idea that can get you on your way to success in electronics troubleshooting.

Let's face it, learning valuable new skills isn't something you just breeze through. Especially in a modern technological field like electronics troubleshooting. You've got to really *want* success if you're going to build your skills properly.

But, oh boy, the rewards when you do! In today's world, the ones who really *know* electronics troubleshooting find that people... even industries... look for their help.

What about you? How much do you want the thrill of success... of being in demand? Enough to roll up your sleeves and work for it?

### Why it pays to build troubleshooting skills.

Suppose the automated production controls on an assembly line break down. Imagine how much money the manufacturer can lose when help doesn't come *fast*! And it takes a skilled electronics troubleshooter to move in... locate the problem... solve it... and get the lines moving again.

Or take a TV station. Breakdowns are costly in broadcasting where time is money. Viewers won't sit forever waiting for sound or the picture to come back. Before they change channels, the station needs to get back on the air again—with the help of a skilled troubleshooter.


No question about it. Building new skills in electronics troubleshooting is an investment in your future. It's well worth the effort.

### Why you should get CIE to help you do it.

Troubleshooting starts with *ideas*... principles. CIE's Auto-Programmed® Lessons help you get the idea—at your own most comfortable pace. Step by step at home, you explore each principle—each theory—until you understand it thoroughly and completely. Then you start to use it.
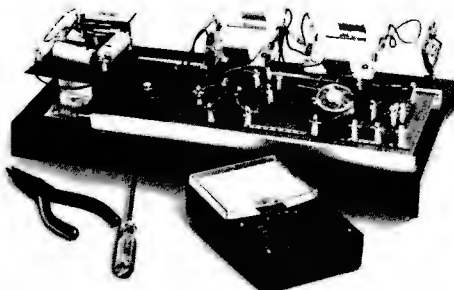
### How CIE helps you turn ideas into reality.

If you're a beginner, you start with CIE's Experimental Electronics Laboratory. You actually perform over 200 experiments to help you grasp the basics. Plus you use a 3-in-1 Precision Multimeter to get your first taste of the testing, checking, analyzing steps you take in troubleshooting!



### How 3 practical steps help you build troubleshooting skills.

You'll take your first practical step in professional troubleshooting when you build your own 5MHz triggered-sweep, solid-state oscilloscope.

As a trained troubleshooter, you'll use your oscilloscope the way a doctor uses his X-ray machine. As a student, you learn how to "read" waveform patterns on a big, 8cm. x 10cm. screen... how to "lock them in" for closer study... how to understand and interpret what they tell you.

Your second practical, skill-building step begins when you get your Zenith 19-inch diagonal, solid-state color TV—featuring nine removable modules! Now's your chance to apply the new skills you learned with your oscilloscope!

With CIE's guidance, you perform actual service operations—the kind you'd handle on the job as a trained troubleshooter! Using the TV, you learn to trace signal flow... detect and locate malfunctions... restore perfect operating standards... just as you would with any sophisticated electronics equipment.



Finally, step three rounds out your experience as you work with a completely solid-state color bar generator—actually a TV signal transmitter that produces ten different display patterns on your TV screen!

You study a gated color bar rainbow... crosshatch lines... dot patterns.

You explore digital logic circuits... observe the action of a crystal-controlled oscillator!

This practical, "hands on" training takes concentration and effort. But it's enjoyable and rewarding. And it's a great way to prepare for a troubleshooting career!

### Why it's important to get your FCC License.

For some troubleshooting jobs, you *must* have your FCC License. For others, employers often consider it a mark in your favor. It's government-certified proof of specific knowledge and skills!

Almost 4 out of 5 CIE graduates who take the exam get their Licenses. More than half of CIE's courses can prepare you for it... and the broadest range of career opportunities!

### Free catalog!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name of this magazine. We'll send you a copy of CIE's FREE school catalog—plus a complete package of independent home study information! For your convenience, we'll try to have a representative call to help you with course selection. Mail the card or coupon... or write: CIE, 1776 East 17th Street, Cleveland, Ohio 44114.

### CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

☐ YES... I want to succeed in electronics. Send me my FREE CIE school catalog—including details about troubleshooting courses—plus my FREE package of home study information!

NAME (please print)

ADDRESS APT.

CITY

STATE

ZIP


AGE PHONE (area code)

Check box for G. I. Bill information:

☐ Veteran ☐ Active Duty

PE-28

**Mail today!**

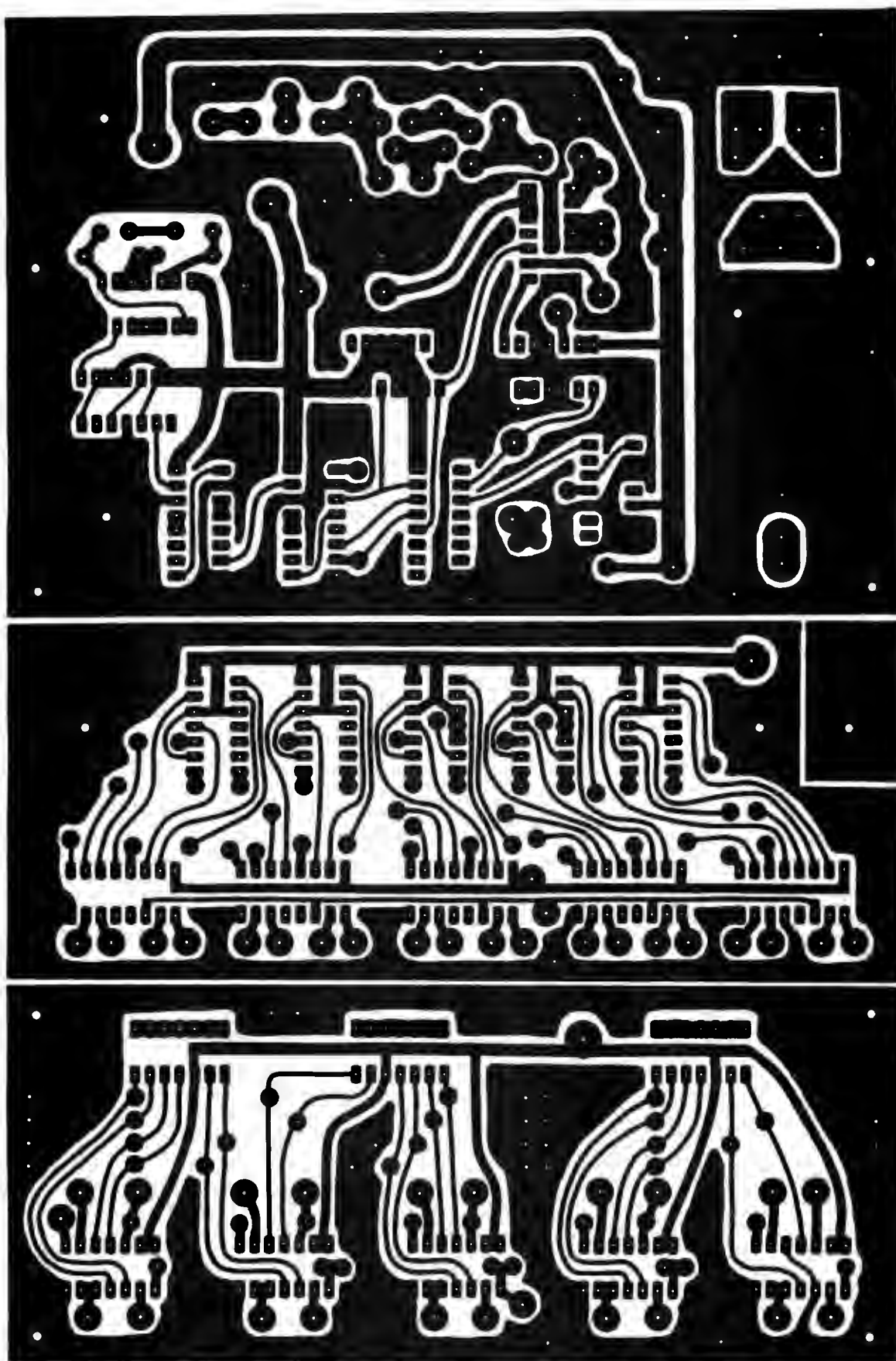

*Fig. 4. Etching and drilling guides for main (top), display (center), and counter (bottom) pc boards.*

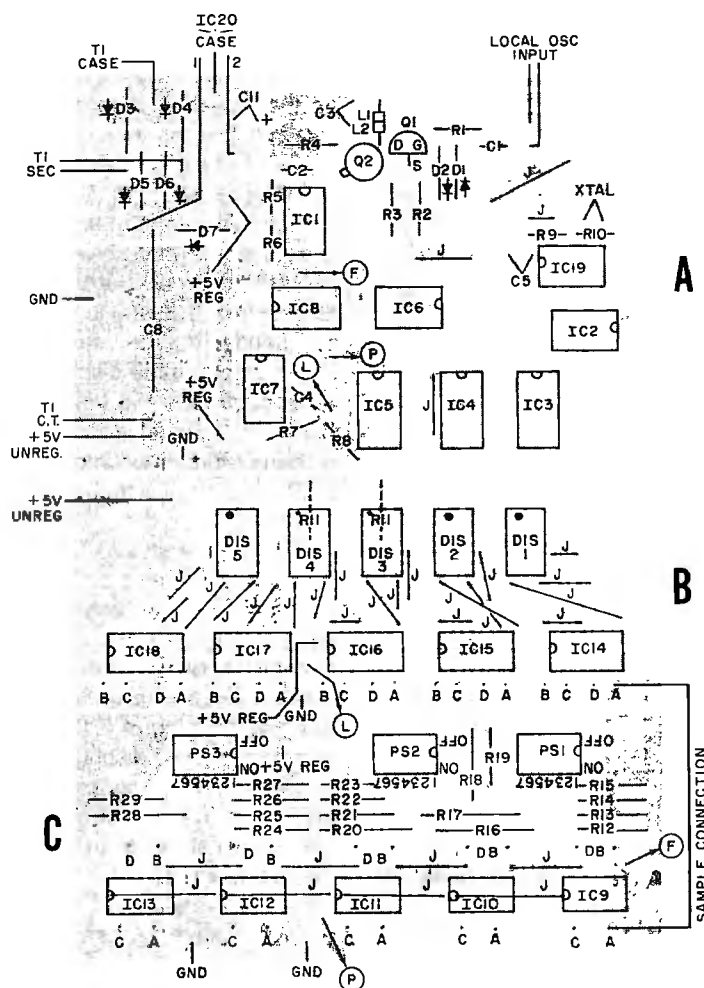


Fig. 5. Parts placement guides for main (top), display (center), and counter (bottom) pc boards.

a combination full-wave and bridge rectifier using a single 12.6-volt, center-tapped transformer. Two dc outputs are provided. The bridge rectifier (D3 through D6) delivers pulsating dc to C8 which acts as a filter. The filtered dc (+16 volts) is then applied to IC20, an LM309K voltage regulator, which is protected against transients by D7, C9 and C10. A well-regulated +5-volt dc output is thus provided for the TTL IC's and the input circuit.

Another +5-volt dc source is derived from the center tap of T1, D3 and D4. The three components form a full-wave rectifier, but its output is unfiltered and unregulated. This output is used to power the seven-segment readouts (DIS1 through DIS5). The unfiltered, pulsating dc has a ripple frequency of 120 Hz, which is great enough to prevent display flicker and results in a display brightness comparable to that obtained with a steady dc source. Removing the display current demand from the regulated supply substantially reduces the amount of heat generated in the power transformer

and voltage regulator IC, but causes no adverse effects. Display segment current limiting is performed internally by the 9374 IC's which also contain internal latch memories. No external current limiting resistors or bistable latch IC's are required, as is often the case with other decoder/driver chips.

**Construction.** The project should be assembled using printed circuit boards and IC sockets or Molex Soldercons. Transistor sockets (standard and TO-3) are also recommended for Q1, Q2, and IC20. The author used three pc boards in his prototype (Fig. 3). The boards can be interconnected with short lengths of No. 20 stranded hookup wire. Suitable etching and drilling guides are shown in Figs. 4 and 5 (A, B, and C) for the Main, Display, and Counter boards, respectively. Use the minimum amount of heat necessary for good solder connections. Be sure to observe polarities and pin basings of discrete semiconductors, IC's, and electrolytic capacitors.

Figure 3 shows how the boards and

power supply components were mounted in the project enclosure. The Counter and Main pc boards were secured to the bottom of the cabinet using 3/4-inch (1.9 cm) threaded metal spacers, while the Display board was mounted behind a bezel on the front of the case using 1/2-inch (1.3-cm) threaded metal spacers. Voltage regulator IC20 must be properly heat sinked and mounted on the exterior of the enclosure's rear panel. Use heat sink compound to insure proper heat transfer, and be sure to connect a length of hookup wire between the regulator socket's center ground bus and the Main pc board's ground. Also, make sure that IC20's mounting screws are in firm contact with the IC's case and the TO-3 socket's ground bus. The author also recommends grounding the power transformer's case.

Because TTL IC's are high-current switching devices, the steep edges of their output waveforms contain large amounts of r-f energy. Unless certain precautions are taken, this r-f will produce high noise levels at the receiver output. First, a metal case must be used—but it must also be perforated or vented to allow heat to dissipate. Second, both the project's and receiver's enclosures must be tied to a good earth ground. Third, both sides of the ac power line must be bypassed with 0.01-μF disc ceramic capacitors (C6 and C7).

**Checkout and Use.** A typical receiver's local oscillator is shown schematically in Fig. 6. Whether the receiver uses a FET, tube, or transistor oscillator, the point where the local oscillator signal must be tapped off is the same—at the capacitor coupling the output of the oscillator to the mixer. The author suggests that the signal be sampled on the local oscillator side of the coupling capacitor. For the following three popular SW receivers, the appropriate points are: Realistic DX-160, junction of C12 and R32 (drain of Q8); Lafayette HA-600A, junction of C6 and R21; Heathkit GR-78, junction of C308, R203, and R204. (Note: if you are using a tube-type receiver, beware of high voltage!) The connection should be made with small-diameter coaxial cable such as RG-58-U. You might find it desirable to mount an RCA phono jack on the back of receiver and bring the coax from the local oscillator output to this point. Then you can interconnect the display and receiver with a short coaxial jumper terminated with an RCA phono plug. Alternatively, you can terminate one end of the jumper with small alligator clips, as

**TABLE A**  
CONVERTING DECIMAL NUMBERS TO BCD

Number	8	4	2	1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

**TABLE B**  
COUNTER BOARD PROGRAMMING ASSIGNMENTS

Programming section	PS3	PS2	PS1
Programming input number	7654321	7654321	7654321
BCD designation	81-8241	8241-82	41-8241
Actual programming*	1111001	0011100	1010010
Counter controlled	IC13	IC12	IC11
Frequency displayed (receiver off)	9	9	.5
			4
			4 MHz

\*0=no jumper or open switch (OFF),  
1=jumper or closed switch (ON).

was done with the prototype (Fig. 3). The clip would then be attached to the proper tie point within the receiver.

The counters will be programmed with DIP switches (seven spst switches mounted in a DIP) or with wire jumpers on the counter board. If you are using DIP switches, make sure that all switches are in the OFF position. If wire jumpers are to be used, do not install any of them yet.

Turn the power switch (S1) on. The display should read 0.000 with the second zero to the left of the decimal point blanked off. Insert No. 22 solid jumpers across the IC sockets at the number 5 positions of PS1 and PS3 and at the number 3 position of PS2 (see compo-

nent placement guide). Or, if DIP switches are used, close the switches at these positions. Then momentarily insert a jumper across the other IC socket positions and verify that the corresponding counter responds according to Table B. For DIP switches, this is accomplished by turning the remaining switches on and off. As voltage is applied to each programming input, the BCD value of that input will be displayed on the corresponding LED readout.

After completing the checkout procedure turn the power off and connect the hot and ground sides of the coaxial jumper to receiver's local oscillator output and chassis, respectively. Turn on the receiver and tune it to WWV or

WWVH at 5 MHz. Tune the receiver to the station's carrier as accurately as possible. You can best do this by turning on the bfo—if your receiver has one—and zero beating the carrier. If no bfo is available, tune in the carrier for maximum signal strength. Now turn the project on. The readout will display a frequency somewhat above or below that of WWV's carrier. Subtract the number display from 105.000 to obtain the number needed for counter programming. For example, if the display reads 5.456 MHz, subtract 5.456 from 105.000. You will obtain a remainder of 99.544, which is then programmed into the counters in BCD form as illustrated in TABLES A and B.


The display should now read 5.000 MHz. Programming can be verified by tuning in an AM broadcast station of known frequency for maximum signal strength. Observe the displayed frequency. If it is off by 1 kHz or so, adjust the programming of IC9 so that the correct frequency is displayed. The project is now properly programmed for receivers with a fixed i-f for all bands and no further adjustments are needed. When the receiver is turned off but the project left on, the readout will display the number you have programmed into the counters.

Some multiple conversion receivers, such as the Heath GR-78, will require different programming for different bands. Thumbwheel switches with BCD outputs can be mounted on the front panel and used in place of jumpers or DIP switches. This will greatly speed programming.

The project is *not* suitable for use with those multiple conversion receivers having second (lower) i-f's with variable frequency (local) oscillators operating below the first i-f. In such a case, the tunable oscillator's output frequency is highest when the receiver is tuned to the lowest frequency within a given band. Conversely, the oscillator's output frequency is lowest when the receiver is tuned to the highest frequency within the band. However, receivers using this type of i-f generally have dial mechanisms with wide bandsread and frequency readout to the nearest one or five kilohertz. Therefore, they do not need the kind of improvement this project can provide.

For inexpensive SW receivers, however, this project is an enormous asset. Not only will it greatly enhance the user's enjoyment of shortwave listening, it will also make station tuning and logging a "breeze."

Fig. 6. Typical local oscillator circuit

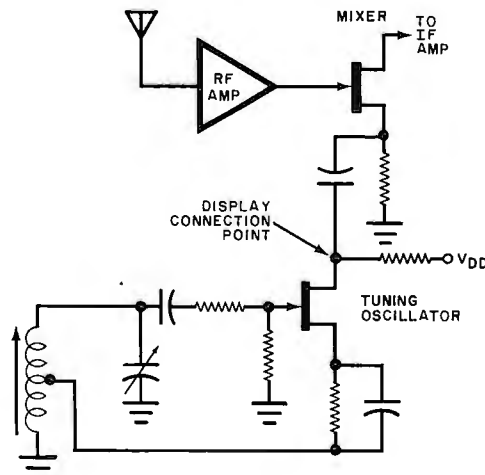

**W**HILE MOST modern power supplies are designed to protect themselves against overloads and short circuits, the protection often doesn't go far enough. In many modern projects—particularly those involving computers—the load on the power supply can cost a great deal more than the supply itself. A practical power supply for modern projects, then, should protect both itself and the load. With an inexpensive 723 precision voltage regulator IC and a handful of components, you can build such a "full-protection" power supply.

Unlike most other regulator IC's, the 723 can be programmed to automatically drop the output current to a small fraction of maximum under overload and short-circuit conditions. This "foldback" current is similar to conventional current limiting up to the maximum current rating of the supply. But while a conventional current limiter will keep right on pumping maximum current into the load, the foldback circuit will go to maximum and then signal the series-pass transistor in the 723 to drop the output current to a mere fraction of its capability.

The actions of both conventional and foldback limiting are graphically illustrated in Fig. 1. Note the downward slope of the short-circuit current,  $I_{SC}$ , for the foldback characteristic as opposed to the zero slope of the line for conventional current limiting.

The functional diagram of the 723 is shown in Fig. 2. Pin designations on the diagram are for the dual in-line (DIP) configuration of this IC. Below the diagram are the pin designations for the round (TO-100) configuration of this IC. Some of the IC's more important maximum specifications are: 40 V from +V and  $V_C$  to -V; 150 mA maximum current for internal series-pass transistor; 900 mW DIP (800 mW round) maximum power dissipation; 0.001- $\mu$ F frequency-compensation capacitor; 0.03% regulation at load; input-output voltage differential, 30 V minimum. On the TO-100, pin 5 is connected to the case.

**Regulation Differences.** A basic current limiter using a 723 is shown in Fig. 3. This circuit can be programmed to operate in either a low- (2-to-7-) or high- (7-to-35-) volt range by proper selection of voltage-divider resistors  $R1$  and  $R2$ . (Note: To avoid confusion during calculations, two  $R1$ - $R2$  divider networks are shown. The resistor values calculated will be the same in both divider networks.)

If only the high-voltage range is de-

# Current "Foldback" Protects Power Supply & Load

BY JEROME MAY

*How a 723 IC  
can be used for  
both load and  
supply regulation.*


sired, switch  $S1$  goes to HI, and  $V_{REF}$  goes to the noninverting, or +, input of the error amplifier in the 723 through a 5000-ohm resistor ( $R4$ ). The output current of the IC is sensed by  $R3$  and fed to the  $Q2$  current sense amplifier in the 723. When the potential across  $R3$  exceeds about 0.7 volt,  $Q2$  diverts any increase in base current from the error amplifier to  $Q1$  inside the IC. This limits the available current from the 723 to the IC's rated maximum. Unfortunately, if the load resistance goes to zero, this maximum current will still be pumped into the load.

Now, consider the foldback modification shown in Fig. 4. (This circuit is identical to the Fig. 3 circuit except that  $R5$  and  $R6$  have been added as shown.) The ratio of  $R5/R6$  shifts the operating point of  $Q2$  inside the 723 so that, when the voltage drop across  $R3$  biases on  $Q2$ , any increase in the drop across  $R3$  (beyond the point at which the transistor first starts to conduct) diverts increasing current away from the base of the 723's  $Q1$  transistor. Thus, the output current "folds back" after the maximum programmed current is obtained. Note, however, that because a finite voltage drop is required to keep the 723's  $Q2$  transistor conducting, the output current can never go to zero; it simply folds back to a small fraction of the maximum current the IC can deliver.


**Calculations.** To program a 723 for the current-foldback regulator, first determine values for  $R1$  and  $R2$  to fix the output voltage. To determine the foldback current ("knee" in Fig. 1),  $R3$  is calculated after selecting convenient values for  $R5/R6$ .

If the output is to be less than 7 volts, the  $R1A$ - $R2A$  divider network goes directly to the 723's  $V_{REF}$  input with  $S1$  in the LO position as shown in Fig. 3. The basic formula from which to work is  $V_O = V_{REF} R2A/(R1A + R2A)$ , from which we obtain  $R1A = R2A(V_{REF} - V_O)/V_O$  and  $R2A = V_O R1A/V_{REF} - V_O$ . Assume that the desired  $V_O = 5$  volts and that  $V_{REF} = 6.2$  volts. Select an arbitrary value of several thousand ohms—say, 10,000 ohms—for  $R2A$ . Therefore,  $R1A = 10,000(6.2 - 5)/5 = 2400$  ohms. Hence, for a 5-volt output, the values of  $R1A$  and  $R2A$  should be 2400 and 10,000 ohms, respectively.


Should you desire an output of greater than 7 volts,  $S1$  should be set to HI, which bypasses  $R1A$  and  $R2A$  by switching in  $R4$  and placing the  $R1B$ - $R2B$  divider in the circuit. The basic for-

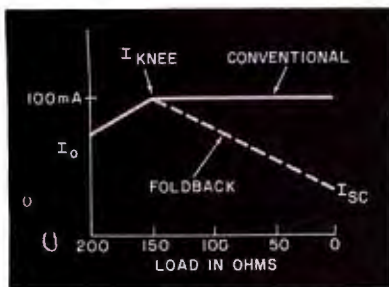


**Fig. 1. Dashed line shows downward slope of short-circuit current for the foldback characteristic.**

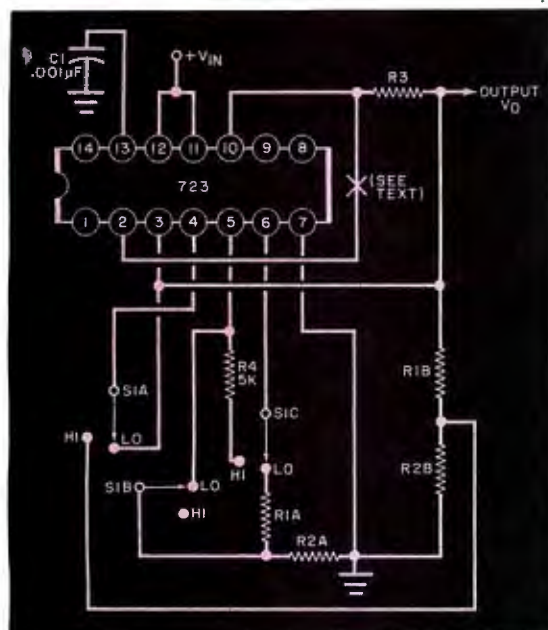


**Fig. 3. Basic current limiter can operate in either a low (2 to 7 volts) or high (7 to 35) range by proper selection of resistors R1 and R2. See Fig. 4 for added circuit at point "X".**

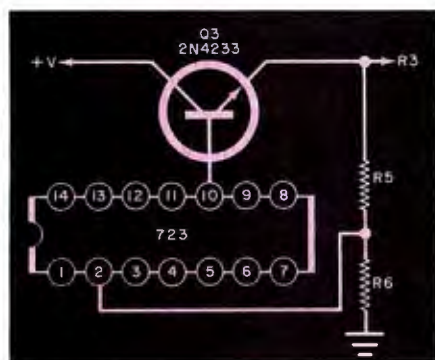

**Fig. 5. Use of an npn series-pass transistor to increase capacity.**

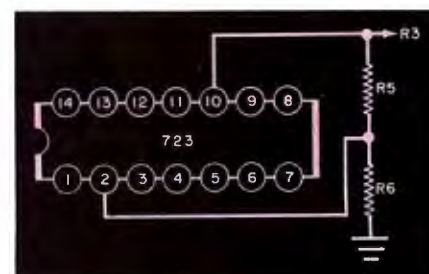

**Fig. 4. Voltage divider at "X" in Fig. 3 shifts operating point.**

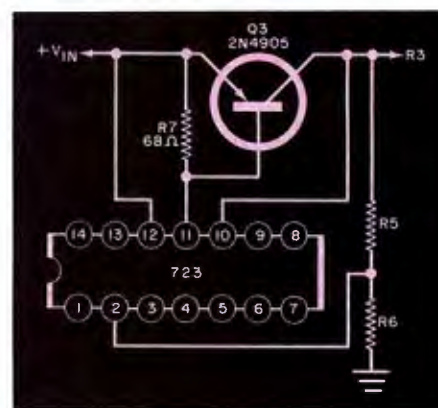

**Fig. 6. If a pnp transistor is used as series-pass element, add a bias resistor.**

mula here is  $V_O = V_{REF} (R1B + R2B) / R2B$ . Therefore,  $R1B = R2B(V_O - V_{REF}) / V_{REF}$  and  $R2B = V_{REF} R1B / (V_O - V_{REF})$ . This time, let us assume that the output is to be 15 volts and that  $V_{REF}$  remains the same at 6.2 volts. Again arbitrarily selecting a value of 10,000 ohms for  $R2B$ ,  $R1B = 10,000 (15 - 6.2) / 6.2 = 14,193$  ohms.

Now, select the maximum current the supply is to deliver to the load. For example, assume that at  $V_O = 15$  volts, you want an  $I_{MAX}$  of 100 mA. Now, select values for  $R5$  and  $R6$  (Fig. 4 shows how these components connect into the basic circuit). Assume that  $R5$  and  $R6$  have values of 1000 and 10,000 ohms, respectively. (Note: The smaller the ratio

of  $R5/R6$ , the lower will be the resistance for  $R3$  to provide the required limiting. Bear in mind that the short-circuit current will be reduced for larger values of  $R3$ .)

From the equation  $I_{MAX} = [V_O R5 + 0.7(R5 + R6)] / R3R6$ , we obtain  $R3 = [V_O R5 + 0.7(R5 + R6)] / I_{MAX} R6$ . Therefore,  $R3 = [15(1000) + 0.7(1000 + 10,000)] / (0.1 \times 10,000) = 22.7$  ohms. Since the formula for short-circuit current is  $I_{SC} = 0.7(R5 + R6) / R3R6$ ,  $I_{SC} = 0.7(1000 + 10,000) / (22.7 \times 10,000) = 35$  mA. This is about a third of the actual current the 723 supply is designed to deliver. The short-circuit current can be reduced, but then new values of the ratio  $R5/R6$  will have to be se-

lected to determine the 100-mA foldback point.


A current of 35 mA at 15 volts is a hefty half-watt to dissipate on an IC chip. Therefore, a better approach to the design of the supply would be to use an external series-pass transistor with adequate heat-sink protection. The circuit utilizing an npn series-pass transistor (Q3) is shown in Fig. 5. If all you have available is a pnp transistor, you can use it, along with an additional bias resistor (R7), as shown in Fig. 6. In either case, if the circuit is to be used to power a particular project, be sure the transistor's voltage, current, and power dissipation figures are capable of accommodating the load at full power. ◇

# EARN \$1000 OR MORE PER ORDER IN YOUR SPARE TIME SELLING OUR SIDING HOME-KITS.

Our HOME-KIT is a complete covering of aluminum, steel, or vinyl siding for a home. They're available in 14 sizes and 22 colors. They're easy to apply and easy to sell because our dealer prices (your cost) allow you to buy at about 1/3rd of the national average installed price.

Each new dealer must install a HOME-KIT on his own home in order to gain application experience and have something to show to his prospective customers.

Fill in the coupon on this page and send it to us. We'll promptly mail you your FREE FRANCHISE (if still available in your county) and FREE DEALERSHIP. You'll also receive FREE SAMPLES of our product and our 48 page CONFIDENTIAL DEALER'S MANUAL AND WHOLESALE PRICE LIST. The manual is extremely valuable. It explains how to apply siding, discusses each type of siding material available, and tells you how to sell it.

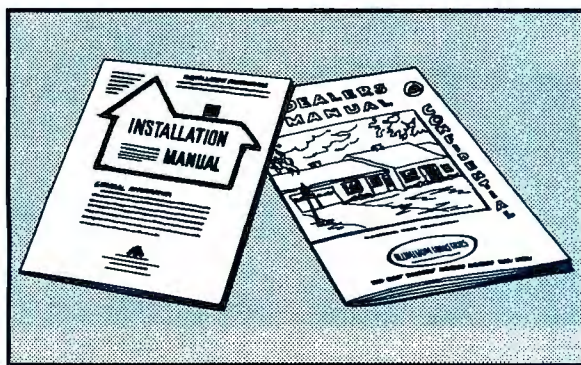

Your first HOME-KIT includes a complete set of professional siding applicator's tools and detailed, yet easy to follow, step-by-step, illustrated instructions... all free of additional charges. Plus, a FREE 50 lesson course on everything you'll ever have to know about selling and applying siding.

Once you decide to become an Aluminum Industries dealer, all of our merchandising, advertising and sales experience (over 30 years of it) becomes available to you... FREE!

## SELL YOUR CUSTOMERS ON MONTHLY PAYMENTS.

HOME-KITS can be sold on monthly payments. No down payment is required. Details are in your free CONFIDENTIAL DEALERS MANUAL AND WHOLESALE PRICE LIST.

PLEASE... do not delay. We can only award a limited number of active franchises in any county. As soon as we receive your inquiry, we'll reserve your franchise for you until you decide whether or not to become a dealer. But act now, before your county is closed.

### NOTICE

If, after applying a HOME-KIT to your home you decide that you would rather not become an Aluminum Industries dealer, you are under no obligation to do so. But we think that once you see how easy a HOME-KIT is to apply and how beautiful and maintenance free it makes your home, you will find it is quite easy and very profitable to sell HOME-KITS to your friends and neighbors.



**ALUMINUM  
INDUSTRIES  
OF ARKANSAS**

Dept. PE-27  
300 Phillips Rd.  
North Little Rock, AR 72117

### APPLICATION FOR DEALERSHIP [ PE-27 ]

WITHOUT OBLIGATION, please mail me all of the materials mentioned above including my FREE 48-page CONFIDENTIAL DEALER'S MANUAL AND WHOLESALE PRICE LIST, FRANCHISE & DEALERSHIP, AND SAMPLES. I own a home which needs to be re-sided and I understand that I must purchase a HOME-KIT for my home before I can sell them to the public. **NOTE:** No salesman will knock on your door, we distribute exclusively by mail.

My name is: \_\_\_\_\_ (please print)

I would like to be considered for a: ☐ Part-time dealership ☐ Full-time dealership

Address of property I own which needs re-siding: STREET \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

This property is in \_\_\_\_\_ county.

My mailing address is: STREET \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

My present occupation is: \_\_\_\_\_

My phone number is: \_\_\_\_\_

SIGNATURE \_\_\_\_\_ DATE \_\_\_\_\_



# Conference TALK TIMER

BY WALTER W. SCHOPP

*Compact, versatile project  
has selectable time intervals.*

**I**T IS a well-known fact that public speakers frequently run over their allotted time. This "Talk Timer" is an ideal device for keeping speakers within their time limits and getting a conference moving on schedule. Its use need not be confined to conferences, however. It can be used in any timing application in the kitchen, in the radio shack, near the telephone, etc.

When the unit is turned on and the RESET button is pressed, a green light glows for the TALK period (adjustable from 5 to 60 minutes). At the end of that time, a yellow light comes on, and the SUMMARIZE period (adjustable from 5 to 15 minutes) begins. When the total time is up, a red light comes on.

The project can be built easily at a total parts cost of about \$30.

**About the Circuit.** The Talk Timer has a fairly low parts count due to the fact that two Exar XR-2400 IC's are used. Each chip contains a 555 timer and eight flip-flops (divide-by-two counters) in a 16-pin DIP. Each open-collector flip-flop output is accessible at a specific pin, and any number of them can be connected together. The result is a summed output signal with a period from RC to 255RC, where RC is the time con-

stant of the timing resistor and capacitor.

The schematic diagram of the Talk Timer is shown in Fig. 1. Duration of the "talk" period is controlled by IC1, and that of the "summarize" period by IC2. A 15-second time constant is used in each timer, determined by R7, R8, and C2 for IC1 and R14, R15, and C8 for IC2. Because this time constant is fairly short, reasonably sized capacitors can be used. Also, adjustment of R8 and R15 is much easier for this interval than for one considerably longer. (The overall accuracy of each timer depends on that of its reference time constant.) For the "talk" period, the 4RC through 128RC outputs of IC1 are selectively summed to give an output signal with a duration of 5 to 60 minutes in 5-minute increments. For the "summarize" period, the 4RC through 32RC outputs of IC2 are combined to give an output signal of 5, 10, or 15 minutes.


When power is initially turned on, both timers are reset. All three lamps (I1-I3) glow, and the unit is ready for operation. When RESET switch S1 is depressed, one pole momentarily disconnects SCR1 and SCR2 from the unregulated +7.5-volt supply (point A). This turns off the SCR's and lamps I2 (SUMMARIZE) and I3 (STOP). Lamp I1 (TALK) will glow

again when S1 is released. The other pole of S1 applies a pulse from capacitor C3 to the reset terminal of IC2 (pin 10) and to the reset and trigger (pin 16) terminals of IC1. Thus, IC1 starts timing and its output goes low.

At the end of the selected "talk" period, the output of IC1 goes high and causes SCR1 and I2 to conduct. Simultaneously, a pulse is applied to the trigger input of IC2. This IC then times out the SUMMARIZE period. At the end of that interval, IC2's output goes high and turns on SCR2. This activates I3 and the Sonalert (if used). The Talk Timer can then be reset for the next speaker by depressing S1. Also, the unit can be reset at any time during the TALK and SUMMARIZE intervals by pressing RESET.

A suitable power supply providing regulated and unregulated outputs is shown schematically in Fig. 2. For stability, the two timing chips are connected to the 6.8-volt regulated output (point B). The rest of the circuit (the SCR's and indicator lamps) is connected to the unregulated output.

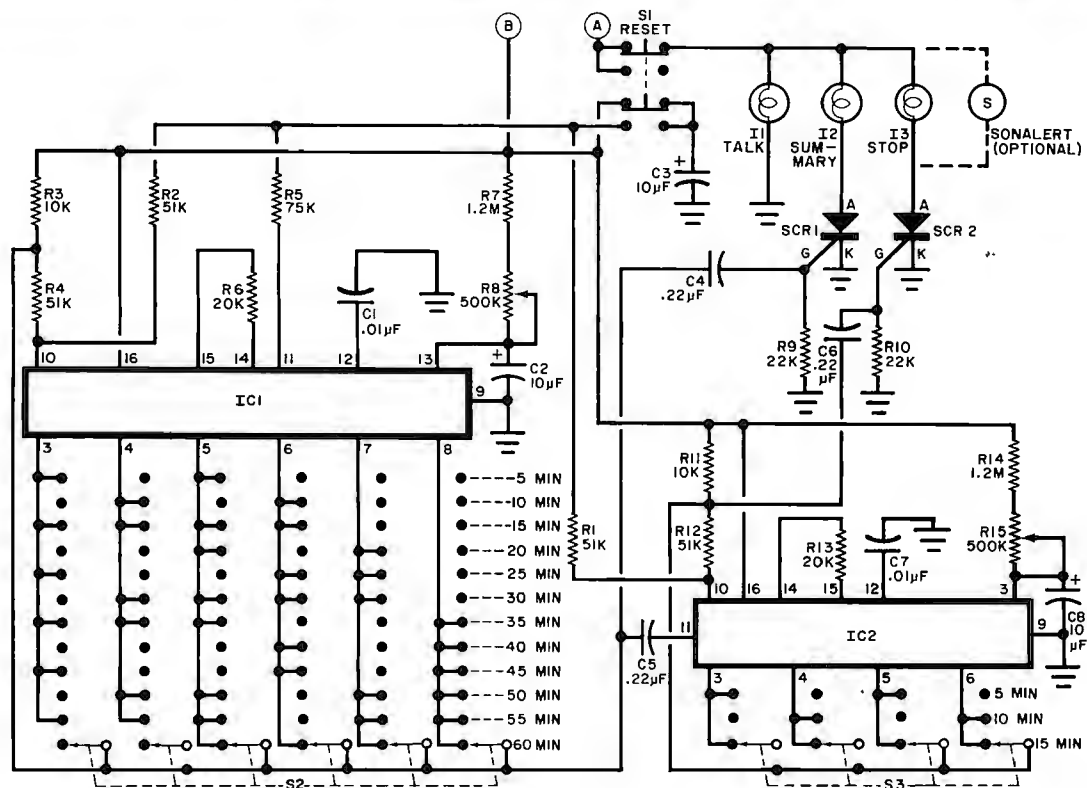**Construction.** Assembly techniques and parts placement are not critical. Printed circuit or perforated board can be used, with hard wire or wrapped wire



### PARTS LIST

C1, C7—0.01- $\mu$ F disc ceramic capacitor  
 C2, C3, C8—10- $\mu$ F, 25-volt tantalum capacitor  
 C4 through C6—0.22- $\mu$ F Mylar capacitor  
 I1 through I3—No. 44 or 47 pilot light  
 IC1, IC2—XR-2240CP programmable timer (Exar)  
 The following fixed resistors are  $\frac{1}{4}$ -watt, 10% tolerance components.

R1, R2, R4, R12—51,000 ohms  
 R3, R11—10,000 ohms  
 R5—75,000 ohms  
 R6, R13—20,000 ohms  
 R7, R14—1.2 megohms  
 R9, R10—22,000 ohms  
 R8, R15—500,000-ohm trimmer potentiometer  
 S1—Dpdt momentary pushbutton switch  
 S2—6-pole, 12-position nonshorting rotary switch (Centralab 2025 or equivalent)

S3—4-pole, 3-position nonshorting rotary switch (Centralab 2011 or equivalent)

SCR1, SCR2—1-ampere, 100-volt silicon controlled rectifier (Radio Shack 276-1059 or equivalent)

Misc.—Lensed lamp holders, printed circuit or perforated board, IC sockets or Molex Soldercons, suitable enclosure, switch knobs, Sonalert (optional), hookup wire, solder, etc.

Fig. 1. Two timer-counter IC's reduce parts count for the project.

connections. The use of sockets or Molex Soldercons is recommended for the IC's. Care should be taken when wiring S2 and S3. The many contacts on these rotary switches make it easy to wire them incorrectly, and make it difficult to find the error after assembly. Lampholders with colored lenses should be used with I1 (green), I2 (yellow), and I3 (red).

**Adjustment.** The only adjustments

that need to be made are the settings of R8 and R15. Using a dc-coupled oscilloscope or high-threshold logic probe, observe the signals at pin 1 of each IC. During the "talk" period, the waveform at pin 1 of IC1 should change state every 15 seconds when R8 is properly adjusted. During the "summarize" period, pin 1 of IC2 will change state every 15 seconds when R15 is set correctly. Try to adjust these RC time constants as

precisely as possible, because the overall accuracy of the Talk Timer depends entirely on them.

No matter what your application may be, the Talk Timer is set up and operated in this manner—connect the project to the ac line, close power switch S4, select the desired talk and summary times with rotary switches S2 and S3, respectively, and activate and reset the system using RESET switch S1. ◇

### PARTS LIST

C9—2500- $\mu$ F, 15-volt electrolytic capacitor  
 C10—0.001- $\mu$ F disc ceramic capacitor  
 D1 through D4—1N4001 rectifier diode  
 D5—6.8-volt, 1-watt zener diode (1N3016B or equivalent)  
 R16—33-ohm,  $\frac{1}{2}$ -watt resistor  
 S4—Spst toggle switch  
 T1—117V/6.3-volt, 1.2-ampere transformer  
 Misc.—Line cord, terminal strips, hookup wire, solder, machine hardware, etc.

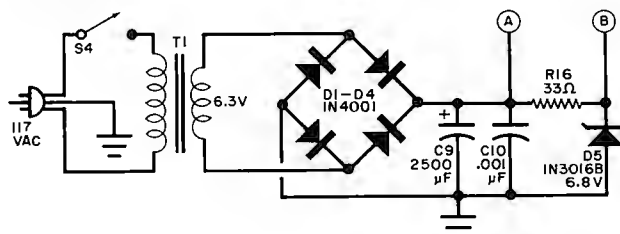


Fig. 2. Schematic of suitable power supply.

# QUIZ-GAME ELECTRONICS

BY MICHAEL S. ROBBINS




*Here's a player-response circuit that will enable you to imitate quiz shows at home or with larger audiences.*

**P**OPULAR TV quiz shows use electrical or electronic apparatus to determine which contestant makes the first response, thereby getting first crack at a

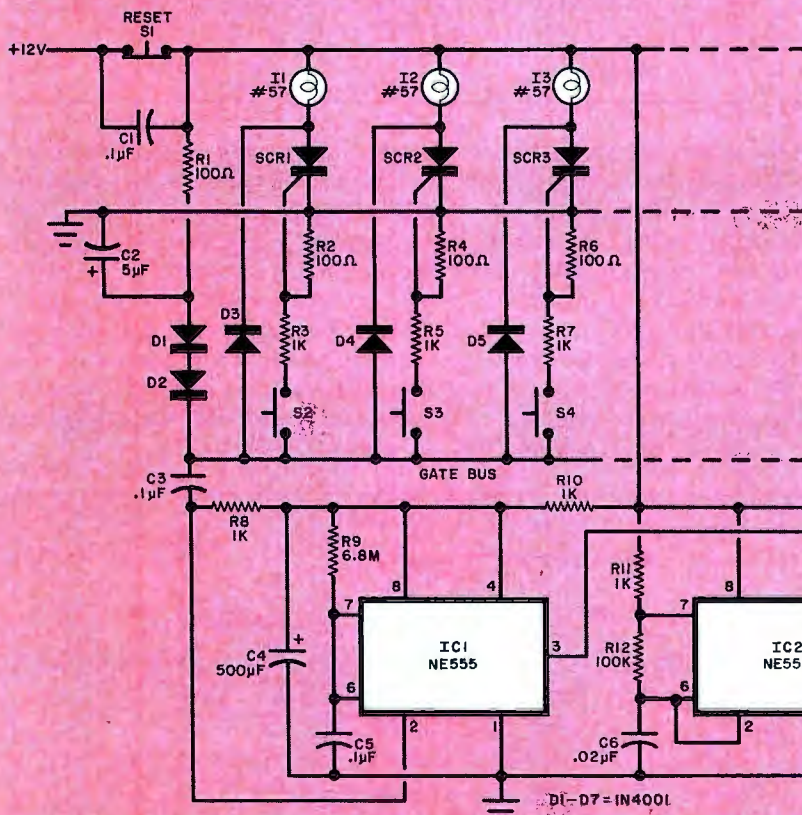question. Here's a simple circuit that will enable high school and college groups to emulate the quiz shows. It can be used for fun at home, too.

The circuit shown will energize a lamp to identify which player pushes his button first, sound an audible alarm, and lock out the buttons of the other players.



## PARTS LIST

- C1, C3, C5—0.1- $\mu$ F, 50-volt disc ceramic capacitor
- C2—5- $\mu$ F, 25-volt electrolytic capacitor
- C4—500- $\mu$ F, 25-volt electrolytic capacitor
- C6—0.02- $\mu$ F, 50-volt disc ceramic capacitor
- C7—10- $\mu$ F, 25-volt electrolytic capacitor
- D1 to D7—1N4001 diode
- I1 to I3—No. 57 pilot lamp
- IC1, IC2—555 IC timer
- R1, R2, R4, R6—100-ohm resistor
- R3, R5, R7, R8, R10, R11—1000-ohm resistor
- R9—6.8-megohm resistor
- R12—100,000-ohm resistor
- S1—Spst normally closed, momentary pushbutton switch
- S2 to S4—Spst normally open, momentary pushbutton switch
- SCR1 to SCR4—HEP R1221 or equivalent
- Misc.—Utility boxes, pc or perforated board, lamp sockets, wire, solder, hardware, etc.

*Schematic diagram for the game circuit. By adding SCR networks, the circuit can be expanded to include any number of players.*

The solid-state design is inexpensive to build and can be expanded to include any number of players and a combination of alarms could be used.

**Circuit Operation.** The heart of the system is an inexpensive SCR. When a contestant presses his button, the gate of his particular SCR (one for each player) is connected to the positive gate bus. The SCR turns on and the indicator is lit. Since the voltage across the SCR is nearly zero during conduction, the normally positive gate bus will be pulled down to almost 0 volts through the diode which ties the bus to the SCR's anode. When this happens, the bus will not be able to supply enough gate current to turn any other SCR on. Thus the other players' buttons are locked out until the referee resets the circuit.

This dip in voltage on the bus activates IC1, a 555 unit operating as a one-shot. A one-second pulse from IC1's output activates IC2, a 555 in the astable mode, producing a tone in the speaker for the same length of time. Since the output of IC2 is a square wave, an appreciable inductive "kick" can appear across the speaker coil. Two clipping diodes are connected across the output of IC2 to protect the transis-

tors inside the 555 from excessive voltage spikes.

Once a pulse of current flows into an SCR, it will conduct indefinitely (the player need not keep his button continuously depressed) until the anode current falls below the holding current,  $I_H$ . When this happens, the SCR turns off. In this circuit, the indicator lamp will continue to glow and all other pushbuttons will be locked out until the referee pushes the RESET button, S1.

The duration and pitch of the tone may be adjusted by changing the values of the timing components associated with IC1 and IC2. For example, changing R9 from 6.8 megohms to 1 megohm will shorten the duration to about 0.2 seconds, while substituting a 10-megohm resistor will extend the interval to about two seconds. Replacing the 100,000-ohm R12 with a 500,000-ohm resistor will raise the frequency of the tone from 350 Hz to about 1000 Hz. Since tastes vary, you might install potentiometers in place of these two fixed resistances, and adjust them to produce the desired pitch/duration combination.

Any small 8-ohm speaker will be sufficient for this application. Power can be obtained from any source capable of producing 500 mA at 9 to 12 volts dc. A

lantern battery or a small full-wave power supply will work fine.

**Construction.** The system can be constructed in several different configurations. One of the most versatile arrangements is to mount each contestant's pushbutton, indicator lamp, and SCR network in a small utility box, which is placed before him. All of the boxes are connected together by a three-conductor cable. The tone generator, RESET button, and power supply can then be installed in a utility box mounted at the referee's position.

An alternative arrangement is to mount all of the circuitry behind a panel on which the indicator lamps are installed. Twisted-pair or zip cord can be used to connect the circuitry to pushbuttons at the contestants' and referee's positions. Other configurations might be suggested by your own particular situation.

Parts placement is not critical, so the circuitry can be assembled on a printed circuit board or a piece of perforated board, mounted in any small, convenient utility box.

All you need now to use the system are contestants, brain teasers and prizes to be won! ◇

# Get More from Your Car with a Mark 10 System.

**The best-selling CDI system of its kind in the world—now at discount prices!**

Would you like more power? Better mileage? And could you stand to eliminate 3 out of 4 of those expensive tune-ups? Well, that's what the MARK 10 capacitive discharge electronic ignition system is all about. Very simply, it boosts the spark to your engine—promoting better combustion, and minimizing combustion contaminants. Spark plug life is extended, all-weather starts are insured, and you can feel an increase in acceleration and overall engine performance—*no matter what kind of car you drive*. Learn more about a MARK 10 CDI system for your car (and take advantage of year-end discount prices), when you write today for a catalog and price list.



**DELTA PRODUCTS, INC.**


P.O. Box 1147, Dept. PE  
Grand Junction, CO 81501  
(303) 242-9000

I want to know more about Mark Ten CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name

Address

City  State  Zip

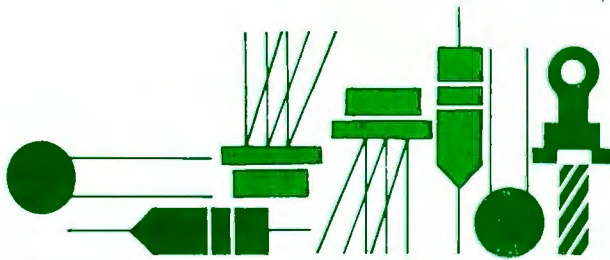

# Solid State

## TIMERS AND COUNTERS

By Lou Garner

**A** NUMBER of semiconductor manufacturers offer special devices designed specifically for use in timing and counting systems quite aside from watch and clock IC's. A typical family may include from two to four or more devices. The 8240, 8250, and 8260, for example, are a family of monolithic programmable timer circuits manufactured by *Intersil, Inc.* (10900 N. Tantau Ave., Cupertino, CA 95014) which can be used in a variety of interesting and exciting projects. Supplied in 16-pin DIP's, TTL compatible, and capable of operation on dc sources of 4 to 18 volts; these devices are suitable for use in process control, appliance and darkroom programmable timers; inventory checking, loading, filling and summing counters; music synthesis, harmonic synchronization and other frequency generation applications; analog-to-digital and digital-to-analog converters; sample and hold circuits; and pattern and waveform generators.

Terminal (pin) connections for the 8240, 8250 and 8260 family are identified in Fig. 1. Each device comprises an accurate low-drift oscillator, a counter section of cascaded master-slave flip-flops and suitable logic and control circuitry. The integral time-base oscillator can be set with an external R-C network or, if preferred, disabled, with the time base supplied by an external clock. The counter outputs are open-collector transistors which can be programmed easily at the external pins using wire connections or standard thumbwheel switches. With additional logic circuitry, timing can be programmed by a computer or microprocessor, thus permitting the devices to be used in complex automated control systems.

The 8260 is designed specifically to time accurate delays in seconds, minutes and hours. It has a maximum count of 59 and a carry-out gate, permitting several units to be cascaded for operation as a clock synchronized by the 60-Hz ac power line. With a maximum count of 99, the 8250 is optimized for decimal counting and delay, and can be programmed by standard binary coded decimal (BCD) thumbwheel switches. Each device has a counting capability of two decades, permitting selection of time delays from 1 RC to 99 RC (RC representing the external timing network), while a carry-out gate allows an expansion to as many decades as is needed. Finally, the 8240 employs conventional binary counting, using eight flip-flops to divide down the base frequency and providing 8 suboctaves of the fundamental simultaneously when operated in the astable mode. When used in the monostable mode, the output collectors can be wired for AND logic to give any combination of pulse widths needed from 1 RC to 255 RC. All three devices offer a typical accuracy of  $\pm 5\%$  and a low drift of only  $\pm 100$  ppm/ $^{\circ}\text{C}$  (typical).

Typical practical applications for the 8240/50/60 family are illustrated schematically in Figs. 2 through 5. These are but a sampling of the circuits featured in the 16-page technical bulletin for the devices as well as Intersil's 23-page *Timer/Counter Applications Brochure*. All of the designs employ standard components and, with neither layout nor lead dress overly cri-

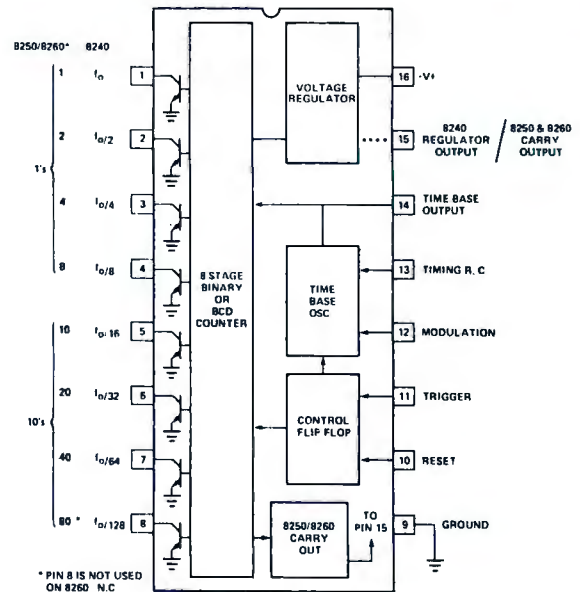


Fig. 1. Pin connections for 8240/50/60.

tical, may be duplicated quite easily in the home laboratory or workshop using conventional construction techniques, provided good wiring practice is observed. Intersil devices are stocked primarily by franchised industrial distributors such as *Arrow, Kierulff, Schweber, Weatherford, and Semiconductor Specialists*.

An unusual, but valuable, application for a timer/counter is shown in Fig. 2—synthesis of a signal bearing a fractional harmonic relationship to an accurate reference frequency. Here, a 100-Hz output signal is developed which is synchronized with and stabilized by a 60-Hz signal derived from the ac power line. In operation, this is achieved by a combination of frequency multiplication and division. The timer/counter's inter-

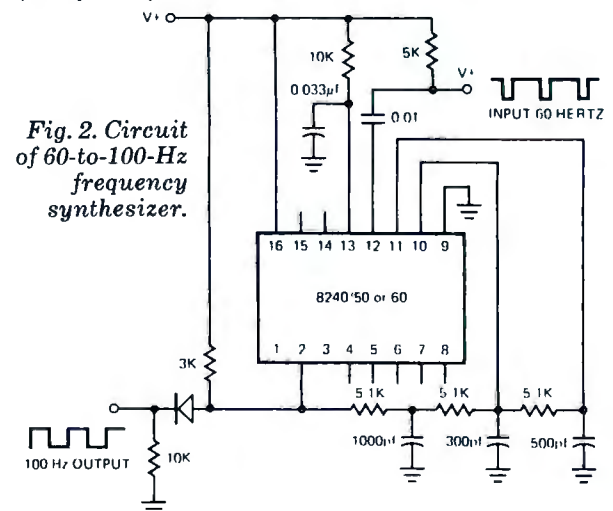


Fig. 2. Circuit of 60-to-100-Hz frequency synthesizer.

nal time base oscillator is set to a multiple of the reference frequency by means of the R-C timing network connected to pin 13 and is synchronized with it as in any harmonic generator. This signal is then divided by the counter chain. In the circuit shown, the 60-Hz reference frequency is multiplied by 5 and divided by 3 to develop the 100-Hz output signal. Frequency synthesizers may be used in a variety of projects—such as special-purpose test generators, clocks for control and process logic systems, tone sources for electronic musical instruments or remote control applications, or references for timing instrumentation.

With a few simple modifications and the addition of a voltage comparator and a flip-flop, a staircase generator may be adapted for use as an analog-to-digital converter, as shown in Fig. 3. If an 8240 is used, the digital output is an 8-bit binary signal, while a type 8250 (with a corresponding change in resistor array ratios) provides a 2-digit BCD output. In operation, an input strobe pulse first resets then triggers the 8240/50 and, at the same time, sets the flip-flop which enables the counter. The staircase signal developed by the 741 op amp counts down until it reaches the analog input voltage level, at which time the type 111 comparator changes state, resetting the flip-flop and stopping the count. The digital word at the timer/counter's eight outputs is the complementary binary (or BCD) equivalent of the analog input. The maximum conversion time is approximately 2.6 ms.

Using three cascaded 8250's and featuring an optional readout display, the programmable event counter circuit given in Fig. 4 can be used in numerous applications. Typically, it can serve to count and limit the number of moves in a game, for loading or package filling to preset quantities, for inventory control, and, with suitable sensors, even for limiting the number of individuals entering (or leaving) a restricted area, such

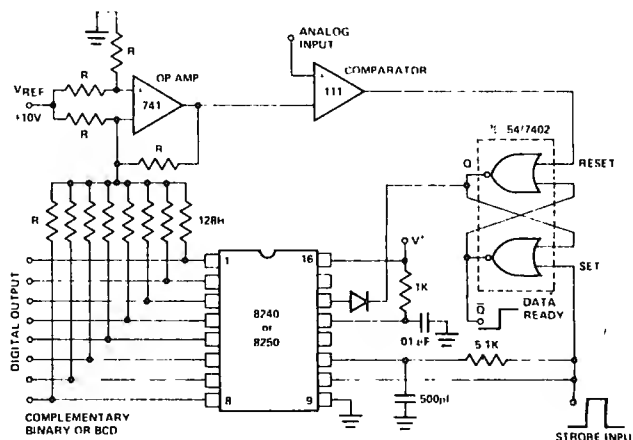


Fig. 3. Analog-to-digital converter circuit.

as an auditorium, dance hall, or production plant. Extremely versatile, its applications are limited only by the imagination and skill of the designer and by the peripheral circuits or devices (such as alarms, solenoids, relays, valves, or motors) with which it is used. In operation, the six decade counter is preset (programmed) to the maximum desired count by means of six BCD thumbwheel switches. Action is initiated when the START COUNT pushbutton switch is closed, enabling both the programmed and the readout display counters, the latter a type 7208. Thereafter, the circuit begins counting the desired items or events, receiving its information in the form of negative-going pulses from its input line. The signal count pulses may be derived from microswitches, photoelectric sources, temperature transducers, pressure switches or other devices, depending on the specific application. The output is developed as a 0-to-5-volt step function; at the start of count-

**NEW**

FROM



THE

**HOBBY~WRAP**

COMPLETE WITH BIT AND SLEEVE

ONLY **\$34<sup>95</sup>**

**Model  
BW-630**





Now you, the hobbyist, can do wire-wrapping professionally with our easy to use Hobby-Wrap gun.

**OK MACHINE & TOOL CORPORATION**

3455 Conner St., Bronx, N.Y. 10475 / (212) 994-6600 / Telex 125091

.025 sq. post,  
AWG 30 wire  
(batteries not included)

# MORE TIMES IN MORE CIRCUITS WITH SENCORE DIGITAL MULTIMETERS

**A NEW BREED OF DVM's  
BACKED BY 25 YEARS OF  
ALL AMERICAN CRAFTS-  
MANSHIP, WITH SIX EX-  
CLUSIVE FEATURES, SO  
YOU CAN BE MORE SURE,  
MORE OFTEN . . . . .  
AND ALL WITH HI & LO  
POWER OHMS FOR MEAS-  
URING ACCURATELY IN  
SOLID STATE CIRCUITS.**




**■ ONE THIRD LESS CIRCUIT LOADING** to make you sure that you are affecting the circuit being tested as little as possible for more accurate measurements. Sencore digitals are 15 megohm, others are 10 megohm.



**E** 2000 DCV range to make you sure that you can measure TV boost volts, scope voltages, medical equipment, etc. Other digitals stop at 1000 volts. High voltage probe extends measuring capabilities to 50 KV.

**■ PROTECTED INSIDE AND OUT** so you can be sure that your meter is working and not in the repair shop. Drop it from 10 feet, apply 1000 volts overload and even apply volts on ohms accidentally and Sencore digitals keep right on working.

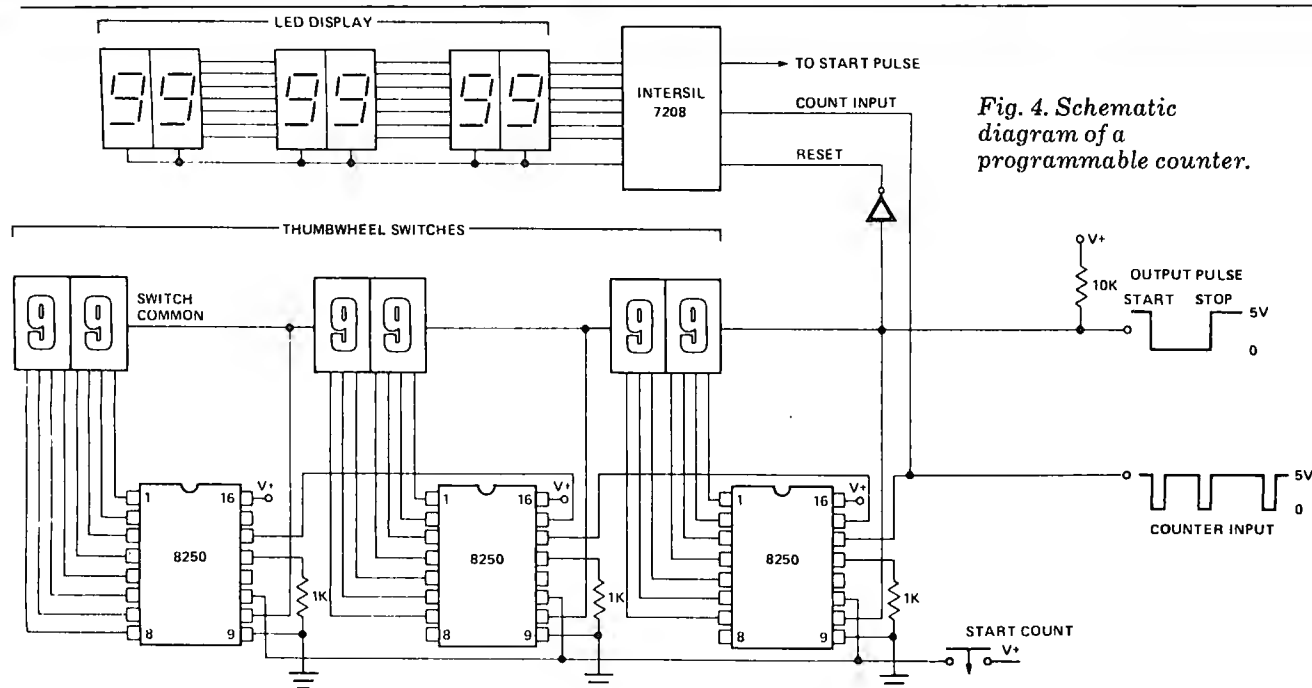

**Fig. 4. Schematic diagram of a programmable counter.**


**Reader's Circuit.** One of our many friends north of the border, Doug Wood (9 Peter Ave., Guelph, Ontario, Can., N1E 1TS), has been experimenting with light-controlled relays and feels that one of his designs may be of interest to other readers. Suitable for use in a variety of remote switching applications, his circuit, shown in Fig. 5, features a pair of light-activated SCR's and two sensitive-reed relays. Doug writes that he has used it as a TV "commercial killer" and for switching a radio receiver, operating the circuit by means of a flash-




**DVM36 \$158**  
3½ digit LED display,  
.5% DCV accuracy,  
battery or AC operated



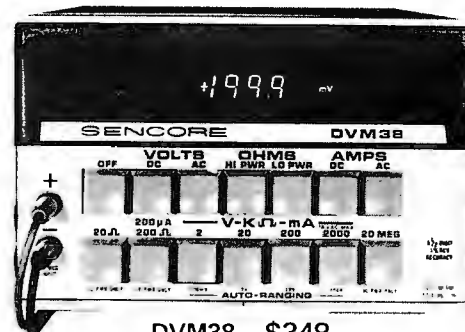**DVM32 \$198**  
3½ digit LED display,  
.5% DCV accuracy,  
battery or AC operated  
with automatic battery saver



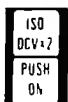**DVM38 \$348**  
3½ digit LED display,  
.1% DCV accuracy,  
AC operated, auto-ranging,  
auto-zero, king size pushbuttons



**[4] BATTERY SAVING FEATURES WHEN INSTRUMENT IS NOT IN USE** so you can be sure that your meter will be ready the next time you need it. Push the button on the probe on the DVM35 and DVM36 and only then do you start drawing current from your battery. An automatic patented circuit does the same job for you automatically when you apply voltage to the DVM32. The DVM38 is AC operated.

**TEN DAY FREE TRIAL**

**[5] 10 DAY FREE TRIAL** to be sure that Sencore digitals are all that we say they are. Simply march into your Sencore distributor and ask for a free trial or pay cash with a promise of a 10 day money back guarantee, if not 100% satisfied. Or, write Sencore, and we will see that our distributor contacts you.




**[6] 100% MADE RIGHT LIFETIME GUARANTEE** so you can be sure your meter was made right. If at any time you discover that a Sencore DVM was not made right, Sencore will make it right, parts and labor free of charge, for the lifetime of the product.

Plus other "make sure" features such as - direct reading with no parallax error - no effect from magnetic fields such as motors & RF fields - lab accuracy with high resolution - auto-polarity auto-zeroing and auto-ranging on the DVM38 . . . and you can see why you can be sure more times, in more circuits, than with any other multimeter on the market today - and for less money than old fashioned analog meters.

**SENCORE** 3200 SENCORE DRIVE  
SIOUX FALLS, S.D. 57107

CIRCLE NO. 55 ON FREE INFORMATION CARD

**Fig. 5. Circuit for a remote light-operated switch.**

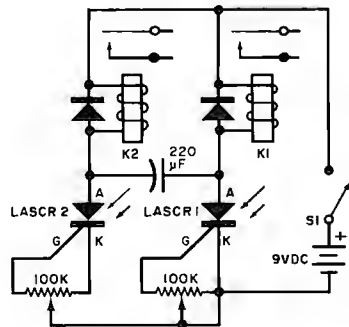

light or camera flash unit. Generally, the more powerful the light source used as a trigger, the greater the control range.

Doug has interconnected two conventional LASCR control circuits with a 220-µF commutation capacitor to form what is essentially a light-activated flip-flop. In operation, the two circuits are activated alternately to provide the required switching action. Consider, for example, that LASCR2 is conducting, energizing K2 and permitting the commutation capacitor to charge through K1 so that LASCR1's anode is at the dc source voltage. If light is now applied to LASCR1, this device will switch to a conducting state, discharging the commutation capacitor and momentarily removing LASCR2's anode voltage, causing this device to switch to an "open" or nonconducting state. When this happens, K2 is de-energized, K1 is energized, and the commutation capacitor is charged in the reverse direction. The circuit will then continue to operate in this state until light is applied to LASCR2, at which time the action reverses, with K2 energized and K1 de-energized. The small diodes across the relay coils serve to damp switching transients and suppress voltage spikes, while the variable resis-


tors in the LASCR gate-cathode circuits act as sensitivity controls.

With neither parts placement nor the wiring arrangement especially critical, the circuit may be duplicated using any preferred construction technique. Doug does suggest, however, that the LASCR's be mounted inside fiberboard, plastic or metal tubes (preferably with flat black interiors) to insure a directional response characteristic and avoid false triggering by extraneous light. The LASCR's are inexpensive low-voltage types (typically, Radio Shack No. 276-1096), and the diodes are general-purpose silicon rectifiers, such as type 1N4001. Standard 100k potentiometers are used as the sensitivity controls. The commutation capacitor should be a nonpolarized type; if this type is not available, one can be made up by connecting two 400- to 500-µF, 10-to-15-volt dc electrolytics in series back-to-back. Although Doug used reed relays for K1 and K2 in his model (typically, Radio Shack No. 275-230), conventional relays may be used if preferred (such as CALECTRO type D1-966). The ON-OFF switch, S1, is a spst toggle, slide or rotary type. Operating power is supplied by a 9-volt battery or line-operated dc power supply.

After the circuit assembly is completed and double-checked for possible errors, the unit's operation can be tested by using a sharply focused flashlight to trigger first one, then the other, LASCR, listening for the relay "clicks" signifying contact opening and closure. Next, the relay (K1 and K2) contacts are connected to switch the external load, taking care to observe the relay contacts' maximum ratings. If heavy power loads are to be switched, it may be necessary to add additional "booster" relays. Finally, the control unit is mounted in its desired operating position and the sensitivity controls are adjusted for optimum performance. The ideal settings are those which insure
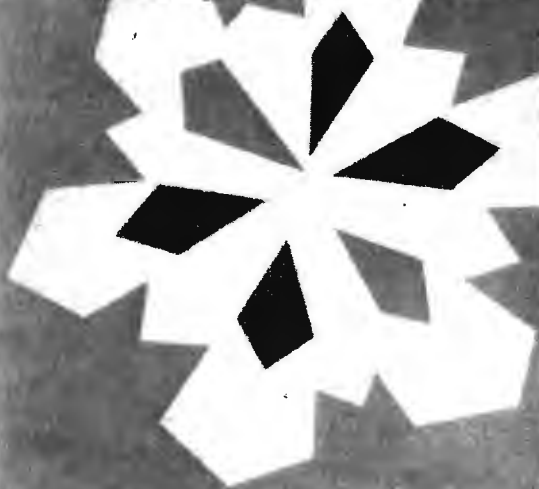
# HEATHKIT<sup>®</sup>

Practical projects for the "inside" season! Special sales and offers too!



**WINTER, 1977**

Digital Clock and Weather Monitor —  
See pages 2, 4, 9



**NEW** — High-Performance  
3-Way Speaker System  
See page 36

**NEW** — Universal  
Color TV Game  
See pages 3, 85


**NEW** — "Touch Control"  
Light Switch  
See pages 77, 96

**NEW** — Two-Way  
Freezer Alarm  
See pages 77, 96

Amateur Radio Equipment —  
See pages 64-75



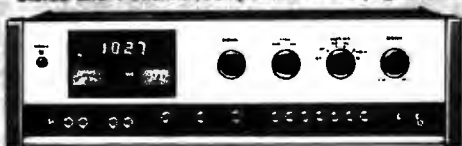Stereo and 4-Channel Components — See pages 25-41



Automotive Accessories —  
See pages 15-23



Self-study  
Electronics  
Courses —  
See pages  
79, 92-94



Color and B & W TV's — See pages 85-91



Test Instruments —  
See pages 42-47, 52-55



© 1976 Heath Company  
See index on page 3

**MAIL ORDER CATALOG**

"Heath" and "Heathkit" are registered trademarks of Heath Company.



# FREE!

Some of the most exciting electronic kits ever to come along are described in this **NEW Heathkit Catalog**.

**NEW! HW-2036 Synthesized 2-meter Amateur Radio Transceiver.**

Our finest 2-meter unit ever, with all the operating convenience and versatility you need for reliable 2-meter communications. Features complete offset capability and a built-in continuous tone encoder to access repeaters, plus new performance specifications that set an industry standard.

**NEW! AR-1515 Stereo FM-AM Receiver.**

Outstanding specifications and performance make the AR-1515 receiver the "heart" of any truly sophisticated stereo system. 70 watts, minimum RMS, per channel into 8 ohms with less than 0.08% total harmonic distortion from 20-20,000 Hz. Plus digital frequency readout and advanced styling others will be sure to copy.

**NEW! GR-2001 Computerized Color TV.**

The most convenient color TV system ever — you "program" it to change channels when you want. You can sequence an entire evening's viewing, then just sit back and relax. You can also "program" children's viewing so they watch only what you want them to watch. You can even have the GR-2001 automatically rotate your outdoor antenna for the best reception from each station. A truly sensational color TV breakthrough!

PLUS nearly 400 other superb, easy-to-build, money-saving products. You'll find a complete line of digital electronic clocks and weather instruments that give you important information "by the numbers" and with

electronic accuracy. Items for your car, home or office including an exciting combination clock/indoor-outdoor temperature monitor with a special temperature alarm.

Our self-study courses are now in use by the thousands! A really effective and low-cost way to teach yourself about electronics for fun, for knowledge, or for profit. We also have a wide selection of popular books covering almost everything in electronics.

There are many more exciting products to read about too! Home convenience items like a practical freezer alarm, a touch-control light switch, intercoms and a unique doorbell that lets you program a tune of your choice. Automotive instruments and accessories that help you keep your car running right for top performance and economy. Marine equipment that will make you a better boater and fisherman. Model aircraft Radio Control gear to give you championship performance. Security systems to protect your home and family. And of course, our world-famous Amateur Radio equipment and test and service instruments.

These are among the nearly 400 quality, fun-to-build kits described in this new Heathkit catalog. Kits for every interest. All with the world-famous Heathkit assembly manual — a step-by-step instruction guide that makes kitbuilding easy and leaves nothing to chance. And all backed by our "We won't let you fail" promise. Find out about the satisfaction, savings and FUN of kitbuilding.

**Send for your  
FREE copy today!**

HEATH

**Schlumberger**

**Heath Company  
Benton Harbor, Michigan 49022**

Please send me my FREE Heathkit Catalog.  
I am not on your mailing list. Dept. 10-26

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

CL-624 Zip \_\_\_\_\_

Send a FREE Catalog to my friend.  
Dept. 10-263

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_

FEBRUARY 1977

CIRCLE NO. 5 ON FREE INFORMATION CARD

# Sinclair DM2 Multimeter

COMPREHENSIVE, ACCURATE, PORTABLE and REALLY RUGGED



State-of-the-art circuit design, incorporating high-quality components, has resulted in a professional, 3-1/2 digit instrument of outstanding performance and reliability at a realistic price.

A custom-designed MOS LSI digital processing IC controls the auto-polarity dual-slope-integration A to D converter. The circuit built around this IC uses a MOSFET op-amp input buffer with 0.1% metal-film resistors. The result is excellent accuracy and stability with a very high basic input impedance. The instrument reads to  $\pm 1999$  and has a basic accuracy on the 1 VDC range of 0.3%  $\pm 1$  digit. Four 8 mm LED displays provide excellent legibility and angle of view. Front panel switch provides battery or line operation. 10 day money-back guarantee. 1 year manufacturer's warranty

Credit Card and Company P.O.'s call (516) 829-5858

## PLEASE SEND ME:

DM2 Multimeter  
(includes AC adapter) \$99.50

Carrying Case \$19.95

Power Pack \$3.90

Add \$3.50 shipping and handling.

Check or money order enclosed

for \$

## Charge my:

☐ BankAmericard ☐ Master Charge

No:

M.C. Bank No.

Exp. Date:

**technology trends**

P.O. BOX 732  
MANHASSET, NY 11030

Signature

Name

Company

Address

City

State Zip

New York residents add City and/or State Taxes.

PE-277

CIRCLE NO. 62 ON FREE INFORMATION CARD

## 1702A MANUAL EPROM PROGRAMMER

Features hex keypad, two digit hex address and two digit hex data display. Controls include load, clear, go! (step), key/copy, data in/data out, and counter up/down. Profile card includes high voltage pulse regulator, timing, 8 bit address and 8 bit data drivers/receivers. Two 6 1/2" x 9" stacked cards with spacers. Allows programming in 20 minutes - copying in 5 minutes. Requires +5, -9, and +80 volts.



ASSEMBLED ..... \$299.95  
KIT ..... \$189.95

## NOW

The best of two worlds... use our 1702 EPROM programmer as a manual data/address entry programmer... or connect it to your processor.

IMSAI/ALTAIR computer interface (requires 3 output ports, +1 input port) and software ..... \$49.95

Briefcase unit with power supplies and interface connectors (assembled and tested only) ..... \$599.95

## ANNOUNCING

Our NEW 16K Byte Pseudo-Static, IMSAI/ALTAIR compatible RAM. Single card slot. Uses less power than equivalent low power RAM. All memory chips socketed. Uses all prime, factory fresh ICs. High quality, two-sided, through-hole-plated circuit board. Crystal controlled, totally invisible refresh system requires NO software management. Just plug it in and use like STATIC memory.

Complete kit ..... \$349.95  
Assembled, tested, and burned in ..... \$549.95

## ASSOCIATED ELECTRONICS

12444 Lambert Circle • Garden Grove, CA 92641  
(714) 539-0735


positive actuation by the controlling light source but avoid false triggering by variations in ambient light levels.

**Device and Product News.** Motorola has introduced a bipolar LSI circuit that should be of interest to advanced experimenters working with microprocessor systems. The new device, called a Priority Interrupt Controller (PIC), allows priority control on the interrupt inputs to a microprocessor and has been dually designated the MC8507/MC-6828 to indicate that its performance has been optimized for the M6800 microprocessor system. However, it also may be used in non-M6800 applications. Basically, the PIC eliminates the software interrupt polling routing in systems containing eight or multiples of eight I/O devices, such as the Peripheral Interface Adapter (PIA), Asynchronous Communications Interface Adapter (ACIA), Synchronous Serial Data Adapter (SSDA), and so on. Functionally, the PIC can change the interrupt vector, reserved in memory for hardware interrupts, into one-of-eight alternate vectors assigned to the I/O service routines. The PIC modifies the low-order bytes of the reserved interrupt address. The MC8507/MC6828 is offered in both ceramic and plastic 24-pin DIP's.

On the other hand, if you're working with conventional logic circuits used in critical areas, you may want to investigate two new IC's announced recently by *Teledyne Semiconductor* (Mountain View, CA 94040). Designed for applications in high (electrical) noise areas, the HiNIL 306 and 307 both contain two 2-input NOR gates and two 3-input NOR gates. The 306 features active pullup outputs and 10-mA output drive currents, which permits it to drive lines up to 10 feet without loss of noise immunity. The 307 has open collectors so the outputs can be collector OR'd. Both devices operate on 10 to 16 V dc. Typical applications include CMOS input interface, industrial controls, medical instrumentation, and marine electronics. The HiNIL 306 and 307 are available in standard 16-pin DIP's in both plastic and ceramic versions.

*National Semiconductor Corporation* (2900 Semiconductor Drive, Santa Clara, CA 95051), has combined classical circuit techniques with an ion-implanted p-channel MOS process to create a new low-cost 8-bit analog-to-digital converter. Designated type MM5357, the new A/D converter contains a chain of 256 identical resistors connected in series, 255 analog switches, a high-impedance input comparator, output latches, and control logic on a single monolithic chip. In operation, conversion is performed using the successive approximation technique, whereby an unknown analog voltage is compared to the voltages at the resistor tie points by means of analog switches. A 10-volt reference applied across the resistor chain sets 256 precision voltages against which the unknown input voltage is compared by the analog switches under control of the on-chip logic. Requiring +5 and -12 V dc sources and dissipating approximately 170 mW, the MM5357 is supplied in an 18-pin Epoxy-B DIP.

National Semiconductor also has developed a new series of monolithic frequency-to-voltage converters with a combination high-gain op-amp-and-comparator. Identified as the LM2907 and LM2917 tachometer speed switches, they are specifically designed to operate relays, lamps, and other components when the input frequency reaches or exceeds a selected rate, and are especially suited for speedometers, tachometers and automotive lock and clutch controls where over-or-under speed sensing is required. The devices use a combination op-amp-and-comparator with a floating transistor as output, and can furnish either a supply-referenced load of 50 mA or a swing-to-ground for zero frequency. ◇

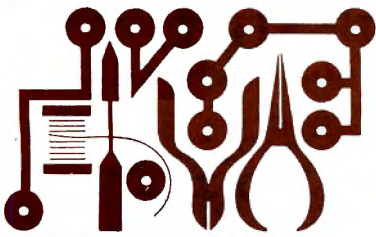

# Experimenter's Corner

By Forrest M. Mims

## FLIP-FLOPS AND DECADE COUNTERS—PART 1

**C**ounting circuits perform many important roles in digital electronics. They are used to measure frequency, compute time, divide pulse streams by a fixed constant, generate signal sequences, and perform many other useful operations.

The common flip-flop is a fundamental counter circuit. The best way to understand a flip-flop is to build an ultra-simple flip-flop from a pair of inverters. But first, let's establish a couple of important definitions.

In digital electronics an electrical signal is either *high* or *low*. These two states are used to represent the binary bits 1 and 0. In positive logic, 1 is high and 0 is low. Negative logic means 1 is low and 0 is high. Since digital logic IC's commonly operate from a single-ended power supply, a high state represents a voltage near the supply voltage. A low state represents a voltage near 0 volt or ground.

With these basic definitions in mind, we can easily design a simple flip-flop from two of the six inverters in a 7404 hex inverter. As you may already know, the signal at the input of an inverter is changed from high to low (or from low to high) at the output. All we have to do to make a simple flip-flop is connect the in-

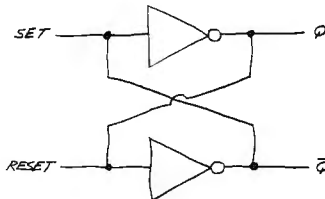


Fig. 1. The basic flip-flop.

verters in crisscross fashion as shown in Fig. 1. When the output of the upper inverter is high, the output of the lower inverter is low. Similarly, when the output of the upper inverter is low, the output of the lower inverter is high. We therefore have a circuit which can occupy one of two stable states. That, of course, is the simplest definition of the flip-flop.

Figure 2 shows a practical version of this ultra-simple flip-flop with an LED state indicator at both outputs. The resistor limits current through the LED's to a safe 10 milliamperes or so. You can assemble the circuit on a molded plastic solderless breadboard (a *must* for experimenters and design engineers alike) in a few minutes. If you don't have a 5-volt supply, use a fresh 6-volt battery and drop the voltage to about 5 volts with a 1N914 diode connected so that it is forward biased between the battery's positive terminal and the circuit.

When power is applied to the circuit,

one of the LED's will glow. Momentarily grounding the SET input will cause only the Q output LED to glow. If the RESET input is momentarily grounded, only the Q-bar LED will glow. Note that the LED continues to glow after the input signal is removed. This memory or latching action is the key to the operation of many kinds of complex logic circuits.

The ultra-simple flip-flop in Fig. 2 is not practical for counting applications. However, it's possible to make a binary counter by using gates instead of inverters, and by adding a couple of gates which allow the circuit to flip or flop only on command from an external clock pulse.

**The 7473 Dual J-K Flip-Flop.** We can actually assemble a clocked flip-flop from the four gates in a 7400 quad NAND Gate, but a far more convenient approach is to use a ready-made version such as the 7473 dual J-K flip-flop. This flip-flop will toggle back and forth between its two output states when connected to a 555 clock circuit as shown in Fig. 3.

The circuit in Fig. 3 makes a nice dual LED flasher—but it also demonstrates the important flip-flop applications of counting and dividing. You can see this by assembling the circuit on a solderless breadboard (which I urge you to do), and disconnecting the cathode of the LED at the Q-bar output (pin 13 of the 7473) and connecting it to the clock output of the 555 (pin 3). Now, if you slow down the clock frequency to a few Hertz by adjusting the 100K pot, you will see that the LED at the Q output of the flip-flop flashes at exactly half the rate of the LED connected to the clock. In other words, the flip-flop is functioning as a divide-by-two counter.

All kinds of possibilities open up if we connect the unused Q output of the flip-flop to the clock input of the second flip-flop in the 7473. Figure 4 shows how to wire things together on your solderless breadboard. Obviously the second flip-

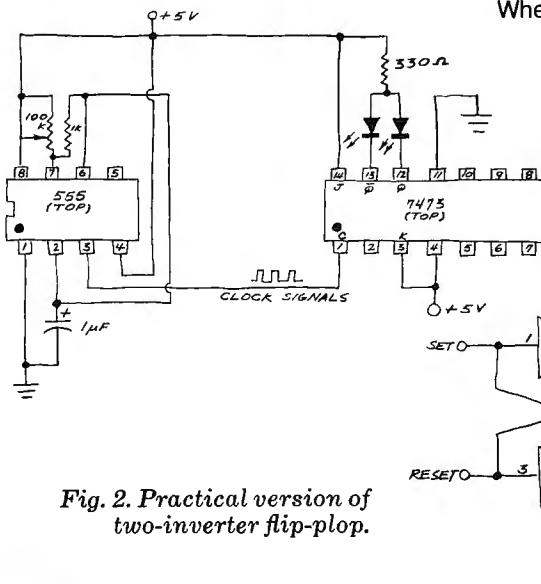


Fig. 2. Practical version of two-inverter flip-flop.

Fig. 3. 7473 flip-flop with 555 clock circuit.

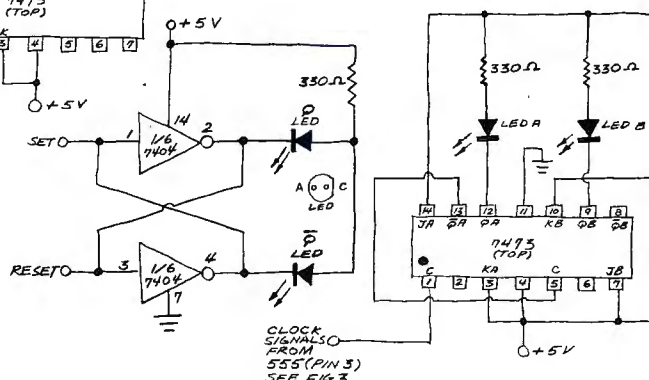


Fig. 4. Two-bit counter made from 7473 dual flip-flop.

flop in this new circuit will receive only half as many clock pulses as the first flip-flop. Therefore its Q LED will flash at only one-fourth the rate of the clock frequency. So now we have a divide-by-four counter. And this gives us a two-bit binary counter circuit.

To see how the circuit operates as a two-bit counter, remove the *CLOCK* LED and arrange the two flip-flop LED's so the one which is connected to the second flip-flop (the 'slow one') is to the left of the other one. By slowing down the clock you'll see this flash sequence (off = 0; on = 1):

## LED B

0  
0  
1  
1  
0

(etc.)

This binary sequence, of course, corresponds to the decimal count 0 . . . 1 . . . 2 . . . 3 . . . 0 . . . etc. The circuit is called a two-bit counter since it recycles when the count exceeds two bits.

A really useful counter can be made by cascading four flip-flops to give four-bit capability. This would permit a deci-

## LED A

0  
1  
0  
1  
1

mal count of from 0 to 15. By means of external connections which automatical-

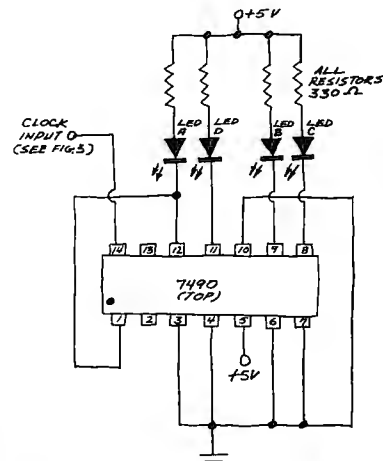


Fig. 5. 7490 four-bit counter.

ly reset the counter when a desired count has been reached, a range of count intervals could then be achieved.

Several quad flip-flop (four-bit) counter chips are available so there is no need to use separate gate or flip-flop packages. Since a 0 to 9 count has more applications than a full 0 to 15 count (at least for us decimal-oriented human beings!) let's take a look at the 7490 Decade Counter.

**7490 Decade Counter.** As its name implies, the 7490 Decade Counter is primarily intended for 0 to 9 counting. To provide a range of applications, one of its internal flip-flops is not connected to the others. This gives two separate counters in one package: a divide-by-two and a divide-by-five. Connecting the A output (pin 12) to the *CLOCK* input of the divide-by-two flip-flop (pin 14) forms a chain of four flip-flops which counts from 0000 to 1001 (0 to 9) before recycling.

Figure 5 shows how to connect the 7490 to the 555 clock of Fig. 3. When the circuit is running, you will obtain the following count sequence:

D	C	B	A	
0	0	0	0	(0)
0	0	0	1	(1)
0	0	1	0	(2)
0	0	1	1	(3)
0	1	0	0	(4)
0	1	0	1	(5)
0	1	1	0	(6)
0	1	1	1	(7)
1	0	0	0	(8)
1	0	0	1	(9)
0	0	0	0	(0)
0	0	0	1	(1)

(etc.)

In simplest terms, the four flip-flops in the 7490 count from 0 to 9 and then recycle.

## Checklist of Books for the Libraries of Technicians, Hobbyists & Students

### GRAND NEW BOOKS—JUST PUBLISHED!

Master Transistor AC Substitution Handbook. 504 p.	\$7.95
Servicing Medical & Bioelectronic Equipment. 336 p.	\$8.95
Model Railroad Electronics. 294 p., 224 il.	\$5.95
Linear IC Applications Handbook. 280p.	\$6.95
Broadcast Engrg./Maint. Hdbk. 532 p., 235 il.	\$19.95
Complete Hdbk. of Locks, Locksmithing. 392 p., 348 il.	\$6.95
Practical Solid-State DC Power Supplies. 156 p., 151 il.	\$6.95
Optoelectronics Guidebk.—with tested projects. 196 p.	\$5.95
Transistor Ignition Systems. 252 p., 162 il.	\$5.95
TV Lighting Handbook. 228 p., 261 il.	\$12.95
How to Repair Home Kitchen Appliances. 294 p., 205 il.	\$5.95
Fun With Electronics. 140 p., 88 il.	\$3.95
Talk-Back TV: Two-Way Cable Television. 238 p., 54 il.	\$5.95
Understanding/Use Modern Signal Generators. 294 p.	\$6.95
106 Easy Electronic Projs.—Beyond Transistors. 224 p.	\$5.95
Using Modern Electr. Serv. Test Eqp. 252 p., 177 il.	\$5.95
Mathematics Unraveled—Commonsense Approach.	\$6.95
Master Tube Substitution Handbook. 322 p., 548 il.	\$4.95
Modern Guide to Digital Logic. 294 p., 222 il.	\$6.95
VHF/UHF Fire, Police, Ham Scanners Man. 250 p., 114 il.	\$5.95
DP AMP Circuit Design & Applications. 280 p., 239 il.	\$6.95
Master Hdbk. of Digital Logic Appl. 392 p., 287 il.	\$7.95
CET License Handbook 2nd ed. 448 p., 381 il.	\$8.95
The Electronic Musical Instr. Manual. 210 p., 385 il.	\$6.95
Microprocessor/Microprogramming Hdbk. 254 p., 176 il.	\$6.95
Sourcebook of Electronic Organ Circuits. 168 p., 101 il.	\$4.95
Build Your Own Working Robot. 238 p., 83 il.	\$5.95
CBer's Handybook of Simple Hobby Projs. 168 p., 114 il.	\$3.95
Fire & Theft Security Systems 2nd ed. 192 p., 114 il.	\$5.95
How to Rpr. Home Laundry Appliances. 280 p., 137 il.	\$5.95
Piloting/Navigation & Pocket Calculator. 392 p., 233 il.	\$8.95

### DO-IT-YOURSELF: AUTOMOTIVE & APPLIANCES

How to Make Your Own Built-In Furniture. 336 p., 758 il.	\$5.95
Homeowner's Handy "Do-It" Manual. 280 p., 84 il.	\$7.95
Building Model Ships From Scratch. 378 p., 84 il.	\$7.95
Homeowner's Guide to Saving Energy. 196 p., 183 il.	\$5.95
Customizing Your Van. 192 p., 150 il.	\$3.95
The Woodworker's Bible. 434 p., 1151 il.	\$5.95
Dog Owner's Medical Manual. 252 p., 237 il.	\$5.95
How to Train a Watchdog. 224 p., 45 il.	\$5.95
Motorcycle Repair Handbook. 392 p., 260 il.	\$6.95
Step-By-Step Guide: Carburetor Tuneup/Overhaul. 224 p.	\$4.95
Complete Hdbk. of Model Railroad. 350 p., 238 il.	\$6.95
Homeowner's Guide to Solar Heating/Cooling. 196 p.	\$4.95
Do-It-Yourself's Guide: Home Plan/Constr. 238 p.	\$4.95
Step-By-Step Guide to Brake Servicing. 238 p., 248 il.	\$4.95
Step-By-Step Guide: Chrysler Eng. Maint./Rpr. 256 p.	\$5.95
Subcontract Your House: Bldg./Remodel. 196 p., 63 il.	\$4.95
Auto Electronics Simplified. 256 p., 202 il.	\$5.95
The Complete Auto Electric Handbook. 210 p., 139 il.	\$5.95
Concrete & Masonry. 392 p., 213 il.	\$5.95
Practical Home Constr./Carpentry Hdbk. 448 p., 180 il.	\$5.95
How to Repair Diesel Engines. 308 p., 237 il.	\$5.95
Central Heating/Air Cond. Repair Guide. 320 p., 285 il.	\$6.95
Small Appliance Repair Guide—Vol. 2. 210 p., 119 il.	\$4.95
Elect. Wiring/Lighting For Home/Office. 2nd ed. 155 il.	\$4.95
How to Repair Small Gasoline Engines. 204 p., 282 p.	\$6.95
How to Repair Home/Auto Air Cond. 208 p., over 100 il.	\$4.95

### ELECTRONICS TECHNOLOGY/COMPUTERS/CALCULATORS

Modern Electronics Math. 686 p., 424 il.	\$9.95
Master Hdbk. of 1001 Prac. Electr. Circ. 602 p., 1250 il.	\$9.95
Impedance. 196 p., 90 il.	\$5.95
Intro to Medical Electronics-2nd ed. 320 p., 126 il.	\$7.95
Computer Programming Handbook. 518 p., 114 il.	\$8.95
Computer Technician's Handbook. 480 p., over 400 il.	\$8.95
Microelectronics. 266 p., 228 il.	\$5.95
Basic Digital Electronics. 214 p., 117 il.	\$4.95
Switching Regulators/Power Supplies. 252 p., 128 il.	\$6.95
Adv. Appl. for Pocket Calculators. 304 p., 275 il.	\$5.95
Tower's Intern. Transistor Selector. 140 p., (7" x 10")	\$4.95
Elect. Conversion Symbols/Formulae. 224 p., 252 il.	\$4.95
Effective T'shooting With EVM/Scope. 238 p., 185 il.	\$5.95
Getting the Most Out of Electronic Calculators. 204 p., 281 il.	\$4.95
Aviation Electronics Handbook. 406 p., 227 il.	\$8.95
How to Test Almost Everything Electr. 160 p., 144 il.	\$3.95
Digital Logic Electronics Handbook. 308 p., 226 il.	\$6.95
Modern Applications of Linear IC's. 276 p., 301 il.	\$9.95
10-Minute Test Tech. For PC Svcs. 216 p., 114 il.	\$4.95
Electr. Unraveled—New Commonsense Approach. 228 p.	\$5.95
How to Tshoot/Repair Electr. Test Eqp. 252 p., 143 il.	\$6.95
Understanding/Using the Oscilloscope. 272 p., 170 il.	\$5.95
Industrial Electr.: Principles & Practice. 416 p., 380 il.	\$8.95
Dictionary of Electronics. 420 p., 487 il.	\$4.95

### COLOR TV SERVICING

Color TV Trouble Facts—Probs/Sols 3rd ed. 434 p.	\$5.95
Solid-State Color TV Photo/Sym. Guide. 224 p., 169 il.	\$5.95
Beginner's Guide to TV Repair. 176 p., 50 il.	\$4.95
T'shooting With the Dual-Trace Scope. 224 p., 252 il.	\$5.95
TV Troubleshooter's Hdbk.—3rd ed. 448 p., over 300 il.	\$4.95
Color TV Case Histories Illustrated. 238 p., 219 il.	\$5.95
TV Schematics: Read Between the Lines. 252 p., 188 il.	\$5.95
Logical Color TV Troubleshooting. 240 p., 151 il.	\$5.95

TV Bench Servicing Techniques. 228 p., 177 il.	\$4.95
Modern Radio Repair Techniques. 260 p., 36 il.	\$4.95
How to Interpret TV Waveforms. 256 p., 250 il.	\$4.95
All-In-One TV Alignment Handbook. 304 p., 145 il.	\$5.95
TV Tuner Schematic/Servicing Manual. 224 p., 287 il.	\$6.95
How to Use Color TV Test Instruments. 256 p., 230 il.	\$5.95
Home-Call TV Repair Guide. 144 p., 20 il.	\$3.95
Pinpoint TV Troubles in 10 Minutes. 327 p., 394 il.	\$5.95

### CB COMMUNICATIONS & HAM RADIO

CB Schematic Svcs. Manuals each 200 p., \$5.95. Vol 1 Kris Browning, Hy-gain, Penney's, Vol. 2 Teaberry, Unimetrics, Pearce-Simpson, Siltronix, Vol. 3 E.F. Johnson, SBE-Linear, Sonar, Royce, Vol. 4 Pace Fanon/Courier.	\$7.95
2nd Class FCC Encyclopedia. 602 p., 445 il.	\$7.95
Complete Shortwave Listener's Hdbk. 288 p., 101 il.	\$6.95
CB Radio Operator's Guide—2nd ed. 256 p., 139 il.	\$5.95
How to Hear/Speak CB in a Short-Short. 172 p., 85 il.	\$3.50
Pictorial Guide to CB Radio Install/Rpr. 256 p., 304 il.	\$5.95
Practical CB Radio T'shooting & Repair. 236 p., 108 il.	\$5.95
Complete FM 2-Way Radio Hdbk. 284 p., 111 il.	\$6.95
Amat. FM Conversion/Constr. Projs. 256 p., 187 il.	\$5.95
Bdct Ann'r. 3rd Class FCC Study Guide. 168 p., 19 il.	\$3.95
How to Be A Ham—Incl. Latest FCC Rules. 192 p., 25 il.	\$3.95
Commercial FCC License Handbook. 444 p., 150 il.	\$5.95
The 2-Meter FM Repeater Circuits Hdbk. 312 p., 194 il.	\$6.95
RTTY Handbook. 320 p., 230 il.	\$6.95
Citizens Band Radio Service Manual. 228 p., 84 il.	\$5.95
AMATEUR RADIO STUDY GUIDES: Novice \$5.95 General \$7.95 Advanced \$5.95 Extra \$5.95 Incentive \$4.95	

### HOBBY ELECTRONICS

How to Read Electronic Circuit Diagrams. 192 p., 140 il.	\$4.95
21 Simple Trans. Radios You Can Build. 140 p., 122 il.	\$3.95
Basic Electricity/Beginning Electronics. 252 p., 191 il.	\$5.95
Radio Control for Models. 350 p., 417 il.	\$6.95
MOSFET Circuits Guidebook. 196 p., 104 il.	\$4.95
Prac. Circuit Design for the Experimenter. 196 p., 119 il.	\$4.95
111 Digital & Linear IC Projects. 210 p., 275 il.	\$5.95
Radio Astronomy for the Amateur. 252 p., 96 il.	\$5.95
Build-It Book of Mini Test Meas. Instr. 238 p., 151 il.	\$4.95
RF & Digital Test Eqp. You Can Build. 252 p., 217 il.	\$5.95
Miniature Projects For Electr. Hobbyists. 168 p., 77 il.	\$3.95
Practical Triac/SCR Projs. For The Exp. 192 p., 146 il.	\$4.95
Integrated Circuits Guidebook. 196 p., 119 il.	\$5.95
Solid-State Circuits Guidebook. 252 p., 227 il.	\$5.95
Electronics For Shutterbugs. 204 p., 109 il.	\$5.95
Prac. Test Instruments You Can Build. 204 p., 157 il.	\$4.95
How to Build Solid-State Audio Circuits. 320 p., 190 il.	\$5.95
Radio-Electronics Hobby Projects. 192 p., 214 il.	\$4.95
Handbook of IC Circuit Projects. 224 p., 136 il.	\$4.95
Solid-State Projs. for the Experimenter. 224 p., 228 il.	\$4.95
Electronic Experimenter's Guidebook. 182 p., 86 il.	\$4.95
125 One-Transistor Projects. 192 p., 125 il.	\$4.95
64 Hobby Projects for Home & Car. 192 p., 159 il.	\$4.95

### AUDIO, Hi-Fi & ELECTRONIC MUSIC

Electronic Music Circuit Guidebook. 224 p., 180 il.	\$6.95
Q & A About Tape Recording. 264 p., 102 il.	\$5.95
Handbook of Multichannel Recording. 322 p., 196 il.	\$7.95
Auto Stereo Service & Installation. 252 p., 245 il.	\$5.95
Srv. Cassette & Cartridge Tape Players. 294 p., 196 il.	\$6.95
Experimenting With Electronic Music. 180 p., 103 il.	\$4.95
Cassette Tape Recorders, How Work/Car Repair. 204 p.	\$4.95
Acoustic Techniques for Home & Studio. 224 p., 168 il.	\$5.95
Pictorial Guide to Tape Recorder Rprs. 256 p., 320 il.	\$4.95
How to Repair Musical Instrument Amps. 288 p., 50 il.	\$5.95
Jap. Radio, Record, Tape Player Srvcs. Manual. 228 p.	\$6.95
Servicing Electronic Organs. 196 p., 158 il.	\$7.95
Tape Recording for Fun & Profit. 224 p., over 200 il.	\$5.95

### ALL-IN-ONE COLOR & B&W TV SCHEMATIC/SERVICING MANUALS

Each vol. has complete service data, parts lists, full-size schematics, and all other info needed. Each 8 1/2" x 11", 196 pgs. Each only \$5.95 unless marked. COLOR TV: Adm. Vol. 1 □ Vol. 2 \$6.95 □ GE Vol. 1 □ Vol. 2 □ Vol. 3 □ Jap. Vol. 1 □ Vol. 2 \$4.95 □ Vol. 3 \$4.95 □ Vol. 4 □ Vol. 5 □ Magnavox Vol. 1 \$4.95 □ Vol. 2 \$4.95 □ Vol. 3 □ Airline □ Mot. Vol. 1 \$4.95 □ Vol. 2 □ Philco □ RCA Vol. 1 □ Vol. 2 □ Vol. 3 □ Vol. 4 □ Vol. 5 □ Sears □ Serv. Modular Rec'r. Vol. 1 \$6.95 □ Vol. 2 \$4.95 □ Syl. Vol. 1 □ Vol. 2 □ Toshiba □ Zenith Vol. 1 □ Vol. 2 □ Vol. 3 □ Vol. 4 □ B&W TV: Adm. \$7.95 □ GE \$7.95 □ Jap. \$6.95 □ Mag. \$4.95 □ Mot. \$4.95 □ Philco \$4.95 □ RCA \$7.95 □ Syl. \$4.95 □ Zenith \$7.95 □

### NO RISK COUPON-MAIL ENTIRE AD

TAB BOOKS, Blue Ridge Summit, Pa 17214

Please send me books checked above

□ I enclose \$\_\_\_\_\_ send postpaid

□ Please invoice on 10-day FREE trial

Name \_\_\_\_\_ Phone \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

SAVE POSTAGE by remitting with order. Foreign add 10%. Pa. residents add 6%. PE-27




Have a problem or question on circuitry, components, parts availability, etc? Send it to the Hobby Scene Editor, POPULAR ELECTRONICS, One Park Ave., New York, NY 10016. Though all letters can't be answered individually, those with wide interest will be published.

By John McVeigh
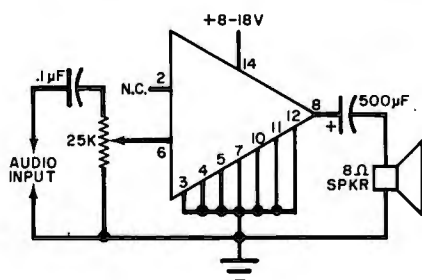
## LOW-POWER AUDIO AMP

**Q.** Can you show me a schematic for an audio amp to boost signals from my crystal set?—Rick Laird, Omaha, NE

**A.** The LM380 audio amplifier is well suited for this application. It has a high input impedance, requires a single-ended power supply, and will deliver up



to 2.5 watts or more of output power to an 8-ohm speaker. Note that seven pins of the IC are tied together and grounded. They should be connected to a heat sink (such as a large copper "land" on a pc board) at least six square inches (38.7 cm<sup>2</sup>).

## 40-CHANNEL CB MODIFICATION

**Q.** I own a Royce Model 1-602A 23-channel mobile transceiver and would like to have it modified to cover the expanded Citizens Band. Can I do this?—Don J. Chillstrom, Wickenburg, AZ.

**A.** As a general rule, 23-channel transceivers will not be able to be adapted to


cover the 17 new channels. In fact, the FCC has specifically prohibited the use of external add-on circuits to expand channel coverage. However, there is one twist. Some manufacturers of PLL-synthesis transceivers are offering to "re-manufacture" rigs to cover the full 40 channels. The use of phase-locked loops in frequency generation makes this rather simple. The principal modification involves adding more combinations to the  $\div N$  part of the synthesizer. The FCC has not objected to this program. Your transceiver uses crystal synthesis, and therefore cannot be so modified. Note, however, that it is permissible to use receiving converters with any receiver. Such a converter could be teamed up with your car radio for full-band coverage. A representative circuit appeared in the October 1976 issue of POPULAR ELECTRONICS.

## CRYSTAL CHECKER

**Q.** Do you have a simple circuit for checking crystals in the 2- to 6-MHz range?—William J. Bills, Maitland, FL.

**A.** This tester can be used with crystals over the 0.1-to-10-MHz range. The lamp

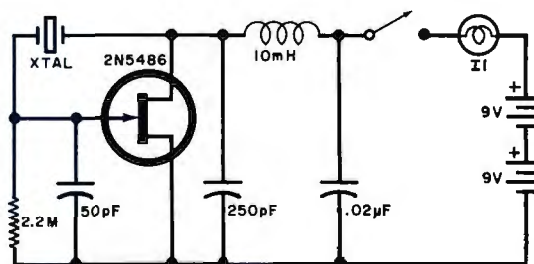(a GE 1869, 10-volt, 14-mA type or equivalent) will light when the crystal is not in the circuit or is bad and when the switch is closed. When a good crystal is installed, the circuit oscillates and current through the lamp drops below 10 mA. The lamp will then dim or go out.




## TONE-ACTIVATED RELAY

**Q.** I have built a digital clock using a Mostek MK50252N chip which incorporates a "beeper" alarm. Is there a circuit I can add which will convert the beeps into a steady dc level, which will in turn cause a transistor to conduct and energize a relay? I would like to use the alarm function to turn appliances on.—Paul D'Ermielie, Staten Island, NY.

**A.** One way of performing this function is to use a tone decoder IC like the 567. This chip has been featured in the Experimenter's Corner and has an output stage that can sink up to 100 mA. All you

would have to do is select the proper values of resistance and capacitance for response at the output frequency of the alarm. Here's another solution. In the circuit shown, the diode produces pulsating dc which is smoothed out by the RC combination with a time constant of about one second. (Values can be changed for a different time constant). When the capacitor charges up sufficiently, it will source base current for the switching transistor, which will turn on and energize the relay. When the beeper stops, the transistor will cut off. Any general-purpose switching transistor can be used. Be sure that the relay coil is compatible with the transistor, and that its contacts can handle the current demand of the appliances.

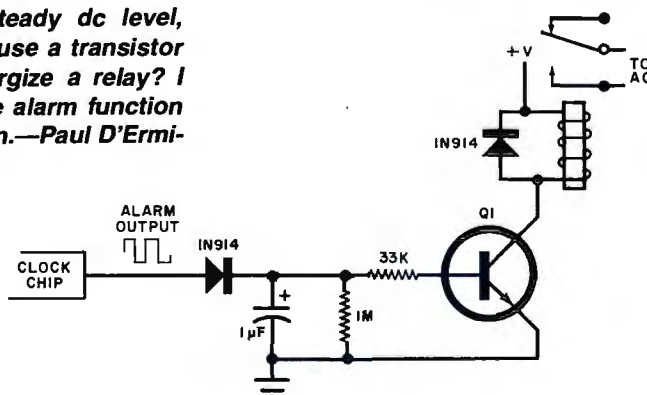




# Product Test Reports
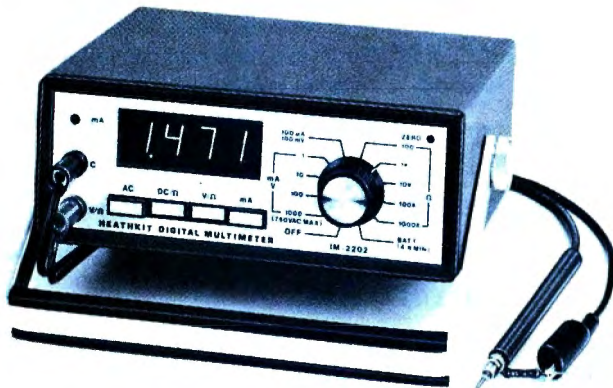
## HEATHKIT MODEL IM-2202 DIGITAL MULTIMETER KIT

*3½ digits with gas-discharge display for field and bench testing.*



**T**HE COST of owning a high-accuracy digital multimeter has dropped considerably over the past couple of years. Today, you can buy for less than \$250 a DMM with features and accuracy that rival laboratory-grade instruments of only a few years ago. One instrument that reflects this trend is the Model IM-2202 DMM from Heathkit. Its low price brings to the user a 3½-digit display, 0.5% to 0.2%,  $\pm 1$ -digit accuracy on dc, and the capability of measuring ac and dc voltage and current and resistance over wide ranges. In addition, the DMM has built-in ac and rechargeable nickel-cadmium cell dc power supplies that make it equally suitable for bench and field servicing.

The Model IM-2202 DMM measures 8¼" W × 8" D × 3" H (21 × 20.3 × 7.6 cm) with its handle folded to the rear and weighs 7 lb (3.2 kg). Available only in kit form, it sells for \$199.95.

**Technical Details.** The DMM's white control panel labelled in black is clean and functional. Arranged in a column along the left side of the panel are three banana jacks labelled from top to bottom MA, C (common), and V/Ω for the test-cable inputs. To the right of the jacks is the display window, below which is a bank of four pushbutton switches that are labelled AC, DC, V/Ω, and MA. The right third of the panel is occupied

by a large range/function switch that also has positions for power OFF and BATT (battery check, specified on the panel at 4.6 volts minimum). Accessible through a small hole in the upper right corner of the panel is the screwdriver-adjustable ZERO control.

There are five dc-voltage ranges that go to 100 mV and 1, 10, 100, and 1000 volts full-scale. The input resistance is 50 megohms on the 100-mV range, 500 megohms on the 1000-volt range, and 10 megohms on the remaining ranges. The accuracy of the instrument is specified at 0.5%,  $\pm 1$  digit using the built-in references and 0.2%,  $\pm 1$  digit using laboratory standards. The DMM can safely handle an overload of 300 volts on the 100-mV and 1-volt ranges and 1000 volts on the three highest ranges.

The ac voltage ranges are the same as for the dc-voltage function, except that on the 1000-volt range the maximum specified input is 750 volts. Input impedance is 10 megohms, paralleled by 120 pF on the two lowest ranges and 60 pF on the upper ranges. The overload capability is 250 volts on the 100-mV and 1-volt ranges and 750 volts on all other ranges. The accuracy of the instrument is 1.0%,  $\pm 1$  digit over a frequency range of from 40 to 1000 Hz (except 40 to 10,000 Hz on the 100-mV and 1-volt ranges) using the built-in references. Using laboratory references, the

accuracy is 0.5%,  $\pm 1$  digit from 40 to 1000 Hz, except to 2000 Hz on the 750-volt range.

Current in both the ac and the dc function can be measured to 100  $\mu$ A and 1, 10, 100, and 1000 mA full-scale. The voltage drop in dc is 100 mV on the 100- $\mu$ A and 1-mA ranges, 150 mV on the 10- and 100-mA ranges, and 300 mV on the highest range. On ac, the drop is 100 mV on the three lowest ranges, 150 mV on the 100-mA range, and 300 mV on the 1000-mA range. Accuracy on dc is 0.5% (except 1% on the 1000-mA range),  $\pm 1$  digit with the built-in references and 0.2% (except 0.5% on the 1000-mA range) with laboratory standards. Ac accuracy is 1.0% (1.5% on the 1000-mA range),  $\pm 1$  digit from 40 to 10,000 Hz on the built-in references and 0.5% (1.0% on the 1000-mA range),  $\pm 1$  digit from 40 to 10,000 Hz. The input is coupled through a 3-ampere fuse to shunt diodes for overload protection with inputs exceeding about 1.2 volts.

There are also five resistance ranges that go to 100, 1000, 10,000, 100,000 ohms and 1 megohm full-scale. Test current is 1.0 mA on the first two ranges, 0.1 mA on the 10,000-ohm range, 1.0  $\mu$ A on the 100,000-ohm range, and 10  $\mu$ A on the highest range. The open-circuit potential at the test probes is 12 volts. Accuracy is 2%,  $\pm 1$  digit using the built-in references. Positive input protection to 400 volts is provided by a blocking diode, while negative input protection is provided by a 0.03-ampere fuse and a shunt diode.

The DMM has a maximum display count of 1999, and its overrange capability is 100% on all but the 1000-volt dc and 750-volt ac ranges. Normal-mode rejection is stated as 35 dB or better, while common-mode rejection is 80 dB or better. The instrument can be operated 1500 volts above power line ground during line operation. The stated operating temperature is from 10°C to 40°C.

The instrument can be operated on either 110 to 130 or 220 to 260 volts 50 or 60 Hz line power, depending on an internal setting. It consumes 5 watts of power during battery charging.

The displays used are large ½" (12.7-mm) seven-segment orange gas-discharge types. Both + and - are displayed when taking dc measurements, depending on the polarity at the input to the DMM. An over range condition is indicated in the display by a flashing 1 in the half-digit location. The meter also features dual-slope A/D (analog-to-digital) conversion, automatic blanking of leading zeros, rechargeable nickel-cad-

mium cells that come standard, a carrying handle that doubles as a convenient tilt stand, and nonskid rubber feet.

**About the Kit.** Although this is a relatively complex digital multimeter, the kit is fairly easy to assemble owing to the well-written and well-illustrated assembly manual that comes with it. But for a handful of components, all parts mount on three printed circuit boards, including the function selecting pushbutton switches and the rotary range/function switch.

High-quality components and materials are used throughout the instrument. The printed circuit boards are epoxy-fiberglass, two of the three are double-sided with plated-through holes, and all three are silk-screened to show component values and orientation. Except for three resistors, all resistors are 5% tolerance or better. All hardware lines up exactly so that bolting together is a breeze.

There is very little in the way of tedious point-to-point wiring with this kit. The DMM uses a factory-prepared cable harness and switches that mount directly on the input circuit board. This reduces considerably the time required to assemble the kit and virtually eliminates the wiring errors that often crop up when

using point-to-point wiring in a complex kit.

During assembly, we ran into one minor snag. We could not obtain the proper display indication on the highest resistance range during calibration. However, when we changed one component (supplied by Heath), everything worked out fine. All told, it took us approximately 17 hours to assemble and calibrate the DMM.

**User Comment.** We calibrated the DMM using both its built-in references and laboratory references. Using the built-in references, the instrument's accuracy on all ranges and functions equalled or bettered the published specifications. When we used laboratory references, the accuracy we obtained was well within the published specifications. Needless to say, this DMM provides greater accuracy than needed for less than laboratory-grade testing.

There are several things about this DMM that appealed to us. First off, it is very easy to operate. The range/function switch is large and easy to handle and its position labelling is clear and unambiguous. Pushbutton function selection is convenient. And the large gas-discharge displays are easy to read from

any angle, up close, and at a distance. Even the test cable plugs have built-in convenience. When they are plugged into the front panel, the plugs still allow another instrument, such as an oscilloscope, to be plugged into them.

Though the Model IM-2202 is not as compact as some take-along battery-powered field-service DMM's, its larger size and weight offer the advantage of higher accuracy than usual. The intermediate size of the instrument also assures that it will not get lost on a crowded workbench or accidentally brushed off the bench onto a hard floor.

In both test-bench and field-service environments, the DMM acquitted itself admirably. After having used it for several months under all kinds of servicing conditions, we checked out its calibration. There was no significant change, and in most cases no detectable change.

The Model IM-2202 is a good-looking instrument that should fill the needs of most professionals and amateurs. It is also very reasonably priced for a highly accurate instrument that can be operated on both ac and dc power and comes standard with nickel-cadmium cells and recharging circuitry.

CIRCLE NO 104 ON FREE INFORMATION CARD

## SHARP MODEL CB-800A CB MOBILE AM TRANSCEIVER

*23-channel digital LED-display rig with excellent overload characteristics.*

**W**ITH new 40-channel CB rigs moving into the market place, this probably represents the last 23-channel mobile CB unit we will test. Nonetheless, 23-channel CB transceivers represent good value for the money; in some cases, unbelievable bargains. And the manufacturer of the CB transceiver examined here advises that this 23-channel unit will remain in its product line for a while.

The Model CB-800A AM CB transceiver from Sharp uses digital frequency synthesis and features a LED numeric display to indicate the channel in use. As a special feature, when the transceiver is set to Channel 9, the display flashes to tell the user that this emergency channel is in use. The transceiver has an unusually low price of only \$149.95 to provide these latest technical features.

The usual lineup of controls and features are offered by the transceiver. These include: volume and variable

squelch controls, S/r-f meter, switchable automatic noise limiter, Delta tune, PA operation, external-speaker jack, detachable dynamic microphone, full legal power output, TVI traps, 10.8-to-15.6-volt dc, negative- or positive-ground power requirements, voltage regulation, line filtering, and reverse-polarity protection.

The mobile transceiver measures 7 $\frac{1}{8}$ "D  $\times$  5 $\frac{3}{4}$ "W  $\times$  2 $\frac{1}{4}$ "H (20  $\times$  14.6  $\times$  5.7 cm).


**General Description.** The double-conversion receiver has i-f's located at 11.275 MHz and 455 kHz. A diode-protected r-f stage and two mixer stages are arranged in common-emitter configurations. A ceramic filter in the emitter circuit of the second mixer, plus two cascaded ceramic filters at the output of the mixer provide the 455-kHz selectivity. The i-f section, detector, second-conversion oscillator, and an agc amplifier for

the i-f strip are incorporated into a single IC chip. Two outboard transistors provide another amplified agc loop for the r-f and first mixer stages and the squelch section. A series-gate anl following the detector drives an audio amplifier stage. The audio stage, in turn, drives an IC that contains the remainder of the audio section, including the output amplifier.


The digital frequency synthesis system employs a phase-locked loop (PLL). A single IC includes a 10.240-MHz crystal oscillator and a network that divides by 1024 to furnish the 10-kHz standard reference signal. A FET voltage-controlled oscillator (vco) that operates in the 38.240-to-38.530-MHz range provides the heterodyning signal to produce the 11.275-MHz i-f at the first mixer. The comparison reference from the vco is obtained by mixing the output from the vco with the 36-960-MHz crystal-controlled signal to produce difference frequencies in the range of 1.280 to 1.570
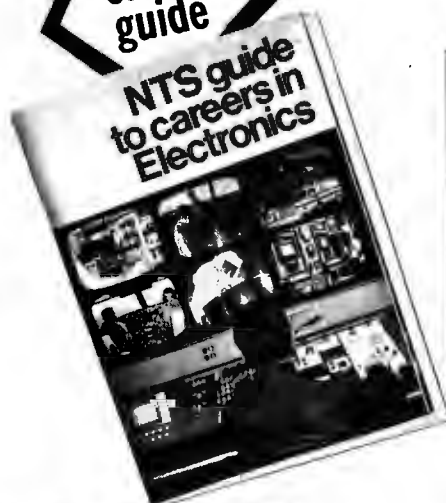
# The better the training the better you'll


Send for  
**FREE**  
illustrated  
career  
guide



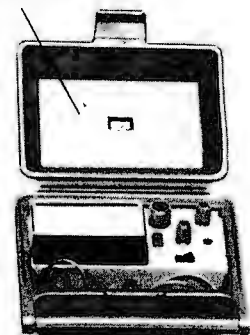COMPU-TRAINER  
IN-CIRCUIT TRANSISTOR TESTER  
TROUBLESHOOTER  
VOM



SOLID-STATE  
OSCILLOSCOPE

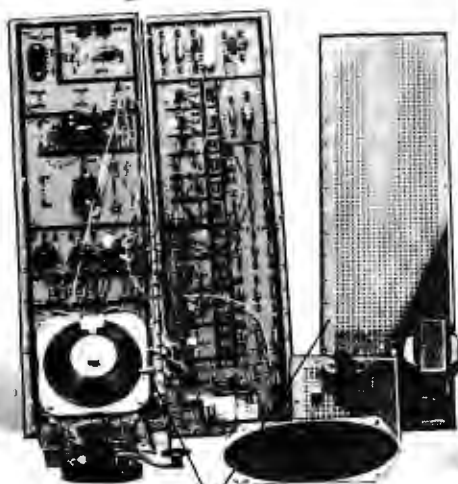

ELECTRO-LAB



(Simulated TV Reception)

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath GR-2001 computerized color TV (25" diagonal)** with varactor diode tuning and digital read-out channel selection; (optional programming capability and digital clock avail.).

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

**Choose from 12 NTS courses** covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

**Compare our training; compare our lower tuition.** We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

# and the equipment be equipped.

COMPARE OUR  
KITS AND LESSONS.  
COMPARE OUR  
TUITION.



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

**NO OBLIGATION. NO SALESMAN WILL CALL**

**APPROVED FOR VETERAN TRAINING**

Get facts on new 2-year extension

**NATIONAL TECHNICAL SCHOOLS**

TECHNICAL-TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools  
4000 So. Figueroa St., Los Angeles, Calif. 90037

## NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa St., Los Angeles, Calif. 90037

Dept. 205-027

Please send FREE Color Catalog and Sample Lesson.  
NO OBLIGATION. NO SALESMAN WILL CALL.

- |   |  |
|---|--|
| <input type="checkbox"/> Color TV Servicing           | <input type="checkbox"/> Electronics Technology      |
| <input type="checkbox"/> B & W TV and Radio Servicing | <input type="checkbox"/> Computer Electronics        |
| <input type="checkbox"/> Electronic Communications    | <input type="checkbox"/> Basic Electronics           |
| <input type="checkbox"/> FCC License Course           | <input type="checkbox"/> Audio Electronics Servicing |


NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_ APT # \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

Please fill in Zip Code for fast service \_\_\_\_\_

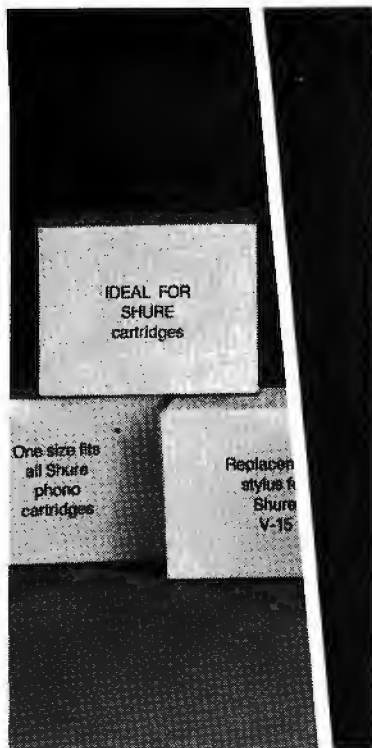
- ☐ Check if interested in G.I. Bill information.  
☐ Check if interested ONLY in classroom training in Los Angeles.


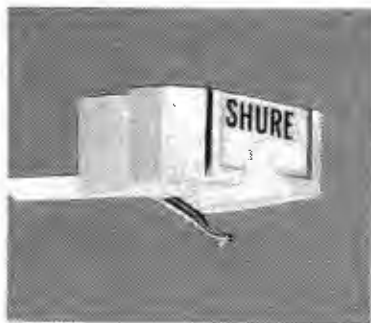
## Needle in the hi-fi haystack

*Even we were astounded at how difficult it is to find an adequate other-brand replacement stylus for a Shure cartridge. We recently purchased 241 random styli that were not manufactured by Shure, but were being sold as replacements for our cartridges. Only ONE of these 241 styli could pass the same basic production line performance tests that ALL genuine Shure styli must pass. But don't simply accept what we say here. Send for the documented test results we've compiled for you in data booklet # AL548. Insist on a genuine Shure stylus so that your cartridge will retain its original performance capability—and at the same time protect your records.*

Shure Brothers Inc.  
222 Hartrey Ave., Evanston, IL 60204  
In Canada: A.C. Simmonds & Sons Limited



Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

MHz. The difference frequencies are reduced to the 10-kHz vco comparison signal through an IC that can be programmed to divide by a number between 128 and 157. The two reference signals are applied to an IC phase comparator that properly tunes the vco and PLL according to the desired channel selected by the channel-selector switch. The second-conversion crystal oscillator operates at a frequency of 11.730 MHz.

The outputs of the vco and an 11.275-MHz crystal oscillator are combined in a mixer in the transmitter. Spurious responses are minimized by bandpass filter circuits. The rest of the transmitter consists of a buffer amplifier and driver and power amplifiers. The output of the power amplifier goes through a dual-Pi filter for matching to 50-ohm loads. TVI traps tuned to 54 and 51 MHz minimize second- and third-harmonic radiation. As is usually the case, speech amplification and collector-modulation of the driver and power amplifier stages in the transmitter are obtained from the receiver's audio-amplifier section. Automatic modulation control (amc) is included here. Antenna and other circuit transfers are accomplished with a relay.

The channel LED display is activated through the selector switch and a diode-switching array. Flashing of the display on Channel 9 is controlled by a multi-vibrator.

**Measurements.** The sensitivity of the receiver measured 0.5  $\mu\text{V}$  (rated 0.7  $\mu\text{V}$ ) for 10 dB (S + N)/N with 1000 Hz at 30% modulation. The overall audio response at 6 dB down was nominally 500 to 2625 Hz. The maximum available sine-wave power output was 2 watts at 2.5% THD with a 1000-Hz tone and an 8-ohm load. On PA, the output measured 2.5 watts.

Primary image rejection for signals near 49.6 MHz was greater than 80 dB, while secondary-image rejection for signals 910 kHz lower than the CB signal was 64 dB. I-f signal rejection was 60 to 64 dB, depending on the channel in use. Additional unwanted signals were 56 dB down for frequencies approximately 200 kHz below the CB signal. Other unwanted signals were a minimum of 60 dB down. Adjacent-channel rejection at 1 dB desensitization was 55 dB on both sides of each channel.

The agc held the audio output change to within 7 dB with an 80-dB input-signal change at 1 to 10,000  $\mu\text{V}$ . The meter indicated S9 with a nominal 3.5- $\mu\text{V}$  signal. The squelch threshold range for normal output was 0.3 to 10,000  $\mu\text{V}$ .

Operating the transceiver at 13.8 volts dc, the transmitter's output measured 3.75 watts, depending on the channel in use. During modulation, amc compression began near 85% modulation and held to 15 dB compression beyond this point with close to 100% modulation at 4.5% THD. Adjacent-channel splatter was down 50 dB with a 1000-Hz test tone. With voice operation, the splatter held to at least 55 dB down. The overall 6-dB down response was nominally 275 to 4500 Hz. The transmitter's frequency tolerance was within 5 Hz of +105 Hz on any channel.

**User Comment.** The transceiver is neatly styled, with a black case and panel and satinized silver-colored trim. The chrome-finished control knobs add a nice accent. Small lever switches handle the anl and Delta-tune functions. (Delta tune shifts the receiver's frequency a fixed amount of about  $\pm 1000$  Hz). The VOLUME and SQUELCH controls are rotary potentiometers, the positions of which can be readily observed and felt.


The LED display and S/r-f meter are located behind an oblong window. However, the meter is very small and can be difficult to read under some conditions. When the transceiver is switched to PA operation, the letters "PA" appear in the LED display. (Under very high ambient-light conditions, all the segments of the LED's sometimes reflect light, which can obscure the channel numerals.)

The anl system was highly effective on very short and rapid noise spikes, although its performance was not as good on slow repetitive and broader pulses. Nevertheless, the overall performance in a noisy vehicle was good. Due to an elaborate line-filter setup, we were not bothered with vehicle noises induced in the 12-volt supply line. The noise suppression was superior to that used in other mobile transceivers.

We were particularly impressed by the overload characteristics of the receiver, which by measurement did not exhibit distortion with signal inputs of 100,000  $\mu\text{V}$ . Furthermore, no distortion or blocking effects were audibly noted from a CB transmitter located 30' (9.1 m) removed from the transceiver's antenna.

Another plus for this transceiver is that its receiver audio response falls off fairly rapidly below 1000 Hz. This results in a somewhat high-pitched sound that lacks boominess. It gives the advantage of better-than-usual intelligibility from a bottom-facing speaker in mobile installations.

CIRCLE NO. 105 ON FREE INFORMATION CARD

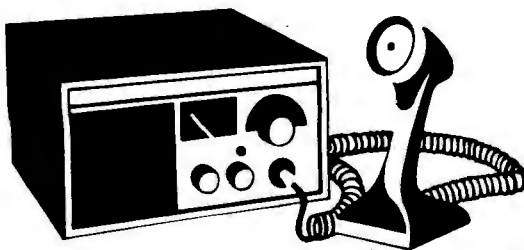

# CB Scene

By Ray Newhall, KWI6010

## PURAC—A VOICE FOR CB'ERS

**T**HE THIRD quarterly general meeting of the Personal Use Radio Advisory Committee (PURAC) to the FCC was held in Norfolk, Virginia, on October 28. The FCC hosted the gathering in a theater near their Field Operations branch offices. More than 100 representatives of CB industry, clubs, and leading publications; law enforcement agencies; the broadcasting industry; insurance companies; hams, and individual CB'ers were there to discuss their common problems, to hear the FCC's problems and to advise the FCC on the future course of personal-use radio communications.

In the past, FCC communications with radio users have always consisted of their "legal eagles" talking with other "legal eagles," and they understood each other. Now with such extensive use of CB by the general public, the FCC has found that it cannot effectively communicate with the public so it sent out a call for help from the CB industry and the CB'ers themselves. Public response at the first three meetings was better than the FCC had hoped. PURAC has become the vehicle by which any interested CB'er can work actively on a task group of his choice to help make CB a more viable, useful means of personal communications. He can talk with the FCC "wheels" face-to-face and be heard.

PURAC, chaired by John Johnson of the FCC, is organized into ten "task areas," each headed by a "Task Coordinator". An FCC representative has also been assigned to work actively in each of the task areas. The task/study areas are as follows:

1. *Operator Training Programs:* Recommend syllabus, methods and training programs for CB operators. Task Coordinator: Dave Garner

2. *Technical Standards:* Recommend material for, and organization of, the Technical Regulations sub-part of Part 95. Task Coordinator: Lee Bergren

3. *Part 95 Readability:* Recommend reorganization and rewrite of Part 95 to improve readability. Coordinator: Randy Knowles

4. *Disseminating Information:* Recommend systems for distributing information on CB topics to the CB public in the fastest, most economical, most accurate manner. Coordinator: Bill Bradford

5. *User Rule Compliance:* Recommend approaches and methods for improving user rule compliance. Coordinator: Stuart Lipoff

6. *Electromagnetic Compatibility:* Recommend susceptibility requirements and interference limits necessary to achieve electromagnetic compatibility between CB units and other electronic devices. Coordinator: John Sodolski

7. *Public Safety Uses of Personal Radio:* Recommend improvements in Part 95 to enhance the contributions of CB to public safety. Coordinator: Nathan Maryn

8. *Equipment Theft:* Recommend methods for reducing the number of CB sets stolen from users. Coordinator: Manny Hoffman

9. *Local Interference Problems:* Recommend remedial solutions for on-going complaints of interference created by CB transceivers. Coordinator: Stu Meyer

10. *Personal Use Radio Communication Needs:* Advise on current and future two-way radio communication needs of the general public, and recommend segments of the radio spectrum to meet those needs. Coordinator: Ted Andros

Each task/study group is staffed by volunteers who have offered their time to contribute to one or more sub-committee tasks. POPULAR ELECTRONICS has pledged to work actively on many Task Groups. This columnist will be pleased to assist any reader who wants to take part in PURAC activities by putting him in touch with the appropriate Task Coordinator. We will also pass-on well-considered, constructive suggestions from our readers. The next general meeting of PURAC will be held in Washington, D.C., on January 27, 1977.

**PURAC Progress Report.** It is far too early to expect major results from PURAC, since the first two general meetings were concerned primarily with organization, ground rules, and the subjects to which PURAC should address itself. Also, major shifts in attitude and performance in a bureaucracy such as the FCC are slow in coming, and rules-

making procedures take even longer. None-the-less, some changes have already taken place as a result of PURAC:

- Engraved serial numbers will be required on all CB rigs manufactured since January 1, 1977. This does not itself solve the theft problem, but it is a step in the right direction.

- This writer had the opportunity to preview a TV tape on CB and its problems produced by a group of TV stations as a means of educating the public about CB and its relation to the TVI problem.

- By the time you read this, there will be a newly reorganized edition of Part 95 available. It separates the technical requirements from operating regulations, so that all information a CB'er needs to know is in one spot. (The new issue does not yet reflect all rules changes.) Although this first revision is still in "legalese," Task Group 3 is currently rewriting it in English for a future edition. These new editions do not obsolete the editions in circulation in January, 1977, because they do not represent substantial changes in content.

The FCC has now issued more than 12 million CB licenses, and there are more than 18 million CB transmitters in use, according to FCC estimates. The FCC recently conducted test samplings in a number of areas across the nation and determined that fewer than 10% of the CB'ers are now operating without licenses, but that still represents well over a million operators who would rather risk a \$10,000 fine than pay 80¢ per year for the right to operate legally.

Following the 40-channel announcement in July, license applications fell-off about 8% to 10% for each of the next three months, and were down to a level of about 300,000 per month by October. FCC expects them to increase again shortly after the beginning of 1977.

Incidentally, the average turn-around time for issuing licenses during the period from July through September was under 17 days, and the FCC now believes it can continue to issue them in that time frame even though the demand may increase. There was one instance late last spring when a whole block of licenses were erroneously sent to the wrong Zip Codes and were lost by the Postal Service. It was necessary for them to be reissued and remailed.

Nearly 10% of all applications for Class D licenses must be returned to the applicants. The FCC urges CB'ers to read Form 505 carefully. Each month, 20,000 applications are returned because the wrong fee was enclosed. (The license fee of \$4.00 for a Class D license

# HAM CB SWL

they come through **LOUD AND CLEAR** in the all-new **1977 COMMUNICATIONS HANDBOOK**

Here is everything you want to know need to know about Citizens' Band, Amateur Radio, Shortwave Listening.



DON'T TURN A DIAL. In fact don't even buy a dial or anything else until you've checked out the 1977 Communications Handbook. Whatever your radio specialty — whether you're an old hand or just getting started — this vital "how-to" guide will help you get greater value, greater enjoyment out of every minute you spend with your equipment.

The all-new 1977 **COMMUNICATIONS HANDBOOK** is scheduled to go on sale nationally March, 1977

**YOU CAN RESERVE YOUR COPY NOW AT THE SPECIAL PRE-PUBLICATION PRICE OF ONLY \$1.50 POSTPAID.**

Regular newsstand price is \$1.95; mail order \$2.50.

So to make sure you come through "Loud and Clear" in 1977...

**RESERVE YOUR COPY NOW AND SAVE WITH THIS SPECIAL PRE-PUBLICATION OFFER AVAILABLE TO READERS OF POPULAR ELECTRONICS MAGAZINE ONLY.**

## PRE-PUBLICATION RESERVATION FORM

Communications Handbook PE-277  
Consumer Service Division  
595 Broadway, New York, N.Y. 10012

Enclosed is \$1.50. Please reserve my copy of the 1977 Communications Handbook to be mailed to me when published. (Residents of Cal., Col., Fla., Ill., Mich., Mo., N.Y. State, D.C. and Tex. add applicable sales tax.) OUTSIDE U.S.A. \$2.

Print Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

has been in effect since March 1976, and the license is valid for a five-year period.) Each month, 10,000 license applications are returned because the applicant is too young. An applicant *must* be 18 years of age to be granted a Class D CB license, though the restriction that the applicant must be a U.S. citizen has been removed.

Much of the business of the third general meeting of PURAC concerned the growing problems of CB-related electromagnetic interference. In addition to the obvious increase in noise, skip, and adjacent channel interference on CB itself, of more concern is the staggering increase in CB-caused TVI (television interference) and interference with solid-state audio equipment.

The leading causes of TVI are:

1. Harmonic radiation from CB units.
2. Use of illegal linears.
3. TV and audio equipment deficiencies.
4. Attempted "fringe" reception by the TV viewer.

We are not too concerned with the last two causes listed because CB is not at fault (more about this later). However, we *must* be concerned with the first two because they represent about one third of all TVI problems and they are the fault of CB users and equipment. The new rules make it the *legal* responsibility of the CB'er to correct this type of interference wherever a complaint has been filed.

Harmonic radiations occur at multiples of the operating or fundamental frequency. For CB, these would occur at 54 MHz (TV Channel 2), 81 MHz (TV Channel 5), 108 MHz, etc. The new regulations have attempted to reduce harmonic radiations generated by rigs built after January 1, 1977 by requiring that harmonics be suppressed at least 60 dB down from the power output of the fundamental frequency (the old specification required about 49 dB suppression). Thus new transceivers will be limited to 4 microwatts of harmonic output. The TV manufacturers wanted CB harmonics suppressed by 100 dB, but FCC set these comments aside with the warning that CB manufacturers had better prepare now for stiffer limitations in the future.

How can the CB'er tell whether TVI is caused by his rig or the TV receiver? It is very simple once the CB'er understands harmonic radiation. If the TV exhibits TVI only on channel 2 or channel 5 when the transmitter is keyed, it is probably the fault of the CB rig. If TVI shows up on other channels as well, the fault is prob-

ably that the TV receiver cannot filter out strong signals at 27 MHz.

However, there is seldom a single cause of TVI. The FCC warns that, in most cases of bad interference, there are usually at least two system malfunctions before TVI becomes a problem. If the cause can be traced to the CB rig, then the CB'er *must* either correct it or cease operations. If the TV receiver is at fault, most TV manufacturers will supply corrective information and free parts, if necessary. Even though the fault is in the TV, it is in the interest of the CB'er to work with his neighbor to help him solve the problem.

Actually, harmonic radiation problems do not always originate in the CB transmitter, but they may also be introduced by any device which is inserted into the antenna lead line, such as an SWR meter or a coaxial switch. A linear amplifier in the line, even when *turned-off*, may increase the harmonic radiation by 9 dB or more. The increase in harmonic radiation when the linear is turned on may be much more than that.

On the point of linears, the FCC has determined that nearly all TV receivers within 500 feet of an operating linear will experience serious TVI, and nearly half the TV sets within a quarter mile will be affected. These figures are for linears which operate properly. Those which are not properly matched can cause even greater problems, but they are easily detected by FCC monitoring equipment. The FCC is aware that some stations are operating linears. Accordingly, the FCC has pledged to get them off the air, and if the illegal operators do not get rid of them voluntarily, it is prepared to seize their equipment and take the outlaws to court.

**Consumer Electronics Legislation.** At the present time, the FCC does not have any control power to set electromagnetic immunity standards for TV or other electronic communication or home entertainment devices which are not intended to transmit r-f emissions.

The Communications Reform Act of 1976, the so-called "Bell Bill" because it was largely written by telephone company lawyers and strengthened the monopolistic position of the communications utility companies, ran out of time when Congress adjourned. But it is bound to be revived by the 95th Congress. Extensive hearings are planned by both House and Senate committees. We believe that any such reform review should consider *all* our country's communications problems. ◇



# Amateur Radio

By Herbert S. Brier

## SPEECH PROCESSORS

**Y**OU HAVE probably noticed that speech processors are being used more and more by radio amateurs. This recent trend prompted me to procure a logarithmic speech processor and see exactly what such a device can do to an SSB signal. My last involvement with speech processors was in the good-old AM days, when a good processor made a moderate improvement in the readability of weak voice signals. When the signals were subject to selective fading, processed signals often sounded louder but were actually *less* readable than when the processor was turned off. Consequently, our expectations for the new processor were not of the highest. However, after using it on the air for many months, we are convinced that the new generation of speech processors actually does what the designers claim—improve SSB signal readability up to six dB when conditions are worst. On the other hand, when signals are loud and clear, the majority of operators—especially locals—prefer the sound of unprocessed signals.

Historically, from the beginning of telephone and radiotelephone communications, engineers have worked to improve the efficiency of voice circuits. In ordinary conversation, the human voice can occupy a nominal bandwidth of 56 to 5700 Hz and a dynamic range up to 85 dB. Because the bandwidth of any signal is directly related to the highest frequency transmitted, extensive tests were conducted to determine the highest voice frequencies that had to be transmitted to preserve the readability of the reproduced speech. This was found to be nominally 3000 Hz. It was also found that frequencies below 500 Hz or so could be attenuated without reducing readability appreciably, although eliminating too many of them made the speech sound tinny.

As a result of such studies, international and domestic telecommunications regulations specify a 3000-Hz bandwidth for voice circuits. Many users prefer to transmit frequencies between 400 and 2500 Hz; others prefer 400 to 2800

Hz. Tailoring the modulating frequencies transmitted by a SSB transmitter is simple. Select the desired filter bandwidth—2100 Hz, for example. Then displace the (suppressed) carrier frequency by an amount equal to say, the lowest modulating frequency above the high-frequency knee of the filter selectivity curve (for lower sideband transmissions). Shift the carrier frequency by the same amount *below* the low-frequency knee for upper sideband transmissions.

**Amplitude Variations.** It has been found that voice frequencies logarithmically centered around 100 Hz contain most of the speech energy and vary widely in amplitude but contribute little to the readability of the speech. In contrast, the frequencies between 300 and 3000 Hz do not contain much energy and do not vary much in amplitude but contain most of the spoken intelligence. Viewing the output signal of a voice-modulated SSB transmitter on an oscilloscope reveals that the lower voice components produce the highest modulation peaks, with the high-frequency peaks about 12 dB lower. Early speech processors increased the transmitter's speech amplifier gain to bring the amplitude of the higher frequency components up to the desired level. Those processors also chopped off the amplitude of all voice peaks to the threshold voltage of a stage. Feeding the clipped signals through a low-pass filter with a cutoff frequency of 3000 Hz kept the high-frequency harmonics generated by the clipper from modulating the transmitter. Unfortunately, the low-order harmonics of the clipped low frequencies still remained in the voice passband, making the processed speech sound "different" but barely more readable than unprocessed speech.

**Logarithmic Speech Processors.** The wide availability of versatile IC amplifiers has given new life to transmitter speech processors. In the logarithmic speech processor described in *QST* for August 1974, the microphone signal is

first amplified 20 to 30 dB more than it would otherwise be. It is then passed through a high-pass filter with a low-frequency cutoff of approximately 50 Hz to remove most of the low-frequency, variable amplitude component. The signal is next fed to a logarithmic amplifier and clipper. The signal from the clipper—now a more-or-less constant-amplitude, 300-to-3000-Hz signal—goes through a low-pass filter with a 2950-Hz cut-off frequency to remove the high-frequency distortion products from the signal before it is applied to the microphone connector of the transmitter.

Another more-elaborate logarithmic speech processor (described in *QST* for March 1976) full-wave rectifies the audio signal before feeding it to the logarithmic amplifier and clipper. The output signal drives an exponential amplifier whose output modulates the transmitter. This processor also uses an input high-pass filter and an output low-pass filter.

## Operating a Speech Processor.

The first step in getting good results from a speech processor is to adjust the transmitter and its microphone gain control so that the transmitter r-f output peaks are not being clipped before the speech processor is placed in the line. Tune up the transmitter into a dummy load and turn the microphone gain control so that the maximum output peaks displayed on an oscilloscope just start to decrease in height. Next, turn on the processor with the microphone connected to the processor input and its output connected to the transmitter microphone jack. With the processor input and output controls full on, talk into the microphone while backing down the output control until the maximum pattern height on the oscilloscope is the same as after the mike gain adjustment. The processor input gain control is adjusted to match propagation conditions. In general, the better conditions are, the less processing should be used. When signals are strong and interference is weak, some operators turn off their processors entirely.

One of the most annoying characteristics of some speech processors is the loud roar that replaces the operator's voice when he stops talking. This roar is usually most evident when transmissions are controlled with a push-to-talk switch (PTT) rather than by VOX. We discovered by experiment that VOX operation with a short delay to cut off the roar generated by a noisy blower eliminated the criticism of the signal elicited by PTT operation. ◇



Cabinets clockwise from top: CPU, Dual-cassette drive, Keyboard, 9" Monitor.

# Meet The Digital Group

If you are seriously considering the purchase of a microcomputer system for personal or business use...or just beginning to feel the first twinges of interest in a fascinating hobby...the Digital Group is a company you should get acquainted with.

For many months now, we've been feverishly (and rather quietly) at work on our unique, high-quality product—a microcomputer system designed from the inside out to be the most comprehensive, easy-to-use and adaptable system you'll find anywhere. And our reputation has been getting around *fast*. In fact, you may have already heard a little something about us from a friend. We've found our own best salesmen are our many satisfied customers.

There's a good reason. Simply, the Digital Group has a lot to offer: state-of-the-art designs, a totally complete systems philosophy, unexcelled quality, reasonable software, affordable prices and the promise that our products will not become rapidly obsolete, even in this fast-moving, high-technology field.

## The Advantages

Here are a few specific advantages of our product line:

- We offer interchangeable CPUs from different manufacturers (including the new "super chip"—the Z-80 from Zilog) which are interchangeable at the CPU card level. That way, your system won't become instantly obsolete with each new design breakthrough. The major portion of your investment in memory and I/O is protected.
- Digital Group systems are complete and fully featured, so there's no need to purchase bits and pieces from different manufacturers. We have everything you need, but almost any other equipment can be easily supported, too, thanks to the universal nature of our systems.
- Our systems are specifically designed to be easy to use. With our combination of TV, keyboard, and cassette recorder, you have a system that is quick, quiet, and inexpensive. To get going merely power on, load cassette and go!
- Design shortcuts have been avoided—all CPUs run at full maximum rated speed.
- All system components are available with our beautiful new custom cabinets. And every new product will maintain the same unmistakable Digital Group image.

## The Features

Digital Group Systems—CPUs currently being delivered: Z-80 by Zilog 8080A/9080A 6800 6500 by MOS Technology

All are completely interchangeable at the CPU card level. Standard features with all systems:

- Video-based operating system

- Video/Cassette Interface Card  
512 character upper & lower case video interface  
100 character/second audio cassette interface
- CPU Card  
2K RAM, Direct Memory Access (DMA)  
Vectored Interrupts (up to 128)  
256 byte 1702A bootstrap loader  
All buffering, CPU dependencies, and housekeeping circuitry
- Input/Output Card  
Four 8-bit parallel input ports  
Four 8-bit parallel output ports
- Motherboard

Prices for standard systems including the above features start at \$475 for Z-80, \$425 for 8080 or 6800, \$375 for 6500.

## More

Many options, peripherals, expansion capabilities and accessories are already available. They include rapid computer-controlled cassette drives for mass storage, memory, I/O, monitors, prom boards, multiple power supplies, prototyping cards and others. Software packages include BASICs, Assemblers, Disassemblers, Text Editors, games, ham radio applications, software training cassettes, system packages and more (even biorhythm).

## Sounds neat—now what?

Now that you know a little about who we are and what we're doing, we need to know more about you. In order for us to get more information to you, please take a few seconds and fill in our mailing list coupon. We think you'll be pleased with what you get back.

-----

the digital group


P.O. Box 6528  
Denver, Colorado 80206  
(303) 777-7133

OK, I'd like to get to know you guys better.  
Send me the whole package!

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_

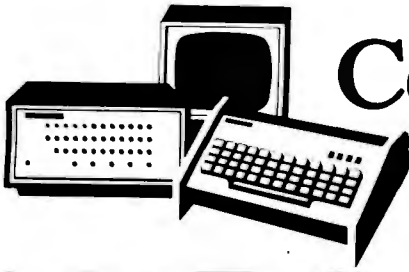

# Computer Bits

By Stephen B. Gray

## COMPUTER STORES

**T**HE FIRST hobby-computer store opened in Los Angeles in July 1975. Now, a year and a half later, there are well over 100 of them across the country. Why such a rapid rise? As one store owner observed, a computer store "provides the place, the people and the knowledge to help out the hobbyist." It provides the hobbyist with a place to look over different computers, to ask questions, and often the chance to try out a computer, hands-on. In this way, he can look before he leaps.

**A Typical Store.** At one time there were two basic types of stores. Both sold a variety of peripherals, but one sold only MITS Altair computers, while the other sold several other makes. The former type of store can concentrate on a single line of computers, and develop an expertise in the sales, operation and service of a minimum number of main-frame machines. Now, however, as different models pour into the marketplace, some stores that previously sold only the 8800b and 680b computers also carry others. A substantial number, though, still prefer to concentrate on the two Altair models, offering a host of peripherals to go with them.

If you walk into a typical computer store today, you'll find at least one operating computer connected to a Teletype or to a keyboard terminal and a TV monitor or receiver, or to a complete CRT terminal. Sometimes a peripheral or two are also on-line, such as a cassette-storage device, or a graphics terminal or printer. Other computers are on counters or in display cases, along with memory boards, Teletype paper and tape, extender boards, power supplies, TV monitors, interface boards, printers, terminals, breadboards, keyboards, etc. Not every store will have all these, but many do.

Test equipment is also on the shelves, including logic probes, logic monitors, perhaps a pulse generator, and maybe even a frequency counter. Some tools

may also be on display, such as for wire-wrapping, soldering and desoldering. There are computer stores that also carry basic tools such as pliers, screwdrivers, soldering irons, etc.

A good supply of parts is essential, since half of the hobby computers built from kits don't work when first turned on. Not all of that is caused by solder bridges and miswiring. So, to repair the damage, the hobbyist may need IC's, LED's, and IC sockets, which most stores carry, along with breadboarding hardware, hookup wire, etc.

**Books and Software.** Many stores devote a large amount of space to books. As one store manager put it, "We carry books about everything on computers and data processing except the social issues." That store has books on hardware design, digital techniques, flowcharting, even on multiple regression and telecommunications. They have programming texts on assembler,

BASIC, APL, FORTRAN, ALGOL, and several other languages. They also carry software books, offering assembly-language programs (such as the Scelbi series on the 8080 and 8008) and BASIC programs (including "101 BASIC Computer Games"). In addition to programs being offered as listings in these books, the store also has many programs on PROM memory chips, on paper tape, and on cassette.

Magazine racks are used by many stores to display up to half a dozen different hobby magazines. And there's always a bulletin board, with notices of meetings, "For Sale" ads for computer hardware, listings of computer courses, etc.

You may also find T-shirts, lettered with slogans such as "Does Not Compute," "Real Time Operator," or "Baud Rated."

**Chains.** Most of the stores are independently owned. There are several chains, one with over a dozen stores, mainly in California, another with half a dozen in the Northeast. Late last year, an industrial electronics distributor announced plans to establish computer display counters in their twelve U.S. branches, with "working models of five microprocessor kits, three non-assembled kits, plus four additional microprocessor chips not in kit form. Two complete developmental systems will be available. In addition, books, power supplies, tape readers, and accessories in kit form will be carried."

## COMING UP IN THE MARCH

### Popular Electronics®

#### SPECIAL FOCUS ON CB, including:

- The New 40-Channel CB Radios & FCC Rules and Regulations
- Crystal/Synthesized/PLL Frequency-Generation Methods
- Sunspots and Their Predicted Effect on Communications

**BUILD A DIGITAL  
BICYCLE SPEEDOMETER  
PROGRAMMING IDEAS FOR  
THE COSMAC "ELF"  
AUDIO AMPLIFIER OUTPUT STAGES**

# how often could you use an Xcelite® "99"?



**it's every  
tool you  
need 99%  
of the time...  
an Xcelite original!**

## it's a screwdriver




...for slotted, Phillips, Frearson, Bristol, clutch head, Scrulox® screws; in inch and metric size Allen hex and Allen hex ballpoint socket types; and Pozidriv® style.

## it's a nutdriver

...in inch and metric sizes, regular, stubby, and magnetic, for hex nuts, screws, and bolts.

## it's a reamer

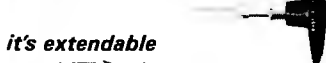

## it's extendable



...for greater reach and torque.

## 5 DIFFERENT HANDLE STYLES


...regular and Tee, with and without reversible ratchet; junior, and stubby; all with Xcelite's unique spring device for quick blade insertion and removal. All shockproof, breakproof (UL).

## 85 INTERCHANGEABLE BLADES

...all the popular types and sizes. All precision-made, genuine Xcelite quality. Fit all five handles.
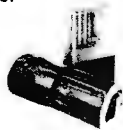
## IN SETS, KITS, OR PIECEMEAL

...roll-up service kits, compact, stand-up, plastic-cased sets; or individually as needed.



in stock at leading  
electronic distributors... nationwide

**Weller-Xcelite  
Electronics Division**



**The Cooper Group**

P. O. BOX 728,  
APEX, NORTH CAROLINA 27502

CIRCLE NO. 64 ON FREE INFORMATION CARD

The company's president says, "The industrial distributor has never really catered to the hobbyist, but always allowed cash sales because many engineers and buyers from industry bought small quantities for their personal use. With the advent of the microprocessor, a whole new market of "Computerists" has developed. These people are engineers, programmers, and technicians from industry who are learning, designing, and programming microprocessor systems at home. They want a place to browse, read, have hands-on practice, and see what they are buying."

**Repair Facilities.** Some computer stores offer repair services. One store in New York fixes an item free if you bought it there and if it's still within the warranty period. After that, the charge is \$10 to \$12 an hour. The alternative is to send your computer or pc board or peripheral to the manufacturer, and if the warranty has expired, you pay \$15 to \$22 an hour, plus shipping. The most common problems with computers built

board, or a memory board, or the rest of the computer, you can narrow it down by taking the two or three boards into a computer store that has a machine like yours in operation. They'll plug in your boards, one at a time, after first checking for shorts that might cause trouble, and you'll soon have a better idea of where the problem is. There's no charge for this informal checkout, unless you want the store to go further in localizing the problem. However, since there are usually several hobbyists in a computer store at almost any time of the day, especially during the lunch hour and after work, you might get some very useful advice from someone who had the same problem.

**Idea Exchange.** Because computer stores are often meeting places for computer "freaks," they are good places to go to listen in, if you're a beginner, and to join in the conversation, once you've learned the ropes. You can learn what others think of this or that computer or pc board or program, you can often find



*The Computer Mart (New York) typifies hobbyist stores around country.*

from kits are solder bridges and miswiring. If the kit has otherwise been put together correctly, and if the store has a good digital electronics technician, you might save time and money by having your computer, or board, or whatever, repaired right there. One store manager expects his repair business to increase as more and more people with little or no electronics knowledge or ability try to build a computer, so he's expanding his service department.

If you can't get your computer to work, and don't know if it's the fault of the CPU

out from the store manager what new products are about to become available, and you can often watch one of the store assistants checking out a new piece of equipment. You can also often watch other hobbyists using the store's computer to check out some new program or peripheral, and thus help you decide if it's something you want to get into.

In short, there's no better place than a good computer store to see what's available, to find out what's going to be on the market, to chat with others afflicted with computeritis, and to get help. ◇

# Unique full-function 8-digit wrist calculator... available only as a kit.

A wrist calculator is the ultimate in common-sense portable calculating power. Even a pocket calculator goes where your pocket goes—take your jacket off, and you're lost!


But a wrist-calculator is only worth having if it offers a genuinely comprehensive range of functions, with a full-size 8-digit display.

This one does. What's more, because it is a kit, supplied direct from the manufacturer, it costs only a very reasonable \$19.95. And for that, you get not only a high-calibre calculator, but the fascination of building it yourself.
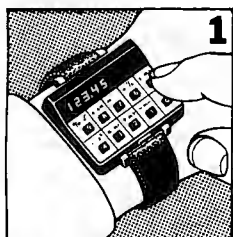
## How to make 10 keys do the work of 27


The Sinclair Instrument wrist calculator offers the full range of arithmetic functions. It uses normal algebraic logic ('enter it as you write it'). But in addition, it offers a % key; plus the convenience functions  $\sqrt{x}$ ,  $1/x$ ,  $x^2$ ; plus a full 5-function memory.

All this, from just 10 keys! The secret? An ingenious, simple three-position switch. It works like this.



1

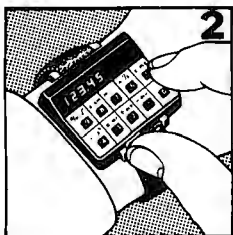1. The switch in its normal, central position. With the switch centered, numbers—which make up the vast majority of key-strokes—are tapped in the normal way.



2

2. Hold the switch to the left to use the functions to the left above the keys...

3. and hold it to the right to use the functions to the right above the keys.

The display uses 8 full-size red LED digits, and the calculator runs on readily-available hearing-aid batteries to give weeks of normal use.



3

## Assembling the Sinclair Instrument wrist calculator

The wrist calculator kit comes to you complete and ready for assembly. All you need is a reasonable degree of skill with a fine-point soldering iron. It takes about three hours to assemble. If anything goes wrong, Sinclair Instrument will replace any damaged components free: we want you to enjoy assembling the kit, and to end up with a valuable and useful calculator.

Actual Size

## Contents

Case and display window.

Strap.

Printed circuit board.

Switches.

Special direct-drive chip (no interface chip needed).

Display.

Batteries.

Everything is packaged in a neat plastic box, and accompanied by full instructions.

The only thing you need is a fine-point soldering iron.

All components are fully guaranteed, and any which are damaged during assembly will be replaced free.

The wrist-calculator kit is available only direct from Sinclair Instrument. Take advantage of this 10 day money-back offer.

Send the coupon today.

To: Sinclair Instruments Inc.  
6 Commercial Street  
Hicksville, NY 11801

PE-2

Please send me

\_\_\_\_\_ Sinclair wrist calculator kit(s) at \$19.95\$

Sales tax (NY residents) \_\_\_\_\_

Shipping & handling (\$2.50 per unit) \_\_\_\_\_

Enclosed is check/MO (payable to  
Sinclair Instruments Inc.)

TOTAL

\$

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

I understand that you will refund the purchase price of the kit in full if I return it in saleable condition within 10 days of receipt.

KIT  
ONLY  
\$19.95

Sinclair Instruments Inc.  
6 Commercial Street  
Hicksville, N.Y. 11801

Put Professional Knowledge and a  
**COLLEGE DEGREE**  
in your Electronics Career through  
**HOME STUDY**

**Earn Your DEGREE**

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of independent study.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then continues through the B.S.E.E. degree level. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write or phone (no collect calls please) and ask for BULLETIN E-77

**Grantham School of Engineering**  
2000 Stoner Ave., Los Angeles, CA 90025

• Telephone (213) 477-1901 •

**Worldwide Career Training thru Home Study**  
CIRCLE NO. 34 ON FREE INFORMATION CARD

**The POLY 88 Microcomputer System is here!**



POLY 88 is a complete, solid and trustworthy personal computer. No technological background is required to enjoy this versatile machine.

The POLY 88 is the invaluable tool for the home and office. With it, children can play or even develop their own mathematical and scientific games. Simple or Complex equations and projections can be programmed, stored and altered in the BASIC programming language. The POLY 88 starts at \$595 in kit form.

If you are in need of a quality tool, the POLY 88 is it.

**PolyMorphic Systems**

737 S. Kellogg, Goleta, CA 93017  
(805) 967-2351

CIRCLE NO. 51 ON FREE INFORMATION CARD

# NOAA WEATHER RADIO OPERATING LOCATIONS

The National Oceanic and Atmospheric Administration (NOAA) National Weather Service is the sole government-operated radio system for communicating attack or weather disaster warnings directly to the public—as well as regular weather reports. A vhf high-band receiver or scanning monitor is required to pick up these broadcasts.

Transmitter Site	Call Letters	Frequency (MHz)	Illinois		
			Chicago	KWO-39	162.55
<b>Alabama</b>			<b>Indiana</b>		
*Birmingham	KIH-54	162.55	Evansville	KIG-76	162.55
*Cheha	KIH-58	162.475	Indianapolis	KEC-74	162.55
*Dozier	KIH-59	162.55			
*Florence	KIH-57	162.475	<b>Iowa</b>		
Huntsville	KIH-20	162.40	Des Moines	KEC-75	162.55
*Louisville	KIH-56	162.475	<b>Kansas</b>		
Mobile	KEC-61	162.55	Wichita	KEC-59	162.55
*Montgomery	KIH-55	162.40	<b>Kentucky</b>		
*Tuscaloosa	KIH-60	162.40	Ashland	KIH-39	162.55
<b>Alaska</b>			Bowling Green	KIH-45	162.40
Anchorage	KEC-43	162.55	Covington	KIH-42	162.55
Seward	KEC-81	162.55	Hazard	KIH-40	162.475
<b>Arizona</b>			Lexington	KIH-41	162.40
Phoenix	KEC-94	162.55	Louisville	KIH-43	162.475
<b>California</b>			Mayfield	KIH-46	162.475
Coachella	KIG-78	162.40	Somerset	KIH-44	162.55
Crescent City, Calif./	KIH-37	162.55	<b>Louisiana</b>		
Brookings, Ore.			Baton Rouge	KHB-46	162.40
Eureka	KEC-82	162.40	Lake Charles	KHB-42	162.55
Los Angeles	KWO-37	162.55	Morgan City	KIH-23	162.475
Monterey	KEC-49	162.40	New Orleans	KHB-43	162.55
Point Arena	KIH-30	162.40	<b>Maine</b>		
Sacramento	KEC-57	162.40	Ellsworth	KEC-93	162.40
San Diego	KEC-62	162.40	Portland	KDO-95	162.55
San Francisco	KHB-49	162.55	<b>Maryland</b>		
San Luis Obispo	KIH-31	162.55	Baltimore	KEC-83	162.40
Santa Barbara	KIH-34	162.40	Salisbury	KEC-92	162.40
<b>Colorado</b>			<b>Massachusetts</b>		
Denver	KEC-76	162.55	Boston	KHB-35	162.40
<b>Connecticut</b>			Hyannis	KEC-73	162.55
New London	KHB-47	162.40	<b>Michigan</b>		
<b>Florida</b>			Alpena	KIG-83	162.55
Daytona Beach	KIH-26	162.40	Clio	KIH-29	162.40
Jacksonville	KHB-39	162.55	Detroit	KEC-63	162.55
Key West	KIH-25	162.40	Grand Rapids	KIG-63	162.55
Miami	KHB-34	162.55	Marquette	KIG-66	162.55
Panama City	KGG-67	162.55	Sault Sainte Marie	KIG-74	162.55
Pensacola	KEC-86	162.40	Traverse City	KIH-22	162.55
Tallahassee	KIH-24	162.40	<b>Minnesota</b>		
Tampa	KHB-32	162.55	Duluth	KIG-64	162.55
West Palm Beach	KEC-50	162.40	Minneapolis	KEC-65	162.55
<b>Georgia</b>			<b>Mississippi</b>		
Atlanta	KEC-80	162.55	*Ackerman	KIH-51	162.475
Savannah	KEC-85	162.40	*Booneville	KIH-53	162.55
<b>Hawaii</b>			*Bude	KIH-48	162.55
Hilo	KBA-99	162.55	Gulfport	KIH-21	162.40
Honolulu	KBA-99	162.55	*Iverness	KIH-50	162.55
Kokee	KBA-99	162.40	Jackson	KIH-38	162.40
Mt. Haleakala	KBA-99	162.40	*McHenry	KIH-47	162.475

*Oxford	KIH-52	162.40
*Rose Hill	KIH-49	162.55
*Beaufort	WXJ-23	162.475
*Columbia	WXJ-20	162.40
*Florence	WXJ-22	162.55
*Greenville	WXJ-21	162.55
<b>Missouri</b>		
Kansas City	KID-77	162.55
St. Joseph	KEC-77	162.40
St. Louis	KDO-89	162.55
<b>Nebraska</b>		
*Omaha	KIH-61	162.40
<b>New Jersey</b>		
Atlantic City	KHB-38	162.40
<b>New Mexico</b>		
Albuquerque	KIG-84	162.40
<b>New York</b>		
Buffalo	KEB-98	162.55
New York City	KWO-35	162.55
Rochester	KHA-53	162.40
<b>North Carolina</b>		
Cape Hatteras	KIG-77	162.55
New Bern	KEC-84	162.40
Wilmington	KHB-31	162.55
<b>Ohio</b>		
Akron	KDO-94	162.40
Cleveland	KHB-59	162.55
Columbus	KIG-86	162.55
Sandusky	KHB-97	162.40
<b>Oklahoma</b>		
Tulsa	KIH-27	162.55
<b>Oregon</b>		
Astoria	KEC-91	162.40
Coos Bay	KIH-32	162.40
Eugene	KEC-42	162.40
Newport	KIH-33	162.55
Portland	KIG-98	162.55
<b>Pennsylvania</b>		
Erie	KEC-58	162.40
Philadelphia	KIH-28	162.475
Pittsburgh	KIH-35	162.55
<b>South Carolina</b>		
Charleston	KHB-29	162.55
Myrtle Beach	KEC-95	162.40
<b>Tennessee</b>		
Nashville	KIG-79	162.55
<b>Texas</b>		
Brownsville	KHB-33	162.55
Corpus Christi	KHB-41	162.55
Dallas	KEC-56	162.40
Fort Worth	KEC-55	162.55
Galveston	KHB-40	162.55
Houston	KGG-68	162.40
Pharr	KHB-33	162.40
<b>Utah</b>		
Salt Lake City	KEC-78	162.55
<b>Vermont</b>		
Burlington	KIG-60	162.40
<b>Virginia</b>		
Manassas	KHB-36	162.55
Norfolk	KHB-37	162.55
<b>Washington</b>		
Neah Bay	KIH-36	162.55
Seattle	KHB-60	162.55
Yakima	KIG-75	162.55
<b>Wisconsin</b>		
Green Bay	KIG-65	162.55
Milwaukee	KEC-60	162.40

\*Stations expected to be in operation by end of 1977.

# FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



## MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER

**SEND TODAY!**

McIntosh Laboratory, Inc.  
East Side Station P.O. Box 96  
Binghamton, N.Y. 13904  
Dept. PE

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

If you are in a hurry for your catalog please send the coupon to McIntosh.  
For non rush service send the *Reader Service Card* to the magazine.

CIRCLE NO. 44 ON FREE INFORMATION CARD

★ **FREE!** ★

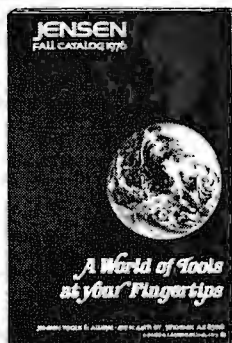

## NEW CATALOG OF HARD-TO-FIND PRECISION TOOLS

Jensen's new 128-page catalog is jam-packed with more than 2800 quality items. Your single source for hard-to-find precision tools used by electronic technicians, scientists, engineers, instrument mechanics, schools, laboratories and government agencies. This wanted catalog also contains Jensen's world-famous line of more than 40 tool kits. Plus 10 pages of useful "Tool Tips" to aid in tool selection. Send for your free copy today!




**JENSEN TOOLS and ALLOYS**  
4117 N. 44th Street, Phoenix, Arizona 85018

## DIXIE SAVE ON Brand Name Audio Components BY MAIL
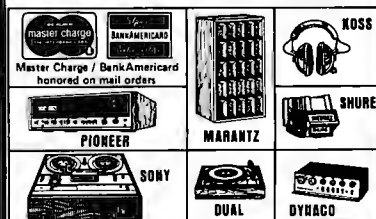
### Write Today for Our FREE Audio Catalog

DIXIE is one of the oldest and largest audio component mail order houses in the country. Our prices on brand name components are actually LOWER than "Discounters". See our new catalog or call us for a price quote. Everything shipped factory-sealed with full manufacturer's warranty.



### DIXIE HI-FIDELITY

PE-2

2040 Thalbro Street, Richmond, Va. 23230  
804-257-4241

Please rush me your FREE Audio Catalog and complete information. I understand there is no obligation.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE NO. 40 ON FREE INFORMATION CARD

# CB

where the  
ACTION'S  
at

Millions of 2-way CB radios are in use—millions of new ones are being sold annually to new CBers and for replacing old units—what a market for repair service. It's the biggest thing in electronics since color TV. There's only one thing wrong with CB growth—the lack of technicians capable of servicing CB radios. That's why many TV shops are expanding into CB and why new CB shops are opening up all over the country. Going CB servicing rates run from \$12 to \$24 per hour.

To get into CB radio servicing, full-time or part-time, you need test equipment, an FCC operator license and to learn how. To learn how, you can buy the **CB RADIO REPAIR COURSE** for cash, on a monthly payment plan, or charge the cost to your BankAmericard or Master Charge account.

To make it easy to study, this 70-lesson course employs the **PROGRAMMED** teaching technique and sticks to the target—CB radio. Study at your own pace as you receive the self-examining lessons. We can't guarantee that you will become a CB expert since that depends on you.

To get the facts about this course, write a letter or card or mail the coupon below today. No salesman will call.

**CB RADIO REPAIR  
COURSE, INC.**

Dept. PE-27

531 N. Ann Arbor  
Oklahoma City, OK 73127

Please send information about your Course to:

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE NO. 16 ON FREE INFORMATION CARD

## INTRODUCING



## The NEW PHLANGER KIT

Phil Spector's original "Big Hurt" sound is **EXACTLY** duplicated using PAIA's new constant time delay **PHLANGER**. This unit features a 1024 stage Charge Coupled Device analog shift register that exactly duplicates the effect of 2 tape recorders running out of synchronization.

Multiple user controls allow effects ranging from chorusing, voice doubling and reverb to full "Jet Plane" effects. Optional foot pedals provide hands free control of internal oscillator sweep speed or manual spectrum sweeping.

#1500.....PHLANGER Kit.....\$59.95  
(plus shipping for 4 lbs.)

**PAIA** — FREE CATALOG —  
ELECTRONICS DEPT. 2-P  
1020 W. WILSHIRE BLVD.  
OKLAHOMA CITY, OK 73116

CIRCLE NO. 48 ON FREE INFORMATION CARD

## Operation Assist

If you need information on outdated or rare equipment—a schematic, parts list, etc.—another reader might be able to assist. Simply send a postcard to Operation Assist. POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. For those who can help readers, please respond directly to them. They'll appreciate it. (Only those items regarding equipment not available from normal sources are published.)

**Blaupunkt** Verona type 20103 hi-fi radio. Any service material, especially dial cord restringing info. Lewyn F. Cutten, Jr., 102 W. Idaho St., Ellensburg, WA 98926.

**Hallicrafters** S-20-R shortwave receiver. Any information or owner's manual or photocopy. Bradley Richelson, 8 Randolph St., Plymouth, NH 03264.

**RCA** military receiver Model RAL-6, type CRV-46156. Serial 172, Rect. Power Unit # CRV-20131. Circa December 29, 1941. Covers 0.3 to 23 MHz. Schematic diagrams or any other info. George Tobin, New Gloucester, ME 04260.

**Superior Instruments Co.** Model TV-11 Tube Tester, Model 76 CR bridge and signal tracer, Model 77 VTVM. Instruction manuals and schematics. John Schreyer, W2KQV, 610 Bay 25 St., Far Rockaway, NY 11691.

**Philco-Tropic** Model 39-750. Schematic and/or service manual and parts source. Irving Leiboff, 667 E. 34 St., Brooklyn, NY 11203.

**Hammarlund** Model SP-600J receiver. Alignment information. W. Harwood, Box 563, Hudson Hope, BC, Canada V1C 1V0.

**Paco** Model C-20 Resis-Capacity Ratio Bridge. Instruction manual and schematic. Jose Varas, 515 4th St., Union City, NJ 07087.

**Realistic** Model 105 Tube Tester. Schematic and/or operations manual. Dr. Ali Allmaker, Woodcock Rd., Williamstown, MA 01267.

**Jetronic** Model AN-USM-81 oscilloscope. Need schematic and instruction manual. Ben Goble, Rockmont College, 8801 W. Alameda Ave., Lakewood, CO 80226.

**Radson** Model RT-70A radio telephone. Operation manual and wiring diagram. John K. Jakvis, DR 520, Schertz, TX 78154.

**Panoramic** Model LP-1 sonic analyzer. Need schematic, manual or source of information. Gregory A. Marks, 1737 Sanford, Ann Arbor, MI 48103.

**De Vry** 5" oscilloscope and transistor voltmeter. Construction manual or schematics needed. Paul Etchason, 406 W. Monroe, Kokomo, IN 46901.

**Arkay** FL-10 amplifier. Need service or operating manual and schematic. Edwin L. Dews, 703 Tammy, San Antonio, TX 78216.

**Friden** Model 132 electronic calculator. Schematic and/or service manual. Steven Eubanks, 8833 Westlawn Blvd., Olmsted Falls, OH 44138.

**Kaar** Model TR 327 Citizens Band radio. Schematic and alignment data. M. W. Murphy, Rt. 2 Box 554, Hayden Lake, ID 83835.

**RCA** Model 816K superheterodyne receiver. Need any available information. Jim Burrell, Rte. 2, Sallis, MS 39160.

**Bendix** RT-221AE-28 aircraft transceiver. Need service manual or schematic. George Kapsokavakis, 23 Kolotroni St., Kerkira, Greece.

**Knightkit** VTVM. Need schematic and calibration instructions. Don Bradley, P. O. Box 1213, Uallejo, CA 94590.

**Friden** Model 5023 computer. Operating and service manuals. John G. Peters, 1905 Victory Blvd., Unit 11, Glendale, CA 91201.

**Ultronic Systems** Videomaster 7700 computer terminal. Need service manual, modem requirements and any available data. Charles E. Gerhardt, 2134 Springhill, Dallas, TX 75228.

**Hallicrafter** Model S-40B receiver. Schematic or any available information. Ron J. Jones, 4871 Kingridge Dr., San Jose, CA 95124.

**Alexander** Model ALX CR900 battery-ac tape recorder. Need schematic and service manual. Mr. Bailey, 426 Slocum Ave., Neptune, NJ 07753.



## World's First Solid State Potentiometer

- No Moving Parts
- Nothing to Wear Out
- 100% Environment Proof

Available early 1977 along with revolutionary new non-capacitive Solid State Switch. So simple to adopt to your specific application . . . enables any engineer or amateur to design and fabricate space age instrument controls, rheostats, terminal keyboards, etc.

To reserve your kit now and for more information, call us or mail coupon today!

I'm interested! Please send me your **FREE BROCHURE** about the Kit.

Name \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

**CDT Semiconductors, Inc.**

1191 Chess Drive • Foster City, CA 94404  
(415) 574-2541

CIRCLE NO. 41 ON FREE INFORMATION CARD

## CONFUSED BY ELECTRONIC IGNITION CLAIMS

The  
**PROOF is in  
PERFORMANCE!**



Amazing MEGASPARK, the advanced-design Opto-Electronic Breakerless Ignition System, **FITS ANY CAR!** Replaces points and condenser — gives longer spark plug life. Increases performance, mileage and driving satisfaction while cutting fuel and maintenance costs dramatically. Learn the facts and don't settle for less than the best. Models from \$29.50 to \$64.50

The only unit that gives you all these features:

- LIFETIME WARRANTY
- DIFFERENTIAL AMPLIFIER CIRCUITRY
- FULL INTERNAL VOLTAGE REGULATION
- AUTOMATIC OVERCURRENT PROTECTION

Rush name and address for FREE information package including catalog and discount offer. Or call toll-free 24-hours 800-648-4711, Ext. 22.

**MEGASPARK™**  
by **ISI** Ignition Systems Inc.  
2547 8th Street  
Berkeley, CA 94710  
(415) 845-3584

CIRCLE NO. 36 ON FREE INFORMATION CARD

POPULAR ELECTRONICS

# WHY THE BOX?



Perfect listening.

All Stax Earspeakers™ connect through an adaptor box to your power amp, integrated amp or receiver, just like speakers. The box permits a vastly superior electrostatic principle to be used in Stax personal listening instruments.

Results? Incredible transients. Response curves that match the human ear perfectly. And no “flaking” of preamp circuitry that occurs with those non-box “headphones” that plug into the front panel.

Why the box? Because you can tell the difference.

## STAX: The inventor of the electrostatic earspeaker.

Distributed in the U.S. by:



**American Audioport**  
Columbia, MO 65201

## VOICE ACTIVATED SWITCH



Reg. **1.98**  
**99c**

Activates devices such as lights, tape recorders etc. Comes with 5' leads. 3 x 1". Operates on 4.5 VDC. Shpg. wt. 1/2 lb.

XM-556

## 8-TRACK Blank Tape



Reg. **69c**  
**39c**

40-Min. Blank tapes for quality reproduction. Just the right length for recording most LP's etc. Shpg. wt. 1/2 lb.

TA-907

## ELECTROLYTIC CAPACITOR KIT



REG. **\$5**  
**1.70**

Package of 50 axial and radial lead types. Low voltage, high capacity types. Shpg. wt. 1 lb.

CD-407

## SOLDERING IRON



REG. **3.29**  
**1.79**

Easy to use pencil-tip iron for those delicate soldering jobs. Reaches temperature to 250°. 9 1/4" long. 117 VAC. Shpg. wt. 1/4 lb.

TL-448

### HARDWARE AND COMPONENTS

1/4 RPM Timing Motor 115V. AC	MO-277	Reg. .89	.39
1 RPM Timing Motor 115V. AC	MO-289	Reg. .89	.39
3-6V. DC Hobby Motors Kit of 5	MO-333	Reg. 2.00	.59
2-Speed Motor 115V. AC	MO-336	Reg. 4.99	2.49
3600 RPM Motor 115V. AC	MO-361	Reg. 3.00	.99
4000 RPM Appliance Motor 115V. AC	MO-395	Reg. 2.98	.99
6V. Panel Lamp 1-Red 1-Green	PL-065	Reg. 1.79	.79
6V. 30 ma. Lamp W/Leads Pkg. 2	PL-270	Reg. .89	.59
6V. Mini-Screw Base Bulb. Pkg. 2	PL-271	Reg. .69	.59
12V. Bipin Mini Bulbs. Pkg. 2	PL-272	Reg. .89	.69
TV Chester Cord. Pkg. of 2	PL-273	Reg. 1.19	.59
Terminal Strips. Pkg. 40 Ass'd.	PL-274	Reg. 1.29	.59
258474 Output Transistor	MO-501	Reg. 1.30	.50
Fairchild 703 Type IC	TR-174	Reg. 3.79	1.19
Fairchild 717 Type IC	TR-293	Reg. .99	.39
IC Grab Bag. 10 Ass'd. Types	TR-294	Reg. .99	.39
Calculator IC Chip, Horotec 4202	TR-422	Reg. 1.19	.50
SCR Grab Bag. 25 Ass'd. Types	TR-424	Reg. 6.00	2.99
Cadmium Photo Cells. Pkg. of 2	TR-446	Reg. 2.69	.99
Motorola Amplifier IC. 8 Pin D.I.P.	TR-512	Reg. .90	.49
Aluminum Heat Sink 1 1/4 x 1/2 x 12	TR-513	Reg. 1.29	.59
12 Digit Calculator IC	XM-027	Reg. .49	.29
20 Key Calculator Keyboard	XM-330	Reg. 6.00	1.49
3" 7 Seg. L.E.D., Green, Comm. A	XM-339	Reg. 6.00	1.29
3" 7 Seg. L.E.D., Yellow, Comm. A	XM-341	Reg. 2.69	1.39
3" 7 Seg. L.E.D., Red, Comm. A	XM-342	Reg. 2.49	1.39
Sperry 9 Digit Display	XM-370	Reg. 2.49	1.19
3" 7 Seg. L.E.D., Red, Comm. K	XM-399	Reg. 1.49	.79
TI Calculator Keyboard, 20 Key	XM-414	Reg. 2.00	.99
16 Key Switch Pad, Less Keys	XM-523	Reg. 5.00	1.00
23 Key Switch Pad, Less Keys	XM-524	Reg. 1.29	.59
Calculator Keys. Pkg. of 20 Ass'd.	XM-525	Reg. 1.49	.69
455 KHz IF Transformer, Pair	XM-538	Reg. 1.50	.49
Toggle Switch Kit, Pkg. 3 Ass'd.	LI-083	Reg. 2.99	1.00
Mini Toggle Switch D.P.D.T. 3A.	SW-154	Reg. 2.19	1.49
See-Saw Rocker Switch D.P.D.T. 3A.	SW-406	Reg. 1.79	.99
Center-Off Mini Toggle S.P.D.T. 3A.	SW-409	Reg. 1.29	.69
Three Level Push Switch, 8A.	SW-423	Reg. 1.89	1.09
Mercury Switch, S.P.D.T. 5A.	SW-460	Reg. .29	.19
117 V. AC Relay, Mini, S.P.D.T. 2A	SW-586	Reg. 1.69	.49
Mini Rocker Switch, S.P.S.T. 1A.	SW-773	Reg. 2.00	.69
Leaf Switch, S.P.D.T. 5A. Pkg. 2	SW-814	Reg. 1.59	.69
Heavy Duty Toggle, 3 P.D.T. 10A.	SW-838	Reg. .90	.40
117 V. AC Solenoid, 1" Travel	SW-840	Reg. 2.00	.69
11 PC Slide Switch Kit	SW-846	Reg. 1.20	.59
6 & 12V. Trans., 117V. PRI. 5A SEC.	SW-850	Reg. 1.29	.79
12 & 10V. Trans., 117V. PRI. 2A SEC.	TF-048	Reg. 3.00	.90
6.3V. Trans., 117V. PRI. 1A. Sec.	TF-050	Reg. 1.79	.60
	TF-076	Reg. 2.00	1.29

## FREE CATALOG

**Olson electronics**

260 SO. FORGE ST.  
DEPT. IU, AKRON, OHIO 44327

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_ CITY STATE \_\_\_\_\_

ZIP \_\_\_\_\_ ☐ Send Olson Catalog

☐ Free PA Catalog ☐ Ship The Following:

How Many	Stock Number	Description	Price	Total

ENCLOSE POSTAGE AND SALES TAX

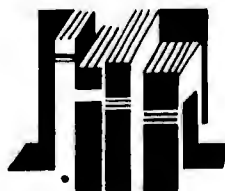

## Electronics Library

### DIGITAL EQUIPMENT SERVICING GUIDE

by Robert G. Middleton

This book was written for the technician whose troubleshooting experience has been limited to linear circuits such as in radio and TV circuits. A great many digital circuits are described here, along with information on how they work, what can go wrong with them, and how to detect and repair the problems. The seven chapters cover basic technology, gates, adders, subtractors, counters, display devices, digital logic in electronic instruments, and digital frequency display.

Published by Howard W. Sams & Co., 4300 W. 62nd St., Indianapolis, IN 46206. 104 pages. \$5.95 soft cover.

### THE RECORDING STUDIO HANDBOOK

by John M. Woram

Eighteen chapters cover the techniques of creative sound recording and just about every aspect of modern recording technology. The book is in eight sections, on basics (the decibel, sound), microphones and loudspeakers, signal-processing devices (equalizers, compressors, phasing, etc.), magnetic recording, noise and noise reduction, recording consoles, recording techniques (recording session, mixdown session), and appendices that include an extensive bibliography.

Published by Sagamore Publishing Co., 1120 Old Country Rd., Plainview, NY 11803. 496 pages. \$35.00 hard cover.

### THE CB OPERATOR'S KIT

by the Editors of Consumers Guide

Packed in a waterproof plastic pouch that fits conveniently into an auto's glove compartment, the kit includes a "CB Operator's Manual & Log," a road map of the US, 10-code card, and a CB decal with space for the operator's call number and handle. The book discusses how CB radio works, how to get your license, basic rules for operation, installing a CB radio in your car, theft prevention, using the channels, the many uses of CB, a coast-to-coast trip using CB, dictionary of CB jargon, and the FCC rules and regulations. A log section provides space to record calls made, while another section is for keeping track of "CB Buddies." The map shows, by state and highway, the channels most frequently used by truckers, emergency personnel and police, and on the back is a list of almost 100 "town handles," from Monkey Town to Cowboy City, plus a large 10-33 sign for display in emergencies.

Published by Simon and Schuster, 630 Fifth Ave., New York NY 10020. 192 pages. \$5.95 soft cover.

# SAVE!

MONEY • TIME • FREIGHT

QUALITY STEREO EQUIPMENT AT LOWEST PRICES.

YOUR REQUEST FOR QUOTATION RETURNED SAME DAY.

FACTORY SEALED CARTONS—GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:

A.D.C.	KLH
A.R.	SHURE
DYNACO	KOSS
SONY	FISHER

PIONEER  
AND MORE THAN 50 OTHERS  
BUY THE MODERN WAY  
BY MAIL—FROM

**illinois audio**

Department 217S

12 East Delaware

Chicago, Illinois 60611

312-664-0020

CIRCLE NO. 37 ON FREE INFORMATION CARD

## PLANNING TO MOVE?

Let us know 8 weeks in advance so that you won't miss a single issue of **POPULAR ELECTRONICS**.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly.

Write to: P.O. Box 2772, Boulder, CO 80323, giving the following information:

☐ Change address only ☐ Extend my subscription

**ENTER NEW SUBSCRIPTION**

☐ 1 year \$9.98 ☐ Payment enclosed (1 extra BONUS issue) delivery. ☐ Bill me later

NEW ADDRESS HERE 0203

Name \_\_\_\_\_ please print

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Additional postage per year: For Canada add \$3. For countries outside U.S. and Canada, add \$5—cash in U.S. currency only.

**AFFIX OLD LABEL**

If you have no label handy, print OLD address here.

Name \_\_\_\_\_ please print

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

# ELECTRONICS MARKET PLACE

**NON-DISPLAY CLASSIFIED: COMMERCIAL RATE:** For firms or individuals offering commercial products or services, \$2.25 per word (including name and address). Minimum order \$33.75. Payment must accompany copy except when ads are placed by accredited advertising agencies. Frequency discount: 5% for 6 months; 10% for 12 months paid in advance. **READER RATE:** For individuals with a personal item to buy or sell, \$1.35 per word (including name and address.) No minimum! Payment must accompany copy. **DISPLAY CLASSIFIED:** 1" by 1 column (2-1/4" wide), \$260.00. 2" by 1 column, \$520.00. 3" by 1 column, \$780.00. Advertiser to supply film positives. For frequency rates, please inquire.

**GENERAL INFORMATION:** First word in all ads set in caps at no extra charge. All copy subject to publisher's approval. All advertisers using Post Office Boxes in their addresses **MUST** supply publisher with permanent address and telephone number before ad can be run. Advertisements will not be published which advertise or promote the use of devices for the surreptitious interception of communications. Ads are not acknowledged. They will appear in first issue to go to press after closing date. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st. Send order and remittance to **POPULAR ELECTRONICS**, One Park Avenue, New York, New York 10016, Attention: Hal Cymes.

## FOR SALE

**FREE!** Bargain Catalog—I.C.'s, LED's, readouts, fiber optics, calculators parts & kits, semiconductors, parts. Poly Paks, Box 942PE, Lynnfield, Mass. 01940.

**GOVERNMENT** and industrial surplus receivers, transmitters, snooperscopes, electronic parts, Picture Catalog 25 cents. Meshna, Nahant, Mass. 01908.

**LOWEST Prices Electronic Parts.** Confidential Catalog Free. KNAPP, 3174 8th Ave. S.W., Largo, Fla. 33540.

**ELECTRONIC PARTS,** semiconductors, kits. **FREE FLYER.** Large catalog \$1.00 deposit. **BIGELOW ELECTRONICS**, Bluffton, Ohio 45817.

**RADIO—T.V. Tubes—**36 cents each. Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

**AMATEUR SCIENTISTS,** Electronics Experimenters, Science Fair Students... Construction plans—Complete, including drawings, schematics, parts list with prices and sources... Robot Man — Psychedelic shows — Lasers — Emotion/Lie Detector — Touch Tone Dial — Quadraphonic Adapter — Transistorized Ignition — Burglar Alarm — Sound Meter... over 60 items. Send 50 cents coin (no stamps) for complete catalog. Technical Writers Group, Box 5994, University Station, Raleigh, N.C. 27607.

**METERS—**Surplus, new, used, panel or portable. Send for list. Hanchett, Box 5577, Riverside, CA 92507.

**MECHANICAL, ELECTRONIC** devices catalog 10 cents. Greatest Values — Lowest Prices. Fertik's, 5249 "D", Philadelphia, Pa. 19120.



## ORGAN KITS KEYBOARDS

THE ULTIMATE IN DESIGN AND SOUND

Demo Record & Brochure \$1.00

Wurlitzer reproductions  
**DEVTRONIX ORGAN PRODUCTS, Dept. C**  
5872 Amapola Dr. • San Jose, CA 95129

**JAPANESE TRANSISTORS,** all transistors original factory made. Free catalog. West Pacific Electronics, P.O. Box 3879, Torrance, CA 90510.

**ELECTRONIC ignition:** Capacitor-Discharge, pointless. Auburn Sparkplugs. Wheel Stabilizers. Information 20 cents. Anderson Engineering, Epsom, N.H. 03234.

**BUGGED???** New locator finds them fast. Write, Clifton, 11500-L N.W. 7th Avenue, Miami, Florida 33168.

**YOU WILL SAVE BIG MONEY!** Surplus, Clearouts, Bankruptcy, Inventory, Deals. Catalog \$1 (redeemable). ETCOA Electronics, Box 741, Montreal, H3C 2V2. U.S. Inquiries.

**HEAR POLICE/FIRE Dispatchers!** Catalog shows exclusive directories of "confidential" channels, scanners. Send postage stamp. Communications, Box 56-PE, Commack, N.Y. 11725.

**SURPRISE!** Build inexpensively, the most Unusual Test Instruments, Futuristic Gadgets using Numerical Readouts! Catalogue Free! GBS, Box 100A, Green Bank, West Virginia 24944.

**SOUND SYNTHESIZER KITS—**Surf \$12.95, Wind \$12.95, Wind Chimes \$17.95, Electronic Songbird \$6.95, Musical Accessories, many more. Catalog free. PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

**UNSCRAMBLERS:** Fits any scanner or monitor, easily adjusts to all scrambled frequencies. Only 4" square \$29.95, fully guaranteed. Dealer inquiries welcomed. PDQ Electronics, Box 841, North Little Rock, Arkansas 72115.

**RECONDITIONED** Test Equipment. \$0.50 for catalog. Walter's Test Equipment, 2697 Nickel, San Pablo, CA 94806.

**POLICE, Fire monitors, scanners, crystals, CB Transceivers, New Crystal-less scanners.** Discount priced. Box 19224, Denver, CO 80219.

**TELETYPE EQUIPMENT** for sale for beginners and experienced computer enthusiast. Teletype machines, parts, supplies. Catalogue \$1.00 to: ATLANTIC SALES, 3730 Nautilus Ave., Brooklyn, NY 11224. Tel: (212) 372-0349.

**CARBON FILM RESISTORS.** Brand new as low as 1.7 cents. Discounts of 20%. Prompt delivery. FREE samples/specifications. COMPONENTS CENTER, Box 134P, N.Y., N.Y. 10038.

**WHOLESALE C.B.,** Scanners, Antennas, Catalog 25 cents. Crystals: Special cut, \$4.95. Monitor \$3.95. Send make, model, frequency. G. Enterprises, Box 461P, Clearfield, UT 84015.

**NON SEMI SURPLUS.** Monthly picture flyer. Quality. Low prices. Send 25 cents. U.S. only. Startronics, Box 683, McMinville, OR 97128.

## ADVANCED IC ELECTRONICS

### High Quality Components at Reasonable Prices!

**AMI EVK 99 6800 based Microcomputer Kit**... \$149.00  
Expandable to drive EPROM programming, 1024 Bytes RAM, 2048 Bytes ROM, 2048 Bytes EPROM, linear, TV, videobase DMA, SV, Kit consists PCB, 6800, 6880, 6820, (2) 6830, (4) 6810, operating manual and complete instructions. Also Available... Tiny Basic for 6800 Coming Soon... 16K RAM add-on memory. Write for More Details.

**8080A Chip Set Special**... \$77.95  
1 - AMD 8080A  
32 - AMD 9102 APC (500ms) Rams  
**FUNCTION GENERATOR KIT**, \$25.95  
PCB, function chip, instructions, and external components

**MULTITEL KIT**... \$50.00  
PCB, instructions plus  
GI AY5-9100 push button dialer

**AY5-9200** repack dialer  
**AY3-9400** Multi Freq. gen.  
**AY5-9500** CMOS clock gen.

**JUST LIKE THE OTHER GUYS BUT LESS MONEY!!**

**NEW MOS/LSI TV GAME CHIP**  
GI's AY3-8500-1 in Stock  
6 TV Games on a single IC.  
Unit Qty: 39.95  
Qty (5): 33.95  
Qty (10): 29.95

**MICROPROCESSORS**  
AMD 8080A... \$24.90  
AMD 2901... \$30.95  
AMI 6800... \$24.90  
GI CP1600... \$59.90

**6800 SUPPORT DEVICES**  
6880 Modern... \$15.90  
68820 PIA... \$10.95  
68810 RAM... \$9.90  
68850 ACIA... \$9.90

S2350 UART	7.90
S1883 UART	4.95
S6834-1 EPROM	22.90
S6800 Prog. Manual	14.95
S6800 Hardware Manual	14.95

8080 SUPPORT DEVICES	
8212 I/O Port	\$ 3.70
8224 Clock	2.95
8216 Driver	4.90
8225 Driver	5.90
8225 Controller	8.95
9551 Prog. Interface	19.90
9555 Prog. Interface	19.90

## U.S. GOV'T ELECTRONIC SURPLUS

• Nationally Known - World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

**300-AMP., 200-VOLT RECTIFIER**  
(ITEM #22-1048) - FOUR STAR SPECIAL WEST-INGHOUSE, heavy duty unit. Excellent for use in 12 or 24-volt fast chargers, high current power supply systems, etc. 3-5/8" x 1-3/8". 7/8" stud. (1 lb.)

**\$6.95** List Over \$20.00

**SNAP-AROUND VOLT-AMMETER**  
(ITEM #21-1028) - "MINIProbe" clamp type AC ammeter-voltmeter. Small enough to carry in shirt pocket. Will measure 0 to 50-ampères, 0 to 250-volts. Furnished with test leads. Overall size 4-1/2" x 2-3/4" x 1". (1 lb.) List \$33.00

**\$22.95**

**STANDARD DIAL TELEPHONE**  
(ITEM #715) - Same as used on commercial systems in U.S.A. Use as extension to private system. Connect several together for local intercom system. Instructions furnished.

**\$8.79** Original Cost \$24.50 (9 lbs.)

**RUNNING TIME METER**  
(ITEM #2188) - Record number of operating hours of electric lights, electrical devices such as refrigerators, furnaces, etc. Records total hours, tenths and hundredths to 9,999.99 hours. For 115-volts, 60-cycles. 4 1/4" x 3" x 2 1/4". (2 lbs.)

**\$4.39** Cost \$29.00

**SPECIAL SALE Correspondence Course in ELECTRICAL ENGINEERING**  
Prepaid in U.S.A. **\$11.79** Outside U.S.A. **\$12.79**

(ITEM #9-181) - Technical training at low cost! Lincoln Engineering School suspended Correspondence Course because of rising costs. Limited number of Electrical Engineering Courses are available without exams and grading services. Consists of fifteen lesson books, each with associated exams and standard answers. Book showing how to build prize-winning Home Experimental Laboratory Bench included at no extra cost.

**SURPLUS CENTER**  
DEPT. PE-027 LINCOLN, NEBR. 68501

ALL ITEMS SHIPPED F.O.B. LINCOLN, NEBR.  
Order Direct From Ad - Send For FREE Catalog

7400TTL				LINEAR				CMOS			
SN7400N	13	SN7454N	15	SN74155N	.98			CD4000	23	CD4030	.65
SN7401N	13	SN7455N	15	SN74156N	.98			CD4001	23	CD4035	1.19
SN7402N	13	SN7456N	15	SN74157N	.98			CD4002	23	CD4040	2.44
SN7403N	13	SN7457N	15	SN74158N	.98			CD4006	249	CD4042	1.19
SN7404N	15	SN7458N	15	SN74159N	.98			CD4007	23	CD4044	4.49
SN7405N	20	SN7459N	15	SN74160N	.98	LM105H	3.48	CD4009	49	CD4046	2.49
SN7406N	19	SN7460N	15	SN74161N	.98	LM108H	3.49	CD4010	23	CD4047	1.99
SN7407N	27	SN7461N	15	SN74162N	.98	LM114H	2.19	CD4012	23	CD4050	.55
SN7408N	23	SN7462N	15	SN74163N	.98	LM130H	1.99	CD4013	23	CD4051	.55
SN7409N	23	SN7463N	15	SN74164N	.98	LM1300N	1.99	CD4015	1.09	CD4052	1.39
SN7410N	15	SN7464N	15	SN74165N	.98	LM1301A	.94	CD4016	1.09	CD4053	1.39
SN7411N	25	SN7465N	15	SN74166N	.98	LM1301ACN	.94	CD4017	1.09	CD4054	1.39
SN7412N	32	SN7466N	15	SN74167N	.98	LM1301AN	.94	CD4018	1.09	CD4055	1.39
SN7413N	44	SN7467N	15	SN74168N	.98	LM1301A	.94	CD4019	1.09	CD4056	1.39
SN7414N	44	SN7468N	15	SN74169N	.98	LM1302H	.84	CD4020	1.09	CD4057	1.39
SN7415N	44	SN7469N	15	SN74170N	.98	LM1302H	.84	CD4021	1.09	CD4058	1.39
SN7416N	44	SN7470N	15	SN74171N	.98	LM1302H	.84	CD4022	1.09	CD4059	1.39
SN7417N	34	SN7471N	15	SN74172N	.98	LM1302H	.84	CD4023	1.09	CD4060	1.39
SN7418N	34	SN7472N	15	SN74173N	.98	LM1302H	.84	CD4024	1.09	CD4061	1.39
SN7419N	34	SN7473N	15	SN74174N	.98	LM1302H	.84	CD4025	1.09	CD4062	1.39
SN7420N	16	SN7474N	15	SN74175N	.98	LM1302H	.84	CD4026	1.09	CD4063	1.39
SN7421N	29	SN7475N	15	SN74176N	.98	LM1302H	.84	CD4027	1.09	CD4064	1.39
SN7422N	48	SN7476N	15	SN74177N	.98	LM1302H	.84	CD4028	1.09	CD4065	1.39
SN7423N	36	SN7477N	15	SN74178N	.98	LM1302H	.84	CD4029	1.09	CD4066	1.39
SN7424N	28	SN7478N	15	SN74179N	.98	LM1302H	.84	CD4030	1.09	CD4067	1.39
SN7425N	28	SN7479N	15	SN74180N	.98	LM1302H	.84	CD4031	1.09	CD4068	1.39
SN7426N	28	SN7480N	15	SN74181N	.98	LM1302H	.84	CD4032	1.09	CD4069	1.39
SN7427N	28	SN7481N	15	SN74182N	.98	LM1302H	.84	CD4033	1.09	CD4070	1.39
SN7428N	28	SN7482N	15	SN74183N	.98	LM1302H	.84	CD4034	1.09	CD4071	1.39
SN7429N	28	SN7483N	15	SN74184N	.98	LM1302H	.84	CD4035	1.09	CD4072	1.39
SN7430N	28	SN7484N	15	SN74185N	.98	LM1302H	.84	CD4036	1.09	CD4073	1.39
SN7431N	28	SN7485N	15	SN74186N	.98	LM1302H	.84	CD4037	1.09	CD4074	1.39
SN7432N	30	SN7486N	15	SN74187N	.98	LM1302H	.84	CD4038	1.09	CD4075	1.39
SN7433N	30	SN7487N	15	SN74188N	.98	LM1302H	.84	CD4039	1.09	CD4076	1.39
SN7434N	30	SN7488N	15	SN74189N	.98	LM1302H	.84	CD4040	1.09	CD4077	1.39
SN7435N	30	SN7489N	15	SN74190N	.98	LM1302H	.84	CD4041	1.09	CD4078	1.39
SN7436N	30	SN7490N	15	SN74191N	.98	LM1302H	.84	CD4042	1.09	CD4079	1.39
SN7437N	30	SN7491N	15	SN74192N	.98	LM1302H	.84	CD4043	1.09	CD4080	1.39
SN7438N	30	SN7492N	15	SN74193N	.98	LM1302H	.84	CD4044	1.09	CD4081	1.39
SN7439N	15	SN7493N	15	SN74194N	.98	LM1302H	.84	CD4045	1.09	CD4082	1.39
SN7440N	15	SN7494N	15	SN74195N	.98	LM1302H	.84	CD4046	1.09	CD4083	1.39
SN7441N	84	SN7495N	15	SN74196N	.98	LM1302H	.84	CD4047	1.09	CD4084	1.39
SN7442N	58	SN7496N	15	SN74197N	.98	LM1302H	.84	CD4048	1.09	CD4085	1.39
SN7443N	74	SN7497N	15	SN74198N	.98	LM1302H	.84	CD4049	1.09	CD4086	1.39
SN7444N	74	SN7498N	15	SN74199N	.98	LM1302H	.84	CD4050	1.09	CD4087	1.39
SN7445N	74	SN7499N	15	SN74200N	.98	LM1302H	.84	CD4051	1.09	CD4088	1.39
SN7446N	74	SN7500N	15	SN74201N	.98	LM1302H	.84	CD4052	1.09	CD4089	1.39
SN7447N	74	SN7501N	15	SN74202N	.98	LM1302H	.84	CD4053	1.09	CD4090	1.39
SN7448N	74	SN7502N	15	SN74203N	.98	LM1302H	.84	CD4054	1.09	CD4091	1.39
SN7449N	15	SN7503N	15	SN74204N	.98	LM1302H	.84	CD4055	1.09	CD4092	1.39
SN7450N	15	SN7504N	15	SN74205N	.98	LM1302H	.84	CD4056	1.09	CD4093	1.39
SN7451N	15	SN7505N	15	SN74206N	.98	LM1302H	.84	CD4057	1.09	CD4094	1.39
SN7452N	15	SN7506N	15	SN74207N	.98	LM1302H	.84	CD4058	1.09	CD4095	1.39
SN7453N	15	SN7507N	15	SN74208N	.98	LM1302H	.84	CD4059	1.09	CD4096	1.39

## ADVANCED IC ELECTRONICS

HIGH QUALITY COMPONENTS AT REASONABLE PRICES!  
P.O. BOX 19577, IRVINE, CALIFORNIA 92713

# FREE

IC or FET's WITH  
\$5 & \$10 ORDERS.<sup>†</sup>  
DATA SHEETS  
WITH MANY ITEMS.

DIODES	TRANSISTORS	TRANSISTORS	TRANSISTORS	LINEAR IC's
ZENERS & RECTIFIERS	2N706 \$0.24	2N4091 3/51	2N5638 2/51	LM304K-5 \$1.75
1N456 to 1N458	2N718 .48	2N4082 3/51	2N5640 2/51	LM304T-5 1.75
1N458 to 1N460	2N720 .48	2N4121 3/51	2N5643 .50	LM304T-12 1.75
1N460 to 1N462	2N722 .48	2N4122 3/51	2N5647 .50	LM304T-15 1.75
1N462 to 1N464	2N724 .48	2N4124 3/51	2N5651 .50	LM304T-17 1.75
1N464 to 1N466	2N726 .48	2N4125 3/51	2N5652 .50	LM304T-18 1.75
1N466 to 1N468	2N728 .48	2N4126 3/51	2N5653 .50	LM304T-19 1.75
1N468 to 1N470	2N730 .48	2N4127 3/51	2N5654 .50	LM304T-20 1.75
1N470 to 1N472	2N732 .48	2N4128 3/51	2N5655 .50	LM304T-21 1.75
1N472 to 1N474	2N734 .48	2N4129 3/51	2N5656 .50	LM304T-22 1.75
1N474 to 1N476	2N736 .48	2N4130 3/51	2N5657 .50	LM304T-23 1.75
1N476 to 1N478	2N738 .48	2N4131 3/51	2N5658 .50	LM304T-24 1.75
1N478 to 1N480	2N740 .48	2N4132 3/51	2N5659 .50	LM304T-25 1.75
1N480 to 1N482	2N742 .48	2N4133 3/51	2N5660 .50	LM304T-26 1.75
1N482 to 1N484	2N744 .48	2N4134 3/51	2N5661 .50	LM304T-27 1.75
1N484 to 1N486	2N746 .48	2N4135 3/51	2N5662 .50	LM304T-28 1.75
1N486 to 1N488	2N748 .48	2N4136 3/51	2N5663 .50	LM304T-29 1.75
1N488 to 1N490	2N750 .48	2N4137 3/51	2N5664 .50	LM304T-30 1.75
1N490 to 1N492	2N752 .48	2N4138 3/51	2N5665 .50	LM304T-31 1.75
1N492 to 1N494	2N754 .48	2N4139 3/51	2N5666 .50	LM304T-32 1.75
1N494 to 1N496	2N756 .48	2N4140 3/51	2N5667 .50	LM304T-33 1.75
1N496 to 1N498	2N758 .48	2N4141 3/51	2N5668 .50	LM304T-34 1.75
1N498 to 1N500	2N760 .48	2N4142 3/51	2N5669 .50	LM304T-35 1.75
1N500 to 1N502	2N762 .48	2N4143 3/51	2N5670 .50	LM304T-36 1.75
1N502 to 1N504	2N764 .48	2N4144 3/51	2N5671 .50	LM304T-37 1.75
1N504 to 1N506	2N766 .48	2N4145 3/51	2N5672 .50	LM304T-38 1.75
1N506 to 1N508	2N768 .48	2N4146 3/51	2N5673 .50	LM304T-39 1.75
1N508 to 1N510	2N770 .48	2N4147 3/51	2N5674 .50	LM304T-40 1.75
1N510 to 1N512	2N772 .48	2N4148 3/51	2N5675 .50	LM304T-41 1.75
1N512 to 1N514	2N774 .48	2N4149 3/51	2N5676 .50	LM304T-42 1.75
1N514 to 1N516	2N776 .48	2N4150 3/51	2N5677 .50	LM304T-43 1.75
1N516 to 1N518	2N778 .48	2N4151 3/51	2N5678 .50	LM304T-44 1.75
1N518 to 1N520	2N780 .48	2N4152 3/51	2N5679 .50	LM304T-45 1.75
1N520 to 1N522	2N782 .48	2N4153 3/51	2N5680 .50	LM304T-46 1.75
1N522 to 1N524	2N784 .48	2N4154 3/51	2N5681 .50	LM304T-47 1.75
1N524 to 1N526	2N786 .48	2N4155 3/51	2N5682 .50	LM304T-48 1.75
1N526 to 1N528	2N788 .48	2N4156 3/51	2N5683 .50	LM304T-49 1.75
1N528 to 1N530	2N790 .48	2N4157 3/51	2N5684 .50	LM304T-50 1.75
1N530 to 1N532	2N792 .48	2N4158 3/51	2N5685 .50	LM304T-51 1.75
1N532 to 1N534	2N794 .48	2N4159 3/51	2N5686 .50	LM304T-52 1.75
1N534 to 1N536	2N796 .48	2N4160 3/51	2N5687 .50	LM304T-53 1.75
1N536 to 1N538	2N798 .48	2N4161 3/51	2N5688 .50	LM304T-54 1.75
1N538 to 1N540	2N800 .48	2N4162 3/51	2N5689 .50	LM304T-55 1.75
1N540 to 1N542	2N802 .48	2N4163 3/51	2N5690 .50	LM304T-56 1.75
1N542 to 1N544	2N804 .48	2N4164 3/51	2N5691 .50	LM304T-57 1.75
1N544 to 1N546	2N806 .48	2N4165 3/51	2N5692 .50	LM304T-58 1.75
1N546 to 1N548	2N808 .48	2N4166 3/51	2N5693 .50	LM304T-59 1.75
1N548 to 1N550	2N810 .48	2N4167 3/51	2N5694 .50	LM304T-60 1.75
1N550 to 1N552	2N812 .48	2N4168 3/51	2N5695 .50	LM304T-61 1.75
1N552 to 1N554	2N814 .48	2N4169 3/51	2N5696 .50	LM304T-62 1.75
1N554 to 1N556	2N816 .48	2N4170 3/51	2N5697 .50	LM304T-63 1.75
1N556 to 1N558	2N818 .48	2N4171 3/51	2N5698 .50	LM304T-64 1.75
1N558 to 1N560	2N820 .48	2N4172 3/51	2N5699 .50	LM304T-65 1.75
1N560 to 1N562	2N822 .48	2N4173 3/51	2N5700 .50	LM304T-66 1.75
1N562 to 1N564	2N824 .48	2N4174 3/51	2N5701 .50	LM304T-67 1.75
1N564 to 1N566	2N826 .48	2N4175 3/51	2N5702 .50	LM304T-68 1.75
1N566 to 1N568	2N828 .48	2N4176 3/51	2N5703 .50	LM304T-69 1.75
1N568 to 1N570	2N830 .48	2N4177 3/51	2N5704 .50	LM304T-70 1.75
1N570 to 1N572	2N832 .48	2N4178 3/51	2N5705 .50	LM304T-71 1.75
1N572 to 1N574	2N834 .48	2N4179 3/51	2N5706 .50	LM304T-72 1.75
1N574 to 1N576	2N836 .48	2N4180 3/51	2N5707 .50	LM304T-73 1.75
1N576 to 1N578	2N838 .48	2N4181 3/51	2N5708 .50	LM304T-74 1.75
1N578 to 1N580	2N840 .48	2N4182 3/51	2N5709 .50	LM304T-75 1.75
1N580 to 1N582	2N842 .48	2N4183 3/51	2N5710 .50	LM304T-76 1.75
1N582 to 1N584	2N844 .48	2N4184 3/51	2N5711 .50	LM304T-77 1.75
1N584 to 1N586	2N846 .48	2N4185 3/51	2N5712 .50	LM304T-78 1.75
1N586 to 1N588	2N848 .48	2N4186 3/51	2N5713 .50	LM304T-79 1.75
1N588 to 1N590	2N850 .48	2N4187 3/51	2N5714 .50	LM304T-80 1.75
1N590 to 1N592	2N852 .48	2N4188 3/51	2N5715 .50	LM304T-81 1.75
1N592 to 1N594	2N854 .48	2N4189 3/51	2N5716 .50	LM304T-82 1.75
1N594 to 1N596	2N856 .48	2N4190 3/51	2N5717 .50	LM304T-83 1.75
1N596 to 1N598	2N858 .48	2N4191 3/51	2N5718 .50	LM304T-84 1.75
1N598 to 1N600	2N860 .48	2N4192 3/51	2N5719 .50	LM304T-85 1.75
1N600 to 1N602	2N862 .48	2N4193 3/51	2N5720 .50	LM304T-86 1.75
1N602 to 1N604	2N864 .48	2N4194 3/51	2N5721 .50	LM304T-87 1.75
1N604 to 1N606	2N866 .48	2N4195 3/51	2N5722 .50	LM304T-88 1.75
1N606 to 1N608	2N868 .48	2N4196 3/51	2N5723 .50	LM304T-89 1.75
1N608 to 1N610	2N870 .48	2N4197 3/51	2N5724 .50	LM304T-90 1.75
1N610 to 1N612	2N872 .48	2N4198 3/51	2N5725 .50	LM304T-91 1.75
1N612 to 1N614	2N874 .48	2N4199 3/51	2N5726 .50	LM304T-92 1.75
1N614 to 1N616	2N876 .48	2N4200 3/51	2N5727 .50	LM304T-93 1.75
1N616 to 1N618	2N878 .48	2N4201 3/51	2N5728 .50	LM304T-94 1.75
1N618 to 1N620	2N880 .48	2N4202 3/51	2N5729 .50	LM304T-95 1.75
1N620 to 1N622	2N882 .48	2N4203 3/51	2N5730 .50	LM304T-96 1.75
1N622 to 1N624	2N884 .48	2N4204 3/51	2N5731 .50	LM304T-97 1.75
1N624 to 1N626	2N886 .48	2N4205 3/51	2N5732 .50	LM304T-98 1.75
1N626 to 1N628	2N888 .48	2N4206 3/51	2N5733 .50	LM304T-99 1.75
1N628 to 1N630	2N890 .48	2N4207 3/51	2N5734 .50	LM304T-100 1.75
1N630 to 1N632	2N892 .48	2N4208 3/51	2N5735 .50	LM304T-101 1.75
1N632 to 1N634	2N894 .48	2N4209 3/51	2N5736 .50	LM304T-102 1.75
1N634 to 1N636	2N896 .48	2N4210 3/51	2N5737 .50	LM304T-103 1.75
1N636 to 1N638	2N898 .48	2N4211 3/51	2N5738 .50	LM304T-104 1.75
1N638 to 1N640	2N900 .48	2N4212 3/51	2N5739 .50	LM304T-105 1.75
1N640 to 1N642	2N902 .48	2N4213 3/51	2N5740 .50	LM304T-106 1.75
1N642 to 1N644	2N904 .48	2N4214 3/51	2N5741 .50	LM304T-107 1.75
1N644 to 1N646	2N906 .48	2N4215 3/51	2N5742 .50	LM304T-108 1.75
1N646 to 1N648	2N908 .48	2N4216 3/51	2N5743 .50	LM304T-109 1.75
1N648 to 1N650	2N910 .48	2N4217 3/51	2N5744 .50	LM304T-110 1.75
1N650 to 1N652	2N912 .48	2N4218 3/51	2N5745 .50	LM304T-111 1.75
1N652 to 1N654	2N914 .48	2N4219 3/51	2N5746 .50	LM304T-112 1.75
1N654 to 1N656	2N916 .48	2N4220 3/51	2N5747 .50	LM304T-113 1.75
1N656 to 1N658	2N918 .48	2N4221 3/51	2N5748 .50	LM304T-114 1.75
1N658 to 1N660	2N920 .48	2N4222 3/51	2N5749 .50	LM304T-115 1.75
1N660 to 1N662	2N922 .48	2N4223 3/51	2N5750 .50	LM304T-116 1.75
1N662 to 1N664	2N924 .48	2N4224 3/51	2N5751 .50	LM304T-117 1.75
1N664 to 1N666	2N926 .48	2N4225 3/51	2N5752 .50	LM304T-118 1.75
1N666 to 1N668	2N928 .48	2N4226 3/51	2N5753 .50	LM304T-119 1.75
1N668 to 1N670	2N930 .48	2N4227 3/51	2N5754 .50	LM304T-120 1.75
1N670 to 1N672	2N932 .48	2N4228 3/51	2N5755 .50	LM304T-121 1.75
1N672 to 1N674	2N934 .48	2N4229 3/51	2N5756 .50	LM304T-122 1.75
1N674 to 1N676	2N936 .48	2N4230 3/51	2N5757 .50	LM304T-123 1.75
1N676 to 1N678	2N938 .48	2N4231 3/51	2N5758 .50	LM304T-124 1.75
1N678 to 1N680	2N940 .48	2N4232 3/51	2N5759 .50	LM304T-125 1.75
1N680 to 1N682	2N942 .48	2N4233 3/51	2N5760 .50	LM304T-126 1.75
1N682 to 1N684	2N944 .48	2N4234 3/51	2N5761 .50	LM304T-127 1.75
1N684 to 1N686	2N946 .48	2N4235 3/51	2N5762 .50	LM304T-128 1.75
1N686 to 1N688	2N948 .48	2N4236 3/51	2N5763 .50	LM304T-129 1.75
1N688 to 1N690	2N950 .48	2N4237 3/51	2N5764 .50	LM304T-130 1.75
1N690 to 1N692	2N952 .48	2N4238 3/51	2N5765 .50	LM304T-131 1.75
1N692 to 1N694	2N954 .48	2N4239 3/51	2N5766 .50	LM304T-132 1.75
1N694 to 1N696	2N956 .48	2N4240 3/51	2N5767 .50	LM304T-133 1.75
1N696 to 1N698	2N958 .48	2N4241 3/51	2N5768 .50	LM304T-134 1.75
1N698 to 1N700	2N960 .48	2N4242 3/51	2N5769 .50	LM304T-135 1.75
1N700 to 1N702	2N962 .48	2N4243 3/51	2N5770 .50	LM304T-136 1.75
1N702 to 1N704	2N964 .48	2N4244 3/51	2N5771 .50	LM304T-137 1.75
1N704 to 1N706	2N966 .48	2N4245 3/51	2N5772 .50	LM304T-138 1.75
1N706 to 1N708	2N968 .48	2N4246 3/51	2N5773 .50	LM304T-139 1.75
1N708 to 1N710	2N970 .48	2N4247 3/51	2N5774 .50	LM304T-140 1.75
1N710 to 1N712	2N972 .48	2N4248 3/51	2N5775 .50	LM304T-141 1.75
1N712 to 1N714	2N974 .48	2N4249 3/51	2N5776 .50	LM304T-142 1.75
1N714 to 1N716	2N976 .48	2N4250 3/51	2N5777 .50	LM304T-143 1.75
1N716 to 1N718	2N978 .48	2N4251 3/51	2N5778 .50	LM304T-144 1.75
1N718 to 1N720	2N980 .48	2N4252 3/51	2N5779 .50	LM304T-145 1.75
1N720 to 1N722	2N982 .48	2N4253 3/51	2N5780 .50	LM304T-146 1.75
1N722 to 1N724	2N984 .48	2N4254 3/51	2N5781 .50	LM304T-147 1.75
1N724 to 1N726	2N986 .48	2N4255 3/51	2N5782 .50	LM304T-148 1.75
1N726 to 1N728	2N988 .48	2N4256 3/51	2N5783 .50	LM304T-149 1.75
1N728 to 1N730	2N990 .48	2N4257 3/51	2N5784 .50	LM304T-150 1.75
1N730 to 1N732	2N992 .48	2N4258 3/51	2N5785 .50	LM304T-151 1.75
1N732 to 1N734	2N994 .48	2N4259 3/51	2N5786 .50	LM304T-152 1.75
1N734 to 1N736	2N996 .48	2N4260 3/51	2N5787 .50	LM304T-153 1.75
1N736 to 1N738	2N998 .48	2N4261 3/51	2N5788 .50	LM304T-154 1.75
1N738 to 1N740	2N1000 .48	2N4262 3/51	2N5789 .50	LM304T-155 1.75
1N740 to 1N742	2N1002 .48	2N4263 3/51	2N5790 .50	LM304T-156 1.75
1N742 to 1N744	2N1004 .48	2N4264 3/5		

# FREE INFORMATION:

Learning more about a product that's advertised or mentioned in an article in this month's issue is as simple as one, two, three. And absolutely free.

**1** Print or type your name and address on the attached, card.

Use only one card per person.

**2** Circle the number(s) on the card that correspond to the number(s) at the bottom of the advertisement or article for which you want more information.

(Key numbers for advertised products also appear in the Advertisers' Index.)

**3** Simply mail the card.

This address is for our product Free Information Service only. Editorial inquiries should be directed to POPULAR ELECTRONICS, One Park Avenue, New York, N.Y. 10016.

Use only one card per person

## POPULAR ELECTRONICS

PE2773

Use only one card per person.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

(Zip Code must be included to insure delivery.) (Void after Apr. 30, 1977)

Do you own any of the following?

- ☐ Digital VOM ☐ Multimeter ☐ Function Generator  
☐ Oscilloscope ☐ Frequency Counter ☐ Transistor Tester  
☐ Microcomputer ☐ None of the above

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120

## POPULAR ELECTRONICS

PE2772

Use only one card per person

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

(Zip Code must be included to insure delivery.) (Void after Apr. 30, 1977)

Do you own any of the following?

- ☐ Digital VOM ☐ Multimeter ☐ Function Generator  
☐ Oscilloscope ☐ Frequency Counter ☐ Transistor Tester  
☐ Microcomputer ☐ None of the above

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120

## POPULAR ELECTRONICS

PE2771

Use only one card per person.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

(Zip Code must be included to insure delivery.) (Void after Apr. 30, 1977)

Do you own any of the following?

- ☐ Digital VOM ☐ Multimeter ☐ Function Generator  
☐ Oscilloscope ☐ Frequency Counter ☐ Transistor Tester  
☐ Microcomputer ☐ None of the above

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120

# FREE INFORMATION:

First Class  
Permit No. 217  
Clinton, Iowa


## BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

**Popular Electronics**

P.O. Box 2905  
Clinton, Iowa 52732

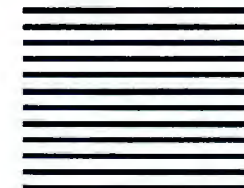

First Class  
Permit No. 217  
Clinton, Iowa


## BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

**Popular Electronics**

P.O. Box 2905  
Clinton, Iowa 52732

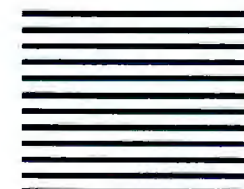

First Class  
Permit No. 217  
Clinton, Iowa


## BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

**Popular Electronics**

P.O. Box 2905  
Clinton, Iowa 52732

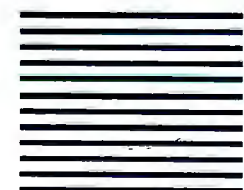

# HAM CB SWL

They come through LOUD AND CLEAR in the all new 1977 COMMUNICATIONS HANDBOOK

## DON'T TURN A DIAL

In fact don't even buy a dial or anything else until you've checked out the 1977 COMMUNICATIONS HANDBOOK. Whatever your radio specialty — whether you're an old hand or just getting started — this vital "how-to" guide will help you get greater value, greater enjoyment out of every minute you spend with your equipment.



COMMUNICATIONS HANDBOOK  
is scheduled to go on sale  
nationally, March, 1977


**YOU CAN RESERVE YOUR COPY NOW AT THE SPECIAL PRE-PUBLICATION PRICE OF ONLY \$1.25 POSTPAID.**

(Regular newsstand price is \$1.75; mail order price \$2.25).

*first time ever published!*

## CITIZENS BAND HANDBOOK

by the editors of POPULAR ELECTRONICS

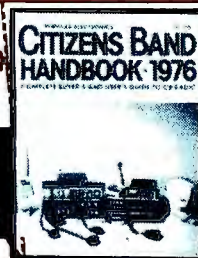

all the authoritative information you need on CB two-way radios to make an intelligent buying decision for transceivers, antennas and accessories. Here's a partial look at what the experts have packed into one volume:

- Over 500 CB models fully described with technical specs, features, latest prices and photos.
- Lab test evaluations on mobile and base station transceivers, both AM and SSB, spell out what the rigs can really do.
- Latest FCC Rules and Regulations, discussed in down-to-earth language, so you fully know what you can and cannot do legally.
- Manufacturers' specifications "decoded" to help you read a "spec sheet" with ease.
- All about CB antennas — the true key to "talk power."
- CB language translation chart.
- How emergency CB associations can save your life!
- How phase-lock-loop digital synthesizers work.
- The latest Flash Report on upcoming CB units presented at the first all-CB-manufacturers show.

This packed-with-information Handbook is the Citizens Band publication you've been waiting for! **Only \$1.75!**

## HERE'S HOW TO ORDER

Mail your order along with your name, address and remittance to Consumer Service Division, 595 Broadway, New York, N.Y. 10012. Specify title being ordered.

COMMUNICATIONS HANDBOOK — Pre-publication price \$1.25, postpaid (\$2 outside U.S.A.). Shipped in March when published.  
CITIZENS BAND HANDBOOK — \$2.25 (\$1.75 plus 50¢ for postage and handling, \$3 outside U.S.A.). Shipped immediately.

Residents of CA, CO, FL, IL, MI, MO, NY, DC and TX add applicable sales tax. Postage and handling charges non-taxable.

# Poly Pak's EXCLUSIVE

Avg. Ship.  
Wt. 6 ozs.

**\$1.98**

Every kit carries  
a money back  
guarantee!

INCLUDES  
"100%"  
MATERIAL  
TOO!!!!

YOUR  
CHOICE  
OF ANY  
KIT

## BARREL KITS

### 100'S OF BARRELS PURCHASED!

For the first time anywhere, Poly Pak merchandisers introduce a new way in buying the economical way. Raw stock from the "barrel". Remember the "good ole days"? They're back again. The same way merchandisers

throughout the United States buy from various factories... their overruns in barrels. Poly Pak has done the same. Therefore you are getting the same type of material as the RE-TESTERS DO!

TEST 'EM YOURSELF 'N SAVE!

Buy 10  
BARREL KITS  
AND CHOOSE THE  
11TH KIT Free

### OP AMP SPECIALS

LM301H	5 for \$1.19
LM301V	5 for 1.19
LM307V	4 for 1.19
LM308V	2 for 1.19
LM309H	3 for 1.19
LM322N	3 for 3.00
LM324N	3 for 3.00
LM339N	3 for 1.19
LM370N	3 for 2.50
LM373N	3 for 5.00
LM377N	3 for 4.00
LM380V	2 for 1.19

LM381N	3 for 4.00
LM385N	3 for 1.19
LM558V	3 for 1.19
LM565N	3 for 2.50
LM703H	5 for 1.19
LM709H	4 for 1.19
LM710N	2 for 1.19
LM723N	2 for 1.19
LM747V	4 for 1.19
LM747H	2 for 1.19
LM748V	5 for 1.19
LM1800N	3 for 2.50
LM709H	4 for 1.19
LM4250H	3 for 2.50

Code H=TOS case, V=Mini Dip, N=DIP.

### BARREL KIT #205 MINI BLOCK CAPACITORS

100 for \$1.98

Unbelievable! Worth \$60. High precision submini caps for all applications. Wt. 3 ozs. Cat. No. 2E3528

### BARREL KIT #203 CALCULATOR KEYBOARDS

10 for \$1.98

It's true! 20-key, 4 function keyboards at ridiculous give-away. Wt. 12 ozs. Cat. No. 2E3524

### BARREL KIT #184 1/2-WATT METAL FILM

150 for \$1.98

100% metal film resistors. Long leads. 2E3413

### BARREL KIT #182 JUMBO RED LEDS

15 for \$1.98

100% material, use cancellation from factory dumps, 3V, 10 mils. For 100's of projects, red lens. Cat. No. 2E3369

### BARREL KIT #157 MOLEX CONNECTORS

75 for \$1.98

12 ozs. Nylon, white cable connectors, ass't. factory over-run. NO PICKLE! Mixed in barrel. Cat. No. 2E3324

### BARREL KIT #154 CLOCK CHIPS

20 for \$1.98

We ordered an assortment of clock chip, alarm, calendar, beepers, who knows, all mixed. Cat. No. 2E3306

### BARREL KIT #158 MAGNIFIED MAN-3's

12 for \$1.98

MAN-3 7-seg readout, with built-in magnifier. Factory discontinued line. 100% material. Cat. No. 2E3325

### BARREL KIT #157 MOLEX CONNECTORS

75 for \$1.98

12 ozs. Nylon, white cable connectors, ass't. factory over-run. NO PICKLE! Mixed in barrel. Cat. No. 2E3324

### BARREL KIT #138 CALCULATOR CHIPS

15 for \$1.98

Stationary type. Can be MM5734, 38, etc. Untested. Cat. No. 2E3258

### BARREL KIT #133 C-MOS IC'S

60 for \$1.98

Deliberately thrown in barrels we can't test! The famous CD4000 series. How good? Who knows? Cat. No. 2E3257

### BARREL KIT #118 MOLEX SOCKETS

100 for \$1.98

100% good. Double plug. Calculator maker dump! We got a million of 'em. Used for IC sockets, etc. Cat. No. 2E3135

### BARREL KIT #112 MICRO MINI LEDS

40 for \$1.98

All the tiny leds, axial, upright of Monsanto, Litronix, variety of colors. Yield 50% or better. 2E3135

### BARREL KIT #93 HALF WATERS

200 for \$1.98

Resistor factory tried to fool us by mixing 100% color-coded resistors in barrel. But value is there. 4 oz. 2E3046 Untested

### BARREL KIT #92 3 AMP EPOXY RECTIFIERS

100 for \$1.98

Cosmetic rejects, electrical fine business! You check 'em, it's not for us. Ass't. voltages. 2E3204

### BARREL KIT #76 1-WATT ZENERS

100 for \$1.98

Factory same as 100-mw's. Never-to-see-again offer. 6, 8, 10, 12, 15V. under 1000. 2E3041 Untested.

### BARREL KIT #75 400MW ZENERS

100 for \$1.98

Factory out of biz! Amazing offer: 6, 8, 10, 12 to 15V. You test. Hermetically sealed glass cap. Double plug. Cat. No. 2E2740

### BARREL KIT #61 POLYSTYRENE CAPS

100 for \$1.98

Finest caps made. As a sample we bought 10 barrels from factory, mixed values; all good. Cat. No. 2E2729

### BARREL KIT #58 SLIDE SWITCHES

30 for \$1.98

All shapes, sizes, spst, apst, momentaries, etc. Tremendous shop pak for 100's of switching projects. Cat. No. 2E2726 100% good

### BARREL KIT #39 2N3055 HOBBY TRANSISTORS

15 for \$1.98

Failure of the famous 2N3055. 2E2617 100%

### BARREL KIT #37 1 AMP "BULLET" RECTIFIERS

100 for \$1.98

Famous style, ass't. voltages, silicon, axial includes all types of voltages to 1KV. Cat. No. 2E2615

### BARREL KIT #26 PLASTIC TRANSISTORS

100 for \$1.98

Includes TO-18, TO-18, etc., assorted 2N numbers, unmarked etc. Cat. No. 2E2603 Untested.

### BARREL KIT #25 METAL CAN TRANSISTORS

100 for \$1.98

Includes TO-5, TO-18, etc., assorted 2N numbers, unmarked etc. Cat. No. 2E2603 Untested.

### BARREL KIT #14 PRECISION RESISTORS

200 for \$1.98

Marked and unmarked 1/2, 1/4, 2 watts. Cat. No. 2E2411

### BARREL KIT #12 POWER TAB TRANS

40 for \$1.98

PNP, plastic TO220 type. Assorted 2N numbers. Cat. No. 2E2426 Untested.

### BARREL KIT #8 SUBMINIATURE IF TRANSFORMERS

100 for \$1.98

Amazing, includes 455kc, osc, antenna, who knows? From transistor radio manufacturers. 100% 2E2422

### BARREL KIT #7 VOLUME CONTROL BONANZA

30 for \$1.98

100% good. Singles, duals, variety of values, styles, big ones - small ones. Cat. No. 2E2421

### BARREL KIT #3 LINEAR OR AMPS, DIPS

75 for \$1.98

Untested. Includes 709's, 741's, 706's, 660 series, 555 includes 2E2416

### BARREL KIT #11 POWER TAB TRANSISTORS

40 for \$1.98

PNP, plastic TO220 type. Assorted 2N numbers. Cat. No. 2E2411

### BARREL KIT #10 ROMS-REGISTERS

75 for \$1.98

28 to 40 pin devices, marked, internal factory numbers, etc. 2E2424

### BARREL KIT #5 SCRS, TRIACS, QUADRACS

30 for \$1.98

Raw factory stock! All the 10 amp types. Cat. No. 2E2419 Untested.

### BARREL KIT #4 "4000" RECTIFIERS

100 for \$1.98

Untested. IN4000 series, May include 40, 50, 100, 200, 400, 600, 800 and 1000 voltages. 2E2417

### BARREL KIT #3 LINEAR OR AMPS, DIPS

75 for \$1.98

Untested. Includes 709's, 741's, 706's, 660 series, 555 includes 2E2416

### BARREL KIT #2 PREFORMED DISCS

100 for \$1.98

Hi-Fi mfr's shelf inventory but he dumped 'em in barrels. Preformed, for PC use. Mixed values too! 2E2605

### BARREL KIT #17 LINEAR & 7400 DIPS

100 for \$1.98

Untested. Marked and unmarked, internal numbers of factory stock. No. 2E2431

### BARREL KIT #16 MOSFET TRANSISTORS

60 for \$1.98

All 4 lenders TO-18 case, includes 11P transistors too! Cat. No. 2E2429

### BARREL KIT #15 MOSFET TRANSISTORS

60 for \$1.98

All 4 lenders TO-18 case, includes 11P transistors too! Cat. No. 2E2429

### BARREL KIT #14 "4000" RECTIFIERS

100 for \$1.98

Untested. IN4000 series, May include 40, 50, 100, 200, 400, 600, 800 and 1000 voltages. 2E2417

### BARREL KIT #13 LINEAR OR AMPS, DIPS

75 for \$1.98

Untested. Includes 709's, 741's, 706's, 660 series, 555 includes 2E2416

### BARREL KIT #12 POWER TAB TRANS

40 for \$1.98

PNP, plastic TO220 type. Assorted 2N numbers. Cat. No. 2E2426 Untested.

### BARREL KIT #11 POWER TAB TRANSISTORS

40 for \$1.98

PNP, plastic TO220 type. Assorted 2N numbers. Cat. No. 2E2411

### BARREL KIT #10 ROMS-REGISTERS

75 for \$1.98

28 to 40 pin devices, marked, internal factory numbers, etc. 2E2424

### BARREL KIT #9 SUBMINIATURE IF TRANSFORMERS

100 for \$1.98

Amazing, includes 455kc, osc, antenna, who knows? From transistor radio manufacturers. 100% 2E2422

### BARREL KIT #8 SUBMINIATURE IF TRANSFORMERS

100 for \$1.98

Amazing, includes 455kc, osc, antenna, who knows? From transistor radio manufacturers. 100% 2E2422

### BARREL KIT #7 VOLUME CONTROL BONANZA

30 for \$1.98

100% good. Singles, duals, variety of values, styles, big ones - small ones. Cat. No. 2E2421

### BARREL KIT #6 SUBMINIATURE IF TRANSFORMERS

100 for \$1.98

Amazing, includes 455kc, osc, antenna, who knows? From transistor radio manufacturers. 100% 2E2422

### BARREL KIT #5 SCRS, TRIACS, QUADRACS

30 for \$1.98

Raw factory stock! All the 10 amp types. Cat. No. 2E2419 Untested.

### BARREL KIT #4 "4000" RECTIFIERS

100 for \$1.98

Untested. IN4000 series, May include 40, 50, 100, 200, 400, 600, 800 and 1000 voltages. 2E2417

### BARREL KIT #3 LINEAR OR AMPS, DIPS

75 for \$1.98

Untested. Includes 709's, 741's, 706's, 660 series, 555 includes 2E2416

### BARREL KIT #2 PREFORMED DISCS

100 for \$1.98

Hi-Fi mfr's shelf inventory but he dumped 'em in barrels. Preformed, for PC use. Mixed values too! 2E2605

### BARREL KIT #17 LINEAR & 7400 DIPS

100 for \$1.98

Untested. Marked and unmarked, internal numbers of factory stock. No. 2E2431

### BARREL KIT #16 MOSFET TRANSISTORS

60 for \$1.98

All 4 lenders TO-18 case, includes 11P transistors too! Cat. No. 2E2429

### BARREL KIT #15 MOSFET TRANSISTORS

60 for \$1.98

All 4 lenders TO-18 case, includes 11P transistors too! Cat. No. 2E2429

### BARREL KIT #14 "4000" RECTIFIERS

100 for \$1.98

Untested. IN4000 series, May include 40, 50, 100, 200, 400, 600, 800 and 1000 voltages. 2E2417

### BARREL KIT #13 LINEAR OR AMPS, DIPS

75 for \$1.98

Untested. Includes 709's, 741's, 706's, 660 series, 555 includes 2E2416

### BARREL KIT #12 POWER TAB TRANS

40 for \$1.98

PNP, plastic TO220 type. Assorted 2N numbers. Cat. No. 2E2426 Untested.

### BARREL KIT #11 POWER TAB TRANSISTORS

40 for \$1.98

PNP, plastic TO220 type. Assorted 2N numbers. Cat. No. 2E2411

### BARREL KIT #10 ROMS-REGISTERS

75 for \$1.98

28 to 40 pin devices, marked, internal factory numbers, etc. 2E2424

### BARREL KIT #9 SUBMINIATURE IF TRANSFORMERS

100 for \$1.98

Amazing, includes 455kc, osc, antenna, who knows? From transistor radio manufacturers. 100% 2E2422

### BARREL KIT #8 SUBMINIATURE IF TRANSFORMERS

100 for \$1.98

Amazing, includes 455kc, osc, antenna, who knows? From transistor radio manufacturers. 100% 2E2422

### BARREL KIT #7 VOLUME CONTROL BONANZA

30 for \$1.98

100% good. Singles, duals, variety of values, styles, big ones - small ones. Cat. No. 2E2421

### BARREL KIT #6 SUBMINIATURE IF TRANSFORMERS

100 for \$1.98

Amazing, includes 455kc, osc, antenna, who knows? From transistor radio manufacturers. 100% 2E2422

### BARREL KIT #5 SCRS, TRIACS, QUADRACS

30 for \$1.98

Raw factory stock! All the 10 amp types. Cat. No. 2E2419 Untested.


### BARREL KIT #4 "4000" RECTIFIERS

100 for \$1.98

MOVING MUST DUMP Junk cheap. Write for list. Pat. Box 532, Logansport, Ind. 46947.

MICROCOMPUTER coding forms: 100 for \$6. Write for more details. BMS, Box 5121, Jackson, MS 39216.

## Digital Clock for Vehicles

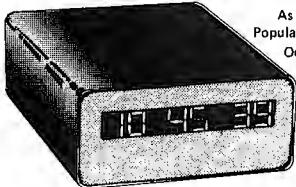

As described in Popular Electronics October 1976.

**\$29.95**  
+ \$2.50 P&H  
COMPLETE KIT  
LESS CASE

Kit includes all resistors, capacitors, transistors, diodes, IC's, crystal, etched and drilled PCB, assembled display board, switches, and step-by-step assembly instructions.

OPTIONAL CASE WITH LENS: \$4.50.

COMPACT SIZE: 2.5" x 1.2" x 2.8"

Outside U.S.A.: Add \$3.00 P&H ordinary mail, \$5.00 Air.

ALPHA ELECTRONICS (TEXAS) P.O. BOX 64776-D  
DALLAS, TEXAS 75266, PH: (214) 369-7309

## ADVANCED MICROCOMPUTER PRODUCTS



Photo of expanded EVK 99

**TV GAME KITS**

- 1. EVK 99 consists of the following only:**  
Qty. (1) PC8 10K x 12  
(1) 6800 1 bit CPU  
(1) 6850 ACIA (Asynchronous Communication Interface Adapter)  
(1) 6800A PIA (Peripheral Interface Adapter)  
(1) 6850 ROM Subroutine Program Library (11 6801 15K ROM)  
(4) 6801 1 RAM  
(1) Operating Manual & Instructions  
To implement fully expanded system additional IC's are required. (See Photo)
- 2. UNIVERSAL KLUGE BOARD \$98.00**  
Completely compatible to the EVK system. This board allows the user to add any additional parts he desires. It has 4400 holes, holds 96 16 pin IC's or others on 2, 4, 8, 16 or greater centers. 2.50 pin, 1.70 pin for cable, 1.75 pin RS232 connector.
- 3. 16K BYTE RAM BOARD \$77.95**  
16K x 8 or 8K x 16 organization. Uses 2102's or 2102Z's and adapts to slow memory.
- 4. 6 SLOT MOTHER BOARD \$29.95**  
Connectors mount on 75° centers. May be plugged together for expanded applications.
- 5. EXTENDER BOARD \$46.50**  
For use with back plane above in card cage configuration. New boards are now in development including cassette I/O and others. If you want more information drop us a line.

## IC MARKET PLACE

### ★ LINEAR

LM105	3.50	LM200K-5.2	1.45	LM3818	1.79
LM106H	2.50	LM202K-12	1.45	LM3827N	1.79
LM107H	80	LM202K-15	1.45	LM3830N	1.79
LM108H	80	LM202K-15	1.45	LM3830N	1.79
LM109H	80	LM202K-15	1.45	LM3830N	1.79
LM200H	80	LM202K-15	1.45	LM3830N	1.79

### ★ 7400 TTL

7400N	18	7445N	39	74129N	44	74185N	\$2.10
7401N	18	7446N	39	74130N	44	74186N	\$2.10
7402N	18	7447N	39	74131N	44	74187N	\$2.10
7403N	18	7448N	39	74132N	44	74188N	\$2.10
7404N	18	7449N	39	74133N	44	74189N	\$2.10
7405N	20	7450N	26	74134N	44	74190N	\$2.10
7406N	20	7451N	26	74135N	44	74191N	\$2.10
7407N	20	7452N	26	74136N	44	74192N	\$2.10
7408N	20	7453N	26	74137N	44	74193N	\$2.10
7409N	20	7454N	26	74138N	44	74194N	\$2.10
7410N	21	7455N	26	74139N	44	74195N	\$2.10
7411N	21	7456N	26	74140N	44	74196N	\$2.10
7412N	21	7457N	26	74141N	44	74197N	\$2.10
7413N	21	7458N	26	74142N	44	74198N	\$2.10
7414N	21	7459N	26	74143N	44	74199N	\$2.10
7415N	21	7460N	26	74144N	44	74200N	\$2.10
7416N	21	7461N	26	74145N	44	74201N	\$2.10
7417N	21	7462N	26	74146N	44	74202N	\$2.10
7418N	21	7463N	26	74147N	44	74203N	\$2.10
7419N	21	7464N	26	74148N	44	74204N	\$2.10
7420N	21	7465N	26	74149N	44	74205N	\$2.10
7421N	21	7466N	26	74150N	44	74206N	\$2.10
7422N	21	7467N	26	74151N	44	74207N	\$2.10
7423N	21	7468N	26	74152N	44	74208N	\$2.10
7424N	21	7469N	26	74153N	44	74209N	\$2.10
7425N	21	7470N	26	74154N	44	74210N	\$2.10
7426N	21	7471N	26	74155N	44	74211N	\$2.10
7427N	21	7472N	26	74156N	44	74212N	\$2.10
7428N	21	7473N	26	74157N	44	74213N	\$2.10
7429N	21	7474N	26	74158N	44	74214N	\$2.10
7430N	21	7475N	26	74159N	44	74215N	\$2.10
7431N	21	7476N	26	74160N	44	74216N	\$2.10
7432N	21	7477N	26	74161N	44	74217N	\$2.10
7433N	21	7478N	26	74162N	44	74218N	\$2.10
7434N	21	7479N	26	74163N	44	74219N	\$2.10
7435N	21	7480N	26	74164N	44	74220N	\$2.10
7436N	21	7481N	26	74165N	44	74221N	\$2.10
7437N	21	7482N	26	74166N	44	74222N	\$2.10
7438N	21	7483N	26	74167N	44	74223N	\$2.10
7439N	21	7484N	26	74168N	44	74224N	\$2.10
7440N	21	7485N	26	74169N	44	74225N	\$2.10
7441N	21	7486N	26	74170N	44	74226N	\$2.10
7442N	21	7487N	26	74171N	44	74227N	\$2.10
7443N	21	7488N	26	74172N	44	74228N	\$2.10
7444N	21	7489N	26	74173N	44	74229N	\$2.10
7445N	21	7490N	26	74174N	44	74230N	\$2.10
7446N	21	7491N	26	74175N	44	74231N	\$2.10
7447N	21	7492N	26	74176N	44	74232N	\$2.10
7448N	21	7493N	26	74177N	44	74233N	\$2.10
7449N	21	7494N	26	74178N	44	74234N	\$2.10
7450N	21	7495N	26	74179N	44	74235N	\$2.10
7451N	21	7496N	26	74180N	44	74236N	\$2.10
7452N	21	7497N	26	74181N	44	74237N	\$2.10
7453N	21	7498N	26	74182N	44	74238N	\$2.10
7454N	21	7499N	26	74183N	44	74239N	\$2.10
7455N	21	7500N	26	74184N	44	74240N	\$2.10
7456N	21	7501N	26	74185N	44	74241N	\$2.10
7457N	21	7502N	26	74186N	44	74242N	\$2.10
7458N	21	7503N	26	74187N	44	7	

7400 TTL			5400 SERIES			MOTOROLA CIRCUITS			JAPANESE CIRCUITS		
7400 .21	7442 1.08	74121 .55	5400 1.00	5475 1.50		MC725P 1.50	MC1741CG .98	AN136 2.90	HA1312 4.05	STK056 11.35	TA7201P 6.40
7401 .21	7448 1.15	74122 .49	5404 1.25	5486 1.90		MC740L 1.55	MC1804P .98	AN203 3.75	HA1322 5.20	STK415 11.50	TA7203P 7.00
7402 .21	7450 2.26	74123 1.05	5410 1.00	5493 2.00		MC790P 1.50	MC1810P .98	AN208 4.75	HA1339 5.20	TA7045M 3.50	TA7205P 6.50
7404 .21	7451 .27	74125 .81	5426 1.25	54100 1.80		MC832P .48	MC2053L .45	AN211 3.30	LA1364 4.70	TA7055P 5.50	TA7800SM 2.50
7405 .24	7453 .27	74126 .81	5432 1.50	54100 1.80		MC100AL 1.25	MC3004L 1.32	AN214 4.90	LA1366 6.00	TA7080P 6.00	TA7800SP 1.95
7406 .45	7454 .41	74132 3.00				MC1008L 1.25	MC3006P 1.44	AN217 3.30	LA1367 5.90	TA7081P 2.25	TA78012M 2.50
7407 .45	7460 .22	74141 1.15				MC1010L 1.25	MC3007P 1.32	AN229 6.35	LA3301 4.85	TA7082P 2.25	TA78012P 1.95
7408 .25	7472 .39	74150 1.10				MC1011L 1.25	MC3021L 2.15	AN234 5.75	LA4030 4.85	TA7083P 2.25	TA78015M 2.50
7409 .25	7473 .45	74151 1.25				MC1036L 12.50	MC3021P 2.15	AN239 6.50	LA4031P 3.50	TA7074P 4.90	TA78015P 1.95
7410 .20	7474 .45	74153 1.35				MC1037L 12.50	MC3060L 2.65	AN241 3.20	LA4051P 4.65	TA7075P 4.90	TC9100P 12.00
7411 .30	7475 .80	74154 1.25				MC1352P 1.05	MC3062L 3.00	AN245 6.50	LD3001 3.35	TA7076P 4.55	UPC16C 2.50
7413 .85	7482 1.75	74155 1.21				MC1406CP 3.95	MC4024P 2.20	AN274 3.95	LD3080 4.00	TA7092P 6.50	UPC20C 3.00
7416 .43	7483 1.15	74157 1.30				MC1468L 2.90	MC4501CP .31	AN277B 3.40	LD3120 3.10	TA7102P 5.15	UPC41C 5.95
7417 .43	7485 1.12	74161 1.45				MC1469P 2.50	MC4502CP 1.18	AN288 4.80	LD3141 2.40	TA7106P 3.25	UPC48C 3.95
7420 .21	7486 .45	74164 1.85				MC1510G 8.00	MC14507CP .82	AN328 4.05	MS112 5.40	TA7120P 2.20	UPC54C 3.90
7422 1.50	7489 2.49	74165 1.85				MC1514L 4.50	MC14510CP 2.40	AN343 3.90	MS115PR 4.80	TA7120P-C 2.20	UPC563H2 8.00
7425 .43	7490 .69	74166 1.70				MC1550G 1.50	MC14511CP 2.76	BA511 3.50	MS155 2.85	TA7122AP 2.30	UPC566H 2.25
7427 .37	7491 1.20	74174 1.95				MC1558 4.37	MC14512CP 1.92	BA521 3.95	SG613 5.40	TA7124P 1.85	UPC575C 4.10
7428 .33	7492 .82	74175 1.95				MC1595L 6.25	MC14519CG .94	HA1158 6.30	STK011 10.50	TA7146P 4.10	UPC1001H2 5.15
7430 .26	7493 .82	74180 1.05				MC1596G 3.31	MC14528CP 1.74	HA1159 6.60	STK015 6.50	TA7150P 4.55	UPC1020H 5.50
7432 .31	7494 .91	74181 3.55				MC1723CG 1.25	MC4044P 4.80	HA1202 3.10	STK025 12.50	TA7153P 6.90	UPC1025 5.50
7437 .47	7495 .91	74191 1.50						HA1306W 5.20	STK032 14.20	TA7200P 6.25	
7438 .40	7496 .91	74195 1.00									
7440 .21	74100 1.25	74197 1.00									
7441 1.10	74107 .49	74298 1.30									

74L SERIES TTL		
74L00 .33	74LS04 .45	74LS113 .98
74L10 .33	74LS10 .39	74LS138 1.89
74L30 .33	74LS20 .39	74LS174 2.50
74L42 1.50	74LS51 .39	74LS386 5.50
74L86 .69	74LS74 .65	74LS153 2.25
74LS00 .39	74LS112 .65	74LS387 1.95

74H00 TTL		
74H00 .33	74H11 .33	74H53 .39
74H01 .33	74H21 .33	74H55 .39
74H04 .33	74H21 .33	74H73 .59
74H05 .35	74H30 .33	74H74 .59
74H10 .33	74H40 .33	74H76 .60

ELECTROLYTIC CAPACITORS		
2.2MF50	AXIAL LEADS .15	
3.3MF10	AXIAL LEADS .15	
3.3MF10	NO POLARITY .15	
10MF25	AXIAL LEADS .15	
10MF50	AXIAL LEADS .15	
10MF150	AXIAL LEADS .20	
25MF35	AXIAL LEADS .15	
30MF25	AXIAL LEADS .15	
47MF25	RADIAL LEADS .15	
47MF50	RADIAL LEADS .20	
100MF16	RADIAL LEADS .15	
100MF25	RADIAL LEADS .20	
500MF50	AXIAL LEADS .60	
1000MF35	AXIAL LEADS .65	

CARBON RESISTORS		
Minimum 5 Pcs Per Value		
QUANTITY		
PRICING 5-25	30-95	100-495
1/4w5% .06	.05	.04
1/4w5% .08	.07	.06
STANDARD RESISTANCE VALUES		
OHMS		
10	270	820 4.7K 27K
15	300	910 5.1K 33K
22	330	1K 6.8K 47K
33	390	1.1K 7.5K 100K
47	470	1.5K 7.5K 100K
100	510	2.2K 8.2K 330K
150	560	2.7K 10K 1.0M
220	680	3.3K 15K
240	750	3.9K 22K

JAPANESE TRANSISTORS * CB, AUDIO, INDUSTRIAL		
2SA52 .60	2SC206 1.00	2SC774 1.75
2SA316 .75	2SC240 1.10	2SC775 2.75
2SA473 .75	2SC291 .65	2SC776 3.00
2SA483 1.95	2SC292 3.00	2SC777 4.00
2SA489 .80	2SC320 .75	2SC778 4.00
2SA490 .70	2SC352 .75	2SC781 3.00
2SA505 .70	2SC353 .75	2SC783 1.00
2SA564 .50	2SC371 .70	2SC784 .70
2SA628 .65	2SC372 .70	2SC785 1.00
2SA643 .85	2SC394 .70	2SC789 1.00
2SA647 2.75	2SC458 .70	2SC793 2.50
2SA678 .75	2SC460 .70	2SC796 2.15
2SA679 3.75	2SC478 .80	2SC797 2.50
2SA682 .85	2SC481 1.85	2SC798 3.10
2SA699 1.30	2SC482 1.75	2SC799 4.25
2SA699A 1.45	2SC491 2.50	2SC802 3.75
2SA705 .55	2SC495 1.10	2SC803 4.00
2SA815 .85	2SC497 1.60	2SC815 .75
2SA816 .85	2SC502 1.50	2SC828 .75
	2SC515 .80	2SC829 .75
2SB22 .65	2SC517 4.25	2SC830 1.60
2SB54 .70	2SC535 .75	2SC838 .70
2SB56 .70	2SC538 .65	2SC839 .85
2SB77 .70	2SC537 .70	2SC922 .55
2SB128 2.25	2SC563 2.50	2SC929 .70
2SB152 4.50	2SC607 1.25	2SC930 .65
2SB173 .55	2SC614 3.80	2SC938 .85
2SB175 .55	2SC615 3.90	2SC943 1.50
2SB178 1.00	2SC616 4.15	2SC945 .65
2SB186 .80	2SC617 4.25	2SC959 3.15
2SB187 .80	2SC620 .80	2SC960 2.75
2SB235 7.00	2SC627 1.75	2SC984 1.50
2SB303 .85	2SC642 3.50	2SC996 4.90
2SB324 1.00	2SC643 3.75	2SC1010 2.80
2SB337 2.10	2SC644 .70	2SC1012 .80
2SB367 1.60	2SC647 2.50	2SC1013 1.50
2SB370 .85	2SC684 2.10	2SC1014 1.50
2SB405 .85	2SC687 2.50	2SC1017 1.50
2SB407 1.85	2SC696 3.00	2SC1018 1.50
2SB415 .85	2SC699 4.75	2SC1030 4.75
2SB461 1.25	2SC710 .70	2SC1051 2.50
2SB463 1.65	2SC711 .70	2SC1060 .75
2SB471 1.75	2SC712 .70	2SC1061 1.65
2SB474 1.50	2SC713 .70	2SC1069 3.50
2SB476 1.25	2SC731 3.00	2SC1079 3.75
2SB481 2.10	2SC732 .70	2SC1080 3.75
2SB492 1.25	2SC733 .70	2SC1098 1.20
2SB495 .85	2SC735 .70	2SC1099 1.15
2SB507 .90	2SC739 .70	2SC1115 2.75
2SB511 .70	2SC715 .70	2SD45 2.00
2SB531 3.00	2SC756 3.00	2SD165 .75
2SB556 3.50	2SC762 1.90	2SD168 .90
2SB135 .95	2SC773 .85	2SD172 1.00

MISC CIRCUITS		
BC184L .60	LM309K 1.95	SN15844N .55
CA3001 .75	LM351AN .70	SN15946 .55
CA3005 .80	LM741CP .40	SN158097N .60
CA3006 1.10	LM1458M .65	SN72560P 4.50
CA3018 1.80	MFC9020 1.15	SN727410N .85
CA3018A 1.60	MR995A 1.05	SN72741C .45
CA3026 2.15	MSC996P7.50	SN72748P .49
CA3035 2.45	N5558 .55	SN7400K-24 1.95
CA3039 1.35	N6598B 5.00	UA709C .40
CA3058 1.90	NE555V .45	UFT73393 2.40
CK707P .45	PA771131 .45	95S879 8.50
CS134J 1.15	PL994551 .45	998079 12.50
CS135J 1.20	RC14370B .35	998979 9.00
CS136 1.25	SC9962P .70	936-5D 1.10
IC3(GE) 1.50	SC9966P 1.25	9313DC 1.20
LM301AN .35	SN15830N .50	93L28DC 2.75

POSITIVE VOLTAGE REGULATORS		
LM340K-5 1.95	LM340K-8 1.95	LM340K-12 1.95
LM340K-15 1.95	LM340K-18 1.95	LM340K-24 1.95
LM340T-6 1.75	LM340T-8 1.75	LM340T-12 1.75
LM340T-15 1.75	LM340T-18 1.75	LM340T-24 1.75

HOBBY SPECIALS		
YOU TEST 'EM SAVE BIG MONEY		
Power Pac 100 Asst. (includes Case T03, T066 TO220, TO202)		\$2.99
Transistor/ Diode Pac 100 Asst. (includes Case T05, T039, T018, D07, 0041)		\$1.99
I.C. Pac 100 Asst. (includes 14 & 16 Pin)		\$3.50
Resistor Pac 50 Asst. (Assorted values)		\$1.50
Mos Fet Pac 10 Asst. (many top #s Case T072)		\$0.99
SCR Pac 100 Asst. (similar to C103 Series) Case to 92, VR:10-100V, I:400MA, IGT:200MA		\$4.00

ZENER DIODES		
1/2 & 1 Watt 10% .30 each UP TO 33V. GREATER THAN 33V CALL FOR PRICING		

POPULAR JEDEC SEMICONDUCTORS		
1N34 .25	2N918 .60	2N2218 .25
1N60 .25	2N930 .25	2N2219A .30
1N270 .40	2N956 .30	2N2219 .25
1N914 .07	2N960 .90	2N2219A .30
	2N962 .95	2N2221 .25
2N173 1.75	2N967 .95	2N2221A .30
2N174 3.50	2N1136 1.75	2N2222 .25
2N178 .90	2N1142 2.25	2N2222A .30
2N327A 1.15	2N1300 1.00	2N2223 1.00
2N334 1.20	2N1301 1.10	2N2270 4.00
2N336 .90	2N1302 1.25	2N2323 1.00
2N338A 1.05	2N1303 .70	2N2324 1.35
2N398B 1.50	2N1304 1.25	2N2325 2.00
2N404 .75	2N1305 .75	2N2326 2.80
2N403 2.50	2N1306 1.35	2N2327 3.80
2N458 1.30	2N1307 .75	2N2328 4.25
2N501A 3.00	2N1308 1.50	2N2329 4.75
2N508A .60	2N1309 .90	2N2368 .25
2N555 .75	2N1552 3.25	2N2369 .25
2N552A 1.25	2N1554 1.25	2N2484 3.20
2N577 6.00	2N1557 1.15	2N2712 .18
2N708 .25	2N1580 2.80	2N2894 .40
2N706B .75	2N1605 .35	2N2903 3.30
2N711 .90	2N1613 .30	2N2904 .25
2N711B 1.10	2N1711 .30	2N2904A .30
2N718 .25	2N1907 4.10	2N2905 .20
2N718A .30	2N2060 1.65	2N2905A .30
2N720A .50	2N2102 .40	2N2906 .25
		2N3645 .20
		2N3646 .14
		2N3730 2.50
		2N3731 3.75
		2N3740 1.00
		2N3771 1.75
		2N3772 1.90
		2N3773 3.00
		2N3819 4.00
		2N3823 .70
		2N3858 .75
		2N3888 .65
		2N3903 .18
		2N3904 .16
		2N3905 .16
		2N3906 .16
		2N3925 3.75
		2N3954 3.50
		2N3955 2.45
		2N3957 1.25
		2N4038 .75
		2N4037 .80
		2N4093 .65
		2N4124 .18
		2N4126 .18
		2N4141 .20
		2N4142 .20
		2N4143 .20
		2N4220A .45
		2N4234 .95
		2N4400 1.80
		2N4401 .18
		2N4402 .16
		2N4403 .20
		2N4409 .16
		2N4410

## CRYSTALS

Part #	Frequency	Case/Style	Price
CY1A	1.000 MHz	HC33/U	\$5.95
CY2A	2.000 MHz	HC33/U	\$5.95
CY3A	4.000 MHz	HC18/U	\$4.95
CY7A	5.000 MHz	HC18/U	\$4.95
CY12A	10.000 MHz	HC18/U	\$4.95
CY14A	14.31818 MHz	HC18/U	\$4.95
CY19A	18.000 MHz	HC18/U	\$4.95
CY22A	20.000 MHz	HC18/U	\$4.95
CY30B	32.000 MHz	HC18/U	\$4.95

XR-2260KB Kit \$27.95

XR-2260KA Kit \$17.95

WAVEFORM GENERATORS	EXAR	XR-2260CP	XR-2260CP
XR-205	\$8.40	XR-2260CP	\$1.55
XR-2206CP	4.49	XR-2260CP	1.55
XR-2207CP	3.85	XR-2260CP	1.55
STEREO DECODERS	MISCELLANEOUS	XR-2260CP	XR-2260CP
XR-1310CP	\$3.20	XR-2260CP	1.55
XR-1310EP	2.20	XR-2260CP	1.55
XR-1800P	3.20	XR-2260CP	1.55
XR-2567	2.99	XR-2260CP	1.55

## CONNECTORS

### PRINTED CIRCUIT EDGE-CARD

.156 Spacing-Tin-Double Read-Dut  
Bifurcated Contacts — Fits .054 to .070 P.C. Cards

15/30	PINS (Solder Eyelet)	\$1.95
18/36	PINS (Solder Eyelet)	\$2.49
22/44	PINS (Solder Eyelet)	\$2.95
50/100 (.100 Spacing)	PINS (Solder Eyelet)	\$6.95

### 25 PIN-D SUBMINATURE

DB25	PLUG	\$3.25
DB25	SOCKET	\$4.95

## 3 1/2 DIGIT DVM KIT



This 0-2 VDC .05 per cent digital voltmeter features the Motorola 3 1/2 digit DVM chip set. It has a 4" LED display and operates from a single +5V power supply. The unit is provided complete with an injection molded black plastic case complete with Bezel. An optional power supply is available which fits into the same case as the 0-2V DVM allowing 117 VAC operation.

A. 0-2V DVM with Case	\$49.95
B. 5V Power Supply	\$14.95

## VECTOR WIRING PENCIL

Vector Wiring Pencil P173 consists of a hand held featherweight (under one ounce) tool which is used to guide and was insulated wire fed off a self-contained replaceable bobbin onto component leads or terminals installed on pre-punched P Pattern Vectorboard. Connections between the wrapped wire and component leads, pads or terminals are made by soldering. Complete with 250 FT of red wire

\$9.95

### REPLACEMENT WIRE — BOBBINS FOR WIRING PENCIL

W36-3-A-Pkg 3	250 ft. 36 AWG GREEN	\$2.40
W36-3-B-Pkg 3	250 ft. 36 AWG RED	\$2.40
W36-3-C-Pkg 3	250 ft. 36 AWG CLEAR	\$2.40
W36-3-D-Pkg 3	250 ft. 36 AWG BLUE	\$2.40

### 1/16 VECTOR BOARD

Part #	0.1" Hole Spacing	P-Pattern	W	1	2	Up
PE-ENOL-C	64P44 062XAP	450	6.50	1.72	1.54	
	169P44 023XAP	450	1.00	.60	.22	
EPOLY GLASS	64P44 062	450	6.50	2.01	1.86	
	169P44 062	450	8.50	2.56	2.21	
	169P44 062	450	17.00	5.04	4.51	
	169P44 062	850	11.00	9.23	8.26	
EPOLY GLASS COPPER CLAD	169P44 062C1	450	17.00	6.80	6.12	

## HEAT SINKS

205-CB	Beryllium Copper Heat Sink with Black Finish for TO-5	\$ .25
291-36H	Aluminum Heat Sink for TO-220 Transistors & Regulators	\$ .25
680-75A	Black Anodized Aluminum Heat Sink for TO-3	\$1.80

### HEXADECIMAL ENCODER 19-KEY PAD

• 1 - 0	• ABCDEF
• Return Key	• Optional Key (Period)
• Key	

\$10.95 each

### 63 KEY KEYBOARD

This keyboard features 63 unenclosed SPST keys, unswitched in any kind of P.C.B. A very solid molded plastic 13 x 4 base suits most applications

\$19.95

HD165 16 LINE TO FOUR BIT PARALLEL KEYBOARD ENCODER \$7.95

## JOYSTICK

These joysticks feature four potentiometers, that vary resistance proportional to the angle of the stick. Sturdy metal construction with plastic components only at the movable joint. Perfect for electronic games and instrumentation.

\*5K Pots \$6.95

\*100K Pots \$7.95

## MICROPROCESSOR COMPONENTS

8080A CPU	\$19.95	MC6800L 8 Bit MPU	\$35.00
8212 8 Bit Input/Output	4.95	MC6820L Periph. Interface Adapter	15.00
8216 Bi-Directional Bus Driver	6.95	MC6810AP1 128 x 8 Static RAM	6.00
8224 Clock Generator/Driver	12.95	MC6830L7 1024 x 8 Bit ROM	18.00
8228 System Controller - Bus Driver	12.95		

CPU'S	RAM'S	ROM'S
8008 8 Bit CPU	1101 256 x 1 Static	5103 512 x 1 Static
8080 Super 8008	1103 1024 x 1 Dynamic	5105 1024 x 1 Static
8080A Super 8008	2101 256 x 4 Static	5107 1024 x 1 Static
	2102 1024 x 1 Static	5109 1024 x 1 Static
	2107 4096 x 1 Dynamic	5111 256 x 4 Static
	2111 256 x 4 Static	5113 16 x 4 Static
	7010 1024 x 1 MCMOS	5115 256 x 4 Static
	7489 16 x 4 Static	5117 1024 x 1 Static
	7491 256 x 4 Static	5119 256 x 4 Static
	8111 256 x 4 Static	5121 256 x 4 Static
	8599 16 x 4 Static	5123 1024 x 1 Static
	9102 1024 x 1 Static	5125 256 x 4 Static
	74200 256 x 1 Static	5127 1024 x 1 Static
	93421 256 x 1 Static	5129 256 x 4 Static
	MS262 2K x 1 Dynamic	5131 4096 Bit (1024 x 4) Three State
		5133 4096 Bit (1024 x 4) Three State

BIPOLAR PROM SPECIAL	THE MINI-BREADBOARD BUDGET KIT
6330-1 256 Bit (32 x 8) Open Collector	Proto Board 100
6330-2 256 Bit (32 x 8) Three State	Proto Board 101
6330-3 1024 Bit (256 x 4) Open Collector	Proto Board 102
6330-4 1024 Bit (256 x 4) Three State	Proto Board 103
6330-5 2048 Bit (512 x 4) Open Collector	Proto Board 104
6330-6 2048 Bit (512 x 4) Three State	

OT-595	OT-165	OT-125	OT-85	OT-75	OT-358
OT type	OT type	OT type	OT type	OT type	OT type
holes	holes	holes	holes	holes	holes
price	price	price	price	price	price

## GEMINI-68 The Unique Microprocessing System

STAND ALONE CPU BOARD — Has 384 bytes of RAM on board, serial I/O (RS-232 and 20 mA current loop, cycle stealing direct memory access (DMA), built in software — selectable echo-back capability. Part # SA-CPU Board \$279.95	
CPU BOARD — Same as above but only has 128 bytes of RAM on board-used with 8K RAM board listed below Part # Gemini 68 CPU Board \$259.95	
8K RAM BOARD — Uses low power static RAMS, 500ns cycle time, 1.5 Amps Max Part # Gemini 68 RAM Board \$269.95	
8K EPROM BOARD — Uses 5204 EPROMS by AMI or NATIONAL. Shipped with all decode and miscellaneous IC's, except the 5204 EPROMS Part # Gemini 68 EPROM Board \$ 89.95	

NOT A KIT — ALL BOARDS ARE COMPLETELY ASSEMBLED, BURNED-IN AND TESTED. COMES WITH COMPLETE DOCUMENTATION. Allow approximately four weeks for delivery

\$5.00 Minimum Order — U.S. Funds Only Spec Sheets - 25¢ — Send 24¢ Stamp for 1977 Catalog  
California Residents — Add 6% Sales Tax Dealer Discount Available — Request Pricing

**NOW OPEN SATURDAYS**

**James ELECTRONICS**

1021-A HOWARD AVE., SAN CARLOS, CA. 94070  
PHONE ORDERS WELCOME — (415) 592-8097  
All Advertised Prices Good Thru February

## Timeband™

A trademark of Fairchild Camera and Instrument Corporation

## DIGITAL ALARM CLOCK \$16.95

- 24-Hour Alarm
- "DOZE" Button
- 100% Solid State
- Large Red Led Display (.8" high)
- AM/PM Indicator
- Seconds Display at touch of button
- SPECIFY BLACK OR IVORY



## DIGITAL WATCHES

Ladies Watch	EXELAR Mens Watch
• 6 Function	• 5 Function
• Bezel Styling	• Quartz Crystal
• 1 Year Guarantee	• Black Leather Band
• Power Source is 1 prec. V DC Battery 00GP	• Model 900
• Specify Gold or Chrome	• Manufacturer Guarantee
	• Specify Gold or Chrome

\$59.95

\$25.00

## 5 FUNCTION ELECTRONIC CALCULATOR HADDOIN MODEL BP

FEATURES:	\$8.95
• 8 Digit Display	
• 5 Functions consists of addition, subtraction, multiplication, division, percentage, with constant on all functions, with full lighting decimal point	
• Power source is 1 prec. V DC Battery 00GP	
• Black superfine grained finish plastic cabinet	

## DIGITAL STOPWATCH

• Bright 6 Digit LED Display	
• Times to 99 minutes 59.99 seconds	
• Crystal Controlled Time Base	
• Three Stopwatches in One	
• Times, Single Event — Split & Taper	
• Size 4.5 x 2.15 x .90 (.43 ounces)	
• Uses 3 Penlite Cells	

Kit — \$39.95  
Assembled — \$49.95  
Heavy Duty Carry Case \$5.95

## DIGITAL QUARTZ CAR CLOCK

Kit: \$29.95	
Assembled: \$39.95	
CASE ONLY (includes hardware, mounting bracket and bezel): \$5.95	

## JE700 CLOCK

The JE700 is a low cost digital clock but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6" x 2 1/2" x 1 1/2". It utilizes a MAN72 high brightness readout and the MM5314 clock chip

\$17.95

115 VAC	
This large digit clock (6" hours & minutes, 3 seconds) features the MM5314 clock chip. It operates from 117 VAC, and will operate in either a 12 or 24 hour mode. The clock is complete with a walnut grain case and has fast set, slow set, and hold time set features	

## JE500 KIT - ALL COMPONENTS & CASE \$34.95 WIRED & ASSEMBLED \$39.95

DIGITAL CLOCK KIT — 3 1/2" INCH DIGITS	4 DIGIT KIT \$49.95	4 DIGIT ASSEMBLED \$59.95
6 DIGIT KIT \$69.95	6 DIGIT ASSEMBLED \$79.95	

This clock features big 3 1/2" high digits for viewing in offices, auditoriums, etc. Each digit is formed by 31 bright 0.2" LEDs. The clock operates from 117 VAC, has either 12 or 24 hr. operation. The 6 digit version is 27" x 3 1/2" x 1 1/2" and the 4 digit is 18" x 3 1/2" x 1 1/2". Kits come complete with all components, case and transformer. Specify 12 or 24 Hour When Ordering

## JE803 PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states: these symbols (H) 1 (LOW) 0 (PULSE) P. The Probe can detect high frequency pulses to 15 MHz. It can't be used at MOS levels or circuit damage will result

\$9.95 Per Kit printed circuit board

## T-L 5V 1A Supply

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only

\$9.95 Per Kit

7400N TTL					
SN7400N	16	SN7455A	25		
SN7401N	16	SN7470N	22	SN74154A	1.00
SN7402N	21	SN7472N	45	SN74155N	90
SN7403N	16	SN7473N	39	SN74156N	90
SN7404N	16	SN7473N	37	SN74157N	90
SN7405A	24	SN7474N	32	SN74160N	1.25
SN7406N	20	SN7475N	30	SN74161N	90
SN7407N	29	SN7476N	32	SN74162N	90
SN7408N	25	SN7479N	50	SN74164A	1.10
SN7409N	25	SN7480N	50	SN74165N	1.10
SN7410N	18	SN7482N	90	SN74166N	1.25
SN7411N	30	SN7483N	70	SN74167N	5.50
SN7412N	33	SN7485N	39	SN74170N	7.00
SN7413N	45	SN7486N	39	SN74172N	8.90
SN7414N	79	SN7488N	3.50	SN74173N	1.50
SN7415N	35	SN7489N	2.39	SN74174N	1.25
SN7416N	35	SN7490N	45	SN74175N	1.25
SN7417N	35	SN7491N	75	SN74176N	90
SN7420N	21	SN7492N	49	SN74177N	90
SN7421N	33	SN7492N	49	SN74180N	90
SN7422N	49	SN7493N	49	SN74181N	2.49
SN7423N	37	SN7494N	49	SN74182N	85
SN7424N	29	SN7495N	79	SN74184N	1.95
SN7425N	29	SN7496N	89	SN74185N	2.25
SN7426N	29	SN7497N	400	SN74186N	15.00
SN7427N	42	SN7498N	39	SN74187N	6.00
SN7428N	29	SN74101N	39	SN74188N	3.50
SN7429N	29	SN74117N	39	SN74190N	1.10
SN7430N	26	SN74122N	39	SN74191N	1.25
SN7431N	26	SN74122N	39	SN74192N	1.25
SN7432N	26	SN74127N	39	SN74193N	1.25
SN7433N	26	SN74127N	39	SN74194N	1.25
SN7434N	26	SN74127N	39	SN74195N	1.25
SN7435N	25	SN74129N	60	SN74196N	1.25
SN7436N	26	SN74129N	60	SN74197N	1.25
SN7437N	26	SN74132N	1.09	SN74198N	1.75
SN7438N	26	SN74132N	1.09	SN74199N	1.75
SN7439N	26	SN74133N	1.15	SN74200N	1.75
SN7440N	26	SN74141N	1.15	SN74201N	1.75
SN7441N	75	SN74142N	4.00	SN74202N	1.75
SN7442N	75	SN74143N	4.50	SN74203N	1.75
SN7443N	75	SN74144N	4.50	SN74204N	1.75
SN7444N	75	SN74145N	4.50	SN74205N	1.75
SN7445N	75	SN74146N	1.15	SN74206N	1.75
SN7446N	69	SN74147N	1.15	SN74207N	1.75
SN7447N	69	SN74148N	2.35	SN74208N	1.75
SN7448N	79	SN74149N	2.35	SN74209N	1.75
SN7449N	26	SN74149N	2.00	SN74210N	1.75
SN7450N	26	SN74150N	1.00	SN74211N	1.75
SN7451N	26	SN74151N	5.00	SN74212N	1.75
SN7452N	26	SN74152N	5.00	SN74213N	1.75
SN7453N	26	SN74153N	89	SN74214N	1.75
SN7454N	26	SN74153N	89	SN74215N	1.75

## FAIRCHILD TECHNOLOGY KITS FAIRCHILD



- Complete Specifications on back of each kit
- Packaged for WALL DISPLAY APPEARANCE
- Dealer's Inquiries Invited — Price List Available

### FAIRCHILD DIGITS

FTK0001	0.5" High Common Cathode Digit	\$1.00
FTK0002	0.5" High Common Anode Digit	1.00
FTK0003	357" High Common Cathode Digit	1.25
FTK0004	0.8" High Common Cathode Digit	2.00
FTK0005	0.8" High Common Anode Digit	2.00

FTK0010	12 Hour 3 1/2 Digit Clock Display	7.00
FTK0011	24 Hour 4 Digit Clock Display	8.00

FTK0020	10 Red LED	1.00
FTK0021	5 Mixed Color LED Lamps	1.00
FTK0022	10 LED Mounting Lamps	1.00
FTK0023	5 Three Piece LED Mounting Assemblies	1.00

FTK0030	5 Flat Lens Photo Transistors	1.00
FTK0031	5 Round Lens Photo Transistors	1.00
FTK0032	3 Flat Lens Photo Darlington	1.00
FTK0033	3 Round Lens Photo Darlington	1.00

### PHOTO ARRAYS

FTK0040	9 Element 1/2" Photo Array	16.00
FTK0041	12 Element 1/2" Photo Array	24.00
FTK0042	Reflective Photo Array	4.00

### COUPLERS

FTK0050	3 General Purpose Dipo Couplers	1.00
FTK0051	Darlington Dipo Coupler	1.00

### MOS CLOCK CIRCUITS

FTK0400	Digital Clock Calendar with BCD Outputs (FCM7001)	7.00
FTK0401	Digital Clock Calendar with BCD Outputs (FCM7002)	7.00
FTK0402	Direct Drive Digital Clock Circuit with AC Output (FCM3817A)	5.00
FTK0403	Direct Drive Digital Clock Circuit with AC Output (FCM3817B)	5.00
FTK0405	Direct Drive Digital Clock Calendar Circuit (FCM7015)	6.00

### KITS

FTK0015	Adjustable Clock Kit	40.00
---------	----------------------	-------

## WIRE WRAP CENTER

**CORDLESS HOBBY-WRAP TOOL-BW-630**

- Battery Operated (Size C)
- Weighs Only 11 Ounces
- Wraps 30 AWG Wire onto Standard DIP Sockets (.025 inch)
- Complete with built-in bit and sleeve

**\$34.95**

**WIRE-WRAP KIT — WK-2-W**

**WRAP • STRIP • UNWRAP**

- Tool for 30 AWG Wire
- Roll of 50 ft. White 30 AWG Wire
- 50 pcs. each 1", 2", 3" & 4" lengths — pre-stripped white wire

**\$11.95**

**WIRE WRAP TOOL WSU-30**

**WRAP • STRIP • UNWRAP — \$5.95**

**WIRE WRAP WIRE — 30 AWG**

25 ft. min. \$1.25 50 ft. \$1.95 100 ft. \$2.95 1000 ft. \$15.00

**SPECIFY COLOR — White - Yellow - Red - Green - Blue - Black**

**THUMBWHEEL SWITCHES**

**THUMBWHEEL SWITCH ONLY**

Ordering: Order desired switch or switches and add necessary accessories for your particular application.

**Series SP Front Mount Assembly**

SP 12 - Single Pole 10 Position - \$2.50  
SP 12 - 10 Position BCD only - 3.00  
SP 21 - 21 Position BCD only - 3.00

**Series SR Rear Mount Assembly**

SR 12 - Single Pole 10 Position - \$2.50  
SR 12 - 10 Position BCD only - 3.00  
SR 21 - 21 Position BCD only - 3.00

**ACCESSORIES**

Part No. Description Price

SP EP - End Plate (Pair) - .40  
SP DP - Driver Plate (each) - .40  
SR EP - End Plate (Pair) - .40  
SR DP - Driver Plate (each) - .40  
SR BB - Blank Body (each) - .40  
SR HB - Half Body (each) - .40

**DIP SWITCH**

These switches feature seven SPST side switches — a molded dip. They are ideally suited for microprocessor applications.

**\$1.95**

TYPE	VOLTS	W	PRICE
1N4751A	5.1	400m	1.00
1N4752	5.6	400m	1.00
1N4753	6.2	400m	1.00
1N4754	6.8	400m	1.00
1N4755	7.5	400m	1.00
1N4756	8.2	400m	1.00
1N4757	9.1	400m	1.00
1N4758	10	400m	1.00
1N4759	11	400m	1.00
1N4760	12	400m	1.00
1N4761	13	400m	1.00
1N4762	15	400m	1.00
1N4763	18	400m	1.00
1N4764	20	400m	1.00
1N4765	22	400m	1.00
1N4766	24	400m	1.00
1N4767	27	400m	1.00
1N4768	30	400m	1.00
1N4769	33	400m	1.00
1N4770	36	400m	1.00
1N4771	39	400m	1.00
1N4772	43	400m	1.00
1N4773	47	400m	1.00
1N4774	51	400m	1.00
1N4775	56	400m	1.00
1N4776	62	400m	1.00
1N4777	68	400m	1.00
1N4778	75	400m	1.00
1N4779	82	400m	1.00
1N4780	91	400m	1.00
1N4781	100	400m	1.00
1N4782	110	400m	1.00
1N4783	120	400m	1.00
1N4784	130	400m	1.00
1N4785	150	400m	1.00
1N4786	180	400m	1.00
1N4787	200	400m	1.00
1N4788	220	400m	1.00
1N4789	240	400m	1.00
1N4790	270	400m	1.00
1N4791	300	400m	1.00
1N4792	330	400m	1.00
1N4793	360	400m	1.00
1N4794	390	400m	1.00
1N4795	430	400m	1.00
1N4796	470	400m	1.00
1N4797	510	400m	1.00
1N4798	560	400m	1.00
1N4799	620	400m	1.00
1N4800	680	400m	1.00
1N4801	750	400m	1.00
1N4802	820	400m	1.00
1N4803	910	400m	1.00
1N4804	1000	400m	1.00
1N4805	1100	400m	1.00
1N4806	1200	400m	1.00
1N4807	1300	400m	1.00
1N4808	1500	400m	1.00
1N4809	1800	400m	1.00
1N4810	2000	400m	1.00
1N4811	2200	400m	1.00
1N4812	2400	400m	1.00
1N4813	2700	400m	1.00
1N4814	3000	400m	1.00
1N4815	3300	400m	1.00
1N4816	3600	400m	1.00
1N4817	3900	400m	1.00
1N4818	4300	400m	1.00
1N4819	4700	400m	1.00
1N4820	5100	400m	1.00
1N4821	5600	400m	1.00
1N4822	6200	400m	1.00
1N4823	6800	400m	1.00
1N4824	7500	400m	1.00
1N4825	8200	400m	1.00
1N4826	9100	400m	1.00
1N4827	10000	400m	1.00
1N4828	11000	400m	1.00
1N4829	12000	400m	1.00
1N4830	13000	400m	1.00
1N4831	15000	400m	1.00
1N4832	18000	400m	1.00
1N4833	20000	400m	1.00
1N4834	22000	400m	1.00
1N4835	24000	400m	1.00
1N4836	27000	400m	1.00
1N4837	30000	400m	1.00
1N4838	33000	400m	1.00
1N4839	36000	400m	1.00
1N4840	39000	400m	1.00
1N4841	43000	400m	1.00
1N4842	47000	400m	1.00
1N4843	51000	400m	1.00
1N4844	56000	400m	1.00
1N4845	62000	400m	1.00
1N4846	68000	400m	1.00
1N4847	75000	400m	1.00
1N4848	82000	400m	1.00
1N4849	91000	400m	1.00
1N4850	100000	400m	1.00

**SCR AND FW BRIDGE RECTIFIERS**

C360 15A @ 400V SCR \$1.95  
C361 15A @ 200V SCR \$1.95  
C362 15A @ 100V SCR \$1.95  
C363 15A @ 50V SCR \$1.95  
C364 15A @ 25V SCR \$1.95  
C365 15A @ 12.5V SCR \$1.95  
C366 15A @ 6.25V SCR \$1.95  
C367 15A @ 3.125V SCR \$1.95  
C368 15A @ 1.56V SCR \$1.95  
C369 15A @ 0.78V SCR \$1.95  
C370 15A @ 0.39V SCR \$1.95  
C371 15A @ 0.19V SCR \$1.95  
C372 15A @ 0.09V SCR \$1.95  
C373 15A @ 0.04V SCR \$1.95  
C374 15A @ 0.02V SCR \$1.95  
C375 15A @ 0.01V SCR \$1.95  
C376 15A @ 0.005V SCR \$1.95  
C377 15A @ 0.002V SCR \$1.95  
C378 15A @ 0.001V SCR \$1.95  
C379 15A @ 0.0005V SCR \$1.95  
C380 15A @ 0.0002V SCR \$1.95  
C381 15A @ 0.0001V SCR \$1.95  
C382 15A @ 0.00005V SCR \$1.95  
C383 15A @ 0.00002V SCR \$1.95  
C384 15A @ 0.00001V SCR \$1.95  
C385 15A @ 0.000005V SCR \$1.95  
C386 15A @ 0.000002V SCR \$1.95  
C387 15A @ 0.000001V SCR \$1.95  
C388 15A @ 0.0000005V SCR \$1.95  
C389 15A @ 0.0000002V SCR \$1.95  
C390 15A @ 0.0000001V SCR \$1.95  
C391 15A @ 0.00000005V SCR \$1.95  
C392 15A @ 0.00000002V SCR \$1.95  
C393 15A @ 0.00000001V SCR \$1.95  
C394 15A @ 0.000000005V SCR \$1.95  
C395 15A @ 0.000000002V SCR \$1.95  
C396 15A @ 0.000000001V SCR \$1.95  
C397 15A @ 0.0000000005V SCR \$1.95  
C398 15A @ 0.0000000002V SCR \$1.95  
C399 15A @ 0.0000000001V SCR \$1.95  
C400 15A @ 0.00000000005V SCR \$1.95  
C401 15A @ 0.00000000002V SCR \$1.95  
C402 15A @ 0.00000000001V SCR \$1.95  
C403 15A @ 0.000000000005V SCR \$1.95  
C404 15A @ 0.000000000002V SCR \$1.95  
C405 15A @ 0.000000000001V SCR \$1.95  
C406 15A @ 0.0000000000005V SCR \$1.95  
C407 15A @ 0.0000000000002V SCR \$1.95  
C408 15A @ 0.0000000000001V SCR \$1.95  
C409 15A @ 0.00000000000005V SCR \$1.95  
C410 15A @ 0.00000000000002V SCR \$1.95  
C411 15A @ 0.00000000000001V SCR \$1.95  
C412 15A @ 0.000000000000005V SCR \$1.95  
C413 15A @ 0.000000000000002V SCR \$1.95  
C414 15A @ 0.000000000000001V SCR \$1.95  
C415 15A @ 0.0000000000000005V SCR \$1.95  
C416 15A @ 0.0000000000000002V SCR \$1.95  
C417 15A @ 0.0000000000000001V SCR \$1.95  
C418 15A @ 0.00000000000000005V SCR \$1.95  
C419 15A @ 0.00000000000000002V SCR \$1.95  
C420 15A @ 0.00000000000000001V SCR \$1.95  
C421 15A @ 0.000000000000000005V SCR \$1.95  
C422 15A @ 0.000000000000000002V SCR \$1.95  
C423 15A @ 0.000000000000000001V SCR \$1.95  
C424 15A @ 0.0000000000000000005V SCR \$1.95  
C425 15A @ 0.0000000000000000002V SCR \$1.95  
C426 15A @ 0.0000000000000000001V SCR \$1.95  
C427 15A @ 0.00000000000000000005V SCR \$1.95  
C428 15A @ 0.00000000000000000002V SCR \$1.95  
C429 15A @ 0.00000000000000000001V SCR \$1.95  
C430 15A @ 0.000000000000000000005V SCR \$1.95  
C431 15A @ 0.000000000000000000002V SCR \$1.95  
C432 15A @ 0.000000000000000000001V SCR \$1.95  
C433 15A @ 0.0000000000000000000005V SCR \$1.95  
C434 15A @ 0.0000000000000000000002V SCR \$1.95  
C435 15A @ 0.0000000000000000000001V SCR \$1.95  
C436 15A @ 0.00000000000000000000005V SCR \$1.95  
C437 15A @ 0.00000000000000000000002V SCR \$1.95  
C438 15A @ 0.00000000000000000000001V SCR \$1.95  
C439 15A @ 0.000000000000000000000005V SCR \$1.95  
C440 15A @ 0.000000000000000000000002V SCR \$1.95  
C441 15A @ 0.000000000000000000000001V SCR \$1.95  
C442 15A @ 0.0000000000000000000000005V SCR \$1.95  
C443 15A @ 0.0000000000000000000000002V SCR \$1.95  
C444 15A @ 0.0000000000000000000000001V SCR \$1.95  
C445 15A @ 0.00000000000000000000000005V SCR \$1.95  
C446 15A @

# GODBOUT

MAIL GODBOUT ELECTRONICS  
BOX 2253, OAKLAND, CALIF. 94614

TERMS add 50¢ to orders under \$10. No COD. Cal res add tax. Mastercharge/BankAmericard call (415) 582-0656, 24 hours. SEND FOR OUR FLYER!

# SEND FOR OUR FREE FLYER

## LIMITED QUANTITY SPECIALS

ALL ITEMS BELOW WHILE THEY LAST AND ARE SUBJECT TO PRIOR SALE.

**LED MOUNTING GIZMO** --- press fits into 1/8" panel or glue to thinner metal. Fits standard size LED (no minis or jumbos)...10/\$1



**SUBMINI PC MOUNT SLIDE SWITCH**  
Center off SPDT. Only 5/8" by 1/4" with pins on 1/8" centers. A VERY GOOD BUY.....10/\$1



**THE REAL THING FROM MONSANTO:**  
MAX-10A seven segment readout with bar, not dot, LEDs. Limit 8 to a customer. Digit is .27" high.....95¢ each



The following are house or military numbered ICs, and include pinout/data---  
988 ONE-SHOT similar to 74121.....4/\$1.00

SN14058 DUAL 4 INPUT AND GATE with open collector or totem pole output.....7/\$1.00

C4347 TRIPLE 3 INPUT NOR GATE house-numbered SP370A.....6/\$1.00

7472 FLIP FLOP house numbered.....5/\$1.00

INTEL 3101-4 BIPOLAR 4X16 RAM super fast, same pinout as 74S189. TTL, single 5 Volt supply.....\$1.50 each

75325.....3/\$2.00

SILICON SIGNAL/SWITCHING DIODES.....35/\$2.00

## WE NOW DISTRIBUTE KNOWLEDGE

We are happy to carry the Adam Osborne & Associates series of books on microcomputers, as lucid and complete a treatment of the subject as we've seen to date. All books postpaid in the USA; set of all three books available for only \$25.00.

- VOL 1 "An Introduction to Microcomputers"** Order book #2001. Gives the basics of up based systems.....\$7.50
- VOL 2 This recent addition gives up-to-date information on microprocessors** --- equivalent to hundreds of pages of data sheets. Order book #3001.....\$12.50
- VOL 3 "8080 Programming for Logic Design"** #4001 \$7.50

## Multi Meter

An outstanding buy... 6 DC Volt ranges, 3 DC current, 5 AC Volts, 2 ohms, and dB scale too. 50 uA movement; plus "off" position damps meter for safe transportation. Includes 34 inch test leads but less 1 AA battery. Small--- a compact 5 1/2" x 3 1/4" x 1 5/8".

Please add \$1 postage and handling.

## \$14.99

CIRCLE NO. 32 ON FREE INFORMATION CARD

# For faster service

# USE ZIP CODE


# on all mail

P.O. Box 4430C Santa Clara, CA 95054  
(408) 988-1640

**Same day shipment.** First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

### INTEGRATED CIRCUITS

7400TTL	SN741574N	59	LM741CH	35	CD4025	25	74C006	1.50
SN7400N	SN741575N	75	LM741N	25	CD4026	3.85	74C0025	10.50
SN7402N	SN741580N	1.10	LM7413N	82	CD4027	55	74C0026	10.50
SN7404N	SN741581N	1.10	LM7414N	1.50	CD4029	1.70	74C0027	12.00
SN7410N	SN741585N	1.89	LM741300N	35	CD4040	1.35	8095	75
SN7414N	SN741587N	1.89	LM741300N	35	CD4041	1.50	8096	75
SN7414N	SN741587N	1.89	LM741300N	35	CD4042	2.00	8097	75
SN7420N	SN741587N	2.05	LM741300N	35	CD4043	2.00	8098	75
SN7420N	SN741587N	2.05	LM741300N	35	CD4044	2.00	8099	75
SN7420N	SN741587N	2.05	LM741300N	35	CD4045	2.00	8100	75
SN7420N	SN741587N	2.05	LM741300N	35	CD4146	2.00	8201	75
SN7420N	SN741587N	2.05						

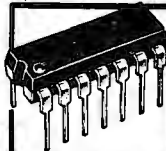

# DIGI-KEY CORPORATION

Quality Electronic Components  
Double-Digit Discounts  
Save You Even More

2102-1	8080A	LM3909
\$1.99	\$24.95	69¢

MA1002A 12 Hour (AM-PM) Version ..... \$10.50  
MA1002C 24 Hour Version ..... \$10.50

0.5" High LED Digits



Special transformer and 6 switches, when ordered with module add \$3.45.

## Hobby-Wrap-30 \$5.95

Strips, Wraps and Unwraps 30 ga. wire on standard wire wrapping pins



# NATIONAL SEMICONDUCTOR CLOCK MODULES



MA1010A 12 Hour (AM-PM) Version ... \$13.00  
MA1010C 24 Hour Version ..... \$13.00

0.84" High LED Digits



Special transformer and 6 switches, when ordered with module add \$3.45



## MA1002 & MA1010 Series Electronic Clock Modules

The MA1002 & MA1010 Series Electronic Clock Modules are assembled and pretested modules which combine a monolithic MOS-LSI integrated clock circuit, 4-digit LED display, power supply and other associated discrete components on a single printed circuit board to form a complete electronic clock movement. The user need only a transformer and switches to construct a digital clock for application in clock-radios, alarm or instrument panel clocks. Time-keeping may be from 50 or 60 Hz inputs and 12 or 24 hour display formats may be chosen. Direct LED drive eliminates RF interference. Time setting is made easy through use of "Fast" and "Slow" scanning controls.

The MA1002A and MA1010A have a 12 hour display with an AM and PM indicator. The MA1002C and MA1010C have a 24 hour display.

Features include alarm "on" and "PM" indicators, "sleep" and "snooze" timers and variable brightness control capability. The modules are extremely compact, the MA1002 measuring 1.375" by 3.05", the MA1010 measuring 1.75" by 3.75". This small size is achieved by bonding the I.C. to the back of the circuit board.

It is highly recommended that the transformer be obtained with the clock module as it is a special dual secondary type not otherwise readily available.

Double Digit Discounts Save You Even More!

## ACE201-K \$24.95

1,032 SOLDERLESS PLUG-IN THE POINTS  
CAPACITY: UP TO 12 14-PIN DIP'S  
TWO 5-way binding posts  
Size: 4-9/16" by 7-1/2"  
Kit form



## WIRE WRAPPING WIRE

Red or Black Kynar insulated pre-cut and stripped 30 or wire  
1" of insulation is removed from each end

Insulation Length	No. in Pkg.	Price per Pkg.
1.0"	100	\$2.50
2.0"	100	\$2.60
2.5"	100	\$2.65
3.0"	100	\$2.75
3.5"	100	\$2.80
4.0"	100	\$2.85
4.5"	100	\$2.90
5.0"	100	\$3.00
6.0"	50	\$1.70
7.0"	50	\$1.80
8.0"	50	\$1.90
9.0"	50	\$2.00
10.0"	50	\$2.10
15.0"	50	\$2.50

## SLIDE SWITCHES

Single Pole Single Throw

.15	1.20/10	10.00/C
.23	2.00/10	19.00/C

## BATTERY HOLDERS

1-AA ... 26¢
2-AA ... 42¢
1-C ... 35¢
2-C ... 42¢
1-D ... 35¢
2-D ... 42¢

## BISHOP GRAPHICS Printed Circuit Drafting

Aids are now available from Digi-Key

## RADIAL ELECTROLYTICS

47/50V... .08	.65/10	22/50V... .12	1.00/10	330/25V... .23	1.86/10
1/50V... .08	.65/10	100/50V... .09	.75/10	470/10V... .21	1.71/10
2.2/50V... .08	.65/10	100/10V... .10	.77/10	470/16V... .23	1.81/10
3.3/50V... .08	.65/10	100/16V... .11	.85/10	470/25V... .29	2.35/10
4.7/50V... .08	.65/10	100/25V... .13	1.10/10	1000/10V... .24	1.96/10
4.7/25V... .11	.68/10	100/50V... .21	1.11/10	2200/25V... .29	2.35/10
10/16V... .08	.65/10	220/10V... .13	1.08/10	1000/25V... .42	3.33/10
10/25V... .08	.65/10	220/16V... .15	1.16/10	2200/10V... .42	3.33/10
10/50V... .10	.75/10	220/25V... .21	1.71/10	2200/16V... .54	4.30/10
22/16V... .08	.65/10	220/50V... .29	2.35/10	2200/25V... .58	4.67/10
22/25V... .09	.70/10	330/10V... .15	1.16/10	3300/16V... .89	7.14/10
		330/16V... .21	1.66/10		

## AXIAL ELECTROLYTICS

47/10V... .11	.90/10	33/25V... .14	1.15/10	330/16V... .29	2.35/10
1/30V... .11	.90/10	33/50V... .19	1.52/10	330/25V... .32	2.54/10
3.3/35V... .12	.95/10	47/16V... .14	1.15/10	470/16V... .32	2.55/10
3.3/50V... .12	1.00/10	47/25V... .17	1.30/10	470/25V... .38	2.75/10
4.7/25V... .11	.90/10	47/50V... .21	1.71/10	1000/10V... .33	2.65/10
4.7/35V... .12	.95/10	100/10V... .14	1.13/10	1000/16V... .39	3.15/10
4.7/50V... .12	1.00/10	100/16V... .17	1.30/10	1000/25V... .56	4.50/10
10/25V... .12	1.00/10	100/50V... .20	1.55/10	2200/10V... .30	2.94/10
10/50V... .14	1.15/10	100/50V... .29	2.30/10	2200/16V... .42	4.95/10
22/16V... .12	1.00/10	220/10V... .18	1.42/10	2200/25V... .75	6.36/10
22/25V... .13	1.05/10	220/16V... .20	1.55/10	3300/16V... .95	7.68/10
22/50V... .17	1.32/10	220/50V... .29	2.35/10	4700/16V... .09	8.10/10
33/16V... .12	1.00/10	220/50V... .40	3.23/10	10000/10V... .115	9.97/10
		330/10V... .14	1.16/10		

## INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS

7400 .21	7476 .32	74181 2.15	4012 .23	4520 1.14
7401 .21	7480 .70	74182 .79	4013 .40	4527 1.88
7402 .21	7482 .70	74184 2.19	4014 .96	4528 .88
7403 .21	7483 .70	74185 2.19	4015 .96	4585 1.23
7404 .21	7485 .89	74188 .30	4016 .40	2102-1 .79
7405 .21	7486 .70	74189 .88	4017 1.05	8080A 24.95
7406 .25	7489 2.19	74190 1.23	4018 1.05	CA3046 .75
7407 .25	7490 .44	74191 1.23	4019 .23	LM211N 1.25
7408 .21	7491 .70	74192 .88	4020 1.14	LM399K 1.80
7409 .21	7492 .44	74193 .88	4021 1.14	LM399K 1.80
7410 .21	7493 .44	74194 .88	4022 .96	LM340T-5 1.25
7411 .21	7494 .70	74195 .88	4023 .23	LM340T-6 1.25
7412 .21	7495 .70	74196 .88	4024 .84	LM340T-8 1.25
7413 .25	7496 .70	74197 .88	4025 .23	LM340T-12 1.25
7414 .89	74100 1.28	74198 1.49	4026 1.68	LM340T-15 1.25
7416 .25	74107 .30	74199 1.49	4027 .40	LM340T-18 1.25
7417 .25	74109 .33	74201 1.49	4028 .89	LM340T-24 1.25
7418 .21	74121 .35	74202 .88	4029 1.14	LM3909N .88
7419 .21	74122 .44	74203 .88	4030 .23	LM3909N .88
7420 .25	74123 .61	74204 .88	4031 1.51	MC1456V 1.00
7421 .35	74125 .40	74205 .88	4032 3.50	MC1458V .53
7422 .35	74126 .80	74206 .88	4033 1.14	MC3302P 1.15
7423 .35	74127 .70	74207 .88	4040 1.14	NE5301 2.04
7424 .35	74128 .80	74208 .88	4041 .79	NE555V .48
7425 .35	74129 .80	74209 .88	4042 .79	NE555V .48
7426 .35	74130 .80	74210 .88	4043 .79	NE568A .88
7427 .35	74131 .80	74211 .88	4044 .79	NE568B .88
7428 .35	74132 .80	74212 .88	4045 .79	NE568C .88
7429 .35	74133 .80	74213 .88	4046 .79	NE568D .88
7430 .35	74134 .80	74214 .88	4047 .79	NE568E .88
7431 .35	74135 .80	74215 .88	4048 .79	NE568F .88
7432 .35	74136 .80	74216 .88	4049 .79	NE568G .88
7433 .35	74137 .80	74217 .88	4050 .79	NE568H .88
7434 .35	74138 .80	74218 .88	4051 .79	NE568I .88
7435 .35	74139 .80	74219 .88	4052 .79	NE568J .88
7436 .35	74140 .80	74220 .88	4053 .79	NE568K .88
7437 .35	74141 .80	74221 .88	4054 .79	NE568L .88
7438 .35	74142 .80	74222 .88	4055 .79	NE568M .88
7439 .35	74143 .80	74223 .88	4056 .79	NE568N .88
7440 .35	74144 .80	74224 .88	4057 .79	NE568O .88
7441 .35	74145 .80	74225 .88	4058 .79	NE568P .88
7442 .35	74146 .80	74226 .88	4059 .79	NE568Q .88
7443 .35	74147 .80	74227 .88	4060 .79	NE568R .88
7444 .35	74148 .80	74228 .88	4061 .79	NE568S .88
7445 .35	74149 .80	74229 .88	4062 .79	NE568T .88
7446 .35	74150 .80	74230 .88	4063 .79	NE568U .88
7447 .35	74151 .80	74231 .88	4064 .79	NE568V .88
7448 .35	74152 .80	74232 .88	4065 .79	NE568W .88
7449 .35	74153 .80	74233 .88	4066 .79	NE568X .88
7450 .35	74154 .80	74234 .88	4067 .79	NE568Y .88
7451 .35	74155 .80	74235 .88	4068 .79	NE568Z .88
7452 .35	74156 .80	74236 .88	4069 .79	NE568A .88
7453 .35	74157 .80	74237 .88	4070 .79	NE568B .88
7454 .35	74158 .80	74238 .88	4071 .79	NE568C .88
7455 .35	74159 .80	74239 .88	4072 .79	NE568D .88
7456 .35	74160 .80	74240 .88	4073 .79	NE568E .88
7457 .35	74161 .80	74241 .88	4074 .79	NE568F .88
7458 .35	74162 .80	74242 .88	4075 .79	NE568G .88
7459 .35	74163 .80	74243 .88	4076 .79	NE568H .88
7460 .35	74164 .80	74244 .88	4077 .79	NE568I .88
7461 .35	74165 .80	74245 .88	4078 .79	NE568J .88
7462 .35	74166 .80	74246 .88	4079 .79	NE568K .88
7463 .35	74167 .80	74247 .88	4080 .79	NE568L .88
7464 .35	74168 .80	74248 .88	4081 .79	NE568M .88
7465 .35	74169 .80	74249 .88	4082 .79	NE568N .88
7466 .35	74170 .80	74250 .88	4083 .79	NE568O .88
7467 .35	74171 .80	74251 .88	4084 .79	NE568P .88
7468 .35	74172 .80	74252 .88	4085 .79	NE568Q .88
7469 .35	74173 .80	74253 .88	4086 .79	NE568R .88
7470 .35	74174 .80	74254 .88	4087 .79	NE568S .88
7471 .35	74175 .80	74255 .88	4088 .79	NE568T .88
7472 .35	74176 .80	74256 .88	4089 .79	NE568U .88
7473 .35	74177 .80	74257 .88	4090 .79	NE568V .88
7474 .35	74178 .80	74258 .88	4091 .79	NE568W .88
7475 .35	74179 .80	74259 .88	4092 .79	NE568X .88
7476 .35	74180 .80	74260 .88	4093 .79	NE568Y .88
7477 .35	74181 .80	74261 .88	4094 .79	NE568Z .88
7478 .35	74182 .80	74262 .88	4095 .79	NE568A .88
7479 .35	74183 .80	74263 .88	4096 .79	NE568B .88
7480 .35	74184 .80	74264 .88	4097 .79	NE568C .88
7481 .35	74185 .80	74265 .88	4098 .79	NE568D .88
7482 .35	74186 .80	74266 .88	4099 .79	NE568E .88
7483 .35	74187 .80	74267 .88	4100 .79	NE568F .88
7484 .35	74188 .80	74268 .88	4101 .79	NE568G .88
7485 .35	74189 .80	74269 .88	4102 .79	NE568H .88
7486 .35	74190 .80	74270 .88	4103 .79	NE568I .88
7487 .35	74191 .80	74271 .88	4104 .79	NE568J .88
7488 .35	74192 .80	74272 .88	4105 .79	NE568K .88
7489 .35	74193 .80	74273 .88	4106 .79	NE568L .88
7490 .35	74194 .80	74274 .88	4107 .79	NE568M .88
7491 .35	74195 .80	74275 .88	4108 .79	NE568N .88
7492 .35	74196 .80	74276 .88	4109 .79	NE568O .88
7493 .35	74197 .80	74277 .88	4110 .79	NE568P .88
7494 .35	74198 .80	74278 .88	4111 .79	NE568Q .88
7495 .35	74199 .80	74279 .88	4112 .79	NE568R .88
7496 .35	74200 .80	74280 .88	4113 .79	NE568S .88
7497 .35	74201 .80	74281 .88	4114 .79	NE568T .88
7498 .35	74202 .80	74282 .88	4115 .79	NE568U .88
7499 .35	74203 .80	74283 .88	4116 .79	NE568V .88
7500 .35	74204 .80	74284 .88	4117 .79	NE568W .88

## WIRE WRAPPING WIRE IN BULK

# AMAZING & HARD-TO-FIND SCIENCE BUYS! ALTERNATE ENERGY • SPACE AGE • HOBBIES

## NEW WIDE FIELD TELESCOPE

Enjoy clearest, brightest, most spectacular wide angle views of stars, moon, comets with our unique, easy-to-use portable 4 1/4", f/4 Newtonian reflector. Only 17", 10 lb.! Take it anywhere.

No. 2001AV \$149.95 Ppd.

There is no other telescope like it.

## SAVE 50%! 8 x 20 MONOCULAR

Top quality Spy Scope, a \$30 value, now \$14.95! Special purchase saves you 50%. 100% coated optics; 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove box.

No. 1568AV...\$14.95 Ppd.

## NASA-CHOSEN FOR APOLLO/SOYUZ

The Astronauts used this super 20X60 binocular (modified) to view Earth! Big 60 mm objective lenses; 173 ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics, more!

(9 1/4 x 8 1/2"; 47.5 oz.)

No. 1556AV.....\$99.95 Ppd.

## GIANT MAGNET, LITTLE PRICE!

Tie a line to our over-150 lb.-lift ceramic magnet and haul up treasure from the sea. 4 ceramic magnets, in series, between steel plates A 1-lb. "giant"!

(1 x 1 1/4 x 4 3/4")

No. 42,318AV...\$11.95 Ppd.

## BUILD A WORKING STEAM ENGINE

Exact 6x8 1/4" hi replica of Single Acting Engine can power erector set assemblies, runs on tap water; you control speed, make whistle blow. Adult supervision. 35 parts.

No. 72,202AV...\$27.50 Ppd.

## SUPER POWER FOR ANY AM RADIO

Antenna assist has pulled in stations 1000 miles off! No wires, clips, grounding. Solid state—no elec. batts., tubes.

No. 72,095AV...\$19.95 Ppd.

ULTRA SELECT-A-TENNA

No. 72,147AV.....\$24.95

## GIANT FREE 164 PG. CATALOG



4500 UNUSUAL BARGAINS FOR HOBBYISTS, SCHOOLS, INDUSTRY

**EDMUND SCIENTIFIC CO.**  
300 Edscorp Bldg.  
Barrington N.J. 08007  
America's Greatest  
Science • Optics • Hobby Center  
(609) 547-3488

## COMPLETE AND MAIL COUPON NOW

EDMUND SCIENTIFIC CO. 300 Edscorp Bldg., Barrington, N. J. 08007



SEND FREE

164 PG. CATALOG AV

Charge my ☐ American Exp.

☐ BankAmericard ☐ Master Chg

Interbank No. \_\_\_\_\_

Card No. \_\_\_\_\_

Expiration Date \_\_\_\_\_

30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund.

Send me the following:

Stock No. Quantity Price Ea.


Add handling charge \$ \_\_\_\_\_ 1.00

Enclosed is ☐ check, ☐ M.O. in amount of \$ \_\_\_\_\_

Signature \_\_\_\_\_

Address \_\_\_\_\_

City, State, Zip \_\_\_\_\_

HELPING TO DEVELOP AMERICA'S TECHNOLOGY FOR OVER 30 YEARS.  
CIRCLE NO. 24 ON FREE INFORMATION CARD

## PLANS AND KITS

## AMAZING ELECTRONIC PRODUCTS

Lasers Super Powered, Rifle, Pistol, Pocket - See in Dark - Pyro-Technical, De-Bugging - Uncramblers - Giant Tesla - Stunwand - TV Disrupter - Energy Producing, Scientific Detection, Electrifying, Chemical, Ultrasonic, CB, Aero, Auto and Mech Devices, Hundreds More - All New Plus Info Unto Parts Service.

INFORMATION unlimited

CATALOG \$1

Box 626 Lord Jeffery PZ. • Amherst, N.H. 03031

FREE KIT Catalog contains Test and Experiment's Equipment Dage Scientific Instruments, Box 1054P, Livermore, CA 94550.

**TIGER SST SIMPLI-KIT**

**FOR THE DO-IT-YOURSELF NOW!** a high quality CD Electronic Ignition System in kit form.

Contains all components and solder to build complete Solid-State Electronic CD Ignition System for your car. Assembly requires less than 3 hours.

- Increases MPG 15%
- Increases horsepower 15%
- Plugs and Points last 50,000 miles
- Eliminates 4 of 5 tune-ups
- Instant starting, any weather
- Dual system switch

Fits only 12 volt neg. ground... Only \$21.95 postpaid

**T-T Star Corporation**  
P.O. Box 1727 Grand Junction, Colorado 81501

FIVE OCTAVE Touch Sensitive Electronic PIANO KIT. Components \$229 airmail U.S.A., Canada. Cief Products, 31, Mountfield Road, Bramhall, Cheshire, England SK7 1LY.

TAPE-SLIDE Synchronizer, lap-dissolve, multiprojector, audiovisual plans, \$8.50. Sampler, \$1.00. Millers, 1896 Maywood, St. Euclid, OH 44121.

TESLA COIL—40" SPARKS! Plans \$7.50. Information 75 cents. Huntington Electronics, Box 2009-P, Huntington, Conn. 06484.

## HIGH FIDELITY

DIAMOND NEEDLES and Stereo Cartridges at Discount prices for Shure, Pickering, Stanton, Empire, Grado and ADC. Send for free catalog. LYLE CARTRIDGES, Dept. P, Box 69, Kensington Station, Brooklyn, New York 11218.

SAVE 50% build your own speaker system write: McGee Radio Electronics, 1901 McGee Street, Kansas City, Missouri 64108.

## BURGLAR ALARMS

DIALING UNIT automatically calls police. \$29.95. Free security equipment catalog. S&S Systems, 5619-C St. John, Kansas City, MO 64123. (816) 483-4612.

ELECTRONIC Smoke Detectors, home and auto burglar alarms. Catalogue \$1.00 refundable. EMS, 5709 Tomahawk Trail, Durham, NC 27704.

## TUBES

RADIO & T.V. Tubes—36 cents each. Send for free Catalog. Cornell, 4213 University, San Diego, Calif. 92105. TUBES receiving, factory boxed, low prices, free price list. Transletronic, Inc., 1365 39th Street, Brooklyn, N.Y. 11218A, Telephone: 212-633-2800.

TUBES: "Oldies", Latest. Supplies, components, schematics. Catalog Free (stamp appreciated). Steinmetz, 7519-PE Maplewood, Hammond, Ind. 46324.

## PERSONALS

MAKE FRIENDS WORLDWIDE through international correspondence. Illustrated brochure free. Hermes-Verlag, Box 110660/Z, D-1000 Berlin 11, Germany.

WARTS. Vergo® Cream is painless, safe, easy, gentle. Buy Vergo® at better pharmacies.

## TREASURE FINDERS

TREASURE may lie beneath your feet! Discover gold, silver, coins, rings, artifacts and more with world-famous, deeper-detecting White's metal detectors. From \$79.50. Dealers world-wide. Free literature! White's Electronics, Dept. PD7-C, 1011 Pleasant Valley Rd., Sweet Home, OR 97386.

## WANTED

GOLD, Silver, Platinum, Mercury wanted. Highest prices paid by refinery. Ores assayed. Free circular. Mercury Terminal, Norwood, MA 02062.

WANTED information to build holograms. 19 Chippewa, Royal Oak, Mich. 48073.

## CLASSIFIED ADVERTISING ORDER FORM

Please refer to heading on first page of this section for complete data concerning terms, frequency discounts, closing dates, etc.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

**WORD COUNT:** 15 WORD MINIMUM. Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zip Code numbers not counted. (Publisher reserves right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols such as 35mm, COD, PD, AC, etc., count as one word. Hyphenated words count as two words. Telephone numbers count as one word.

\_\_\_\_\_ Words \$2.25 (Commercial Rate) \$1.35 (Reader Rate)

☐ Payment of \$ \_\_\_\_\_ enclosed for \_\_\_\_\_ insertion(s).

CHARGE: ☐ American Express ☐ BankAmericard ☐ Master Charge ☐ Diners Club

for \_\_\_\_\_ insertion(s). You will be billed monthly.

Account # \_\_\_\_\_ Expiration Date \_\_\_\_\_

Master Charge interbank # (4 digits above name) \_\_\_\_\_

SIGNATURE MUST BE PROVIDED BELOW

PRINT NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_ PE-277

# 6 Digit LED Clock Kit - 12/24 hr.

**\$995** QTY. 12  
ea. OR MORE

**\$1095** QTY.  
ea. 6-11

**\$1195** QTY.  
ea. 1-5

- KIT INCLUDES**
- INSTRUCTIONS
  - QUALITY COMPONENTS
  - 50 or 60 Hz OPERATION
  - 12 or 24 HR OPERATION

6-LED Readouts (FND-359 Red, com. cathode)  
1-MM5314 Clock Chip (24 pin)  
13-Transistors  
3-Switches  
6-Capacitors  
5-Diodes  
9-Resistors  
24-Molex pins for IC socket

**LARGE .4" DIGITS!**

ORDER KIT #850-4  
AN INCREDIBLE VALUE!

"Kit #850-4 will furnish a complete set of clock components as listed. The only additional items required are a 7-12 VAC transformer, a circuit board and a cabinet, if desired."

Printed Circuit Board for kit # 850-4 (etched & drilled fiberglass) .....\$2.95  
Mini-Brite Red LED's (for colon in clock display) pkg. of 5 ..... 1.00  
Molded Plug Transformer 115/10 VAC (with cord) ..... 2.50  
NOTE: Entire Clock may be assembled on one PC Board or Board may be cut to remote display.  
Kit #850-4 will fit Plexiglas Cabinet II.

## 6 Digit-LED Clock-Calendar-Alarm Kit

This is a complete, top of the line, Kit for the person that wants the best. Some of the many features and options are: 12/24 time, 28-30-31 day calendar, alternates time (8 sec) and date (2 sec) or can display time only and date on demand, 24 hr alarm - 10 minute snooze, alarm set indicator, 50/60 HZ. line operation or use with Xtal time base (#TB-1), built in OSC for battery back-up / AC failure, Aux. timer, CHOICE OF DIGITS.

Kit #7001B 6 - .4" Digits \$39.95  
Kit #7001C 4 - .6" Digits & 2-" [Seconds] \$42.95  
Kit #7001X 6 - .6" Digits \$45.95

Kits are complete (less cabinet) including PC boards, power supply, IC socket, 9 switches, 16 transistors and all parts required for above features and options [All #7001 Kits Will Fit Cabinet I]

**PRINTED CIRCUIT BOARDS** for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout. Specify for #7001B or #7001C (Set of 2) \$7.95

### JUMBO DIGIT CLOCK KIT

A complete Kit (less Cabinet) featuring: six .5" digits, MM5314 IC, 12/24 Hr. time, 50/60 HZ., Plug-Transformer, Line Cord, Switches, and all Parts.  
[Ideal Fit in Cabinet II]

**\$1995 2/\*38.**

### JUMBO DIGIT CONVERSION KIT


Convert small digit LED clock to large .5" displays. Kit includes 6-.5" LED's, Multiplex PC Board & easy hook-up info.

Kit #JD-1CC For common Cathode  
Kit #JD-1CA For common Anode

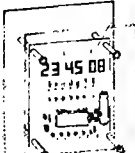**\$995 ea. 2/\*19.**

SEE THE WORKS Clock Kit  
Clear Plexiglas Stand

- 6 Big .4" digits
- 12 or 24 hr. time
- 3 set switches (back)
- Plug transformer
- All parts included
- Plexiglas is
- Pre-cut & drilled
- Size: 6" H. 4 1/4" W. 3"



A SUPER LOOKING  
CLOCK!

Kit #850-4 \$2350 2/\*45.

### 7-SEG LED COMMON CATHODE

COLOR	HT. DEC PT. PREA	
FND-359 RED	.4" RHDP	\$ .95
FND-503 RED	.5" RHDP	\$1.35
DL-750 RED	.6" LHDP	\$1.95
XAN-654 GREEN	.6" NDP	\$1.95
XAN-664 RED	.6" NDP	\$1.95

#### COMMON ANODE

DL-747 RED	.6" LHDP	\$1.95
MAN-72 RED	.3" LHDP	\$1.25
XAN-81 YELLOW	.3" RHDP	\$1.75
XAN-351 GREEN	.3" RHDP	\$1.50
XAN-361 RED	.3" RHDP	\$1.50
XAN-362 RED	.3" LHDP	\$1.50
XAN-662 RED	.6" NDP	\$1.95
XAN-692 RED	.6" NDP	\$1.95

Form Inexpensive  
Sockets  
100 for \$1.25  
Reel of 1000 - \$8.50

MOLEX  
PINS



Fairchild Super Digit  
FND-359

4" Char. Ht.  
7 segment LED  
RED Com. Cath.  
Direct pin  
replacement for  
popular FND-70

95¢ ea. 10/\$8.50  
100/\$79.00

SET OF 6 FND-359  
WITH MULTIPLEX  
PC BOARD \$6.95

25 AMP BRIDGE  
\$1.95 ea.  
3/\$5.00  
100 PIV

TELEPHONE FORMAT  
KEYBOARD  
BY Chomerics

2-1/4"x3"  
5/32"  
thick  
\$4.95  
6/\*28.

CHOTTKY DTL

74S00	.35	930	.09
74S01	.40	932	.09
74S04	.55	937	.09
74S06	.60		
74S09	.55	7447	.95
74S10	.40	7448	.95
74S20	.50	75491	.66
74S22	.45	75492	.66
74S40	.45		
74S50	.45		
74S51	.55		
74S60	.85	LM309H TO-5	.95
74S64	.55	LM309K TO-3	1.25

74S74	.85	7805	TAB .95
74S75	1.75	7812	TAB 1.25
74S78	1.50	7815	TO-3 1.25
74S86	.95	7815	TAB 1.25
74S107	.95	7815	TO-5 .75
74S112	.95	LM340T-18TAB	1.25
74S113	1.40	LM340T-24TAB	1.25
74S114	.95	7824	TO-3 1.25
		723	DIP .75
		723	TO-5 .75

74S133	.75		
74S134	.75		
74S138	.75		
74S139	1.50		
74S151	1.95		
74S153	1.95	MM5312	\$ 4.95
74S155	1.95	MM5314	3.95
74S156	1.95	MM5375 AB	3.95
74S157	1.80	CT-7001	7.95
74S158	2.50	CT-7002	13.95
74S174	2.50	50380	3.95
74S175	2.50	MM5369	2.50
74S181	2.95		
74S182	1.95		
74S251	2.75	3.579545 MHZ.	\$ 1.95

XTAL

60 HZ.  
XTAL TIME BASE KIT

Will enable Digital Clock or Clock-Cal. Kits to operate from 12VDC. Uses MM5369 and 3.58MHZ. XTAL. Req. 5-15VDC/2.5 MA. 1"x2" PC Board. Easy 3 wire hookup Accuracy: + - 2 PPM  
#TB-1 [adjustable]  
Complete kit \$4.95 ea  
Wired & Cal. \$9.95 ea

Visit Our Store  
at 823 S. 21st. Avenue, Hollywood, FL.

**OPTOELECTRONICS, inc.**

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056

WE PAY ALL SHIPPING IN CONTINENTAL USA — OTHERS ADD 5% [10% FOR AIRMAIL]


## MOBILE LED CLOCK

12 OR 24-HOUR OPERATION

12 VOLT AC or DC POWERED FOR FIXED OR MOBILE OPERATION.

SIX LARGE .4" DIGITS!

KIT OR  
ASSEMBLED

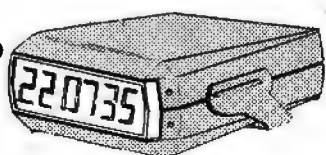

MODEL  
2001

ACCURATE TIME  
WITH ADJUSTABLE  
XTAL TIME BASE

Approx. Size:  
1 3/4" H x 4" W x 4 1/2" D

BATTERY BACK-UP  
FOR POWER FAILURE  
OR TRANSPORTING  
FROM HOUSE TO CAR, ETC.

- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM.
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY — TWO WIRE NO POLARITY HOOK-UP
- OPTIONAL CONNECTION TO BLANK DISPLAY (Use When Key Off in Car, Etc.)
- TOP QUALITY PC BOARDS & COMPONENTS — EXCELLENT INSTRUCTIONS
- MOUNTING BRACKET INCLUDED

KIT #2001 COMPLETE KIT (Less 9V Battery)	2995	3 OR MORE	2795	115 VAC Power Pack #AC-1	250
ASSEMBLED UNITS ORDER #2001 WT. (LESS 9V BATTERY)	3995	3 OR MORE	3795	Assembled Units May Be Mixed With Kits for Qty. Price	

CPU  
8080A  
NS8080AD  
Micro Processor Chip  
Prime National LSI  
40 Pin socket  
\$ .50 with each 8080A!

450 ns MEMORY  
Fairchild 1K Ram  
low, low, low power.  
2102L1PC \$1.95ea.  
25-99 \$1.75 ea.  
100-199 \$1.60 ea.  
200 or more \$1.45 ea.

JUMBO RED LED's 12/\$1.00 50/\$3.95

11C90DC 95H90	\$15.95 9.95	XR2556 XR2567	\$ 1.75 \$ 1.95	OP AMPS 3/31.00 301 TO-5 709 DIP 709 TO-5 741 DIP 741 M-OIP 741 TO-5 747 DIP 748 DIP
DIODES		TRANSISTORS		DISCRETE LED's JUMBORED
IN4002 1A, 100 PIV	12/\$1.00	2N2222 TO-18	5/\$1.00	12/\$1.00
IN4005 1A, 600 PIV	11/\$1.00	2N2554 TO-5	2/\$1.00	301 TO-5
IN4007 1A, 1000 PIV	10/\$1.00	2N2712 TO-98	5/\$1.00	709 DIP
RECTIFIER 2.5A, 1000 PIV	4/\$1.00	2N3415 TO-92	5/\$1.00	741 DIP
IN914 SIL. SIGNAL	20/\$1.00	2N3704 TO-92	5/\$1.00	741 M-OIP
IN4148 (1N914 Equiv.)	20/\$1.00	2N4400 TO-92	5/\$1.00	747 TO-5
OYAC 28V.	4/\$1.00	2N4125 TO-92	5/\$1.00	748 DIP
PLUG TRANSFORMERS		2N4249 TO-92	5/\$1.00	
12VAC at 150 MA	\$2.50	2N4437 TO-92	5/\$1.00	
12VAC at 500 MA	3.50	2N6027 PUT	2/\$1.00	
7 VAC at 1.75VA	2.50	2N5457 N-J-Fet	2/\$1.00	
555 TIMER	2/\$1.00	SWITCHES		PC TRIM POTS
556 DUAL TIMER	.95	ROCKER SPDT	6/\$1.	25K 6/\$1.00
565 PLL	.95	MINI-SLIDE SPDT	5/\$1.	4.7K 6/\$1.00
566 FUNCTION GEN.	1.75	REG. SLIDE DPDT	6/\$1.	
567 TONE DECODER	1.75	PUSH BUTTON N.O. 3/1.		
IC SOCKETS		MINI TOGGLE SPDT	\$1.30	
PINS		MINI TOGGLE DPDT	1.50	
8 .25	\$ .25	TRANSISTOR SOCKET		
14 .25	.25	TO-5/18 GOLD PINS	5/\$1.00	
16 .25	.25	NYLON WIRE TIES		
18 .31	.28	8" TIE WRAP 100/81.95		
24 .60	.45	4" TIE WRAP 100/81.75		
28 .60	.55	MOLEX PINS		
40 .75	.70	REEL OF 1000 8.25		
COMPUTER		STRIP OF 100 1.50		
8080A CPU	19.95	MISC. PRIME IC's		
1702 E Prom	8.95	FAIRCHILD 9316 (74161)	\$ .95	
5203 E Prom	8.95	7523A DUAL CORE SENSE AMP	1.50	
2102L1 PC 1K Ram	1.95	MM 502H TO-5 SHIFT REG	.95	

## PLEXIGLAS CABINETS

Black, White or Clear Cover

Great for Clocks  
or any LED Digital  
project. Clear-Red  
Chassis serves as  
Bezel to increase  
contrast of digital  
displays.



CABINET I

3" H, 6 1/4" W.

5 1/2" D

CABINET II

2 1/2" H, 5" W, 4" D

\$6.50 ea. 2/\*12. ANY SIZE/ COLOR

3"x6"x1/8" RED OR GREY  
PLEXIGLAS FOR DIGITAL BEZELS 95¢ ea. 4/\*3

ORDER BY PHONE OR MAIL  
COD ORDERS WELCOME  
[\$.00 CHG.]  
Orders Under \$15 Add \$.00  
Handling  
Fla. Res. Please Add 4%  
Sales Tax.



## INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING at home all makes including transistor. Experimental kit—trouble-shooting. Accredited NHSC, Free Booklet, NILES BRYANT SCHOOL, 3631 Stockton, Dept. A, Sacramento, Calif. 95820.

EARN ELECTRONICS DEGREE by correspondence. Free information bulletin. Grantham, 2000 Stoner Avenue, Los Angeles, California 90025.

LEARN BASIC Digital Troubleshooting by correspondence. Course includes text and demonstration modules. Educational Technologies, Box 224, Reynoldsburg, Ohio 43068.

FCC EXAMINATIONS: Complete First, Second, Third Questions-Answers. Proven "topical" study method included. \$8.00. "Guaranteed Exams", Box 5516-AB, Walnut Creek, CA 94598.

BREAK INTO TV/RADIO Broadcasting, Disc Recording career. Expert reveals secret avoiding disappointment, wasted time/money. Free information. Box 921, Beverly Hills, Calif. 90213.

# F.C.C. EXAM MANUAL

Tests Answers for FCC First and Second Class Commercial License

PASS FCC EXAMS! Memorize, study — "Test-Answers" for FCC 1st and 2nd class Radio-Telephone licenses. Newly revised multiple-choice questions and diagrams cover all tests listed in FCC exams plus "Self-Study Ability Test" \$9.95 postpaid. Moneyback Guarantee.

COMMAND PRODUCTIONS P.O. BOX 26348-P  
RADIO ENGINEERING DIVISION SAN FRANCISCO, CALIF. 94126

SCORE high on F.C.C. Exams... Over 300 questions and answers. Covers 3rd, 2nd, 1st and even Radar. Third and Second Test, \$14.50; First Class Test, \$15.00. All tests, \$26.50. R.E.I., Inc., Box 806, Sarasota, Fla. 33577.

UNIVERSITY DEGREES BY MAIL! Bachelors, Masters, Ph.D's. Free revealing details. Counseling, Box 317-PE02, Tustin, California 92680.

SELF-STUDY CB RADIO REPAIR COURSE. THERE'S MONEY TO BE MADE REPAIRING CB RADIOS. This easy-to-learn course can prepare you for a career in electronics enabling you to earn as much as \$18.00 an hour in your spare time. For more information write: CB RADIO REPAIR COURSE, Dept. PE027, 531 N. Ann Arbor, Oklahoma City, Okla. 73127.

LEARN WHILE ASLEEP! HYPNOTIZE! Astonishing details, strange catalog free! Autosuggestion, Box 24-ZD, Olympia, Washington 98507.

GRANTHAM'S FCC LICENSE STUDY GUIDE — 377 pages, 1465 questions with answers/discussions — covering third, second, first radiotelephone examinations. \$10.70 postpaid. GSE, 2000 Stoner, Los Angeles, California 90025.

INTENSIVE 5 week course for Broadcast Engineers. FCC First Class license. Student rooms at the school. Radio Engineering Inc., 61 N. Pineapple Ave., Sarasota, FL 33577 and 2402 Tidewater Trail, Fredericksburg, VA 22401.

FREE Educational Electronics Catalog. Home study courses. Write to: Edukits Workshop, Department 721D, Hewlett, N.Y. 11557.

PRACTICAL Electronic training. FCC license. Free home study catalog. Genn Tech., 5540 Hollywood Blvd., Los Angeles, CA 90028. Or, Ra-Tel Electronics, P.O. Box 167, "P" Toronto, Ont., Canada. U.S. Inquiries.

BROADCAST STATION—FM or CABLE; Start your own, become a DJ, get free tapes-records! Free details, "Broadcasting," Box 5516-AB, Walnut Creek, CA 94596.

DRAFTING—Blueprint Reading, Mechanical, Electronic, Architectural home courses \$25.00. Send \$2.00 first lesson. Prior Inc., 23-09 169th Street, Whitestone, New York City 11357.

## 10% OFF WITH \$25 ORDER 15% OFF WITH \$100 ORDER

THESE DISCOUNTS APPLY TO TOTAL OF ORDER — SPECIALS INCLUDED

TTL					
7400	.13	7451	.17	74153	.89
7401	.16	7452	.17	74154	1.20
7402	.15	7454	.17	74155	.97
7403	.15	7460		74156	.97
7404	.16	7461	.35	74157	.99
7405	.19	7465	.35	74158	1.79
7406	.20	7470	.30	74160	1.23
7407	.28	7472	.30	74161	.97
7408	.18	7473	.35	74162	1.39
7409	.19	7474	.28	74163	1.09
7410	.16	7475	.49	74164	.99
7411	.25	7476	.30	74165	.99
7413	.43	7483	.68	74166	1.25
7414	.65	7485	.88	74170	2.10
7416	.35	7486	.80	74173	1.49
7417	.35	7489	2.25	74174	1.23
7420	.16	7490	.43	74175	.97
7422	.30	7491	.75	74176	.89
7423	.29	7492	.48	74177	.84
7425	.27	7493	.48	74180	.99
7426	.26	7494	.78	74181	2.45
7427	.29	7495	.79	74182	.97
7430	.20	7496	.79	74184	1.79
7432	.23	74100	.98	74185	2.28
7437	.25	74105	.98	74187	1.23
7438	.25	74107	.37	74190	.97
7440	.15	74121	.38	74191	1.39
7441	.89	74122	.38	74192	.97
7442	.59	74123	.65	74193	.97
7443	.73	74125	.54	74194	1.23
7444	.73	74126	.58	74195	.97
7445	.73	74132	.89	74196	1.23
7446	.81	74141	1.04	74197	.97
7447	.79	74145	1.04	74198	1.23
7448	.79	74150	.97	74199	1.23
7450	.17	74151	.79	74200	1.45

## LINEAR CIRCUITS

300	Pos V Reg (super 723) TO-5	\$ .71
301	Hi Perf Op Amp mDIP TO-5	.29
302	Volt follower TO-5	.53
304	Neg V Reg TO-5	.80
305	Pos V Reg TO-5	.71
307	Op Amp (super 741) mDIP TO-5	.26
308	Active Per Op Amp mDIP TO-5	.89
309K	5V IA regulator TO-3	1.35
310	V Follower Op Amp mDIP	1.07
311	Hi perf V Comp mDIP TO-5	.95
319	Hi Speed Dual Comp DIP	1.13
120T	Neg Reg 5.1, 12, TO-20	1.39
120K	Neg Reg 5.2, 12 TO-3	1.39
322	Precision Timer DIP	1.19
324	Quad Op Amp DIP	1.64
339	Quad Comparator DIP	1.18
340K	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-3	1.69
340T	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-20	1.49
372	AF-IF Strip detector DIP	2.93
373	AM/FM/SSB Strip DIP	2.42
376	Pos V Reg mDIP	.68
380	2w Audio Amp DIP	1.19
380-8	.6w Audio Amp mDIP	1.25
381	Lo Noise Dual preamp DIP	1.75
382	Lo Noise Dual preamp DIP	1.75
531	High Slew rate Op Amp	1.85
550	Power driver TO-5	4.95
555	Pre V Reg DIP	.79
555	Timer mDIP	.49
556A	Dual 555 Timer DIP	1.19
560	Phase Locked Loop DIP	3.39
562	Phase Locked Loop DIP	3.39
565	Phase Locked Loop DIP TO-5	1.19
566	Function Gen mDIP TO-5	1.95
569	Tone Decoder mDIP	1.26
707	Operational AMP TO-5 or DIP	.62
710	Hi Speed Volt Comp DIP	.35
711	Dual Difference Compar DIP	.26
723	V Reg DIP	.62
733	Diff. video AMPL TO-5	.89
739	Dual Hi Perf Op Amp DIP	1.07
741	Comp Op Amp mDIP TO-5	.32
747	741 Dual Op Amp DIP or TO-5	.71
748	Freq Adj 741 mDIP	.35
1458	Dual Comp Op Amp mDIP	.62
1800	Stereo multiplexer DIP	2.48
3900	Quad Amplifier DIP	.49
7524	Core Mem Sense AMPL DIP	.71
7525	Core Mem Sense AMPL DIP	.90
8038	Voltage contr. osc. DIP	4.25

## 1702A UV ERASABLE PROM

— 2048 bit static PROM 256x8  
elect programmable & erasable TTL/DTL comp.

**\$6.95**

**2102 RAM**  
1024 bit fully decoded static RAM  
DTL TTL compatible — 16 pin DIP **\$ 1.49**

**ALARM CLOCK CHIP**  
MM5375AA 4-6 digit, 12 hour, 60Hz  
snooze alarm, brightness control capability, alarm tone output 24 pin DIP **\$3.95**

**5738 CALCULATOR CHIP**  
8 digit multiplexed — live function —  
chain operation 2 key memories — floating  
decimal — independent constant —  
interfaced with led with only digit driver —  
4 V batt. oper. 24 pin **2.95**

**7001 CLOCK CHIP**  
4-6 digit, 12-24 hr. alarm, timer and date  
circuits — with data **\$5.95**

**DVM CHIP 4 1/2 DIGIT**  
MM5330 — P channel device provides  
all logic for 4 1/2 digit volt meter. 16 pin  
DIP with data **\$6.95**

## TANTALUM CAPACITOR KIT \$19.95

1000µF 25V 10% 1000µF 35V 10% 1000µF 50V 10% 1000µF 63V 10% 1000µF 80V 10% 1000µF 100V 10% 1000µF 125V 10% 1000µF 150V 10% 1000µF 200V 10% 1000µF 250V 10% 1000µF 300V 10% 1000µF 350V 10% 1000µF 400V 10% 1000µF 450V 10% 1000µF 500V 10% 1000µF 550V 10% 1000µF 600V 10% 1000µF 650V 10% 1000µF 700V 10% 1000µF 750V 10% 1000µF 800V 10% 1000µF 850V 10% 1000µF 900V 10% 1000µF 950V 10% 1000µF 1000V 10%

**SPECIAL DEVICES**  
372 AF-IF Strip Detector DIP 2.93  
546 AM Radio Receiver Subsystem DIP .75  
1310 FM Stereo Demodulator DIP 2.90  
1496 Balanced Modulator-Demodulator .99  
1800 Stereo multiplexer DIP 2.48  
ULN2206 FM Gain Block 34db (typ) mDIP 1.18  
ULN2209 FM Gain Block 48db (typ) mDIP 1.35  
2513 Character Generator 64x64 DIP-24 10.20  
2513 Transistor Array DIP-14 .73

**CLOCK CHIPS**  
MM5311 6 digit multiplexed BCD, 7 seg, 12-24  
Hr, 50-60 Hz — 28 pin **4.40**  
MM5312 4 digit multiplexed BCD, 7 seg, 1pps,  
12-24 Hr, 50-60 Hz — 24 pin **1.95**  
MM5314 6 digit multiplexed 12-24 Hr, 50-60 Hz  
24 pin **1.40**  
MM5316 4 digit, 12-24 Hr, 50-60 Hz, alarm  
40 pin **4.95**

**SHIFT REGISTERS**  
MM5013 1024 bit accum. dyn. 1.75  
MM5016 500/512 bit dyn. 1.59  
515-4025 Quad 25 bit 1.59  
2504 1024 bit multiplexed dyn 2.93

**IC SOCKETS**  
**Isolder Tail - low profile**  
8 pin .5 17 24 pin .42  
16 pin .20 28 pin .59  
16 pin .22 40 pin .69  
18 pin .22 40 pin .69

**WIRE WRAP - gold plate**  
14 pin .49

**MULTIPLE DISPLAYS**  
NSN33 3 digit .12" red LED 1.79  
7405 5 digit .11 red LED 1.49  
HP5082- 4 digit .11 red LED 3.25  
7414 9 digit .25 gss diach. 1.79

**FREE CATALOG AVAILABLE ON REQUEST**

Satisfaction guaranteed. Shipment will be made postage prepaid within 3 days from receipt of order. Payment may be made with personal check, charge card (include number and exp. date), or money order. Phone Orders — BofA and M/C card or C.O.D.

Add \$1.00 to cover shipping and handling if order is less than \$10.00.  
California residents add sales tax. Include shipping expense for orders shipped out of U.S. and Canada approx. 10% of order.

**INTERNATIONAL ELECTRONICS UNLIMITED**  
P.O. BOX 3036-R MONTEREY, CA. 93940 USA  
PHONE (408) 659-3171

## FEBRUARY SPECIALS

### LINEAR

301	Hi perf op amp	mDIP .25
311	Hi perf V Comp	DIP .71
555	Timer	mDIP .39
565	Phase Locked Loop	DIP .98
723	V Reg	DIP .56
739	Dual Hi Perf Op Amp	DIP .89
741	Comp Op Amp	mDIP .26
1458	Dual Comp Op Amp	mDIP .54
8864	9 DIG Led Cath Dvr	DIP 1.95
75150	Dual Line Driver	mDIP 1.52
75453	(351) Dual Periph. Driver	mDIP .29
75491	Quad Seq Driver for LED	DIP .62

	7474	.22	74164	.85
\$ .19	7490	.39	74165	.85
.20	74121	.29	74193	.73
.18	74123	.49	9602	.59

### CENTRAL PROCESSING UNIT

8008 **\$19.95**  
8080 **\$19.95**

### Mark I Clock Kit

A six digit clock kit with one double sided P.C. board accommodates MM5314 clock chip and 6 FND359 .375" displays. 12-24 hour, 50-60 Hz. Contains all necessary components, 3 switches and complete assembly instructions with schematics. Connections for remote displays.

**Mark I \$13.95**

### Transformers

117VAC — 12V 300 ma PC Mount. **\$3.95**  
117 VAC — 12V 300 ma wall mount **\$4.95**

### AUTO CLOCK KIT

6 digits .375" red led's  
Operates from 12V DC or AC  
Crystal control for high accuracy  
Supplied with case  
& mounting bracket  
Contains internal 9V battery for operation of timing circuit (without display) when removed temporarily from power.  
Uses 5314 clock circuit  
Supplied with all necessary components and assembly instructions

**\$33.95**  
**COMPLETELY ASSEMBLED \$44.95**

### DISPLAYS

MAN1	\$1.95	ME4	\$.24
MAN2	1.95	MY50	.12
MAN3	.19	NS1100	.12
MAN5	2.25	NS1101	.12
MAN6	2.49	NS1102	.15
MAN7	1.49		
MAN8	2.25	MY5020	.15
MAN6b	2.25	RED	.15
DL164	2.19	GREEN	.15
IND588	1.99	AMBER	.15
NS11	1.99	CLEAR	.15

### OPTO ISOLATORS

MC2D	Opto isolator diode	1.09
MC2T	Opto isolator transistor	.70

Data included with order on request.  
Add \$3.00 ea. if item is ordered below \$1.00

## INVENTIONS WANTED

INVENTORS: Manufacturers Need New Products. Free "Recommended Procedure," by a creative fee-based invention service company. Washington Inventors Service, 422-T Washington Building, Washington, D. C. 20005.

## INVENTORS

### RECOGNITION...FINANCIAL REWARD...OR CREDIT FOR "INVENTING IT FIRST" MAY BE YOURS!

If you have an idea for a new product, or a way to make an old product better, contact us, "the idea people." We'll develop your idea, introduce it to industry, negotiate for cash sale or royalty licensing. Write now without cost or obligation for free information. Fees are charged only for contracted services. So send for your FREE "Inventor's Kit." It has important Marketing Information, a special "Invention Record Form" and a Directory of 500 Corporations Seeking New Products.

**RAYMOND LEE ORGANIZATION**  
230 Park Avenue North, New York, NY 10017  
At no cost or obligation, please rush my FREE "Inventor's Kit No. A-112".

Name \_\_\_\_\_ Please Print  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## TAPE AND RECORDERS

RENT 4-Track open reel tapes—free brochure. Stereo-Parti, P.O. Box 7, Fulton, CA 95401.

RECORDS—TAPES! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. Discount Music Club, 650 Main St., Dept 5-0277, New Rochelle, New York, N.Y. 10801.

EDISON CYLINDER phonograph recordings on cassette. SASE list. Talen, 10605 Double Spur, Austin, TX 78759.

## GOVERNMENT SURPLUS

MANUALS for Govt Surplus radios, test sets, scopes. List 50 cents (coin). Books, 7218 Roanne Drive, Washington, D.C. 20021.

GOVERNMENT SURPLUS. How and where to Buy in your area, send \$2.00. Surplus, 30177-PE Headquarters Building, Washington, D.C. 20014.

## RECORDS

RECORD RATERS WANTED! Anyone qualifies. We ship you nationally released LP's to rate. We pay postage and handling. You pay nothing for LP's. All you pay is small membership fee. Applicants accepted "first come basis." Write: E.A.R.S., Inc., Dept PE, Box 10245, 5521 W. Center Street, Milwaukee, Wisconsin 53210.

# S.D. SALES CO.

P.O. BOX 28810 - D  
DALLAS, TEXAS 75228

## Z-80 CPU CARD KIT FOR IMSAI/ALTAIR

**\$149.<sup>KIT</sup>**

From the same people who brought you the \$89.95 4K RAM kit. We were not the first to introduce an IMSAI/ALTAIR compatible Z-80 card, but we do feel that ours has the best design and quality at the lowest price.

The advanced features of the Z-80 such as an expanded set of 158 instructions, 8080A software compatibility, and operation from a single 5VDC supply, are all well known. What makes our card different is the extra care we took in the hardware design. The CPU card will always stop on an M1 state. We also generate TRUE SYNC on card, to insure that the rest of your system functions properly. Dynamic memory refresh and NMI are brought out for your use. Believe it or not, not all of our competitors have gone to the extra trouble of doing this.

As always, this kit includes all parts, all sockets, and complete instructions for ease of assembly. Because of our past experience with our 4K kit we suggest that you order early. All orders will be shipped on a strict first come basis. Dealers inquiries welcome on this item.

Kit shipped with 2 MHZ crystals for existing 500NS memory. Easily modified for faster RAM chips when the prices come down.  
Z-80 Manual - \$7.50 Separately.

Kit includes Zilog Manual and all parts.

## JUMBO LED CAR CLOCK

**\$16.95  
KIT**

You requested it! Our first DC operated clock kit. Professionally engineered from scratch to be a DC operated clock. Not a makeshift kluge as sold by others. Features: Bowmar 4 digit .5 inch LED array, Mostek 50252 super clock chip, on board precision time base, 12 or 24 hour real time format, perfect for cars, boats, vans, etc. Kit contains PC Board and all other parts needed (except case). 50,000 satisfied clock kit customers cannot be wrong!

FOR ALARM OPTION ADD \$1.50  
FOR XFMR FOR AC OPERATION ADD \$1.50

## 60 HZ CRYSTAL TIME BASE FOR DIGITAL CLOCKS S.D. SALES EXCLUSIVE!

### KIT FEATURES:

- A. 60HZ output with accuracy comparable to a digital watch.
- B. Directly interfaces with all MOS Clock Chips.
- C. Super low power consumption. (1.5 ma typ.) **\$5.95 or 2/\$10.**
- D. Uses latest MOS 17 stage divider IC.
- E. Eliminates forever the problem of AC line glitches.
- F. Perfect for cars, boats, campers, or even for portable clocks at ham field days.
- G. Small Size, can be used in existing enclosures.

**KIT INCLUDES CRYSTAL, DIVIDER IC, PC BOARD  
PLUS ALL OTHER NECESSARY PARTS & SPECS**

## 50HZ CRYSTAL TIME BASE KIT - \$6.95

All the features of our 60HZ kit but has 50HZ output. For use with clock chips like the 50252 that require 50HZ to give 24 hour time format.

SPECIAL

### THIS MONTH'S SPECIALS!

- 300.00 KHZ CRYSTAL - \$1.50
  - 8080A - CPU CHIP by AMD - \$19.95
  - 82S129 - 256 x 4 PROM - \$2.50
  - N.S. 8865 OCTAL DARLINGTON DRIVERS 3 for \$1.00
  - Z-80 - CPU by ZILOG - \$69.95
  - MM5204 - 4K EPROM - \$7.95
- Prices in effect this month ONLY!*

SPECIAL

## 4K LOW POWER RAM BOARD KIT THE WHOLE WORKS - \$89.95


Imesai and Altair 8080 plug in compatible. Uses low power static 21L02-1 500ns. RAM's, which are included. Fully buffered, drastically reduced power consumption, on board regulated, all sockets and parts included. Premium quality plated thru PC Board.

7400-19c	7411-29c	7451-19c	7490-65c	74153-75c
74LS00-49c	7413-50c	7453-19c	74LS90-95c	74154-1.00
7402-19c	7416-69c	7473-39c	7492-75c	74157-75c
74LS02-49c	7420-19c	7474-35c	7493-69c	74161-95c
7404-19c	7430-19c	74LS74-59c	7495-75c	74164-1.10
74LS04-29c	7432-34c	7475-69c	7496-89c	74165-1.10
74S04-44c	7437-39c	7476-35c	74121-38c	74174-95c
74LS04-49c	7438-39c	7480-49c	74123-65c	74181-2.50
7406-29c	7440-19c	7483-09c	74132-1.70	74191-1.25
7408-19c	7447-85c	7486-95c	74S138-1.95	74192-1.25
7410-19c	7448-85c	7488-45c	74141-75c	74193-1.00
TTL INTEGRATED CIRCUITS				
74195-69c				

**STICK IT!**  
in your clock  
in your DVM, etc.!

**Huge Special Purchase**  
Not Factory Seconds  
As sold by others!

**\$3.95**

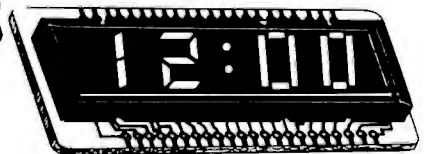

4 JUMBO .50"  
DIGITS ON  
ONE STICK!  
(with colons and  
AM/PM Indicator)

BUY 3 for \$10.

## BOWMAR 4 DIGIT LED READOUT ARRAY

The Bowmar Opto-Stick. The best readout bargain we have ever offered. Has four common cathode jumbo digits with all segments and cathodes brought out. Increased versatility since any of the digits may be used independently to fit your applications. Perfect for any clock chip, especially direct drive units like 50380 or 7010. Also use in freq. counters, DVM's, etc. For 12 or 24 hour format.

## UP YOUR COMPUTER!

### 21L02-1 1K LOW POWER 500 NS STATIC RAM TIME IS OF THE ESSENCE!

And so is power. Not only are our RAM's faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02-1 low power and super fast RAM's. Allows you to STRETCH your power supply farther and at the same time keep the wait light off. **8 for \$12.95**

**\$12.95** S.D. SALES EXCLUSIVE! **\$12.95**  
MOS 6 DIGIT UP-DOWN COUNTER  
40 PIN DIP. Everything you ever wanted in a counter chip. Features: Direct LED segment drive, single power supply (12 VDC TYP.), six decades up/down, pre-loadable counter, separate pre-loadable compare register with compare output, BCD AND seven segment outputs, internal scan oscillator, CMOS compatible, leading zero blanking, 1MHz. count input frequency. Very limited qty. **WITH DATA SHEET**

**WESTERN DIGITAL UART**  
No. TR1602B. 40 pin DIP  
This is a very powerful and popular part.  
**NEW-\$6.95 with data  
LIMITED QUANTITY**

**RESISTOR  
ASSORTMENT**  
1/4 W 5% and 10%  
PC leads. A good mix  
of values. **200/\$2.**

## FAIRCHILD BIG LED READOUTS

A big .50 inch easy to read character. Now available in either common anode or common cathode. Take your pick. Super low current drain, only 5MA per segment typical.

FND 510 Common Anode  
FND 503 Common Cathode  
**PRICE SLASHED! 59c each**

**TERMS:**  
Money Back Guarantee. No  
COD. Texas Residents add 5%  
tax. Add 5% of order for  
postage and handling. Orders  
under \$10. add 75c. Foreign  
orders: US Funds ONLY!

## SLIDE SWITCH ASSORTMENT

Our best seller. Includes miniature and standard sizes, single and multi-position units. All new, first quality, name brand. Try one package and you'll reorder more. **SPECIAL 12/\$1.**

## MOTOROLA POWER DARLINGTON

Back in Stock!  
Like MJ3001. NPN 80V. 10A.  
HFE 6000 TYP. TO-3 case.  
We include a free 723C volt  
reg. with schematic for power  
supply. **SPECIAL-\$1.99**

**CALL YOUR BANK  
AMERICARD OR MASTER  
CHARGE ORDER IN ON  
OUR CONTINENTAL  
UNITED STATES TOLL  
FREE WATTS:**

**1-800-527-3460**  
Texas Residents Call Collect  
**214/271-0022**

**S.D. SALES CO.**  
P.O. BOX 28810-D  
Dallas, Texas 75228

For orders over \$15.00 Choose \$1.00 FREE mdse.

# EDI

## ULTRASONIC TRANSDUCER

Transmits or receives 40K Hz ultrasonic waves. Used in building remote controls, for radios, TV's, appliances, remote switching, signaling and ultrasonic intrusion protecting devices and alarms.

M-1 **2.49**

## DYNAMIC TRANSISTOR CHECKER

Tests transistors in circuit or out of circuit. The Dynamic Transistor Checker lets you match transistors in working circuits to improve the operation. It will test Go and No Go at currents from 5ma to 50ma, and will show current gain, electrical open and short circuits. Tests low, medium and high power transistors both PNP and NPN types. Complete with transistor socket test clips and leads. Uses VM2 or C114 battery. Size of case 6" x 3 1/2" x 2".

F-144 **9.99**

## DC POWER SUPPLY

This DC power supply will deliver four ranges of DC voltages: 5V, 8V, 9V and 12V. It will supply a fully filtered output of one of these voltages at 150 milliamperes capacity. Can be used for any DC power supply within the voltage range and capacity such as operating a small battery radio, operating a small calculator, or powering miscellaneous laboratory experiments. Uses standard 117V 60C AC power. Output binding posts accept wire or banana plugs. With 4" x 1" cord and plug. Size of case 5" x 2 1/2" x 1 1/2".

F-145 **5.99**

## TRANSISTORIZED SIGNAL TRACER

EDI Special!!

This transistorized signal tracer can be used by technicians and service men to audibly trace signals of RF and IF and audio circuits from the antenna to the speaker stage by stage. An ideal tool for servicing audio equipment, amplifiers, tuners, receivers, turntables, etc. Has 2" speaker and test leads. Uses N556 9V transistor battery. Size of case 5" x 2 1/2" x 1 1/2". Leads and instructions included.

Was 17.88

F-171 **9.99**

## ELECTRONIC DUAL TRACE OSCILLOSCOPE CONVERSION INSTRUMENT

Convert Your Old Oscilloscope To Dual Trace With Simpson Model 318-SR.

Now you don't have to trade in your old oscilloscope. You now can easily convert it to an up-to-date dual trace scope with the Simpson model 318-SR conversion instrument. For just a fraction of Simpson's original suggested selling price of \$189.95.

Specifications: Switching Rates Approximately 150,000, 1,500,000 Hz. Signal Frequency Response: ± 100, 0-100K Hz. Maximum Signal Output: 25-Volt Peak to Peak Input Impedance: 100K-Ohm. Maximum Input At Max Gain: 5-Volt Peak to Peak. Dimensions: 11 1/2" x 7 1/2" x 7 1/2".

LIMITED QUANTITY

F-486 EDI Value Price **29.99**

## VOICE ACTIVATED SOLID STATE SWITCH

Locks on when activated and opens when circuit is momentarily disconnected. Features sensitivity adjustment.

S-45 **1.49** 3/4.00

## PANASONIC MODEL 450C-II CD-4 SEMICONDUCTOR TYPE STEREO CARTRIDGE

Special Diamond Stylus Tip • Stylus Pressure Range 1.5 to 2.5 gr.

Special!! **\$59.88 Value**

CB-11 **19.99**

## 24-KY DESK CALCULATOR KEYBOARD

Flash-type type contacts • Complete on circuit board • 12-line logic with 4-line switches • 2 1/2" x 5 1/2" x 1 1/2"

Highest price \$114. Lowest price \$3/5.50

E-206 **1.99**

## SPERRY-RAND UNIVAC KEYPUNCH KEYBOARD ASSEMBLY

A fantastic assembly filled with quality component parts. The ideal training keyboard, a super bargain on a complete "as-is" assembly. Size: 13" x 5 1/2" x 4 1/2". Shipping Wt. 1 1/2 lbs.

N-45 **18.99**

## PKG/10 1 1/2-VOLT HOBBY MOTORS

- High Torque Type, Small in Size
- Ideal For Hobbyists, Experiments, Etc.

X-11 **.99**

## 12 VOLT DC SPOT MINATURE COAXIAL RELAY

• 75 Ohm coil • Designed for efficient transfer of RF energy at extremely low loss

**1.99**

## PRECISION 1-RPM TIMING MOTOR

• Timing Motor For Clocks, Displays, Etc.

• Shipping Wt. 1/4-LB.

G-400 **.39** 3/1.00

## 4-RANGE DIGITAL READOUT INTERVAL TIMER KIT

• 4 time functions: 1-99 Sec., 1-99 Min., 1-99 Hr. • 1/2" High Nixie Tube Readouts • For darkroom use in both processing & enlarging processes • As a timer for sport & contest events (stop switch) • Provides timed 120V AC outlet and S.P. NO contact to trigger buzzer alarm or visual signal • Full Wiring Instructions included • No Cabinet Case Available For Timer.

E-207

100.00

VALUE

• Accurate to 1/10 of 1%

• LED for Visual Timing

**SPECIAL 19.99**

Send for free catalog - satisfaction guaranteed

Min. Order \$3.00 - Allow For Postage

Ill. Residents Add 5% Sales Tax

Prices good thru February 28, 1977 or while stocks last.

Notice: Some items may be of limited quantities and subject to prior sale.

ELECTRONIC DISTRIBUTORS, INC.

DEPT. PE 1-4900 ELSTON

CHICAGO, ILL. 60630

Tel: 312/283-4800

## CLUBS

HEY! Got Old Radio Programs, trade-em. Join International Club. \$2. Winslow, Box 281, Roosevelt, N.Y. 11575.

## REAL ESTATE

BIG...FREE...SPRING 1977 CATALOG! Over 2,600 top values coast to coast! UNITED FARM AGENCY, 612-EP, West 47th, Kansas City, MO 64112.

## EMPLOYMENT OPPORTUNITIES

OVERSEAS JOBS — NOW HIRING! High Pay! All Occupations. Transportation. Computerized Reports — \$2.00. TRANSWORLD, International Airport, 3623-N, Los Angeles, Calif. 90009.

AUSTRALIA — NEW ZEALAND, WANT YOU!!! 50,000 Jobs! Transportation! Latest information, \$2.00. AUSTCO, Box 3623-N, Long Beach, Calif. 90803.

ELECTRONICS/AVIONICS EMPLOYMENT OPPORTUNITIES. Report on jobs now open. Details FREE. Aviation Employment Information Service, Box 240E, Northport, New York 11768.


## RUBBER STAMPS

RUBBER STAMPS, BUSINESS CARDS. Many new products. Catalog: Jackson's, Dept. K, Brownsville Rd., Mt. Vernon, Ill. 62864.
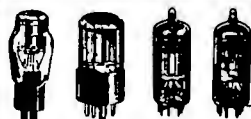
## DO-IT-YOURSELF

MODULAR TELEPHONES now available. Sets and components, compatible with Western Electric concept. Catalog 50 cents. Box 1147W, San Diego, California 92112.

WANT HELP? Where/what to buy, design, build, get working. All areas including audio; CB; Remote-Control; recording; security; telephone; TV; etc. For an informative answer fast, send letter with full particulars and \$8.00 to: E.R. Gunny, Consultant, 7612 Alverstone Avenue, Los Angeles, Calif. 90045.



## 70% OFF LIST!

1AD2	1.59	6AU8	2.15
1B3GT	1.58	6AV6	1.11
1K3	1.58	6AW8A	1.79
1S2A	2.27	6AX4GTB	1.52
1U4	1.58	6AY3B	1.52
1V2	.96	6AZ8	2.30
1X2B	1.56	6BA6	1.34
2AH2	1.59	6BA11	1.95
2AV2	1.26	6BE6	1.47
2D21	1.95	6BH11	1.77
2GK5	1.58	6BJ6	1.65
3A3C	1.61	6BK4C6	2.98
3A5	2.50	6BK7B	2.07
3AT2B	1.56	6BL8	1.10
3BS2	1.70	6BM8	1.10
3CU3A	1.95	6BN6	1.97
3CY3	1.76	6BN8	1.56
3DJ3	1.70	6BN11	2.46
3GK5	1.55	6BQ5	1.56
3HA5	1.53	6BQ7A	2.09
3HQ5	2.27	6BR8A	2.12
3JC6A	2.06	6BX6	1.49
3V4	1.83	6BZ6	1.26
4AU6	1.58	6C4	1.58
4BL8	.92	6CA7	1.60
4BZ6	1.41	6CA4	2.04
4CB6	1.10	6CB6A	1.32
4DT6	1.56	6CG3	1.58
4EH7	1.46	6CD6CA	2.83
4EJ7	1.46	6CG7	1.22
4HS8	1.50	6CG8A	1.73
4JC6A	2.04	6CJ3	1.50
4JD6	1.88	6CL3	1.61
4KE8	2.48	6CL6	2.07
4LJ8	1.80	6CL8	1.95
5A04	4.50	6CM7	1.71
5EW6	1.63	6CU5	1.65
5GH8A	1.88	6CW4	3.30
5GJ7	1.11	6CW5	1.02
5GS7	1.17	6DJ8	2.25
5GK7	1.68	6DL4	2.39
5H26	1.20	6DQ6	2.15
5JK6	1.47	6DT6A	1.32
5JL6	1.47	6DW4	1.50
5KE8	2.48	6DX8	1.01
5LJ8	1.76	6EA8	1.58
5U4GB	1.23	6EB8	2.40
5Y3GT	1.32	6EH7	1.53
5Y4GT	1.14	6EJ7	1.43
6A8	4.69	6EM7	2.25
6AB4	1.53	6EU7	1.61
6AC7	2.36	6EW6	1.43
6AC10	1.73	6EW7	2.38
6AD10	3.68	6F6GT	3.49
6AF4	2.21	6FG6	1.19
6AF9	2.13	6FG7	2.28
6AH6	2.94	6FM7	1.85
6AJ8	1.74	6GES	2.16
6AL3	.92	6GF7A	2.12
6AL5	1.31	6GH8A	1.26
6AN8A	1.82	6GJ7	1.11
6AQ5	1.35	6GK5	1.86
6AQ8	.98	6GK6	1.41
6AR5	.81	6GM6	1.68
6AS8	2.48	6GM8	3.30
6AU4GTA	1.97	6GS7	1.38
6AUSGT	2.41	6GU7	1.67
6AUGA	1.31	6GW8	.98

# EDLIE BARGAIN BONANZA OF HIGHEST QUALITY TUBES

BUY BRAND NEW MANUFACTURER'S BOXED TUBES (Raytheon, Dumont, IEC Mullard, etc.) AT 70% OFF LIST! HERE IS A BIGGER & BETTER LIST THAN WE EVER OFFERED BEFORE...AND REMEMBER... 70% OFF LIST!

ALL TUBES BRAND NEW MANU. BOXED 70% OFF


MINIMUM ORDER \$7.50

MONEY BACK GUARANTEE

Terms: Minimum order \$7.50. Include postage. Either full payment with order or 20% deposit, balance C.O.D.

6GX6	1.38	6JH8	2.51
6H6	2.71	6JM6A	2.16
6HA5	1.53	6JN6	2.03
6HB7	1.55	6JR6	3.54
6HE5	1.91	6JS6C	2.95
6HF5	3.78	6JT6	2.40
6HF8	2.16	6J78	1.91
6HQ5	2.03	6JU6	2.84
6HS5	2.94	6JH8	1.77
6HS6	1.46	6JV8	1.80
6HS8	1.91	6JW8	1.35
6HV5	3.54	6KG6T	1.64
6JZ6	1.28	6K7GT	2.24
6JH6	1.89	6K8	4.69
6J7	2.31	6KA8	1.95
6J10	2.45	6KD6	3.38
6JB6	2.42	6KE8	2.45
6JCSA	1.79	6KM6	3.38
6JD6	1.85	6KT8	2.18
6JEGC	3.35	6KV6A	2.67
6JG6A	2.67	6KZ8	1.64
6JH6	1.43	6L6	4.86

WRITE FOR FREE VALUE PACKED CATALOG

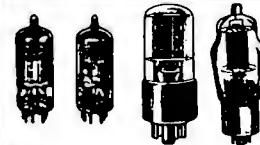

## 70% OFF LIST!

6L7	2.84	12BH7A	1.58
6LB6	3.23	12BY7	1.43
6LE8	2.27	12DQ6B	2.10
6LF6	3.20	12FX5	1.34
6LF8	2.34	12GN7	2.22
6LJ8	1.76	12HL7	1.95
6LM8	1.95	12JB6A	2.55
6LN8	1.05	12MD8	1.77
6LT8	1.64	12SL7	2.31
6LU8	1.92	13GF7A	2.09
6LX8	1.05	13Z10	2.55
6M11	2.76	148L11	3.11
6MB8	1.52	158D11A	2.25
6MD8	2.34	15CW5	.87
6SA7	2.04	15KY8A	2.91
6SG7	2.30	16A8	1.23
6SJ7	2.19	16L8A	2.97
6SK7	2.03	17AY3A	1.52
6SL7GT	2.30	17BE3	1.52
6SN7GT	1.52	17BF11	2.39
6SQ7	2.01	17BR3	1.23
6T8A	1.92	17BS3	1.52
6T10	2.25	17CK3	1.31
6U8A	1.56	17CU5	1.26
6U10	1.62	17DW4	1.41
6V6	3.57	17JN6	2.16
6X4	1.46	17JQ6	1.85
6X5GT	1.47	17JZ8	1.43
6X9	1.82	19CG3	1.58
7F8	6.00	20AQ3	1.17
7V7	3.00	21GY5	2.01
8A8	.93	21HB5	1.92
8AC9	1.88	21JS6	4.30
8AR11	2.46	21JZ6	2.10
8B10	1.80	21LR8	1.89
8BA11	2.25	21LU8	1.86
8BM11	2.30	22JF6	2.66
8BQ11	1.98	22JR6	2.73
8BU11	2.30	22KM6	3.08
8CG7	1.12	23Z9	1.91
8JH8	1.86	24JEGC	3.20
8LT8	1.61	25CG3	1.38
9A08	2.31	29KQ6	3.53
9GH8	1.67	30AE3	1.17
9JW8	1.26	31JS6C	2.89
10CW5	1.02	31LQ6	3.05
10DX8	.98	31LZ6	3.38
10GK6	1.82	33GY7A	2.42
10GN8	1.92	35C5	1.31
10JT8	2.06	35W4	.89
10JY8	1.50	35Z5GT	1.41
10KR8	2.04	36KD6	3.36
11AF9	2.13	38HE7	2.92
11AR11	2.46	38KH7	2.86
11BM8	1.86	40KGA	3.26
11FY7	1.52	42EC4A	1.59
11KV8	2.20	42KN6	2.75
11MS8	1.53	50B5	1.21
12AB5	1.41	50C5	1.23
12AT6	1.13	50EH5	1.47
12AT7	1.37	50GY7A	3.60
12AU7A	1.23	50L6GT	1.95
12AV6	1.02	80	1.88
12AX7A	1.13	6267	2.10
12AZ7A	1.74	6973	1.85
12B4A	1.77	7025A	1.13
12B6A	1.16	7189A	1.73
12BE6	1.22	7199	2.06

EDLIE ELECTRONICS, INC.

2700-KP HEMPSTEAD TPKE., LEVITTOWN, N. Y. 11756



# World's Lowest IC Prices

\* SPECIAL PRICES \*

MEMORIES					
Rams	74152	.90	HIGH SPEED	4007	.16
2102	74155	.60	74H00	4008	.70
Proms	74157	.60	74H01	4011	.16*
82523/123	74160	.75	74H04	4012	.30*
	74161	.75*	74H10	4015	.80
			74H11	4016	.35*
TTL	74163	.75*	74H40	4019	.70
7400	74165	.80	74H51	4020	.90
7402	74173	1.25	74H52	4021	.95
7403	74174	.75	74H74	4023	.16*
7404	74175	.75*	74H103	4024	.75
7407	74177	.70	74H106	4025	.20*
7410	74180	.80		4027	.40
7420	74181	1.50	LOW POWER	4028	.60
7427			SCHOTTKY	4030	.35
			74LS00	4040	.60
	74192	.70*	74LS02	4042	.75
7438	74193	.70*	74LS06	4043	.70
7440	74194	.85	74LS10	4044	.75
7441	74198	1.25	74LS27	4047	.70
	9602	.50*	74LS73	4049	.35*
7445	9300	.75	74LS75	4050	.35*
7447	9312	.70	74LS151	4066	.65
7450			74LS153	4068	.35
7451	SCHOTTKY		74LS157	4069	.16
7473	74S01	.25	74LS161	4071	.16
7474	74S02	.25	74LS163	4073	.16
	74S37	.40	74LS164	4075	.16
7480	74S38	.60	74LS174	4516	.85
	74S85	2.00	74LS175	4528	.75
7493	74S113	.80	74LS193	4585	.85
7495	74S139	1.50	74LS221	4586	.90
74107	74S140	.50	74LS251	4587	.90
74109	74S153	2.50	74LS253	4588	.90
74116	74S172	4.05	74LS257	4589	.90
74118	74S174	2.05	74LS258	4590	.90
74141	74S175	2.05*	CMOS		
74145	74S181	4.5*	4001	16*	.16
74150	74S197	2.20	4002	16	.567V
74151	74S257	1.50	4006	90	1.35

Order Minimum \$10.00. Add \$1.00 shipping and handling charge per order. California residents add 6% sales tax. All orders shipped First Class within 24 hours.

Order the famous lasis 6 volume Programmed Learning Course "Microcomputer Design is a Snap" for \$99.50 and receive a special \$10.00 credit on any group of IC's.

Satisfaction 100% guaranteed.

C.O.D. Orders. Phone (day or night) 408-354-1448

## ELTRON

PO BOX 2542A  
Sunnyvale, CA 94087

Free monthly catalog—Just send us your name and address

CIRCLE NO. 29 ON FREE INFORMATION CARD

## COLOR TV CHASSIS AND PARTS

New 1976 moeld solid state Color TV chassis and parts for use with In-Line black matrix picture tubes. They have the following features: micro-circuit technology; energy save feature; one button color tuning AFC; and super low power consumption.

We basically have two chassis: the TS951 and TS953, used to drive either 13", 15" or 19" picture tubes. Parts to be added to make a complete TV include: UHF and VHF tuners (for 19"); picture tube, tube shield; purity magnets; antenna; yoke; speaker; binding posts; cabinet; controls for 19" (on-off and four-10K pots); and 2nd stage hi-voltage boost (for 13" and 15").

We don't have a complete package, but we do have some parts available at this time. Add a few parts... a TV for 1/2 price!

13" TV Chassis (with tuners & controls)... 6Z60175... \$49.50

15" TV Chassis (with tuners & controls)... 6Z60174... \$49.50

19" TV Chassis (no tuners, no controls)... 6Z60172... \$29.50

VHF Tuner . 6Z60303 \$.85 UHF Tuner . 6Z60304 . \$2.50

Antenna . 5MI00419 . \$1.50 TV Speaker . 6Z60177 . \$3.50

Binding Posts 4MI00442. \$1.50

## INPUT/OUTPUT TERMINAL

These units were removed from a complex computer system. The terminal contains: ASC11 keyboard; CRT; drive circuits; and a complete 128 page tech. manual with operating and repair instructions, which makes it easy to modify the terminal for your applications. (Character generation unit was in a separate control device which is not supplied, but the terminal can be used in conjunction with character generator LSI chips, such as the 2513 or 2516).

The keyboard is ASC11 encoded, with a 50 key alpha-numeric (and others) block keyboard. The CRT displays up to 768 characters, depending on the desired size, approximately typewriter size up to 1/4". Great for microprocessor in/out. Sh. Wt. 35 Lb. Order # 6NB0336 - \$49.50 ea., or 2 for \$95.00, 4 for \$180.00

## B&F ENTERPRISES

POSTAGE: Please add sufficient postage.

119 FOSTER STREET

PEABODY, MA. 01960

Phone (617) 531-5774

SEND FOR OUR FREE CATALOG!

Over 4,000 electronic & optical items

PHONE ORDERS WELCOME! MasterCharge, BankAmericard and American Express Accepted.

## B&F

CIRCLE NO. 13 ON FREE INFORMATION CARD

2522 STATIC SHIFT RE6	\$2.75
INTEL 8080 CPU	\$24.50
2518-HEX 32 BIT SR	\$5.00
2102-1 1024 BT RAM	\$1.80
5280-4K DYNAMIC RAM	\$10.50
5202A UV PROM	\$10.50
MM5203 UV PROM	\$10.50
1702A UV PROM	\$10.75
5204-4K PROM	\$18.95
MINIATURE MULTI-TURN TRIM POTS	
100, 500, 2K, 10K, 100K, 200K	
\$1.50 each	
MULTI-TURN TRIM POTS Similar to Bourns	
3010 style 3/16"x5/8"x1/4"; 50, 100, 1K, 10K, 50K ohms	
\$1.50 ea.	
LIGHT ACTIVATED SCR's	
TO-18, 200V 1A.	\$1.75

### TRANSISTOR SPECIALS

2N3585 NPN Si TO-66	.95
2N3772 NPN Si TO-3	1.60
2N4908 PNP Si TO-3	1.00
2N6056 NPN Si TO-3 Darlington	1.70
2N5088 PNP Si TO-92	4/5 1.00
2N4988 PNP TO-66	.60
2N404 PNP GE TO-5	5/5 1.00
2N3919 NPN Si TO-3 RF	1.50
MP5A 13 NPN Si TO-92	3/5 1.00
2N3767 NPN Si TO-66	.70
2N2222 NPN Si TO-18	5/5 1.00
2N3055 NPN Si TO-3	.80
2N3904 NPN Si TO-92	5/5 1.00
2N3906 PNP Si TO-92	5/5 1.00
2N5296 NPN Si TO-20	.50
2N6109 PNP Si TO-220	.55
2N3638 PNP Si TO-5	5/5 1.00
2N6517 NPN TO-92 Si	3/5 1.00

### CMOS (DIODE CLAMPED)

74C02 - 22	4015 - 95	4035 - 1.10
74C10 - 22	4016 - 40	4042 - .78
4001 - 22	4017 - 1.05	4047 - 2.00
4002 - 22	4018 - 1.00	4049 - .40
4006 - 1.20	4019 - .22	4050 - .40
4007 - 22	4022 - 95	4065 - .80
4008 - 42	4027 - 40	4071 - .72
4010 - 42	4028 - .88	4076 - .70
4011 - 22	4029 - 1.10	4081 - .22
4012 - 22	4030 - .22	4520 - 1.15
4013 - .40		

### LED REDOUTS

FND 500-5" C.C.	\$1.75
HP 7740-3" C.C.	\$1.40
MANV-3" C.A.	\$1.25
NS 33-3 dig. array	\$1.35
DL 747	\$2.50

Send 25¢ for our catalog featuring Transistors and Rectifiers 145 Hampshire St., Cambridge, Mass.

Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage. Minimum Order \$5.00, C.O.D. \$20.00

### PRINTED CIRCUIT BOARD

4-1/2" x 6-1/2" SINGLE SIDED EPOXY BOARD 1/16" thick, unetched	
5.50 ea.	5/52.20
VECTOR BOARD 1" SPACING	
4.5" x 6" SHEET	\$1.25
7WATT LD-65 LASER DIODE IR	\$8.95
2N 3820 P FET	.45
2N 5457 N FET	.45
TIS 43 UJT	.35
ER 900 TRIGGER DIODES	4/51.00
2N6028 PROG. UJT	.65

### VERIPAX PC BOARD

This board is a 1/16" single sided paper epoxy board, 4 1/2" x 6 1/2" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with busses for power supply connector. \$4.00

MV 5891 YELLOW-GREEN BIPOLAR LED \$1.25

FP 100 PHOTO TRANS. \$1.50

RED, YELLOW, GREEN OR

20 AMBER LARGE LED'S .ea. \$ .20

14 PIN DIP SOCKETS \$ .25

16 PIN DIP SOCKETS \$ .28

MOLEX PINS 1000/\$1.00

8 PIN MINI DIP SOCKETS \$ .25

10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 12, 15, 18, 22, 100, 150 or 200V .ea. \$ .60

1 WATT ZENERS 4.7, 5.6, 10, 12, 15, 18 OR 22V .ea. \$ .25

### Silicon Power Rectifiers

PRV	1A	3A	12A	50A	125A
100	.06	.14	.30	.80	.370
200	.07	.20	.35	1.15	4.25
400	.09	.25	.50	1.40	6.50
600	.11	.30	.70	1.80	8.50
800	.15	.35	.90	2.30	10.50
1000	.20	.45	1.10	2.75	12.50

### SILICON SOLAR CELLS

2 1/4" diameter

.4V at 500 ma. . . \$5.00 ea., 6/\$27.50

### REGULATED MODULAR POWER SUPPLIES

+15 VDC AT 100ma	\$27.95
115VAC INPUT	\$24.95
5VDC AT 1A, 115VAC INPUT	\$24.95
12 VDC AT 5 AMP	\$24.95
IN 4148 (IN914)	15/\$1.00

### TANTULUM CAPACITORS

22UF 35V 5/1.00	4.7UF 35V 4/1.00
47UF 35V 5/1.00	6.8UF 35V 3/1.00
68UF 35V 5/1.00	22UF 35V .50
11UF 35V 5/1.00	33UF 35V .50
22UF 20V 5/1.00	30UF 6V 5/1.00
3.3UF 35V 4/1.00	100UF 5V .50
	150UF 15V .50
M7001 ALARM CLOCK CHIP	\$6.00

### NATIONAL MOS DEVICES

MM1402 - 1.75	MM5057 - 2.25
MM1403 - 1.75	MM5058 - 2.75
MM1404 - 1.75	MM5059 - 2.75
MM5013 - 2.50	MM5061 - 2.50
MM5016 - 2.50	MM5555 - 4.75
MM5017 - 2.70	MM5556 - 4.75
MM5055 - 2.25	MM5210 - 1.95
MM5056 - 2.25	MM5260 - 1.75

### TTL IC SERIES

7400 - 15	7442 - 52	74125 - 40
7401 - 15	7445 - 70	74126 - 40
7402 - 15	7446 - 70	74151 - 70
7403 - 15	7447 - 70	74153 - 65
7404 - 20	7448 - 70	74154 - 1.10
7405 - 20	7450 - 20	74155 - 70
7406 - 25	7472 - 33	74157 - 70
7407 - 25	7473 - 35	74161 - 85
7408 - 25	7474 - 35	74164 - 95
7409 - 21	7475 - 49	74165 - 1.05
7410 - 15	7476 - 35	74173 - 1.40
7411 - 20	7480 - 35	74174 - 95
7412 - 20	7483 - 70	74175 - 92
7413 - 45	7485 - 88	74177 - 79
7414 - 70	7486 - 30	74180 - 70
7415 - 25	7489 - 1.85	74181 - 2.10
7417 - 25	7490 - 45	74190 - 1.20
7420 - 20	7491 - 70	74191 - 1.20
7425 - 28	7492 - 50	74192 - 85
7426 - 25	7493 - 45	74193 - 85
7427 - 20	7494 - 35	74194 - 85
7430 - 20	7495 - 70	74195 - 75
7432 - 25	7496 - 70	74196 - 88
7437 - 25	74107 - 32	75324 - 1.75
7438 - 25	74121 - 38	75491 - 65
7440 - 16	74123 - 65	75492 - 65
7441 - 85		

### MINIATURE DIP SWITCHES

CTS-206-4 Four SPST switches in one minidip package.	\$1.75
CTS-206-8 Eight SPST switches in a 16 pin DIP package.	\$2.85

AY-5113-A30K ser./par., par./ser., universal UART. . . . \$6.95

ALCO MINIATURE TOGGLE SWITCHES	
MTA 106 SPDT	\$1.20
MTA 206 DPDT	\$1.70

### Full Wave Bridges

PRV	2A	6A	25A
200	.95	1.25	2.00
400	1.15	1.50	3.00
600	1.35	1.75	4.00

### SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	\$ 7.50
Si 1020 G 20 WATTS	\$12.95
Si 1050 G 50 WATTS	\$25.95

### CCD 110 LINEAR 256 X BIT SELF

SCANNING CHARGED COUPLED DEVICE \$99.00

CCD 301 - 100 x 100 CHARGE COUPLED DEVICE \$135.00

### LINEAR CIRCUITS

LM307 - Op. Amp.	\$ .30
LM 308K 5V 1A REGULATOR	.95
723 - 40 + 40V REGULATOR	.50
301/748-Hi Per. Op. Amp.	.31
320T 5, 12, 15, or 24V NEG REG	\$1.25
709C - Op. Amp.	.31
741A or 741C OP AMP.	.31
710 COMPARATOR	.35
CA 3047 Hi Per. Op. Amp.	.95
340T 5, 8, 12, 15, 18, 24V POS REG. TO-220	\$1.10
101 OPER. AMP. HI PERFORM.	.75
LM 308 Op. Amp., Low Power	.95
747 - DUAL 741	.65
556 - DUAL TIMER	\$1.00
537 - PRECISION OP. AMP.	\$1.70
LM 3900 - QUAD OP. AMP	.49
LM 324 - QUAD 141	\$1.50
560 - PHASE LOCK LOOP	\$2.00
561 - PHASE LOCK LOOP	\$2.00
565 - PHASE LOCK LOOP	\$1.25
566 FUNCTION GEN.	\$1.65
567 - TONE DECODER	\$1.50
LM 1310 FM STEREO DEMOD.	\$2.75
8038 IC VOLTAGE CONT. DSC	\$3.90
LM 370 - AGC SQUELCH AMP.	\$1.15
555 - 2us - 2 HR. TIMER	.45
555 QUAD TIMER	\$2.50
FCD 810 OPTO-ISOLATOR	.80
1458 DUAL OP AMP.	.80
LM 380 - 2W AUDIO AMP.	.95
LM 377 - 2W Stereo Audio Amp.	\$2.50
LM 381 - STEREO PREAMP	\$1.50
LM 382 - DUAL AUDIO PREAMP	\$1.50

# Popular Electronics

## FEBRUARY 1977 ADVERTISERS INDEX

READER SERVICE NO.	ADVERTISER	PAGE NO.
1	A P Products, Inc.	39
2	Ace Electronics	98
3	Acoustic Fiber Sound Systems, Inc.	29
4	Adva Electronics	98
6	Advanced IC Electronics	97
7	Advanced Microcomputer Products	102
8	Allison Automotive Company	48
9	Aluminum Industries of Arkansas	61
65	American Audioport	95
10	Anconra Corp	113
11	Aries, Inc.	115
12	Associated Electronics	74
69	Audio Technica U.S., Inc.	16
13	B&F Enterprises	114
14	B&K Precision, Product of Dynascan	27
17	Bullet Electronics	106
16	CB Radio Repair Course, Inc.	94
	CREI Capitol Radio Engineering Institute	18, 19, 20, 21
	Cleveland Institute of Electronics, Inc.	52, 53, 54, 55
15	Cobra, Division of Dynascan	SECOND COVER
18	Continental Specialties Corporation	2
19	Delta Products, Inc.	65
20	Digi-Key Corporation	107
21	Digital Group, The	88
68	Discwasher, Inc.	FOURTH COVER
	Dixie Hi-Fidelity	93
22	EICO	14
23	Edlie Electronics, Inc.	112
24	Edmund Scientific Co	108
25	Edmund Scientific Co	116
26	Edmund Scientific Co	116
28	Electronic Distributors Inc.	112
29	Eltron	114
30	Empire Scientific Corp	6
32	Godbout Electronics, Bill	106
34	Grantham School of Engineering	92
5	Heath Company	70, 71, 72, 73
35	IMSAI Manufacturing Corporation	30
36	Ignition Systems Inc.	94
37	Illinois Audio	96
38	International Electronics Unlimited	110
67	JS&A	1
39	Jama Electronics	104, 105
40	Jensen Tools and Alloys	93
41	LDF Semiconductor	94
42	Leader Instrument Corp	39
43	MITs	36
44	McIntosh Laboratory Inc.	93
	NRI Schools	8, 9, 10, 11
	National Technical Schools	80, 81, 82, 83
45	New-Tone	103
46	OK Machine & Tool Corporation	67
66	Olson Electronics	96
47	Optoelectronics	109
48	PAIA	94
49	Poly Paks	101
50	Poly Paks	102
51	Polymorphic Systems	92
52	Quest Electronics	106
53	Radio Shack	5
54	S.D. Sales Co	111
55	Sencore	68, 69
56	Shakespeare Company/Antenna Group	33
57	Shure Brothers Inc.	84
	Sinclair Instruments Inc.	91
58	Solid State Sales	114
59	Southwest Technical Products Corp.	7
60	Stanton Magnetics, Inc.	THIRD COVER
	Surplus Center	97
27	Tab Books	76
61	Technics By Panasonic	13
62	Technology Trends	89
63	Tram/Diamond Corporation	35
64	Weller-Xcelitem Inc.	90

CLASSIFIED ADVERTISING  
97, 98, 102, 106, 108, 110, 112, 115

FEBRUARY 1977

## HOME ENTERTAINMENT FILMS

**SPEND CHRISTMAS DOLLARS ON SPORTLITE FILMS!** Don't Wait / See Super Bowl X (Pittsburgh Steelers / Dallas Cowboys), 200' Color, Super or Standard 8, \$19.95 or 200' of B&W, \$8.95 — we pay the postage. 1975 Indy "500" Speedway Spectacular, 200' of Super 8 Eastman Color, \$18.95 PPD with script. 1975 World Series (Red Sox / Cincinnati Reds — 7 games to a virtual draw), same format as football, \$19.95 Color, \$8.95 B&W each PPD. Indicate size. Columbia and Castle Catalogs, 50 cents each; Sportlite order forms, 35 cents (coins or stamps, pls). SPORTLITE, Elect-2, 20 North Wacker, Chicago, IL 60606.

## BUSINESS OPPORTUNITIES

**I MADE \$40,000.00 Year by Mailorder!** Helped others make money! Free Proof. Torrey, Box 318-NN, Ypsilanti, Michigan 48197.

## HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Postcard brings facts about this unusual opportunity. Write today! Barta-DM, Box 248, Walnut Creek, CA 94597.

**HOW TO MAKE \$2,000 WEEKLY** at home using other people's money. Guaranteed. Free Details. Richlieu, Box 25357, Dept. F2, Houston 77005.

**\$200.00 DAY POSSIBLE.** Must know electronics. Preliminaries \$3.50. Box 809, Boynton Beach, Fla. 33435.

**\$250 per thousand, free supplies.** Rush stamped, addressed envelope. Lola Hamilton, E-12, P.O. Box 227, Princeton, ME 04668.

**FREE CATALOGS.** Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

**MAILORDER MILLIONAIRE** helps beginners make \$500 weekly. Free report reveals secret plan! Executive (1K2), 333 North Michigan, Chicago 60601.

**GET RICH** with Secret Law that smashes debts and brings you \$500 to \$5 Million cash. Free report! Credit 4K2, 333 North Michigan, Chicago 60601.

**FREE SECRET BOOK "2042 UNIQUE, Proven Enterprises"** Fabulous "Little Knowns". Work home! Haylings-B, Carlsbad, Calif. 92008.

**SPARE TIME CASH.** Sell famous Hanover Shoes. Samples, sales kits free. No experience needed. No age limit. Big commissions. Hanover Shoe, Dept. 1818, Hanover, PA 17331.

**\$193.00 WEEKLY. GUARANTEED!** Your home. One hour daily. Free details — Professional. Box 24543-X, Saint Louis, Missouri 63141.

**BIG PROFIT** in Real Estate, learn from an expert how to successfully buy and sell residential and investment properties, plus BONUS Real Estate definitions \$2.95: LINPAUL ENTERPRISES, Box 60, Dept. PE 21, West New York, N.J. 07093.

**FREE: CASH NEWSLETTER** with: How To Make \$50 Anytime you need it, guaranteed. Plus: How to start \$20,000+ business (nothing to buy, ever) working five hours weekly. All only \$2: CASHCO, 2232-E Arrowhead Ave., Brooksville, FL 33512.

## BOOKS AND MAGAZINES

**FREE book prophet Elijah** coming before Christ. Wonderful bible evidence. Megiddo Mission, Dept. 64, 481 Thurston Rd., Rochester, N.Y. 14619.

**THE AUDIO AMATEUR**—A quarterly publication for the serious audio constructor. Free prospectus. The Audio Amateur, Box 176Z, Peterborough, N.H. 03458.

**ELECTROPLATING.** Complete amateur's textbook. All metals. Electroplate metallic/nonmetallic items. \$7.00. Details free. Tropic, Box 95-P2, Palm Bay, Fla. 32905.

## MUSICAL INSTRUMENTS

**UP TO 60% DISCOUNT.** Name brand instruments catalog. Freeport Music, 114 G. Mahan St., W. Babylon, N.Y. 11704.

## MISCELLANEOUS

**WINEMAKERS:** Free illustrated catalog yeasts, equipment. Semplex, Box 12276P, Minneapolis, Minn. 55412.

**NEW LUXURY CAR** Without Cost. Free Details! Codex-ZZ, Box 6073, Toledo, Ohio 43614.

**ARIES** brought you the first calculator kit, and the first digital clock kit... and now brings you three of the most innovative electronic kits ever made. The System 300 Electronic Music Synthesizer kit is the most advanced in the world today, regardless of price. The AR-781 is a space-age beauty for any decor. And the wholly solid state AR-830 does the work of a \$400.00 tape memory unit.




**WARNING...** if you're interested in a music synthesizer, don't make a move until you see our catalog first. It's more like a handbook than a catalog, with hundreds of in-depth photographs and descriptions to explain electronic music principles, and to show equipment to do the job. **ARIES** now offers a complete complement of modules, keyboards, and cases, matched to the most rigorous professional standards. Starter systems priced as low as \$395.00.

A clear, ruby-red cylinder shows off all six digits of this modern calendar clock. Easy-to-read numbers show the hours, minutes, and seconds, as well as the month and day every ten seconds. Red LED 7-segment numerals are 0.33" high, in a sturdy cylinder 2-1/2" in diameter and 4-3/4" long, with finished hardwood ends. Time and calendar are controlled by 60 Hz line frequency, with a 12-month movement. Separate time and calendar adjustments. Includes all the components, PC boards, housing, and instructions. Shipping weight 2 lbs. **AR-781 Clock Kit** .....\$34.50



Add finger-touch operation to your old-fashioned dial telephone with an **ARIES AR-830 Automatic Digital Telephone Dialer**. This has the same layout and convenience as Ma Bell, plus other features she doesn't offer yet. For instance... AR-830 always remembers the last number you dialed, in case the line was busy and you want to try again later. Not only that, but the Dialer's memory can store as many as ten of your favorite numbers for one-touch dialing. AR-830 uses standard dialing and muting contacts; consult local tariffs before connecting. Sh. wt. 2 lbs. **AR-830 Dialer Kit** .....\$69.50

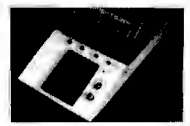

**ARIES INC.**  
BOX 808  
Peabody, Mass., 01960  
(617) 744-2400

CIRCLE NO. 11 ON FREE INFORMATION CARD

## Retail Display Plan

All magazine retailers in the United States and Canada interested in earning an allowance for the display and sale of publications of the Ziff-Davis Publishing Company are invited to write for details. Sales Manager, Select Magazines, 229 Park Avenue South, New York, New York 10003.

## AMAZING & HARD-TO-FIND SCIENCE BUYS! ALTERNATE ENERGY SPACE AGE • HOBBIES

### SUPER POWER FOR ANY AM RADIO

Antenna assist has pulled in stations 1000 miles off! No. wires, clips, grounding. Solid state—no elec., batts., tubes. No. 72,095AVB \$19.95 Ppd. ULTRA SELECT-A-TENNA (OVER 1000 MILES) No. 72,147AVB .....\$24.95



### SOLAR ENERGY CUBE

Demonstration of sunlight converting to kinetic energy! Clear plastic cube in sun with its 3 silicon solar cells powers motor to whirl the propeller. Actually produces 1.5v DC, 825 ma.



No. 42,287AVB (4x4x4") .....\$23.95

### SAVE 50%! 8 x 20 MONOCULAR

Top quality Spy Scope, a \$30 value, now \$14.95! Special purchase saves you 50%. 100% coated optics; 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove box. No. 1568AVB \$14.95 Ppd.



### NASA-CHOSEN FOR APOLLO/SOYUZ

The Astronauts used this super 20X60 binocular (modified) to view Earth! Big 60 mm objective lenses; 173-ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics, more!



No. 1556AVB .....(9 1/4 x 8 1/4"); 47.5 oz) \$99.95 Ppd.

### ELECTRONIC SOUND COLLECTOR

Tune in a whisper at 20 ft., normal conversations up to 100 ft., birdcalls & high freq. sounds at almost 200 ft. Nearly twice as far over water! Check on baby, birds! 18" refl. disc, mike, etc. No. 80,176AVB \$36.25 Ppd.



### LOW COST PORT. INFRA-RED EYE

Self-cont. scope (90° nite vision) has 6032 IR converter tube, f/3.5 telephoto lens, adjust. triplet eyepiece. 1.6X Not avail. to Cal. res. except spec. auth'd.



No. 1683AVB (6.12v DC) .....\$299.95 Ppd.  
No. 1685AVB (SUPER 2.5X BINOC.) \$329.95 Ppd.

### MEASURE WIND SPEED ANYWHERE

Hold handy (16 oz.) low cost Anemometer into the wind, quickly read wind speed on its big dial—from 5 to 70 mph. Acc. to ±3% of full scale (2.1 mph); no batts., adjustments, recalibration req'd.



No. 42,428AVB (7 1/2" HIGH) .....\$19.95 Ppd.

### OUR MYSTICAL MUSICAL MACHINE

... gets it on! Automatic 256-note pseudo-random tone pattern. Adjust beat, vol., pitch; finger 3 photocells to creatively vary tone of continuous "music." Output jack for patching, recorder! 1.3 lb.



No. 72,203AVB (INCL. 9v BATT.)...\$59.95 Ppd.

### 110V FUEL MISER RECLAIMS HEAT

Save your 40% wasted heat to warm a basement, garage, rec. rm. at no extra cost! Direct it your way instead of up the chimney. Fan-forced clean hot air via easy ducting!




No. 19,194AVB (5" DIA.) Shpg. 17 lb. ...\$121.50 FOB  
No. 19,195AVB (6" DIA.)

### QUALITY DETECTOR UNDER \$40

Our fully transistorized BFO unit can locate a quarter at 18". Powerful 6 trans.-oscillator-amplifier circuit. Comp. to others priced 50% more! Aluminum, just 2 lb.



No. 80,222AVB \$39.95 Ppd.

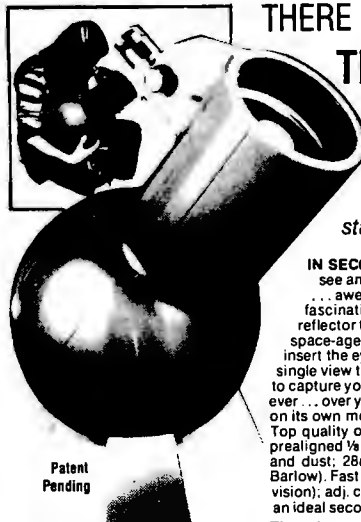

## THERE IS NO OTHER TELESCOPE LIKE IT! THE NEW EDMUND 4 1/4", f/4 NEWTONIAN WIDE FIELD REFLECTOR TELESCOPE

Clear, bright, spectacular wide angle views of stars, moon, comets... easy to use... portable!

IN SECONDS YOU'RE SCANNING THE ASTOUNDING UNIVERSE, able to see and study the breath-taking cosmos as perhaps you never have before... awesome vastness, unbelievable orderliness, stark silent beauty. All the fascinating heavenly mysteries are yours to enter and explore. This new reflector telescope makes it easy for everyone to span a thousand light-years to space-age enjoyment of the heavens and outdoors. No complicated set up! Just insert the eyepiece, focus, and its big 3 1/2" field of view gives you more stars in a single view than any other type of telescope. Bright, crisp, finely resolved images to capture your interest and imagination. It's probably the easiest to use telescope ever... over your shoulder, in your lap, on a tripod. Or just rotate the spherical base on its own mount for use on a table, car hood. Take it anywhere (only 17", 10 lb.). Top quality optical system: 4 1/4", f/4 parabolic primary mirror (1/4 wave, 17" F.L.); prealigned 1/4 wave diagonal on a coated optical window seals optics from moisture and dust; 28mm Kellner eyepiece (gives 15X, higher without other eyepiece or Barlow). Fast focusing (25" to infinity). Bright Scharfian red (doesn't impair night vision); adj. carrying strap. A "first" scope "must", an ideal second scope!

There is no other telescope like it.

NO. 2001AVB \$149.95 Ppd.

### The Edmund BIOSONE II

turns brainwaves into an audible or visual signal. \$149.95

## KNOW YOUR ALPHA FROM YOUR THETA!

For greater relaxation, concentration... monitor your alpha/theta brainwaves.

Features Normally Found Only In Units Selling For More Than \$200.00—And 3 Feedback Modes.

The portable, professional quality Edmund Biosone II boasts 3 feedback modes—LED FM tone, threshold tone; a test mode to check overall system of operation. Easy to use, this beautiful 4-pound, simulated walnut unit (9 1/2 x 5 1/4 x 4 1/4") can be operated at home, in office or clinic. It gives you outputs to allow further monitoring of logic signal, raw EEG, filter output, meter, and FM. Total brainwave monitoring capability, incl. filter select feedback, with wide range calibration sensitivity control (5-100 microvolts). Completely safe, the Edmund Biosone II is similar to an electroencephalograph (EEG), enabling you to identify the electrochemical activity that exists at all times in the human brain. In addition to letting you know when you're most relaxed, Biosone II is a great conversation piece. Included at its low price are a set of electrodes, an earphone jack for private use. Uses latest advances in linear circuitry, runs on two 9v transistor batteries (not included).

STOCK NO. 1668AVB ..... Just \$149.95 ppd.  
LOW COST STARTERS' UNIT, No. 71,809AVB ..... \$59.95 ppd.

## "SEE" MUSIC IN PULSATING COLOR



The Edmund 3-Channel Color Organ \$18.50

COMPLETELY ASSEMBLED! LESS THAN HALF THE PRICE OF OTHER MODELS!

Create your own audio "light show", add a new dimension to your music listening pleasure with the bargain-priced Edmund 3-Channel Sound To Light Control. Lets you modulate 3 independent strings of colored lamps with the intensity of your music. They flash and vary in brightness related to the music's rhythm, pitch and volume—a pulsating light performance to music! You get volume and frequency sensitivity to a peak rating of 300 watts per channel. Just plug in your favorite colored flood or spotlight, and turn on! Great price, too. This high quality, fully assembled unit in metal housing, with 3 individually controlled circuits, is priced at less than half that of others. Complete instructions are included with this terrific value.

ASSEMBLED \$18.50 Ppd.  
NO. 42,309AVB

UNASSEMBLED, IN KIT FORM \$15.95 Ppd.  
No. 42,336AVB ONLY

GIANT FREE  
164 PG. CATALOG



4500 UNUSUAL BARGAINS  
FOR HOBBYISTS,  
SCHOOLS, INDUSTRY

## COMPLETE AND MAIL COUPON NOW

EDMUND SCIENTIFIC CO. 300 Edscorp Bldg., Barrington, N. J. 08007



Send me the following:

Stock No. Quantity Price Ea.


Add handling charge \$1.00

Enclosed is check, M.O. in amount of \$

Signature

Address

City, State, Zip

☐ SEND FREE

164 PG. CATALOG "AVB"

Charge my ☐ American Exp.

☐ BankAmericard ☐ Master Chg.

Interbank No. \_\_\_\_\_

Card No. \_\_\_\_\_

Expiration Date \_\_\_\_\_

30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund.



## EDMUND SCIENTIFIC CO.

300 Edscorp Bldg., Barrington, N.J. 08007 • (609) 547-3488  
America's Greatest Science • Optics • Hobby Center

# According to TRUTONE RECORDS..“The Stanton calibrated 681 series is our total point of reference in our Disc Mastering Operation”



"Carl Rowatti, Chief Engineer, adjusting the Program limiters prior to cutting a master lacquer".

Trutone can be described as a family enterprise... but what a family! Father Lou Rowatti is the President; Son Carl is Vice President and Chief Engineer; and daughter-in-law Adrienne handles the business end of the operation. They have great pride in their family, in their family's enterprise and in their products. That's why they insist on using the best — always.

Trutone Records in Northvale, New Jersey always uses the Calibrated Stanton Triple-E for A-B comparisons between tape and disc. They also use the Triple-E to check the frequency response of the cutter head (they'll record a 1,000 Hz tone and a 10 kHz tone twice a day to check the condition of the cutting stylus and the high end frequency response of the cutter head).

They make test cuts and play them back, using the Triple-E for reference, as high as 15 kHz all the way down to 30 Hz. Carl Rowatti says "We use the Stanton Calibrated 681 series as our total point of reference in our disc master-

ing operation. Everything in the studio is judged — and we think perfectly judged for quality—with this great cartridge".

Professionals can't afford to take chances with quality. That's why they depend on Stanton in their operations.

Each Stanton 681 Triple-E is guaranteed to meet its specifications within exacting limits, and each one boasts the most meaningful warranty possible. An individually calibrated test result is packed with each unit.

Whether your usage involves recording, broadcasting, disco or home entertainment your choice should be the choice of the professionals... the Stanton 681 TRIPLE-E.

Write today for further information to:  
Stanton Magnetics, Terminal Drive,  
Plainview, New York 11803



Lou Rowatti inspects a master lacquer, Adrienne checks the lathe.



Carl Rowatti adjusts the pitch computer on the mastering lathe.



Carl installs the Stanton Calibrated 681 Triple-E on the playback table.



Lou Rowatti (The Prez) adjusting the high frequency limiter in his cutting room.

# RESEARCH DELIVERS


## A Quantum Jump in Record Care

### New D3 Fluid

1. Unmatched activity plus safety to vinyl additives (the critical compounds of longevity).
2. A secret non-adhering anti-static system that is measured in parts-per-billion!
3. A special chemical "release system" (pat. pend.) that allows suspended contaminants to pull away from critical micro-grooves.
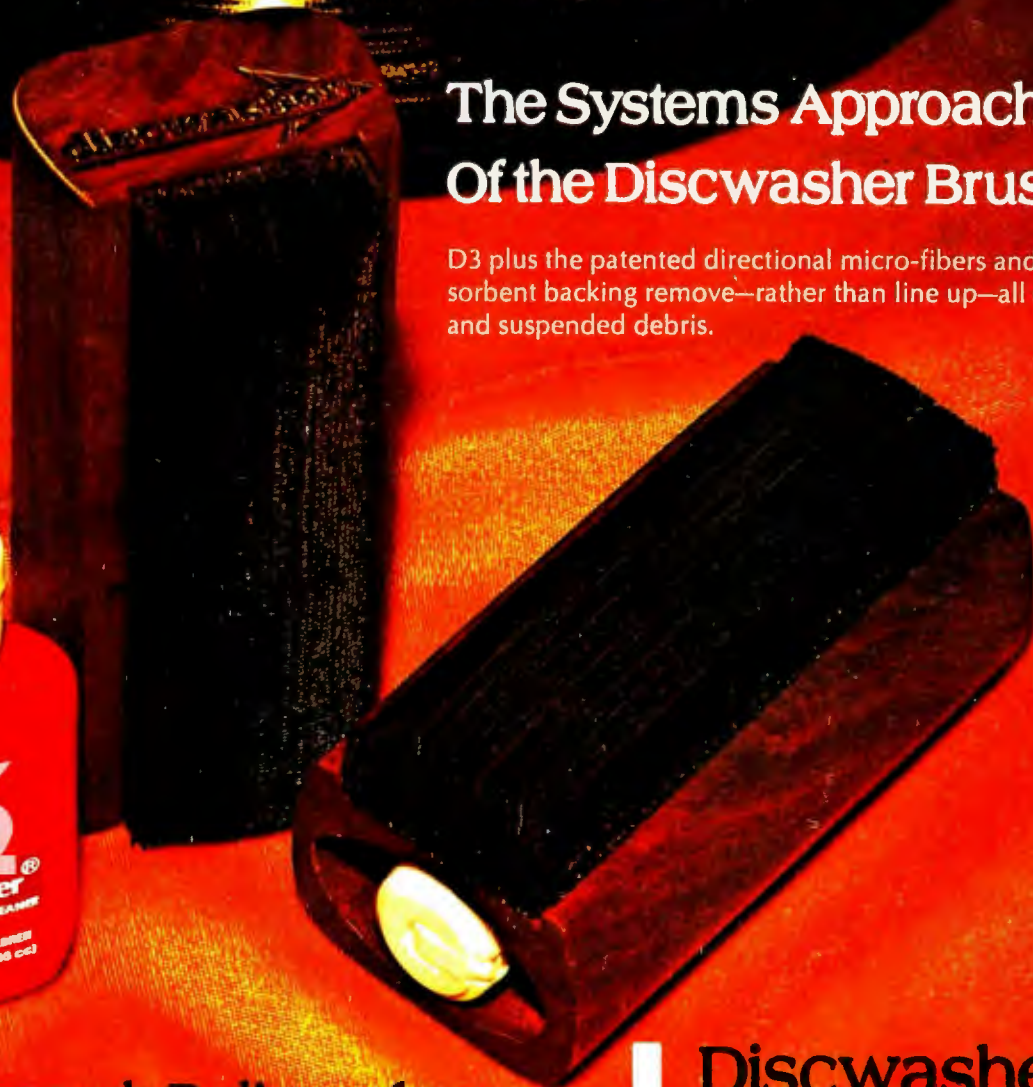
### The Systems Approach Of the Discwasher Brush

D3 plus the patented directional micro-fibers and absorbent backing remove—rather than line up—all dust and suspended debris.



Research Delivers from



**Discwasher  
Group**

1407 N. PROVIDENCE  
COLUMBIA, MO 65201

CIRCLE NO. 68 ON FREE INFORMATION CARD